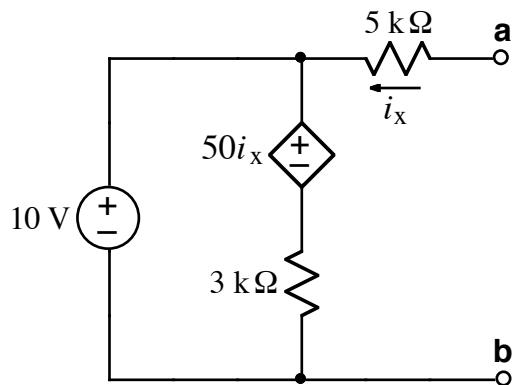



Ex:



- Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.
- If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .

Sol'n: a) $V_{Th} = V_{a,b}$ no load

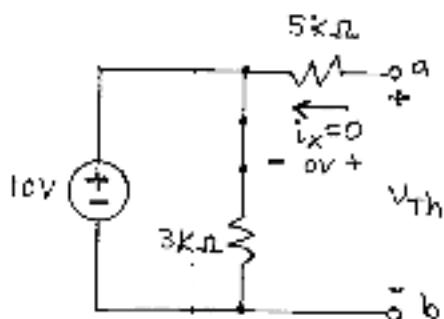
With nothing connected from **a** to **b**,
 $i_x = 0$ and $50i_x = 0V$ acts like a wire



Since $i_x = 0$, there is no voltage drop across the $5\text{k}\Omega$ resistor. An outer voltage loop reveals that $V_{Th} = 10V$.

Because we have a dependent source, we can find R_{Th} using the formula

$$R_{Th} = \frac{V_{Th}}{I_{sd}}$$

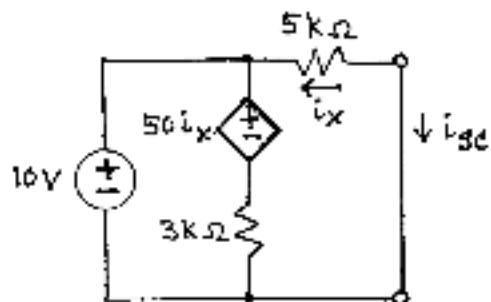


Although we have a dependent source, the 10V source between the top and bottom rails makes the $50i_x$ and $3k\Omega$ components irrelevant.

From an outer V-loop, we have

$$I_{sd} = \frac{10V}{5k\Omega} = 2mA$$

$$\therefore R_{Th} = \frac{V_{Th}}{I_{sd}} = \frac{10V}{2mA} = 5k\Omega$$

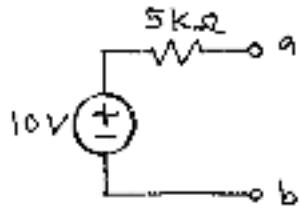Note: The 10V source across the rails allows to ignore the $50i_x$ and $3k\Omega$. We may remove them. Then we observe that we are left with the Thevenin equivalent circuit: $V_{Th} = 10V$, $R_{Th} = 5k\Omega$.



b) $R_L = R_{Th} = 5\text{k}\Omega$ for max pwr transfer

c) $P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(10V)^2}{4 \cdot 5\text{k}\Omega} = \frac{100}{20} \text{ mW}$

$$P_{max} = 5 \text{ mW}$$