HOMEWORK #18 answers



- 1. a = R, b = C, RC = 2.9 ms
- 2. $v_1(t) = \text{constant} -5 \text{ V}$
- 3. a) $v_1(t) = -10 \text{ V}$ before time t_0 and exponentially decays to 0 V after that b) $v_3(t) = -12 \text{ V}$ before time $t_0 + 2 \text{ ms}$ and 0 V thereafter
- 4. $V_3 = 8\sqrt{2} \angle 45^{\circ} \text{ V}$
- 5. $v_3(t) = 8\sqrt{2}\cos(37t + 45^\circ) \text{ V}$