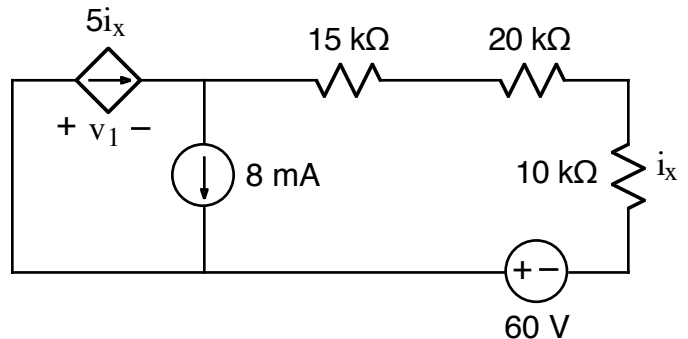


Ex:



Find  $i_x$ ,  $v_1$ , and the power dissipated by the dependent source.

sol'n: First, we observe that  $i_x$  flows thru all 3 resistors since they are in series.

Rather than defining voltages for every resistor, we may use Ohm's law directly to define the voltages as  $v = iR$ . Note that the + and - signs of the voltage measurements must obey the passive sign convention: the current arrow must point toward the - sign of the v-drop measurement.

Turning to v-loop eqns, we discover that all loops pass thru current sources, meaning we should avoid writing those v-loop eqns.

Note: even though the dependent current source is labeled with a v-drop, we should avoid using  $v_1$  in a v-loop. Instead, we can solve the circuit first and then find  $v_1$ .

We now write a current-sum eq'n for the top-center node:

$$-5i_x + 8 \text{ mA} + i_x = 0 \text{ A}$$

$$\text{or } 4i_x = 8 \text{ mA}$$

$$\text{or } i_x = 2 \text{ mA}$$

Now we use a v-loop around the outside of the circuit to find  $v_1$ :

$$-v_1 - i_x 15 \text{ k}\Omega - i_x 20 \text{ k}\Omega - i_x 10 \text{ k}\Omega + 60 \text{ V} = 0 \text{ V}$$

$$\text{or } v_1 = -i_x (15 \text{ k}\Omega + 20 \text{ k}\Omega + 10 \text{ k}\Omega) + 60 \text{ V}$$

$$= -2 \text{ mA} \cdot 45 \text{ k}\Omega + 60 \text{ V}$$

$$= -90 \text{ V} + 60 \text{ V}$$

$$v_1 = -30 \text{ V}$$

The power for the dependent source is

$$p = i \cdot v = 5i_x v_1 = 5(2 \text{ mA})(-30 \text{ V})$$

$$p = -300 \text{ mW}$$