
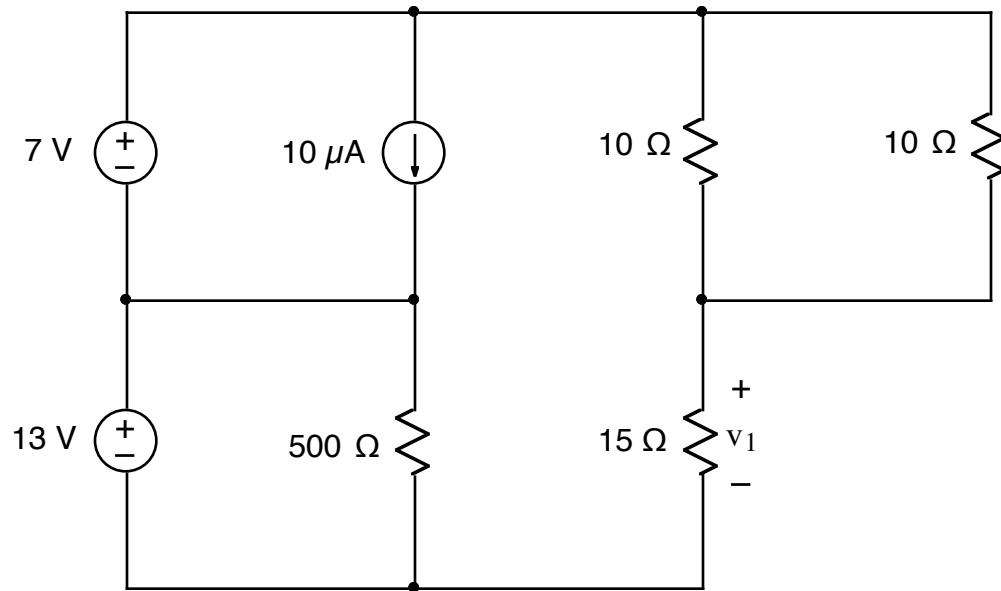


1.

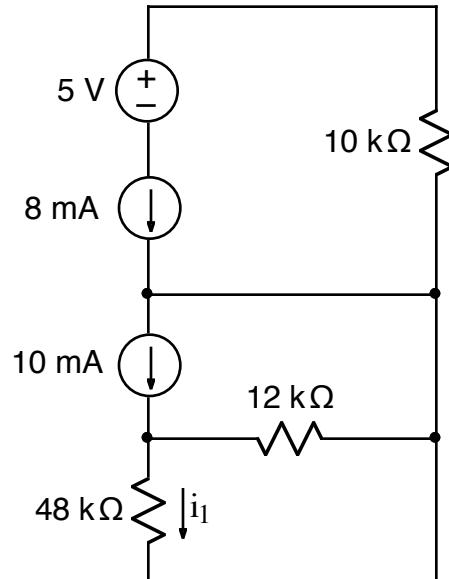


Calculate v_1 .

2.




Calculate i_1 .

3.

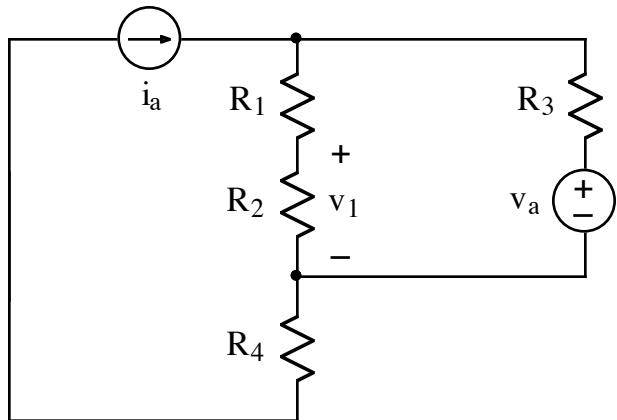


Derive an expression for v_1 . The expression must not contain more than the circuit parameters v_a , i_a , R_1 , R_2 , and R_3 .

4.

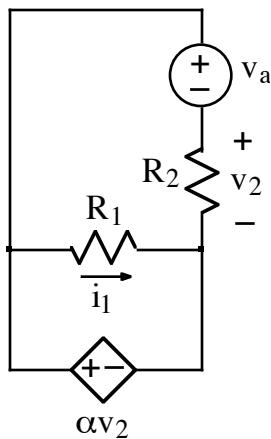

- Derive an expression for i_1 . The expression must not contain more than the circuit parameters α , v_a , R_1 , and R_2 . **Note:** $\alpha \neq 0$.
- Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

5.

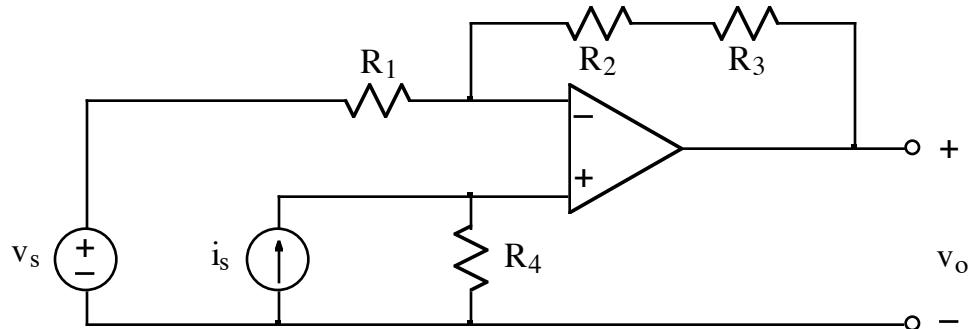

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for v_o in terms of not more than v_s , i_s , R_1 , R_2 , R_3 , and R_4 .