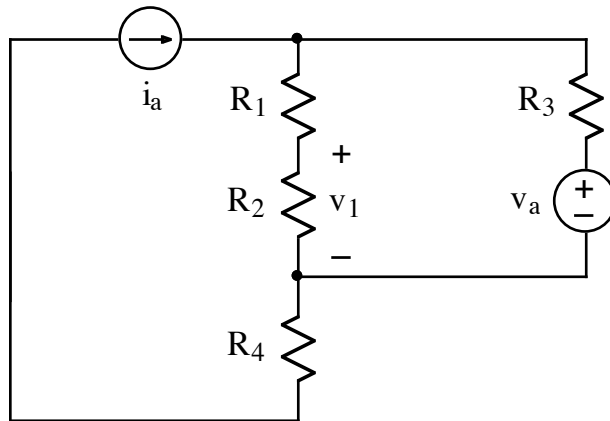


Ex:



Derive an expression for  $v_1$ . The expression must not contain more than the circuit parameters  $v_a$ ,  $i_a$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

SOL'N:

We have the same current in  $R_1$  and  $R_2$ , namely  $i_1$ .

Current  $i_a$  must be the current in  $R_4$ .  $v_4 = i_a R_4$ .

From a current sum at the top-center node:

$$-i_a + i_1 + i_3 = 0A \quad \text{or} \quad i_1 + i_3 = i_a$$

The current sum at the other node is redundant.

We have a  $v$ -loop on the right. (Other  $v$ -loops pass thru  $i_a$  source and are omitted.)

$$+v_1 + i_1 R_1 - i_3 R_3 - v_a = 0V$$

Note: We have used Ohm's law as we go, although we must also use eq'n  $v_1 = i_1 R_2$ .

---

We could solve for  $i_1$ , but the solution approach taken here finds  $v_1$ .

First,  $i_3 = i_a - i_1$  from current sum.

$$\text{Second, } i_1 = \frac{v_1}{R_2}$$

Third, we substitute into the v-loop eq'n:

$$v_1 + i_1 R_1 - (i_a - i_1) R_3 - v_a = 0V$$

$$\text{or } v_1 + \frac{v_1}{R_2} R_1 - \left(i_a - \frac{v_1}{R_2}\right) R_3 - v_a = 0V$$

$$\text{or } v_1 \left(1 + \frac{R_1}{R_2} + \frac{R_3}{R_2}\right) = i_a R_3 + v_a$$

$$\text{or } v_1 = \frac{i_a R_3 + v_a}{1 + \frac{R_1}{R_2} + \frac{R_3}{R_2}} = \frac{(i_a R_3 + v_a) \cdot R_2}{R_1 + R_2 + R_3}$$

Consistency check:  $v_a = 0$ ,  $R_3 = 0\Omega \Rightarrow v_1 = 0V$   
 $R_2$  bypassed

$$\text{our eq'n gives } v_1 = \frac{(i_a \cdot 0\Omega + 0) R_2}{R_1 + R_2 + 0\Omega} = 0V \checkmark$$