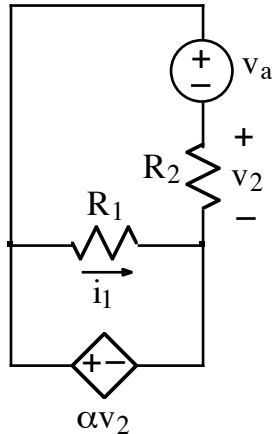


Ex:



- Derive an expression for i_1 . The expression must not contain more than the circuit parameters α , v_a , R_1 , and R_2 . **Note:** $\alpha \neq 0$.
- Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

SOL'N:

a) We have two inner v-loops:

$$-v_a + -v_2 + i_1 R_1 = 0V \quad (\text{top v-loop})$$

↑ using Ohm's law here

$$-i_1 R_1 + \alpha v_2 = 0V \quad (\text{bottom v-loop})$$

From the 2nd eq'n, $\alpha v_2 = i_1 R_1$

$$\text{or } v_2 = \frac{i_1 R_1}{\alpha}$$

$$\text{From 1st eq'n, } -v_a - \frac{i_1 R_1}{\alpha} + i_1 R_1 = 0V$$

$$\text{or } i_1 \left(R_1 - \frac{R_1}{\alpha} \right) = v_a$$

$$\text{or } i_1 = \frac{v_a}{R_1(1 - 1/\alpha)}$$

b) For the consistency check, we choose values of sources and R 's that yield a simpler circuit for which solution is obvious. Many checks may be possible. Only one is required here.

ex: $v_a = 0V$, $R_1 = 1\Omega$, $R_2 = 2\Omega$, $\alpha = 3$.

The circuit has no independent power source. Thus, all currents and voltages = 0. So $i_1 = 0A$.

Now we try our formula from (a):

$$i_1 = \frac{0}{1\Omega(1-1/3)} = 0 \quad \checkmark \text{ (consistent)}$$

ex: $R_1 = \infty\Omega$ (open circuit), $R_2 = 2\Omega$, $\alpha = 3$,
 $v_a = 12V$

If R_1 is open circuit, then $i_1 = 0A$.

Now we try our formula from (a):

$$i_1 = \frac{12V}{\infty\Omega(1-1/3)} = \frac{12V}{\infty\Omega} = 0A$$

Note: Some consistency checks might lead to invalid circuits such as V -sources shorted out. Avoid those. This particular circuit is prone to that problem.