

- 
1.  $i_1 = -41 \text{ A}, v_0 = -91 \text{ V}$
  2. a)  $v_1 = 12 \text{ V}, 5 \text{ mA}$  b)  $2 \text{ mW}$
  3.  $v_1 = 4.7 \text{ V}, v_2 = 4 \text{ V}, v_3 = 5 \text{ V}$
  4.  $i_1 = -2 \text{ mA}, i_2 = -6.002 \text{ A}, i_3 = -3.002 \text{ A}$
  5. a)  $i_1 = -5/3 \text{ mA}, i_2 = 6 \text{ mA}$ , b)  $p = -12 \text{ mW}$