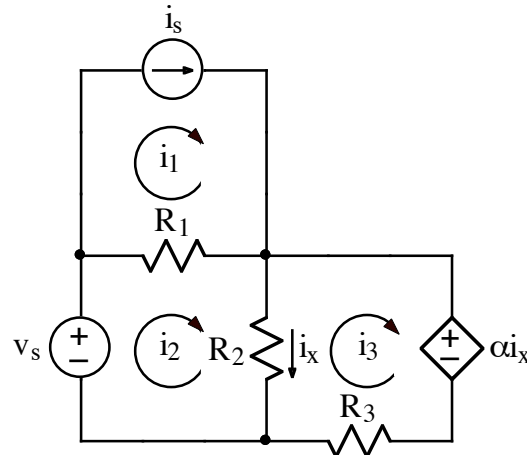


Ex:



For the circuit shown, write three independent equations for the three mesh currents,  $i_1$ ,  $i_2$ , and  $i_3$ . The quantity  $i_x$  must not appear in the equations.

sol'n: First, we define  $i_x$  in terms of mesh currents:

$$i_x = i_2 - i_3$$

Second, we look for current sources on the outside edges of the circuit, as these will define mesh current values.

There is a current source on the top edge that defines  $i_1$ :

$$i_1 = i_s \quad (1)$$

Third, we look for a super mesh. In other words, we look for a current source between loops. Here, there is no super mesh, and we write standard v-loop eqns for  $i_2$  and  $i_3$ .

---

$$+v_3 - i_2 R_1 + i_1 R_1 - i_2 R_2 + i_3 R_2 = 0V \quad (2)$$

$$-i_3 R_2 + i_2 R_2 - \alpha(i_2 - i_3) - i_3 R_3 = 0V \quad (3)$$