

30	<i>Communication</i>
12	Student's work Reproducible from notebook
4	Written in Ink
4	Student Signed every page
4	Student Dated every page
6	TA Signature for every lab session (-3 each session missed)
44	2. <i>Analysis of Op-Amp Circuits</i>
5	2.1. First op-amp circuit: v_o vs R_f measurements
5	2.2. Second op-amp circuit: v_o vs R_f measurements
4	2.3. First op-amp circuit: plot of $y = v_o/v_s$ vs $x = R_f/R_s$
4	2.4. Second op-amp circuit: plot of $y = v_o/v_s$ vs $x = R_f/R_s$
3	2.5. First op-amp circuit: equation for straight line fit
3	2.6. Second op-amp circuit: equation for straight line fit
3	2.7. First op-amp circuit: Matlab [®] <code>polyfit</code> coefficients
3	2.8. Second op-amp circuit: Matlab [®] <code>polyfit</code> coefficients
4	2.9. First op-amp circuit: expression for v_o
4	2.10. Second op-amp circuit: expression for v_o
3	2.11. First op-amp circuit: input resistance for circuit
3	2.12. Second op-amp circuit: input resistance for circuit
6	3. <i>Design, Construction, and Testing of Pre-amps</i>
3	3.1 Pre-amp: design
3	3.2 Pre-amp: test results
10	4. <i>Design, Construction, and Testing of Differential Amplifier</i>
4	4.1. Differential amplifier: expression for v_3
3	4.2. Differential amplifier: design
3	4.3. Differential amplifier: test results
10	5. <i>Measurements of Electromyogram</i>
4	5.1. Plot of electromyogram waveform
3	5.2. Matlab [®] code and calculation of electromyogram power
3	5.3. Matlab [®] code and plot of electromyogram power vs weight