



30	Communication
4	Work recorded in notebook (rather than pasted in)
8	Complete information: task descriptions, diagrams, data, reproducible one year later
4	Written in Ink
4	Student Signed every page
4	Student Dated every page
6	TA Signature for every lab session (-3 each session missed)
6	VI. CONSTRUCTION AND TESTING OF PRE-AMPS [Lab 1a (last section)]
	A. <i>Construction</i>
1	Explanation of task (constructed pre-amps circuits on breadboard)
1	Schematic of pre-amps
1	Explanation of testing (1 V 1 kHz sinusoid in, oscilloscope measure output)
	B. <i>Drawing of Waveforms</i>
3	Careful drawing of oscilloscope screen
6	V. DEMONSTRATING THE NEED FOR PRE-AMPS [Lab 1b]
	B. <i>Procedure</i>
1	Explanation of task (measured voltages for electrode model v-divider)
2	Table II-A filled in with measured values
1	Explanation of task (measured voltages for pre-amp model v-divider)
2	Table II-B filled in with measured values
22	VI. DERIVING AN EXPRESSION FOR THE DIFFERENTIAL AMPLIFIER OUTPUT
	A. <i>Deriving the Expression for v_3</i>
1	Explanation of task (deriving expression for output of diff-amp)
1	Schematic of differential-amp
15	Derivations: v_+ , v_- , and v_3
	B. <i>Differential Gain</i>
5	Derivation of v_3 in terms of \mathfrak{R}
24	VII. DESIGNING, BUILDING, AND TESTING THE DIFFERENTIAL AMPLIFIER
	A. <i>Resistor values for a gain of 500</i>
4	Explanation of how R_1 , R_2 , R_3 , and R_4 chosen
2	List of values for R_1 , R_2 , R_3 , and R_4
	B. <i>Building and Testing the Differential Amplifier</i>
1	Schematic (for circuit in Fig. 6 or for own circuit layout)
1	Explanation of test procedure including 6 V power supply and v-divider
3	Table of values of measured diff-amp output vs input 1 voltage
3	Table of values of measured diff-amp output vs input 2 voltage
	C. <i>Measuring the Gain of the Differential Amplifier</i>
4	Plot of v_3 vs $v_2 - v_1$
4	polyfit() straight line fit of data
2	Calculation of gain of differential amplifier
12	VIII. MEASURING AND ANALYZING EMG'S
	A. <i>Measuring EMG's</i>
1	Explanation of task (used electrodes on biceps to measure EMG)
5	Printout of EMG waveform on oscilloscope
	B. <i>Power versus Weight for EMG signals</i>
1	Explanation of task (Matlab [®] calculation of power in EMG waveform)
	C. <i>Plot of EMG Power versus Weight</i>
5	Matlab [®] plot of power vs weight