



<b>30</b>	<b>Communication</b>
–	IEEE single column, double spaced format, title, author, etc. (–20 pts if not used)
5	Style (written in the style of article, rather than disjointed figures and tables)
5	English (grammar, punctuation, and etc.)
5	Clarity (purpose of each section clearly explained)
3	Succinctness and precise wording (detailed information in as few words as possible)
3	Organization (ease of locating figures/code/equations/etc.)
3	Section numbers and headings (use section numbers shown below)
3	Equations explained (at least one sentence between equations)
3	Figures complete (every figure numbered, captioned, and referred to in text)
<b>5</b>	<b>Abstract</b> (succinct summary of results, including numerical values as appropriate)
<b>10</b>	<b>I. INTRODUCTION</b>
8	Motivation for lab [create EMG circuit, useful for medical diagnostics]
2	State report organization [briefly describe contents of sections that follow]
<b>10</b>	<b>II. ELECTRODE AND PRE-AMP MODELING (Lab 1b Section V)</b>
	A. <i>Electrode model</i>
1	Introduce section [to demonstrate need for pre-amp to drive diff-amp]
1	Explain electrode model [small v-source in series with 1 M $\Omega$ ]
1	Describe experiment simulating electrode driving diff-amp [include Fig. 2a]
1	Mention ratio of electrode model circuit output to input [ $v_2/v_{6V}$ pwr supply]
2	Explain that electrode unable to drive diff-amp [signal too small]
	B. <i>Pre-amp model</i>
1	Explain pre-amp output model [small v-source in series with 10 $\Omega$ ]
1	Describe experiment simulating pre-amp driving diff-amp [include Fig. 2a]
1	Mention ratio of pre-amp model circuit output to input [ $v_2/v_{6V}$ pwr supply]
1	Explain that pre-amp is able to drive diff-amp [signal out $\approx$ input]
<b>5</b>	<b>III. PRE-AMP CONSTRUCTION (Lab 1a Section VI)</b>
1	Describe pre-amp circuit [buffer configuration, output v = input v]
2	Include figure showing pre-amps schematic [Lab 1a Fig. 6b, crop out LED's]
1	Describe testing procedure
1	Describe testing results
<b>25</b>	<b>IV. DIFFERENTIAL AMPLIFIER DESIGN AND TEST (Lab 1b Section VI, VII.A,B)</b>
	A. <i>Analysis of differential amplifier</i>
1	Describe differential amplifier circuit [Lab 1b Fig. 4]
5	Derive the formula for $v_3$
3	Derive the formula for $v_3$ written in terms of $v_{cm}$ and $v_{dm}$
5	Derive the formula for $v_3$ written in terms of $\mathfrak{R}=R_1/R_2=R_3/R_4$
1	Explain that $v_3$ written in terms of $\mathfrak{R}$ is only a function of $v_{dm}$
	B. <i>Design of differential amplifier</i>
1	Describe constraints for design (Lab 1b Section VIII.A)
3	Explain how resistor values were chosen
1	List values of resistors used in diff-amp
	C. <i>Testing of differential amplifier</i>
1	Describe testing procedure [Lab 1b Fig. 7]
3	Show plot of $v_3$ vs $v_{s1}$ and $v_{s2}$ with linear fit superimposed
1	Explain calculation of gain of diff-amp [= slope of plot] and list value of gain
<b>10</b>	<b>V. EMG MEASUREMENT (Lab 1b Section VIII)</b>
	A. <i>Measurement of EMG</i>
1	Explain how electrodes and oscilloscope connected for EMG
3	Show plot of EMG from oscilloscope
	B. <i>Power vs weight for EMG signal</i>
1	Explain how power for EMG calculated [Lab 1b Eqn (6)]
4	Show plot of power vs weight
1	Comment on plot [describe shape, possible measurement errors]
<b>5</b>	<b>CONCLUSION</b> (summarize key results; include numerical values as appropriate)