
30	<i>Communication</i>
12	Student's work Reproducible from notebook
4	Written in Ink
4	Student Signed every page
4	Student Dated every page
6	TA Signature for every lab session (-3 each session missed)
26	2. <i>Design Oscillator</i>
5	2.1. Frequency-Domain Circuit
5	2.2. Balanced Bridge
5	2.3. Oscillation
6	2.4. Oscillation Frequency
5	2.5. Component Values for Oscillation
18	3. <i>Construct and Test Oscillator</i>
4	3.1 Oscillation Frequency for Standard Component Values
5	3.2 Oscillation Frequency for Actual Component Values
5	3.3. Measured Oscillator Waveforms
4	3.4. Tabulated Values
11	4. <i>Analyze Tissue Impedance Model</i>
3	4.1. Circuit for Measuring Tissue Impedance
5	4.2 Component Values for Tissue Impedance Model
3	4.3 Choosing Resistance for Impedance Measurement Circuit
15	5. <i>Measure Tissue Impedance</i>
5	5.1. Measurement of Tissue Impedance and Calculation of Component Values
6	5.2. Calculation of Conductivity, Relative Permeability, and Power Density
2	5.3. Comparison of Measured Values with Published Values
2	5.4. Comparison of Power Density with FDA Limit