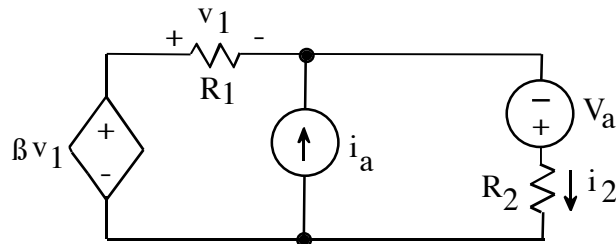


3. (30 points)

- a. Derive an expression for  $i_2$ . The expression must not contain more than the circuit parameters  $\beta$ ,  $V_a$ ,  $i_a$ ,  $R_1$ , and  $R_2$ .




- b. Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

**ans: a)** 
$$i_2 = \frac{(1-\beta)i_a R_1 + V_a}{(1-\beta)R_1 + R_2}$$

- b)** Many possible answers. See solution below.

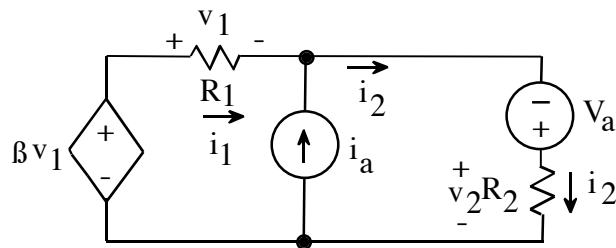**sol'n: (a)** Use Kirchhoff's laws to write several equations. Then eliminate unwanted variables.



We sum currents out of top-center node:

$$-i_1 - i_a + i_2 = 0$$

Note that summing currents out of bottom-center node does not give us anything new. By Ohm's law, we also have

$$i_1 = \frac{v_1}{R_1}$$

Now, we sum voltages around a loop. We choose the outer loop because the inner loops have a current source with unknown voltage drop.

$$\beta v_1 - v_1 + V_a - v_2 = 0 \quad \text{or} \quad (\beta - 1)v_1 + V_a - v_2 = 0$$

By Ohm's law, we also have

$$v_2 = i_2 R_2$$

After the Ohm's law substitutions, we have two equations, and we may eliminate  $v_1$ .

Use the simpler equation first:

$$\frac{v_1}{R_1} + i_a - i_2 = 0 \quad \text{or} \quad v_1 = (i_2 - i_a) R_1$$

Substitute for  $v_1$  in the second equation:


$$(\beta - 1)R_1(i_2 - i_a) + V_a - i_2 R_2 = 0$$

After some algebra, we get

$$i_2 = \frac{(1 - \beta)i_a R_1 + V_a}{(1 - \beta)R_1 + R_2} \quad \text{units consistent} \quad \checkmark$$

(b) There are many possible consistency checks.

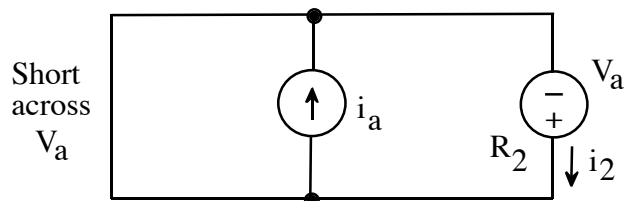- 1)  $i_a = 0$  and  $R_1 = 0$ . Then  $v_1 = 0$ ,  $\beta v_1 = 0$ , and sum  $v$ 's around outer loop gives  $i_2 = V_a/R_2$ . Our formula also gives  $V_a/R_2$ .  $\checkmark$
- 2) Consider  $R_1 = 0$  and  $R_2 = 0$ . As in (1),  $v_1 = 0$  and  $\beta v_1 = 0$ . Since  $R_2 = 0$  we also end up with a short across  $V_a$ :



We expect  $i_2 \rightarrow \infty$  for short across  $V_a$

Our formula gives

$$\lim_{R_2 \rightarrow 0} \frac{V_a}{R_2} = \infty \quad \text{for } i_2 \quad \checkmark$$

← from (1)

3) Consider  $i_a = 0, \beta = 0$ :




$$i_2 = \frac{V_a}{R_1 + R_2} \text{ by Ohm's law}$$

Our formula gives

$$i_2 = \frac{V_a}{R_1 + R_2} \quad \checkmark$$

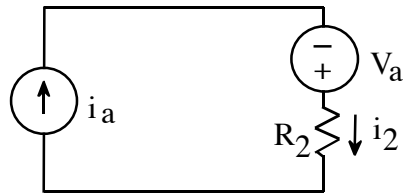4) Consider  $R_1 \rightarrow \infty$  (open circuit)



Clearly  $i_a = i_2$  since the same current flows through elements in series.

Our formula gives:

$$i_2 = \lim_{R_1 \rightarrow \infty} \frac{(1-\beta)i_a R_1 + V_a}{(1-\beta)R_1 + R_2} = \lim_{R_1 \rightarrow \infty} \frac{(1-\beta)i_a R_1}{(1-\beta)R_1} \quad \checkmark$$

$$= i_a$$

5) Consider  $R_2 \rightarrow \infty$  (open circuit): We have  $i_2 = 0$  since no current flows through the open circuit. Our formula gives:

$$i_2 = \lim_{R_1 \rightarrow \infty} \frac{(1-\beta)i_a R_1 + V_a}{(1-\beta)R_1 + R_2} = \frac{\text{const}}{\infty} = 0 \quad \checkmark$$

Many more consistency checks are possible.