

a) Write a numerical expression for $i(t)$, $t \geq 0^+$.

sol'n: Any $i(t)$ or $v(t)$ will be described by the general form of solution whenever we solve a switching problem:

$$i(t) = i(t=0^+) + [i(t \rightarrow \infty) - i(t=0^+)] [1 - e^{-t/RC}]$$


We only need to find $i(t=0^+)$, $i(t \rightarrow \infty)$, and RC .

$i(t=0^+)$: To find $i(t=0^+)$, we need the initial conditions for the circuit. Since there is a capacitor, we need to find $v_C(t=0^+)$. (If there were an inductor, we would need to find $i_L(t=0^+)$.)

Since the voltage on the capacitor cannot change instantly, $v_C(t=0^+) = v_C(t=0^-)$.

To find $v_C(t=0^-)$, we treat C as an open circuit, (because the switch has been closed for a long time, allowing C to charge to final value where current no longer flows).

Circuit model: $t=0^-$ (switch closed)

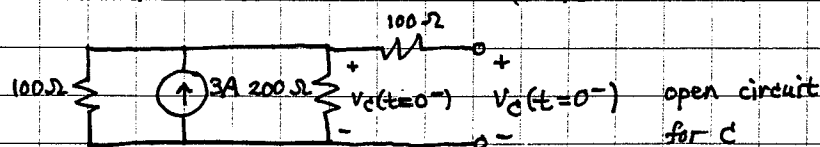


Since no current flows in the 100Ω top right, $v_C(t=0^-)$ also appears across the 200Ω R. (No current in $100\Omega \Rightarrow$ no v drop.)

1.a) (cont) We have $v_c(t=0^-) = 3A \cdot 100\Omega \parallel 200\Omega = 3A \cdot 100\Omega \cdot \frac{1}{2}$


$$v_c(t=0^-) = 3A \cdot 100\Omega \cdot \frac{2}{3} = 200V$$

$$v_c(t=0^+) = v_c(t=0^-) \quad (v_c \text{ cannot change instantly})$$

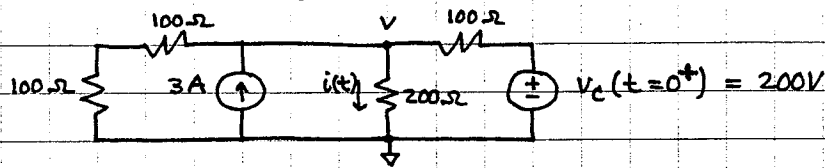For $t=0^+$ we use a v-source to represent C, and we find $i(t=0^+)$: $t=0^+$ (switch open)




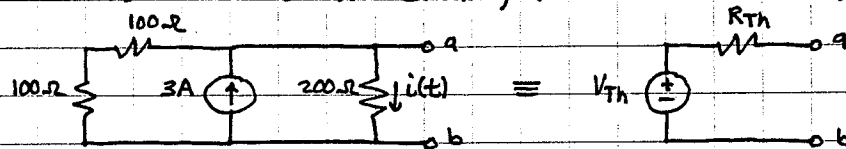We can find $i(t)$ by any method we prefer. My choice is to take a Thevenin equivalent of the left side of the circuit, (thru the 200Ω R).




$$V_{Th} = \text{open circuit } v = 3A \cdot (100\Omega + 100\Omega) \parallel 200\Omega = 3A \cdot 100\Omega = 300V$$

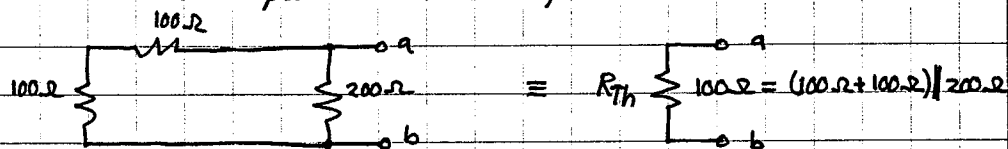R_{Th} = resistance seen when looking into terminals a - b with independent $3A$ source set to zero. (This is the same as connecting a $1V$ source at a - b , measuring current into $'a'$ and taking $R_{Th} = 1V / i_{1V}$. This simpler approach works whenever there are no dependent sources.)



Our circuit is: $t=0^+$

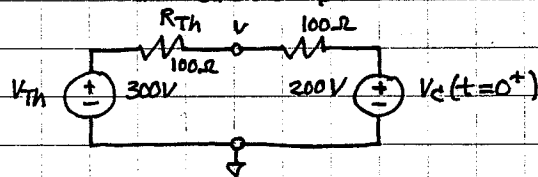


We see that $v = 250V$, (the two 100Ω R's divide the $100V$ drop into two equal v -drops of $50V$ each).

1.a) (cont) Finally, we have $i(t=0^+) = \frac{250V}{200\Omega} = 1.25A$

Note: I used a Thevenin equivalent that had $i(t)$ transformed inside it, but I used it to find the output voltage, V , of the Thevenin equivalent. Then I found $i(t=0^+)$ from the voltage. What I cannot do is try to find $i(t)$ somewhere inside the Thevenin equivalent.

Note: We could use a mesh current, or node- V , or superposition method to find $i(t)$. User's choice. Superposition might be a good choice for finding $i(t=0^+)$.

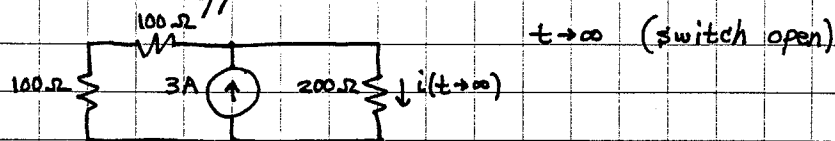$i(t \rightarrow \infty)$: The capacitor will be charged and acting like an open circuit. Again there will be no current thru the 100Ω top right, and $V_C(t \rightarrow \infty)$ will appear across the 200Ω R.



We have a current divider. $i(t \rightarrow \infty) = 3A \cdot \frac{100\Omega + 100\Omega}{100\Omega + 100\Omega + 200\Omega}$

$$i(t \rightarrow \infty) = 1.5A$$

RC: Use the Thevenin equivalent found earlier for $t=0^+$ so we have simple RC circuit. Then $R = R_{Th} + 100\Omega = 200\Omega$.
 $RC = 200\Omega \cdot 1\mu F = 200\mu s$.

$$\therefore i(t \geq 0^+) = 1.25A + (1.5 - 1.25A)(1 - e^{-t/200\mu s}) = 1.5A - 0.25A \cdot e^{-t/200\mu s}$$

1.b) Calculate energy stored in C at $t=0^+$.

← Found in soln to 1.a)


$$\text{sol'n: } w = \frac{1}{2} C V_C^2(t=0^+) = \frac{1}{2} \cdot 1\mu F \cdot (200V)^2 = 0.02 J \text{ or } 20 mJ$$

1. c) Calculate energy stored in C as $t \rightarrow \infty$.

$$\text{sol'n: } w = \frac{1}{2} C v_c^2 = \frac{1}{2} 1 \mu\text{F} \cdot (300\text{V})^2 = 0.045 \text{ J or } 45 \text{ mJ}$$

Note: In part (a), we found $v_c(t \rightarrow \infty) = 300\text{V}$.


2.

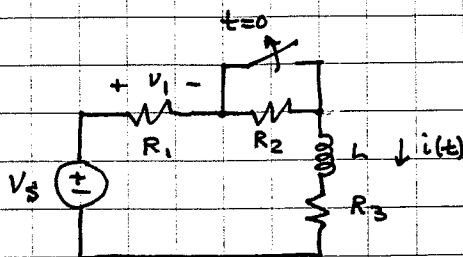

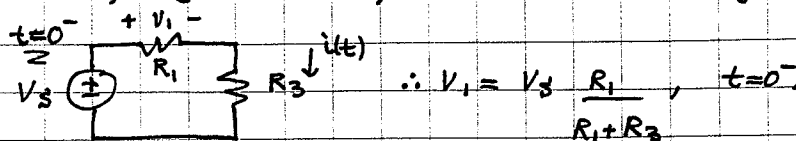a) Write an expression for $v_1(t)$.

sol'n: For $t=0^-$ the L looks like a short circuit or wire.


Also, R_2 shorted by switch. V-divider gives v_1 .



Also, $i(t=0^-) = V_s / (R_1 + R_3) = i(t=0^+)$

With switch open, we can find $i(t)$ through inductor.

We combine R's:

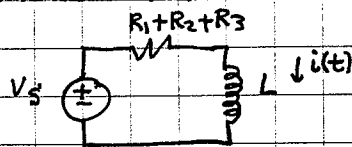

At $t \rightarrow \infty$ we again have L acting like a wire.

$$\therefore i(t \rightarrow \infty) = \frac{V_s}{R_1 + R_2 + R_3}$$

Now use general formula to write $i(t)$:

$$i(t) = i(t=0^+) + [i(t \rightarrow \infty) - i(t=0^+)] [1 - e^{-t/(L/R')}] \quad \boxed{R' = R_1 + R_2 + R_3}$$

$$i(t) = \frac{V_s}{R_1 + R_3} + \left[\frac{V_s}{R_1 + R_2 + R_3} - \frac{V_s}{R_1 + R_3} \right] [1 - e^{-t/(L/R')}]$$

$v_1(t) = i(t) \cdot R_1$ since i_1 also flows through R_1 .

$$\therefore v_1(t) = V_s \cdot \left\{ \frac{R_1}{R_1 + R_3} + \left[\frac{R_1}{R_1 + R_2 + R_3} - \frac{R_1}{R_1 + R_3} \right] [1 - e^{-t/(L/R')}] \right\}$$

2. b) Make one consistency check (other than units).

sol'n: Check: If $V_s = 0$, L always discharged so $v_L(t \geq 0^+) = 0$.

Our answer is multiplied by V_s so we get $v_L(t \geq 0^+) = 0$ if $V_s = 0$. ✓

or Check: If $R_1 = 0$, then $v_L = 0$ for short of 0Ω .

$$\text{Our answer gives } v_L(t \geq 0^+) = V_s \cdot \left\{ \frac{0}{0+R_3} + \left[\frac{0}{0+R_2+R_3} - \frac{0}{0+R_3} \right] 1 - e^{-t/(L/(R_2+R_3))} \right\} = 0 \quad \checkmark$$

Note: We have to be sure we don't get $0/0$ (which we have verified above, assuming $R_2, R_3 \neq 0$).

or Check: If $R_2 = 0$, then open switch doesn't add any R , and L continues to act like wire, and $v_L = V_s \frac{R_1}{R_1+R_3}$.

$$\text{Our answer gives } v_L(t \geq 0^+) = V_s \cdot \left\{ \frac{R_1}{R_1+R_3} + \left[\frac{R_1}{R_1+R_3} - \frac{R_1}{R_1+R_3} \right] 1 - e^{-t/(L/R_1)} \right\} = V_s \cdot \frac{R_1}{R_1+R_3} \quad \checkmark$$

or Check: If $L = 0 \text{ H}$, then we just have wire for L.

Then $v_L = V_s \cdot \frac{R_1}{R_1+R_2+R_3}$ for $t \geq 0^+$.

$$\text{Our answer gives } v_L(t \geq 0) = V_s \cdot \left\{ \frac{R_1}{R_1+R_3} + \left[\frac{R_1}{R_1+R_2+R_3} - \frac{R_1}{R_1+R_3} \right] 1 - e^{-t/(L/R_1)} \right\}$$

$$\text{Now, } e^{-t/0} = e^{-\infty} = 0.$$

$$\therefore v_L(t \geq 0) = V_s \cdot \left\{ \frac{R_1}{R_1+R_3} + \left[\frac{R_1}{R_1+R_2+R_3} - \frac{R_1}{R_1+R_3} \right] \right\} = V_s \frac{R_1}{R_1+R_2+R_3} \quad \checkmark$$