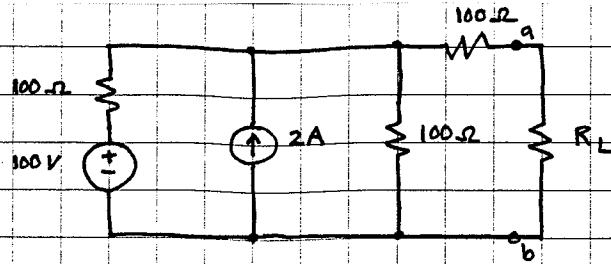



PRACTICE EXAM SOLUTION Probs 3 and 4

3.



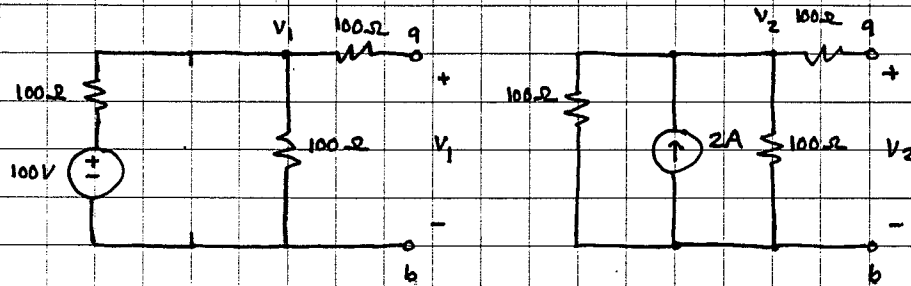a) Calculate the value of  $R_L$  that would absorb maximum power.

Sol'n: Transform into Thevenin equivalent of circuit left of  $R_L$ .  
Use superposition the find  $V_{TH}$ :



$V_{TH} = V_1 + V_2$  In both cases, we have no current thru  $100\Omega$  top right. So no V-drop across it.

$V_1$  from V-divider:

$$V_1 = 100V \cdot \frac{100\Omega}{100\Omega + 100\Omega} = 50V$$


$$V_2 = 2A \cdot 100\Omega \parallel 100\Omega$$

$$= 2A \cdot 50\Omega = 100V$$

$$V_{TH} = V_1 + V_2 = 150V$$

(independent)

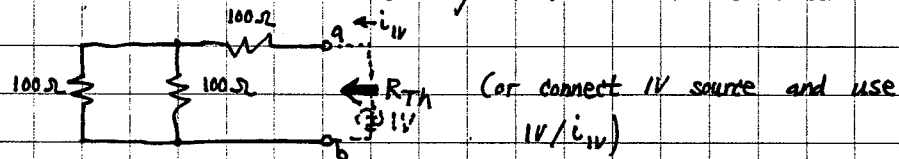For  $R_{TH}$ , we turn sources to zero and see what resistance we have looking in from a-b terminals:




$$R_{TH} = 100\Omega + 100\Omega \parallel 100\Omega = 150\Omega$$

Max power xfer when

$$R_L = R_{TH} = 150\Omega$$

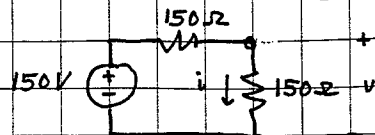3.b) Calculate the value of max power,  $P_L$  chosen for max pow.


sol'n: Our circuit with  $R_L = R_{Th}$  is:



$$pwr\ p = iV = \frac{150V \cdot 75V}{300\Omega}$$

$$p = 37.5\ W$$

4.

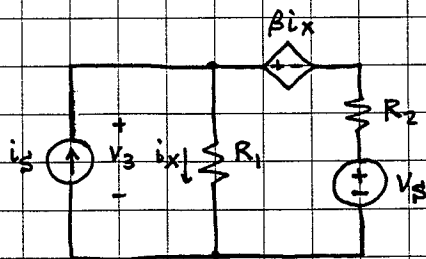


Use superposition. Find expression for  $v_3$  not using  $i_x$ .

sol'n: Turn one independent source on at a time, with other independent sources = 0. Sum currents and v's from each of the models to get total currents and voltages for circuit.

Note: Current source set to 0 is open circuit.  
Voltage " " " " " short circuit, (i.e. wire).

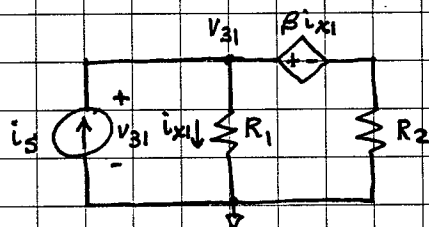Circuit 1:  $i_s \neq 0$ ,  $v_3 = 0$ . Add a "1" subscript to  $i_s$  and  $v_3$ .




$$i_{x1} = \frac{v_{31}}{R_1}$$

Use Node V for  $v_{31}$ :

$$i_s = i_{x1} + \frac{v_{31} - \beta i_{x1}}{R_2} = \frac{v_{31}}{R_1} + \frac{v_{31} - \beta \frac{v_{31}}{R_1}}{R_2}$$

$$i_s = v_{31} \left( \frac{1}{R_1} + \frac{1}{R_2} - \frac{\beta}{R_1 R_2} \right) \quad \text{or} \quad v_{31} = i_s \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} - \frac{\beta}{R_1 R_2}} \right)$$

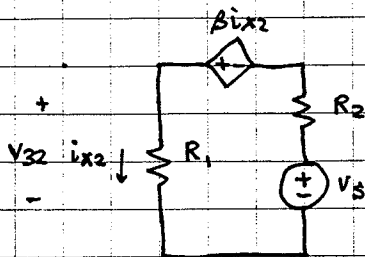4. (cont) Circuit 2:  $v_s \neq 0, i_s = 0$ . Add a "2" subscript to  $i$ 's &  $v$ 's.



Use sum  $V$ 's around loop = 0. (Mesh 1)

$$i_{x2} = \frac{v_{32}}{R_1}$$

$$v_s - i_{x2} R_2 + \beta i_{x2} - i_{x2} R_1 = 0V$$

$$\text{or } v_s - v_{32} \frac{R_2}{R_1} + \beta \frac{v_{32}}{R_1} - v_{32} = 0V$$

$$v_s = v_{32} \left( \frac{R_2}{R_1} + 1 - \frac{\beta}{R_1} \right) \quad v_{32} = \frac{v_s}{\frac{R_2}{R_1} + 1 - \frac{\beta}{R_1}}$$

$$\text{Now } v_3 = v_{31} + v_{32} = \frac{v_s}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} - \frac{\beta}{R_1 R_2} \right)}$$

eqn 1 or  $v_3 = \left( i_s + \frac{v_s}{R_2} \right) / \left( \frac{1}{R_1} + \frac{1}{R_2} - \frac{\beta}{R_1 R_2} \right)$

eqn 2  $v_3 = \left( i_s + \frac{v_s}{R_2} \right) \left( R_1 \parallel R_2 \parallel \frac{-R_1 R_2}{\beta} \right)$  Note:  $R_a \parallel -R_b \equiv \frac{R_a R_b}{R_b - R_a}$

eqn 3  $v_3 = (i_s R_2 + v_s) / \left( \frac{R_2}{R_1} + 1 - \frac{\beta}{R_1} \right) = \frac{R_a (-R_b)}{R_a + (-R_b)}$

Consistency Checks: 1)  $\beta = 0, v_s = 0 \Rightarrow v_3 = i_s \cdot (R_1 \parallel R_2)$

eqn 2 gives  $v_3 = \left( i_s + \frac{0}{R_2} \right) \left( R_1 \parallel R_2 \parallel \frac{-R_1 R_2}{0} \right) = i_s \cdot (R_1 \parallel R_2) \checkmark$

2)  $R_1 = \infty \Rightarrow v_3 = v_s + i_s R_2$

eqn 2 gives  $v_3 = \left( i_s + \frac{v_s}{R_2} \right) \left( \infty \parallel R_2 \parallel \frac{\infty \cdot R_2}{\beta} \right) = \left( i_s + \frac{v_s}{R_2} \right) R_2 \checkmark$

3)  $i_s = 0, \beta = 0 \Rightarrow v_3 = v_s \frac{R_1}{R_1 + R_2}$

eqn 2 gives  $v_3 = \left( 0 + \frac{v_s}{R_2} \right) \left( R_1 \parallel R_2 \parallel \frac{-R_1 R_2}{0} \right) = \frac{v_s}{R_2} \frac{R_1 R_2}{R_1 + R_2} \checkmark$

4)  $R_1 = 1\Omega, R_2 = 2\Omega, v_s = 3V, i_x = 4A, v_3 = 4V, \beta = \frac{1}{8}$

$\beta i_x = \frac{1}{2}V, v_{R_2} = v_3 - (v_s + \beta i_x) = 4 - (3 + \frac{1}{2}) = \frac{1}{2}V \Rightarrow i_{R_2} = \frac{1}{4}A$

$i_s = i_x + i_{R_2} = 4\frac{1}{4}A = 17/4A, R_1 \parallel R_2 \parallel \frac{-R_1 R_2}{\beta} = 1 \parallel 2 \parallel -16 = \frac{2}{3} \parallel -16 = \frac{1}{3} \parallel -48 = +32/46$

eqn 2 gives  $v_3 = \left( \frac{17}{4} + \frac{3}{2} \right) \cdot \frac{32}{46} = \frac{25}{4} \cdot \frac{32}{46} = \frac{32}{8} = 4V \checkmark$