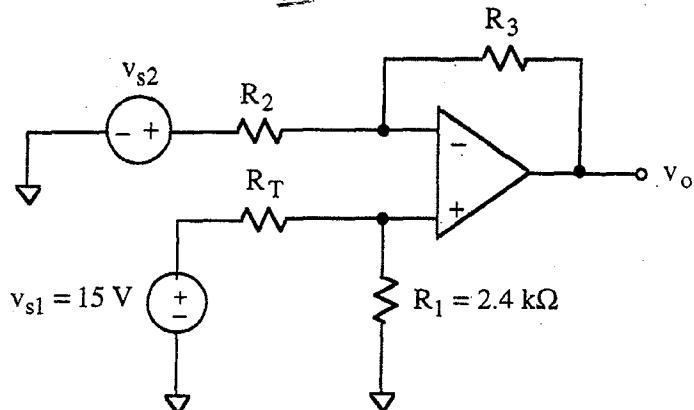


1. (70 points)

Rail voltage = ± 15 V

~~Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by~~

~~$$R_T = R_0 e^{1120 \left(\frac{1}{T} - \frac{1}{300} \right)}$$~~

~~where $R_0 = 2490 \Omega$ and T is temperature in $^{\circ}\text{K}$.~~

Pts10. a. Calculate the numerical values of $R_T(273^{\circ}\text{K})$ and $R_T(373^{\circ}\text{K})$.

25 b. Derive a symbolic expression for v_o . The expression must contain not more than the parameters v_{s1} , v_{s2} , R_T , R_1 , R_2 , and R_3 .

Hint: Use superposition.

25 c. Choose v_{s2} , R_2 , and R_3 that will produce the following:

~~$$\begin{aligned} v_o &= 0 \text{ V} && \text{when } T = 273^{\circ}\text{K} \\ v_o &= 10 \text{ V} && \text{when } T = 373^{\circ}\text{K} \end{aligned}$$~~

10 d. Using the component values you chose in (c), calculate v_o when $T = 323^{\circ}\text{K}$.

sol'n 1.a)

$$R_T(273^\circ\text{K}) = 2490 \times \frac{1}{273} - \frac{1}{300} = 3.6 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2490 \times \frac{1}{373} - \frac{1}{300} = 1.2 \text{ k}\Omega$$

$$R_T(273^\circ\text{K}) = 3.6 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 1.2 \text{ k}\Omega$$

b) Superposition:

$$v_{S1} \text{ on}, v_{S2} \text{ off} \Rightarrow v_p = v_{S1} \cdot \frac{R_1}{R_1 + R_T}, v_h = v_p$$

$$i_f (\text{thru } R_2) = \frac{0 - v_h}{R_2} = -v_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_2}$$

$$i_f (\text{thru } R_3) = \frac{v_h - v_{O1}}{R_3} = -v_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_3}$$

$$i_f (\text{thru } R_2) = i_f (\text{thru } R_3) \Rightarrow -\frac{v_h}{R_2} = \frac{v_h - v_o}{R_3}$$

$$\text{or } v_{O1} = v_h \left(1 + \frac{R_3}{R_2}\right) = v_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right)$$

$$v_{S1} \text{ off}, v_{S2} \text{ on} \Rightarrow v_p = 0V, v_h = v_p$$

$$i_f (\text{thru } R_2) = \frac{v_{S2}}{R_2} \quad i_f (\text{thru } R_3) = -\frac{v_{O2}}{R_3}$$

$$i_f (\text{thru } R_2) = i_f (\text{thru } R_3) \Rightarrow v_{O2} = -v_{S2} \frac{R_3}{R_2}$$

$$v_o = v_{O1} + v_{O2}$$

$$v_o = v_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right) - v_{S2} \frac{R_3}{R_2}$$

c)

$$\text{At } 273^\circ\text{K}, v_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 3.6 \text{ k}\Omega} = 15V \cdot \frac{2}{5} = 6V = v_p$$

$$\text{At } 373^\circ\text{K}, v_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 15V \cdot \frac{2}{3} = 10V = v_p$$

$$v_o = v_p \left(1 + \frac{R_3}{R_2}\right) - v_{S2} \frac{R_3}{R_2}$$

proportional
to v_p

The change in v_o vs change in v_p :

$$\Delta v_o = \Delta v_p \left(1 + \frac{R_3}{R_2}\right)$$

constant

$$\Delta v_p = v_p(373^\circ\text{K}) - v_p(273^\circ\text{K}) = 10V - 6V = 4V$$

$$\Delta v_o = v_o(373^\circ\text{K}) - v_o(273^\circ\text{K}) = 10V - 0V = 10V$$

from prob
statement

Sol(n 1.c) cont.

$$\Delta V_o = \Delta V_p \left(1 + \frac{R_3}{R_2}\right) \quad \text{or} \quad 10V = 4V \left(1 + \frac{R_3}{R_2}\right)$$

$$\therefore 1 + \frac{R_3}{R_2} = 2.5 \quad \text{or} \quad \frac{R_3}{R_2} = 1.5$$

Let $R_3 = 15\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$.

$$V_o(273^\circ\text{K}) = 0V = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2} = 6V(2.5) - V_{S2}(1.5)$$

from prob statement

$$\text{or } V_{S2} = \frac{6(2.5)V}{1.5} \quad \text{or} \quad V_{S2} = 10V$$

d) $R_T(323^\circ\text{K}) = 2490 e^{1120 \left(\frac{1}{323} - \frac{1}{300}\right)} = 1.9\text{ k}\Omega$


$$V_p = 15V \cdot \frac{2.4\text{ k}\Omega}{2.4\text{ k}\Omega + 1.9\text{ k}\Omega} = 8.37V$$

$$V_o = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2} = 8.37(2.5) - 10(1.5) V$$

$$V_o(323^\circ\text{K}) = 5.9V$$

Off by 18% from linear value
of 5V.

1. (75 points)

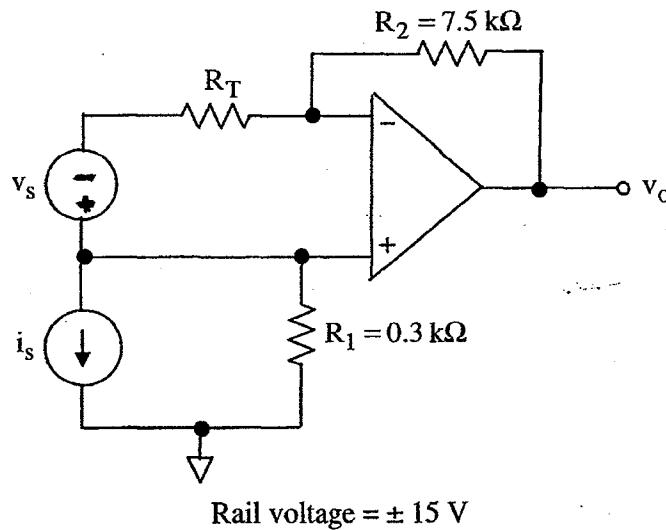

Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2.625 \text{ k}\Omega$, $\beta = 1200^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.

Pts

- 30 a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . Hint: Use superposition.

10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).

15 c. Determine a value for v_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$


10 d. Using your answer to (c), determine a value of i_s such that

$$v_o(T = 273^\circ\text{K}) = 0 \text{ V}.$$

10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

Sol'n: 1.a) Use superposition

Case I: v_s on, i_s off = open

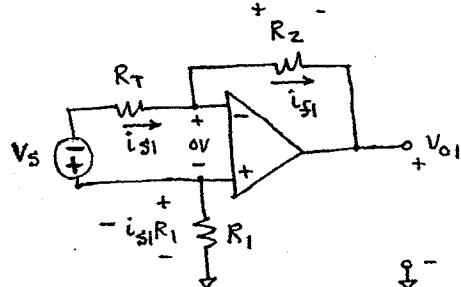

Negative feedback \Rightarrow OV across + and - terminals.

From v loop around v_s , R_T , and +- terminals,

$$\text{we have } i_{s1} = -\frac{v_s}{R_T}.$$

From v loop around R_1 , +- terminals, R_2 , and v_o ,


$$\text{we have } -i_{s1}R_1 + \text{OV} - i_{s1}R_2 - v_{o1} = \text{OV}$$

Now use $i_{s1} = i_{f1}$ and solve for v_{o1} :

$$-\frac{v_s}{R_T} R_1 + \text{OV} - \frac{v_s}{R_T} R_2 - v_{o1} = \text{OV}$$

$$v_{o1} = v_s \frac{R_1 + R_2}{R_T}$$

Case II: i_s on, v_s off = wire

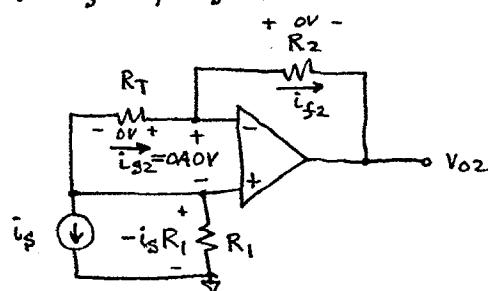

We OV across $R_T \Rightarrow i_s = 0$.

Since $i_{s2} = i_{f2} = 0A$, we have $v_{o2} = v_- = v_+$

$$v_+ = -i_s R_1 \Rightarrow v_{o2} = -i_s R_1$$

Sum

$$v_o = v_{o1} + v_{o2} = v_s \frac{R_1 + R_2}{R_T} - i_s R_1$$

sol'n: 1. b)

$$R_T(273^\circ\text{K}) = 2.625 \text{ k}\Omega$$

$$1200^\circ\text{K} \left(\frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)$$

$$R_T(273^\circ\text{K}) \doteq 3.9 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2.625 \text{ k}\Omega$$

$$1200^\circ\text{K} \left(\frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)$$

$$R_T(373^\circ\text{K}) \doteq 1.2 \text{ k}\Omega$$

$$\begin{aligned} c) 1V &= V_o(373^\circ\text{K}) - V_o(273^\circ\text{K}) = V_S \frac{(R_1 + R_2)}{R_T(373^\circ\text{K})} - i_S R_1 \\ &\quad - \left(V_S \frac{R_1 + R_2}{R_T(273^\circ\text{K})} - i_S R_1 \right) \\ &= V_S (R_1 + R_2) \left(\frac{1}{R_T(373^\circ\text{K})} - \frac{1}{R_T(273^\circ\text{K})} \right) \\ &= V_S (0.3 \text{ k}\Omega + 7.5 \text{ k}\Omega) \left(\frac{1}{1.2 \text{ k}\Omega} - \frac{1}{3.9 \text{ k}\Omega} \right) \\ V_S &= \frac{1.2 \text{ k}\Omega (1 - 3.9 \text{ k}\Omega)}{7.8 \text{ k}\Omega} V = \frac{0.3 \text{ k}\Omega \cdot 4 \parallel 13}{0.3 \text{ k}\Omega \cdot 26} V = \frac{-4 \parallel 13}{(4 - 13) \cdot 26} V \end{aligned}$$


$$V_S = \frac{2}{9} V$$

$$d) 0V = V_o(273^\circ\text{K}) = V_S \frac{R_1 + R_2}{R_T(273^\circ\text{K})} - i_S R_1 = \frac{2}{9} V \frac{7.8 \text{ k}\Omega}{3.9 \text{ k}\Omega} - i_S 0.3 \text{ k}\Omega$$


$$i_S 0.3 \text{ k}\Omega = \frac{4}{9} V \Rightarrow i_S = \frac{4}{9} \frac{1V}{0.3 \text{ k}\Omega} = \frac{4}{2.7} \text{ mA}$$

$$i_S \doteq 1.48 \text{ mA} \approx 1.5 \text{ mA}$$
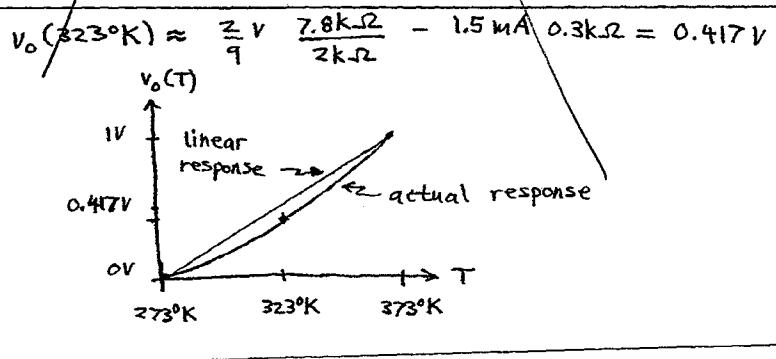
$$e) R_T(323^\circ\text{K}) = 2.625 \text{ k}\Omega e^{1200^\circ\text{K} \left(\frac{1}{323^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 1.97 \text{ k}\Omega \approx 2 \text{ k}\Omega$$



sol(n: 1.a)

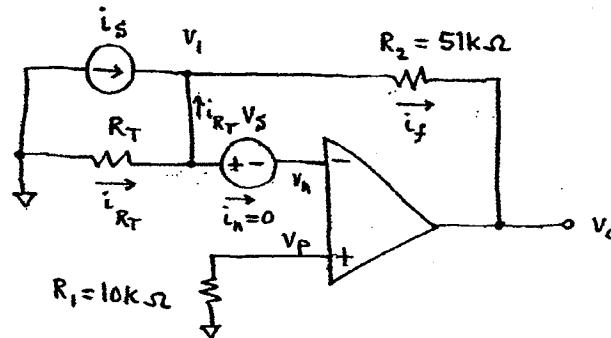

- Find \$v_p\$: \$v_p = 0V\$ since no current in \$R_1\$ so no v-drop for \$R_1\$.

$$v_h = v_p = 0V$$

- Find \$i_f\$ on left side (total current into \$v_1\$ node from \$i_s\$ and \$R_T\$)

\$v_1 = v_h + v_s = v_s\$, and no current flows thru \$v_s\$ since no current flows into op-amp.

$$\therefore i_f \text{ on left side} = i_s + i_{R_T} = i_s + \frac{0 - v_1}{R_T} = i_s + \frac{-v_s}{R_T}$$

- Find \$i_f\$ on right side

$$i_f \text{ on right side} = \frac{v_1 - v_o}{R_2} = \frac{v_s - v_o}{R_2}$$

- Set \$i_f\$ on left side = \$i_f\$ on right side

$$i_s - \frac{v_s}{R_T} = \frac{v_s - v_o}{R_2} \quad \text{or}$$

$$v_o = v_s \left(1 + \frac{R_2}{R_T} \right) - i_s R_2$$

verify: Superposition \$v_s = 0 \Rightarrow i_{R_T} = 0 \Rightarrow v_o = 0V - i_s R_2 \checkmark

$$i_s = 0 \quad i_{R_T} = -\frac{v_s}{R_T} = i_f = \frac{v_s - v_o}{R_2}$$

Same as having \$v_p = v_s \quad v_o = v_s \left(1 + \frac{R_2}{R_T} \right) \checkmark


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000

HOMEWORK #9

Spring 2005

1.

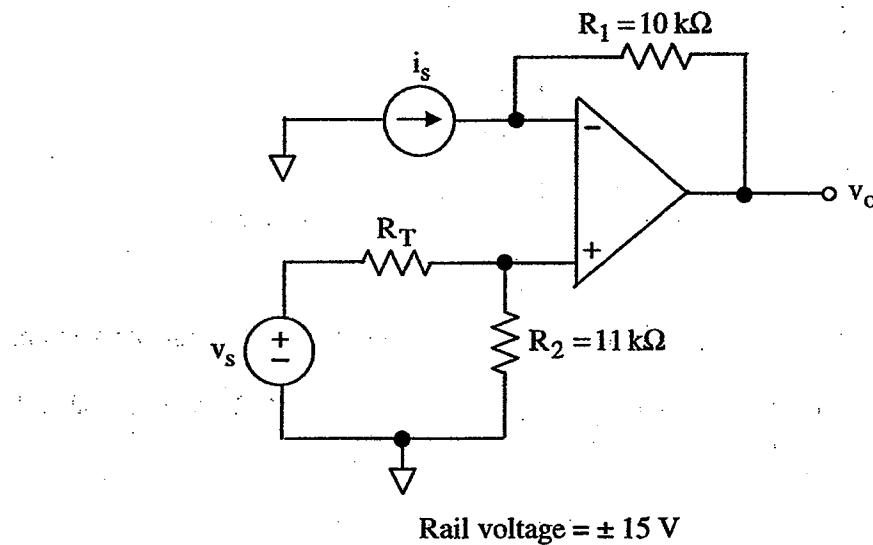


Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 12.25 \text{ k}\Omega$, $\beta = 170^\circ\text{K}$, and T is temperature in $^\circ\text{K}$. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . Hint: Use superposition.

2. a. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- b. Determine a value for v_s such that $v_o(T = 373^\circ\text{K}) = v_o(T = 273^\circ\text{K}) = 1\text{V}$
- c. Using your answer to (c), determine a value of i_s such that $v_o(T = 273^\circ\text{K}) = 0\text{ V}$.
- d. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

sol'n: 1.

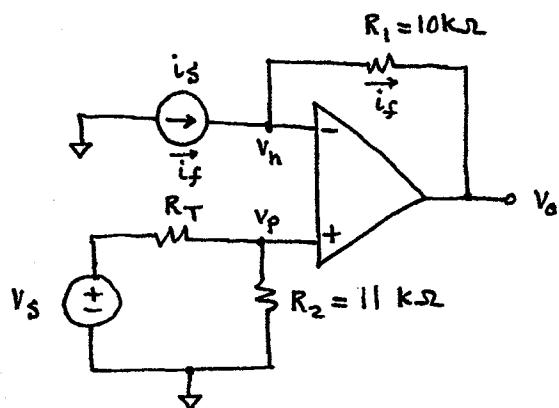Find V_p :

$$V_p = V_s \frac{R_2}{R_2 + R_T} \quad \text{V-divider}$$

$$V_h = V_p$$

Find i_f on left: $i_f = i_s$

$$\text{Find } i_f \text{ on right: } i_f = \frac{V_h - V_o}{R_1}$$

Set i_f 's equal and use $V_h = V_p$

$$i_s = \frac{V_h - V_o}{R_1} \quad \text{or} \quad V_o = V_h - i_s R_1$$

$$V_o = V_s \frac{R_2}{R_2 + R_T} - i_s R_1$$

2.a) ~~$R_T(273^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{\frac{170^\circ\text{K}}{273^\circ\text{K}} \left(\frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 13 \text{ k}\Omega$~~

~~$R_T(373^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{\frac{170^\circ\text{K}}{373^\circ\text{K}} \left(\frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 11 \text{ k}\Omega$~~

~~$R_T(273^\circ\text{K}) = 13 \text{ k}\Omega$~~

~~$R_T(373^\circ\text{K}) = 11 \text{ k}\Omega$~~

b) ~~$\Delta V = V_o(373^\circ\text{K}) - V_o(273^\circ\text{K}) = V_s \frac{R_2}{R_2 + R_T(373^\circ\text{K})} - i_s R_1$~~


~~$- \left(V_s \frac{R_2}{R_2 + R_T(273^\circ\text{K})} - i_s R_1 \right)$~~

~~$\Delta V = V_s \cdot 11 \text{ k}\Omega \cdot \left(\frac{1}{11 \text{ k}\Omega + 11 \text{ k}\Omega} - \frac{1}{11 \text{ k}\Omega + 13 \text{ k}\Omega} \right)$~~

$$V_s = \frac{\Delta V}{11 \text{ k}\Omega} \frac{22 \text{ k}\Omega \cdot 24 \text{ k}\Omega}{24 \text{ k}\Omega - 22 \text{ k}\Omega} = 24 \text{ V}$$

9

1. (75 points)

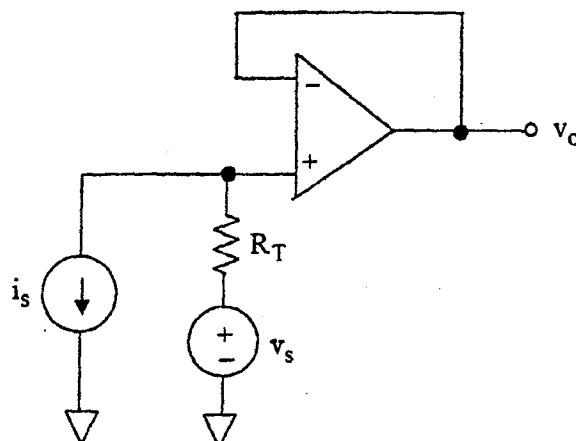

Rail voltage = ± 15 V

Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by


$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2.8 \text{ k}\Omega$, $\beta = 1300^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.


- Pts 6
a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , and R_T . Hint: Use superposition.
- 10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 15 c. Determine a value for i_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$
- 10 d. Using your answer to (c), find the numerical value of v_s such that $v_o(T = 273^\circ\text{K}) = 0\text{ V}$.
- 10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

(10)

sol'n: 1.g) Superposition case I: i_S on, v_S off = wire

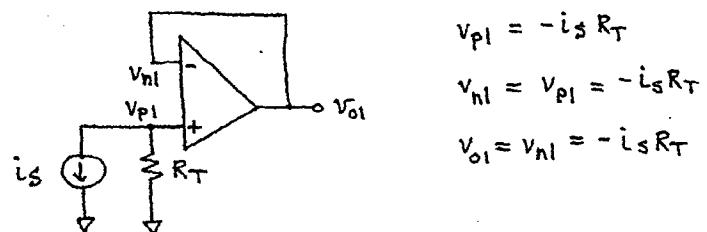

case II: i_S off = open, v_S on

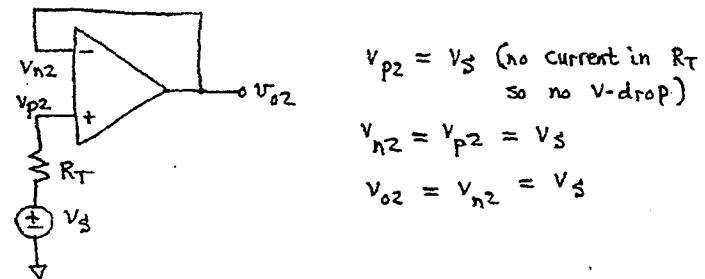

$$v_o = v_{o1} + v_{o2}$$

$$v_o = -i_S R_T + v_S$$

b) $R_T(273^\circ\text{K}) = 2.8 \text{ k}\Omega$ $\frac{1}{R_T(273^\circ\text{K})} = \frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}}$

$$R_T(273^\circ\text{K}) = 4.3 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2.8 \text{ k}\Omega$$
 $\frac{1}{R_T(373^\circ\text{K})} = \frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}}$

$$R_T(373^\circ\text{K}) = 1.2 \text{ k}\Omega$$

c) Change in v_o : $\Delta v_o = -i_S \Delta R_T$ $\Delta \equiv \text{"change"}$
 (for $\Delta T = 100^\circ\text{K}$) $= 1V$ (desired) (v_S constant does not change with T)

$$\Delta R_T = 1.2 \text{ k}\Omega - 4.3 \text{ k}\Omega$$

$$\Delta R_T = -3.1 \text{ k}\Omega$$

$$\therefore i_S = \frac{-\Delta v_o}{\Delta R_T} = \frac{-1V}{-3.1 \text{ k}\Omega} = 0.323 \text{ mA}$$

$$i_S = 0.323 \text{ mA}$$

d) $v_o(273^\circ\text{K}) = 0V = -0.323 \text{ mA} \cdot 4.3 \text{ k}\Omega + v_S$
 $-i_S \cdot R_T$


$$\therefore v_S = 0.323 \text{ mA} \cdot 4.3 \text{ k}\Omega$$

$$v_S = 1.39 \text{ V or } 1.4 \text{ V}$$

HW #10 cont.


Su 2005

2.

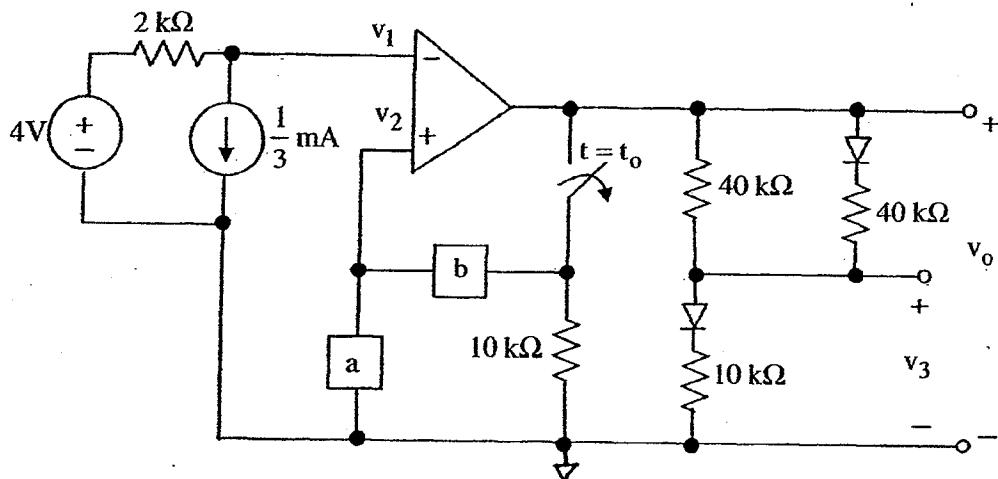

Rail voltages = ± 10 V

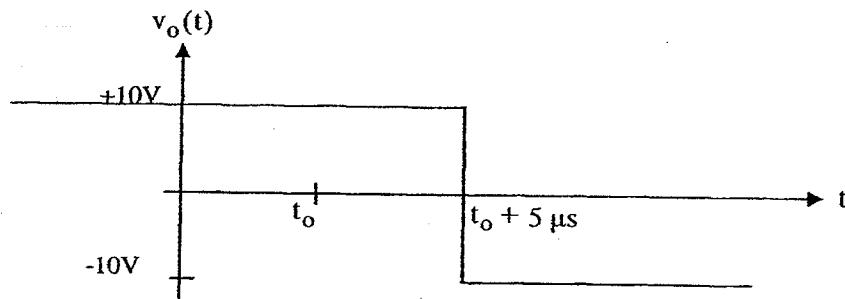After being closed for a long time, the switch closes at $t = t_0$.



- Choose either an R or L to go in box a and either an R or L to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_2(t)$, showing numerical values appropriately.
- Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 5 \mu s$, and for $t_0 + 5 \mu s < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

HW #10 Cont.

ECE 1000

Su 05


Soln: 2.9) Consider possibilities.

$a=R$ and $b=R$ Doesn't work. v_2 would change at t_0 but never again. Delay of $5\mu s$ not possible.

$a=L$ and $b=L$ Doesn't work. Before time t_0 , the L's look like wires and would short v_o to ref. But $v_o = \pm v_{rail} = \pm 10V$. Thus, we would have an invalid circuit.

$a=L$ and $b=R$

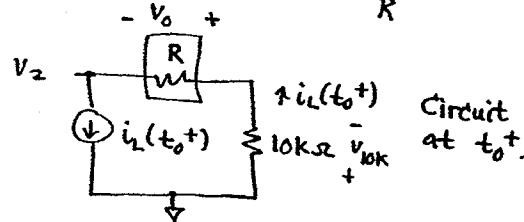Before t_0 , the L looks like a wire, and $v_2 = 0V$. $i_L(t_0^-) = \frac{v_o}{R} = i_L(t_0^+)$.



At t_0^+ , the current in R will be $i_L(t_0^+) = i_L(t_0^-) = \frac{v_o}{R}$ or the same as at t_0^- . Thus, the v-drop for R at t_0^+ will be v_o . Current $i_L(t_0^+)$ flowing in the $10k\Omega$ will cause a voltage drop in series with the drop for R, resulting in a very negative voltage at v_2 . This would cause v_o to go low at $t = t_0^+$ rather than after a delay of $5\mu s$.
 \therefore This case doesn't work.

HW #10 Cont.

Su 05


ECE 1000

Sol'n: 2.a) cont.

$$a=R \text{ and } b=L$$

$$i_L(t_0^-) = \frac{v_0}{R} \text{ as in prev case.}$$
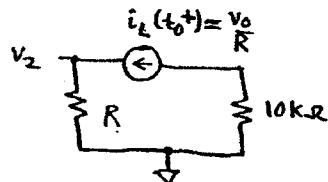
$$\text{At } t_0^+ \text{ with } i_L(t_0^+) = i_L(t_0^-) = \frac{v_0}{R} =$$



$$\text{we have } v_2(t_0^+) = \underbrace{\frac{v_0}{R}}_{i_L(t_0^+)} \cdot R = v_0.$$

So v_2 doesn't change immediately.
This will work!

For $t \rightarrow \infty$ we will have $v_2 = 0V$
since there is no power source.


Using the general formula for
 $v_2(t)$, we have:

$$v_2(t) = v_2(t \rightarrow \infty) + [v_2(t_0^+) - v_2(t \rightarrow \infty)] e^{-t/R_{Th}}$$

$\stackrel{0V}{\text{||}} \quad \stackrel{v_0}{\text{||}} \quad \stackrel{0V}{\text{||}}$

$$\text{where } R_{Th} = 10\text{k}\Omega + R$$

$$v_2(t) = v_0 e^{-t/(10k\Omega + R)}$$

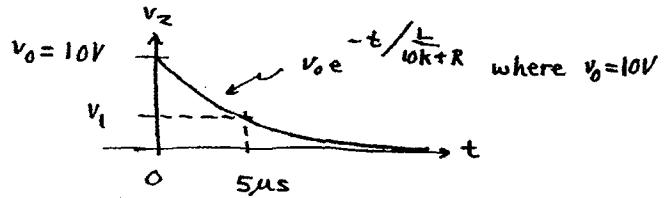

The output, v_2 , will drop at $t_0 + 5\mu\text{s}$ if $v_2(t_0 + 5\mu\text{s}) = v_1$.

[Assume $t_0 = 0$ for convenience.]


Now find v_1 .

HW #10 Cont.

ECE 1000

Su 05

sol'n: 2.a) cont.

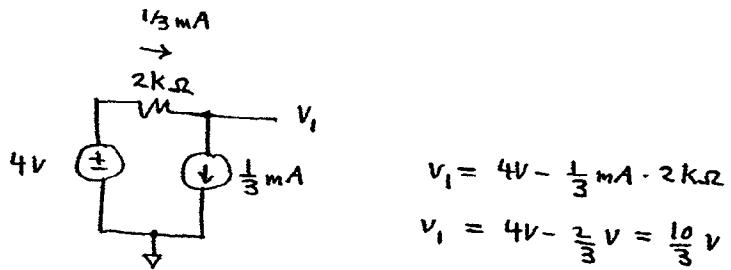

$$\therefore \text{we want } V_2(5\mu s) = V_1 = \frac{10}{3}V$$

$$\text{or } 10V e^{-\frac{5\mu s}{10k\Omega+R}} = \frac{10}{3}V$$

$$-\frac{5\mu s}{10k\Omega+R} = \ln \frac{1}{3} \doteq -1.1$$

$$\text{or } 5\mu s = 1.1 \frac{L}{10k\Omega+R}$$

If we use $R = 12k\Omega$ we get a convenient value for L . Many solutions for R and L will work, however.


$$R = 12k\Omega \text{ gives } L = 5\mu s \cdot \frac{10k\Omega + 12k\Omega}{1.1}$$

$$L = 5\mu s \cdot 20k\Omega = 100mH$$


$$R = 12k\Omega \quad L = 100mH$$

one solution
among many.

b)

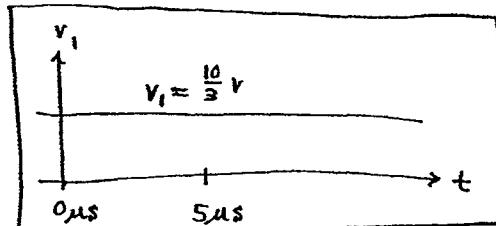

c)

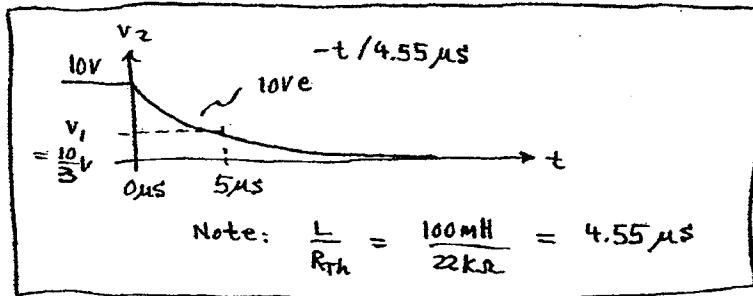


HW #10 Cont.



ECE 1000

Su 05

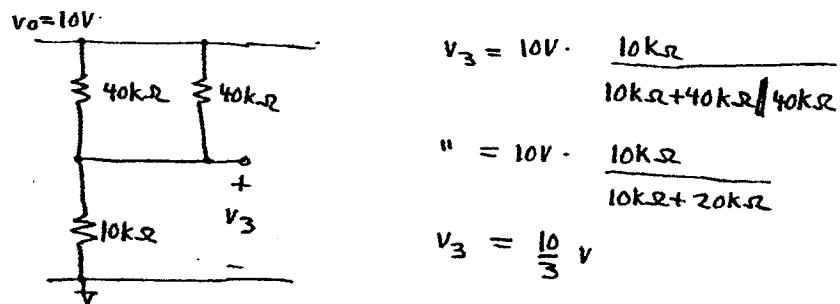sol'n: 2.d) For $v_o = +10V$, both diodes are forward biased and look like wires.



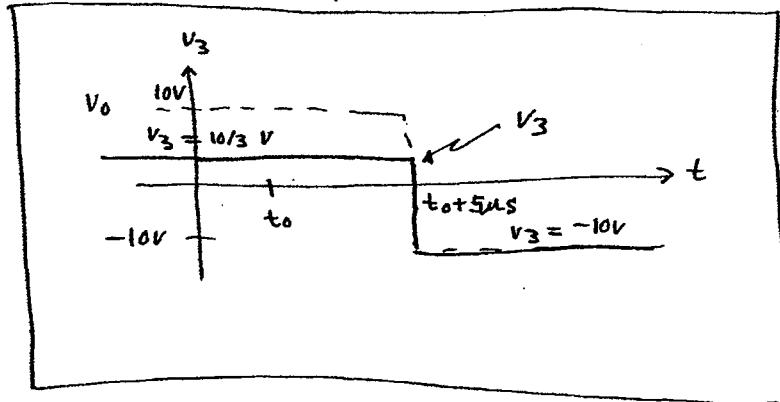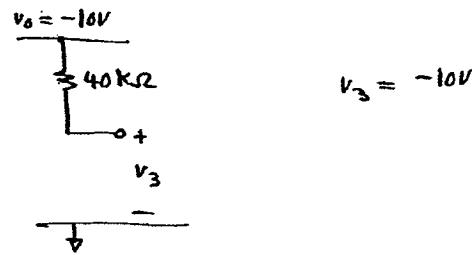For $v_o = -10V$, both diodes are reverse biased and look like open circuits.




UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000


HOMEWORK #10

Spring 2005

1.

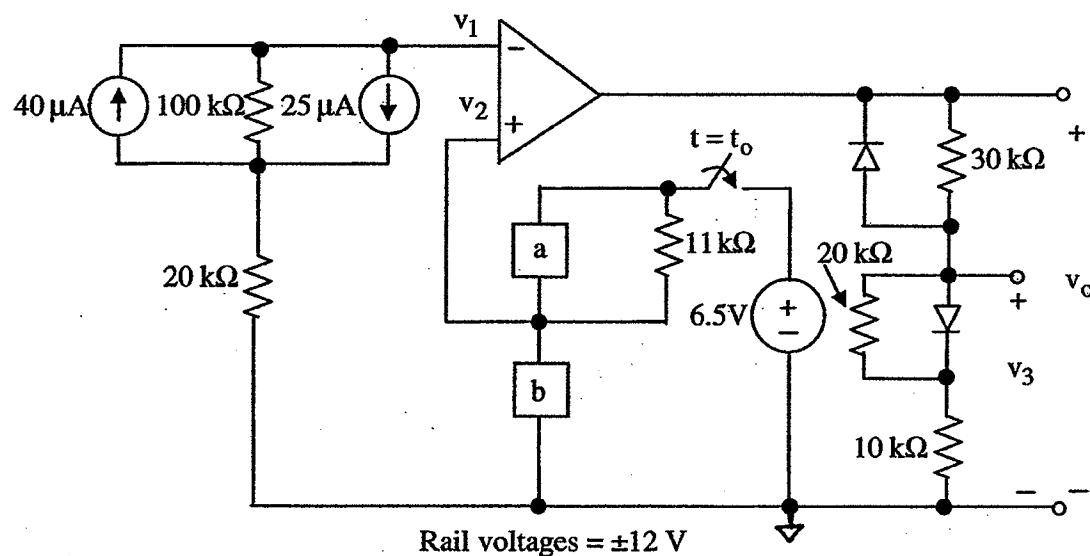

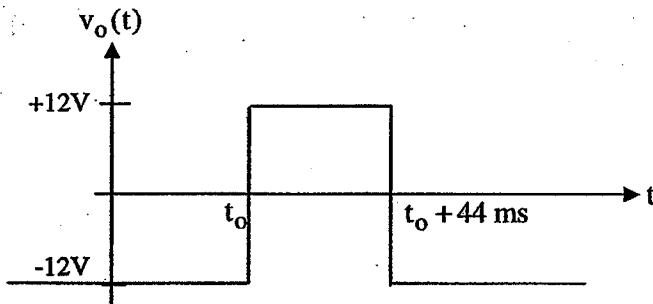After being open for a long time, the switch closes at $t = t_0$.



- a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value. **Hint:** Use $v_2(t \rightarrow \infty) = 1\text{V}$
 - b. Sketch $v_1(t)$, showing numerical values appropriately.
2. a. Sketch $v_2(t)$, showing numerical values appropriately.
- b. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 44\text{ ms}$, and for $t_0 + 44\text{ ms} < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n: 1.a) Consider possibilities.

$a=R$ and $b=R$: v_2 would change at time $t=t_0$ but never change again. Thus, v_o could not go high and then low again.

$a=C_1$ and $b=C_2$: Before $t=t_0$, there would be no path for C_2 in b to discharge. Thus, we would need to know $v_{C_2}(t=t_0^-)$. We would also have $v_{C_1}(t=t_0^-) = 0V$ since C_1 will discharge thru the R in parallel with it.

When the switch closes, we have an invalid circuit if $v_{C_2}(t_0^+) + v_{C_1}(t_0^+) \neq 6.5V$. This means we must have $v_{C_2}(t_0^+) = v_c(t_0^-) = 6.5V$ since $v_{C_1}(t_0^+) = v_c(t_0^-) = 0V$.

But if $v_{C_2}(t_0^+) = 6.5$, nothing changes when the switch closes. Thus, we could not get a waveform that goes high and then low again.

$a=R$ and $b=C$: As in the case of $a=C_1$ and $b=C_2$, we would have some value of $v_c(t_0^-) = v_c(t_0^+)$. Since $v_2 = v_c(t_0^+)$ at $t=t_0^+$, v_o would not change at t_0 . Thus, this will not work.

$a=C$ and $b=R$: The C in a will discharge thru the R in parallel with it. $\therefore v_c(t_0^-) = 0V$. Also, no current flows in R for $t < t_0$ because there is no closed circuit path in which current could flow. Thus, $v_2(t_0^-) = i \cdot R = 0V$.

Sol'n: 1.a) cont.

At $t=t_0^+$, we have $v_2(t_0^+) = 6.5V - v_C(t_0^+)$
or $v_2(t_0^+) = 6.5V$ since $v_C(t_0^+) = v_C(t_0^-) = 0V$.

Thus, v_2 jumps from 0V to 6.5V at t_0 .

If $v_2(t_0^+) > v_1$, then v_o would go high,
(assuming $v_1 > 0V$ and $v_1 < 6.5V$).

After t_0 , C will charge and v_2 will start to drop. If v_2 eventually drops below v_1 , then v_o will go low again.

Thus, this will work.


Now find values of R and C:

v_1 : Since no current flows into the - input of the op amp, no current flows thru the $20k\Omega$ resistor (lower left).

Combining the parallel current sources, we have $40\mu A - 25\mu A = 15\mu A$. This current flows thru the $100k\Omega$ to produce voltage $15\mu A \cdot 100k\Omega = 1.5V$.

$$\therefore v_1 = 2.5V \text{ (constant)}$$

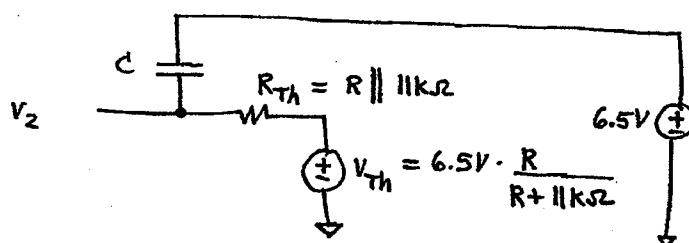v_2 : For $t > t_0$, we use a Thevenin equivalent circuit for the $6.5V$ source, the $11k\Omega$, and R in b.



(19)


Sol'n: 1.a) cont. We use the general RC sol'n for $v_2(t)$:

$$v_2(t) = v_2(t \rightarrow \infty) + [v_2(t_0^+) - v_2(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

To find $v_2(t \rightarrow \infty)$, we observed that, when C is charged, no current flows in R_{Th} .

$$\text{Thus } v_2(t \rightarrow \infty) = V_{Th} = 6.5V \cdot \frac{R}{R+11k\Omega} < 6.5V.$$

From earlier, $v_2(t_0^+) = 6.5V$.

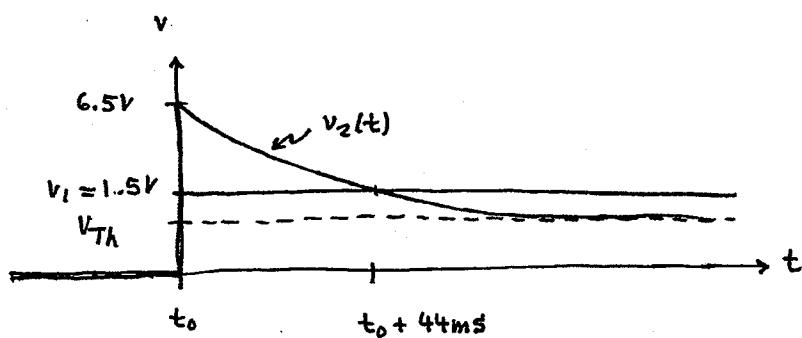

Any $V_{Th} < V_1$ will suffice. For convenience,

$$\text{let } V_{Th} = 1V = 6.5V \cdot \frac{R}{R+11k\Omega} \Rightarrow R = 2k\Omega$$

Assume $t_0 = 0$. For v_0 to switch at $t = 44ms$, we have $v_2(44ms) = V_1 = 1.5V$

$$\text{or } 1V + [6.5V - 1V] e^{-44ms/R_{Th}C} = 0.5V$$

$$\text{or } 5.5V e^{-44ms/R_{Th}C} = 0.5V \quad \text{where}$$

$$R_{Th} = R \parallel 11k\Omega = 2k \parallel 11k\Omega = \frac{22}{13} k\Omega.$$


Take \ln of both sides of exponential RC eqn:

$$-\frac{44ms}{\frac{22}{13} k\Omega \cdot C} = \ln \frac{0.5V}{5.5V} \doteq -2.39$$


$$C = \frac{2}{2.39} \frac{k\Omega}{13} \mu F = 10.9 \mu F$$

$$C = 11 \mu F$$

Sol'n: 1.b) $v_1(t) = 1.5V$ constant

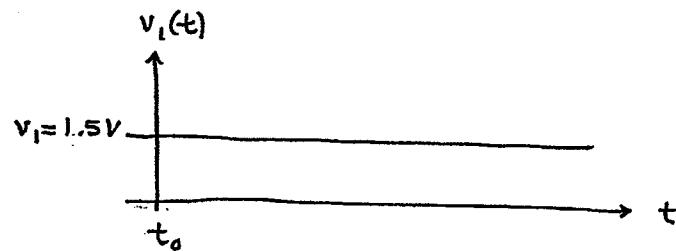

2.a)

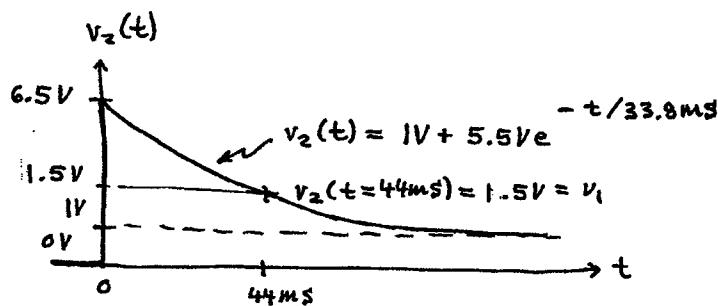


$$\text{Note: } R_{TH} C = \frac{22}{13} \text{ k}\Omega \cdot 20\mu\text{F} = 33.8 \text{ ms}$$

Note: Assume $t_0 = 0$.

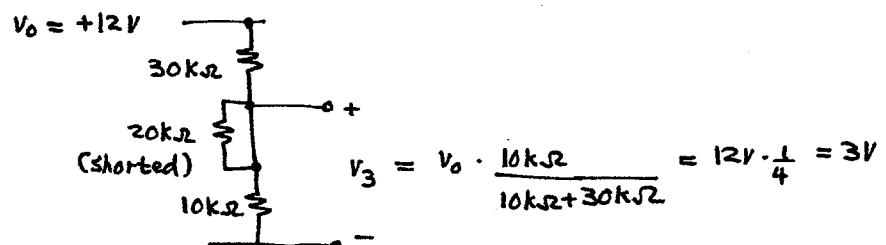
b) When $v_o = +12V$, top diode is reverse biased = open.

The bottom diode is forward biased = wire.




when $v_o = -12V$, top diode is forward biased = wire.


Thus, v_o is shorted to $-12V$.

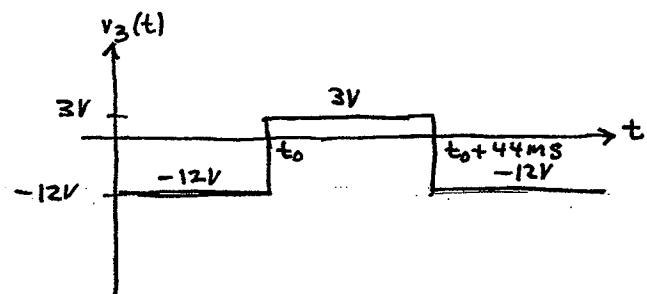

2. (65 points)

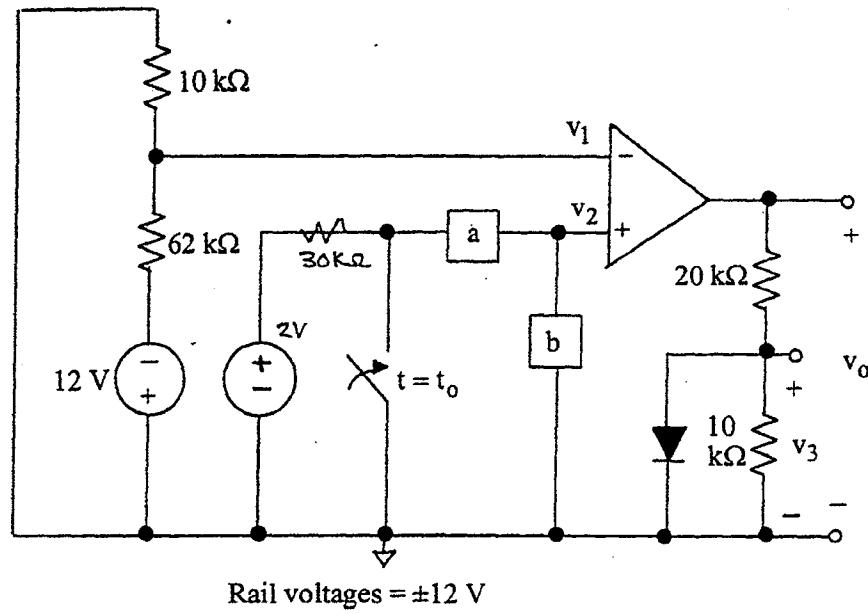

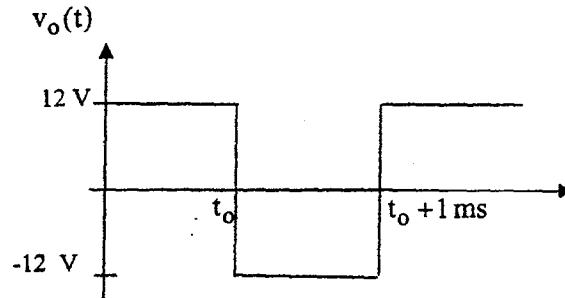After being open for a long time, the switch closes at $t = t_0$.



Pts

- 35 a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value.
- 5 b. Sketch $v_1(t)$, showing numerical values appropriately.
- 15 c. Sketch $v_2(t)$, showing numerical values appropriately.
- 10 d. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 1$ ms, and for $t > t_0 + 1$ ms. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: 2. a) At $t = t_0^-$: $v_1 = -12V \frac{10k\Omega}{10k\Omega + 6k\Omega} V$ -divider

$$v_1 = -\frac{5}{3}V \quad \text{Actually, } v_1 = -\frac{5}{3}V \text{ for all } t$$

$$v_o = +12V \Rightarrow v_2 > v_1 = -\frac{5}{3}V$$

Consider $a=R, b=R$: v_o would never switch because v_2 would be 0V after switch closed, and $v_2 > v_1$ for all time will not work.

Consider $a=C, b=C$: C's will charge to $v_{tot} = 2V$.

Part of 2V across a, part across b.

When switch closes, the C's instantly charge to $v_{tot} = 2V$.

Then their voltages remain fixed.
 $\therefore v_o$ would not switch after 1ms.
 Will not work.

Consider $a=R, b=C$: C will charge to 2V. $v_2 = 2V$

When switch closes, v_2 will start at 0V and charge toward 2V.


$v_2 > v_1$ for all time.

v_o never switches.

Will not work.


Consider $a=C, b=R$: C will charge to 2V at t_0^-

$v_2 > v_1$ so $v_o = +12V$ at t_0^- ✓

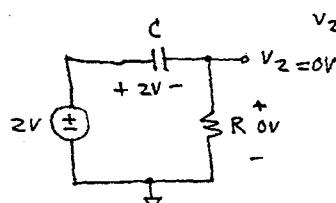

when switch closes, v_c will stay at 2V for $t=t_0^+$:

t_0^+ :

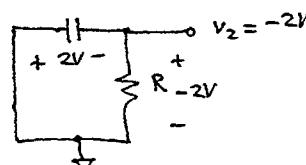

Thus, v_2 drops to -2V.


Then $v_2 < v_1$ and v_o drops to -12V. ✓

$t > t_0$: C charges to 0V and v_2 climbs toward 0V.

We want $v_2 = v_1 = -\frac{5}{3}V$ at $t_0 + 1ms$. ✓

works

sol'n: 2.a) (cont.)

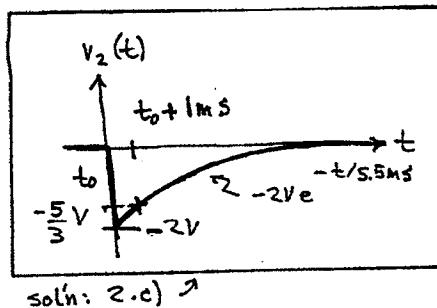

Let $C = 1\mu\text{F}$, $R = 5.5\text{k}\Omega$ or $5.6\text{k}\Omega$ (standard value)


Any $RC = 5.5\text{ ms}$ acceptable if $1\text{pF} < C < 1\text{F}$
and $1\text{M}\Omega < R < 1\text{G}\Omega$.

Note: If R is $\frac{1}{8}\text{W}$ then we would really want $\max i_R^2 R < \frac{1}{8}\text{W}$.

$$\max i_R^2 = \left(\frac{2V}{R}\right)^2 \Rightarrow \max i_R^2 R = \frac{4V^2}{R} < \frac{1}{8}\text{W}$$

$$\therefore R > \frac{4V^2}{1/8\text{W}} = 32\text{M}\Omega \text{ required.}$$


2.b) $v_1 = -\frac{5}{3}V$ for all t

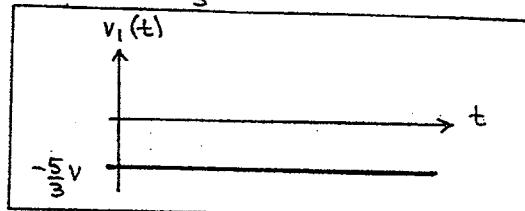

2.c) See plot of $v_2(t)$ in sol'n to 2.a), above.

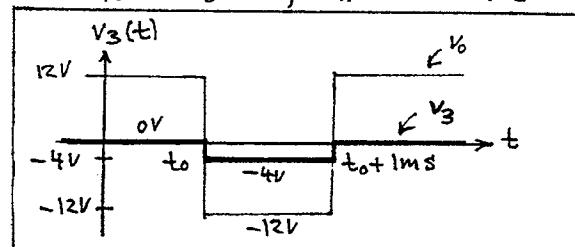
2.d) When $v_o > 0\text{V}$, diode forward biased = wire. $\therefore v_3 = 0\text{V}$

when $v_o < 0\text{V}$, diode reverse biased = open. $\therefore v_3 = v_o \frac{10\text{k}\Omega}{10\text{k}\Omega + 20\text{k}\Omega}$




$$v_3 = -12V \cdot \frac{1}{3} = -4V$$

2. (70 points)

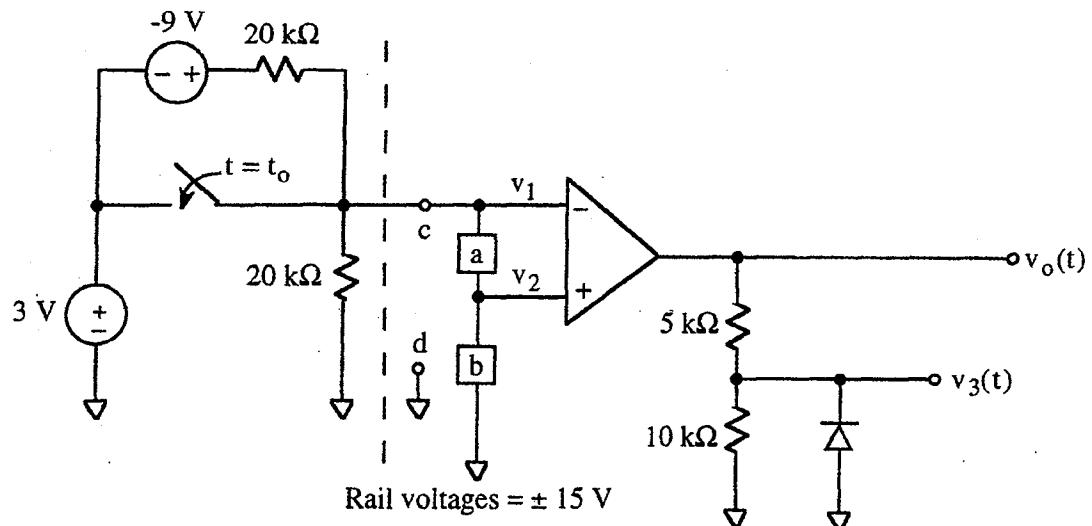

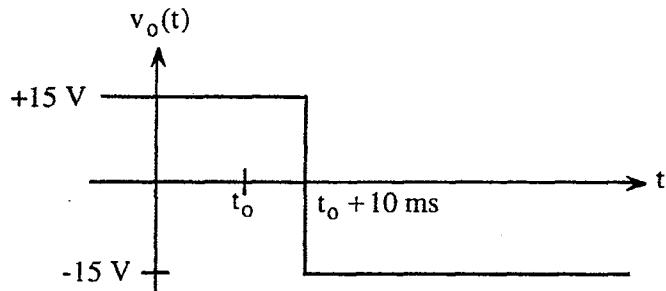
After being open for a very long time, the switch closes at $t = t_0$.



- | | |
|-----|--|
| Pts | |
|-----|--|
- 10 a. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t < t_0$.
- 10 b. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t > t_0$.
- 20 c. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value.
- 20 d. Using the elements found in (b), sketch $v_2(t)$. Show numerical values appropriately.
- 10 e. Sketch $v_3(t)$. Show numerical values for $t < t_0$, $t_0 < t < t_0 + 10$ ms, and $t > t_0 + 10$ ms. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n 2.4) $t < t_0$ switch is open

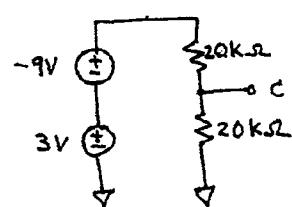


$$V_{Th} = (3V - 9V) \frac{20k\Omega}{20k\Omega + 20k\Omega} = -6V \cdot \frac{1}{2} = -3V$$


C use V-divider

$$R_{Th} = R \text{ looking into } C \text{ with } V \text{ sources shorted}$$
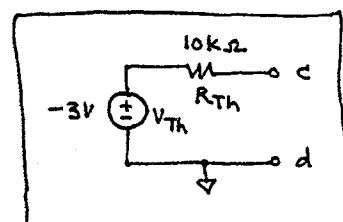
$$= 20k\Omega \parallel 20k\Omega = 10k\Omega$$



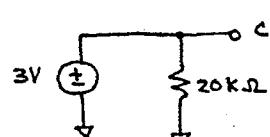
b) $t > t_0$ switch is closed ($-9V$ source and $20k\Omega$ bypassed)



$$V_{Th} = 3V \text{ since } C \text{ connected to } 3V \text{ source}$$

$$R_{Th} = R \text{ looking into } C \text{ with } 3V \text{ source shorted}$$
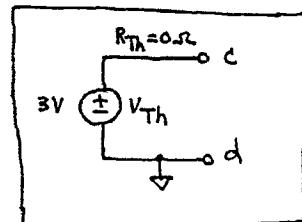
$$= 0\Omega \text{ (20k}\Omega \text{ bypassed by short)}$$




c) R in a and C in b would immediate switching: wrong

\therefore C in a and R in b must be correct.

$t < t_0$ circuit:

$$(t = t_0^-)$$

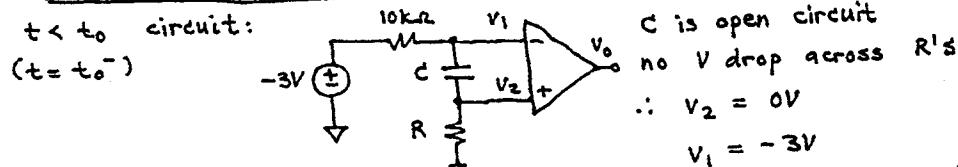


C is open circuit
no V drop across R's
 $\therefore V_2 = 0V$

$$V_1 = -3V$$

$$V_1 < V_2 \Rightarrow V_0 = +15V \text{ (rail)}$$

$t = t_0^+$ circuit:

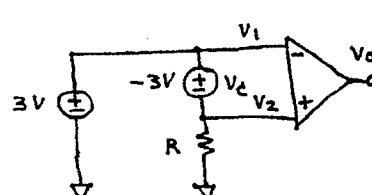


C acts like $-3V$ source

$$\therefore V_1 = 3V$$

$$V_2 = 3V - -3V = 6V$$

$$V_1 < V_2 \Rightarrow V_0 = +15V \text{ (rail)}$$

$t \rightarrow \infty$ circuit:

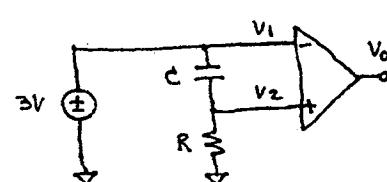

C acts like open circuit
no V drop across R

$$\therefore V_1 = 3V$$

$$V_2 = 0V$$

$$V_1 > V_2 \Rightarrow V_0 = -15V \text{ (rail)}$$

sol'n z.e) cont. Let $t_0 = 0$. Want $v_1 = v_2$ at $\Delta t \equiv 10\text{ms}$ for v_o transition.

$$v_1 = 3V \text{ for } t > t_0 = 0$$

$$v_2 = 3V - v_c \text{ for } t > t_0.$$

$$v_2(t > 0) = v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/RC}$$

$$\text{ " } = 0V + [6V - 0V] e^{-t/RC} = 6V e^{-t/RC}$$


$$\text{We want } v_2(\Delta t) = 3V. \therefore 6V e^{-4t/RC} = 3V$$

$$e^{-4t/RC} = \frac{3V}{6V} = \frac{1}{2} \text{ or } -\frac{4t}{RC} = \ln \frac{1}{2}$$


$$RC = \frac{-\Delta t}{\ln \frac{1}{2}} = \frac{\Delta t}{\ln 2} = \frac{10\text{ms}}{\ln 2} = 14.4 \text{ ms}$$

Use C = 1 \mu\text{F}, R = 14.4 \text{ k}\Omega (15k\Omega is closest standard value)

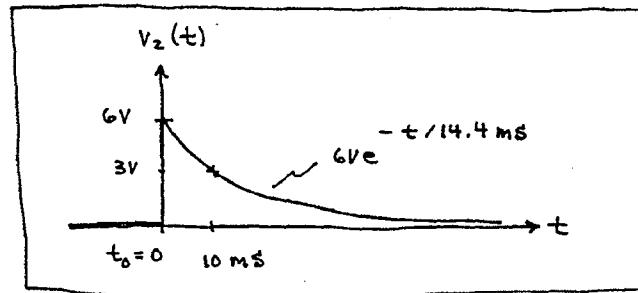
d) $v_2(t < 0) = 0V \quad v_2(t > 0) = 6V e^{-t/14.4\text{ms}} \quad v_2(10\text{ms}) = 3V$



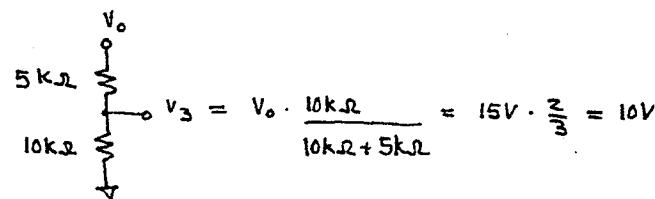
e) When $v_o = +15V$, the diode is reverse biased \Rightarrow open circuit (i.e. disappears)



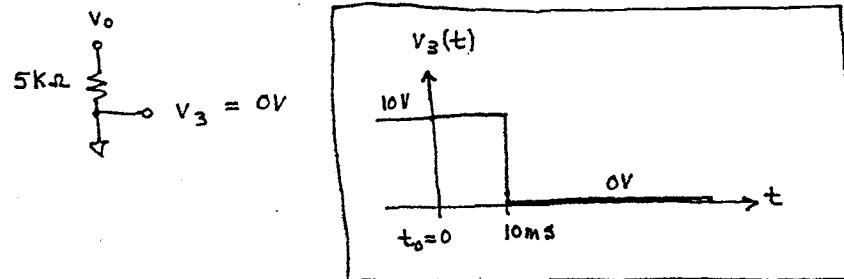When $v_o = -15V$, the diode is forward biased \Rightarrow short




2. (65 points)

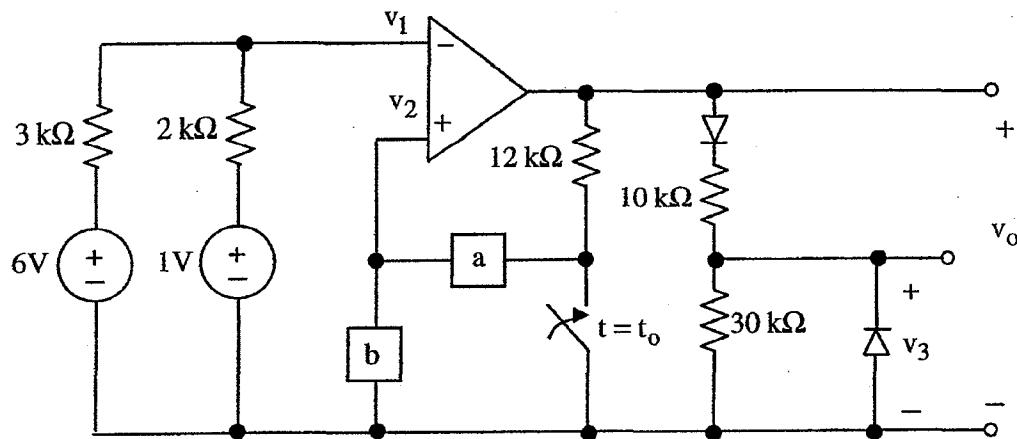

Rail voltages = ± 12 V

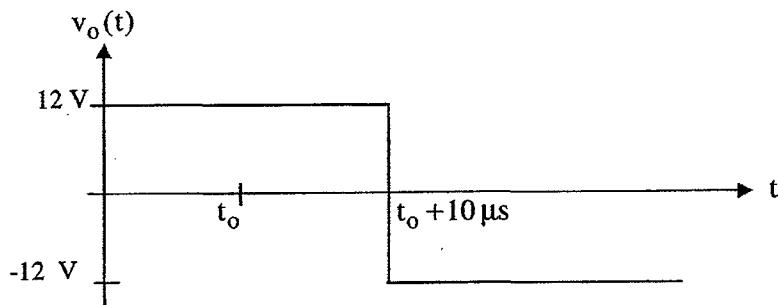After being open for a long time, the switch closes at $t = t_0$.



Pts

- Choose either an R or L to go in box a and either an R or L to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_2(t)$, showing numerical values appropriately.
- Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 10 \mu\text{s}$, and for $t_0 + 10 \mu\text{s} < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n: 2.a) Ignore diode and resistor network on output (since it doesn't affect v_o).

For $t < t_0$, $v_o = +12V \Rightarrow v_2 > v_1$.

Calculate v_1 using node-v method: $\frac{v_1 - 6V}{3k\Omega} + \frac{v_1 - 1V}{2k\Omega} = 0A$


$$v_1 \left(\frac{1}{3k\Omega} + \frac{1}{2k\Omega} \right) = \frac{6V}{3k\Omega} + \frac{1V}{2k\Omega}$$

mult both sides by $6k\Omega$

$$v_1 (2+3) = 6V \cdot 2 + 1V \cdot 3 = 15V, \quad v_1 = \frac{15V}{5} = 3V$$

So we need $v_2 > 3V$.

Circuit model: $v_o = 12V$, switch open

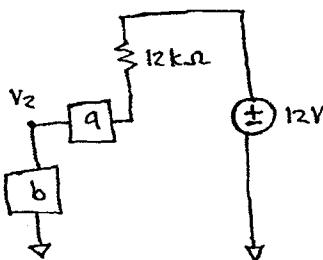

If we have an L, it will be equivalent to a wire.

Consider possibilities:

case I: $a=L$ and $b=L$ $L=\text{wire}$

$v_2 = 0V$ from v divider

Doesn't work.

case II: $a=R$ and $b=L = \text{wire}$

$v_2 = 0V$ from v divider

Doesn't work.

case III: $a=R$, and $b=R_2$

We can choose R_1 and R_2 to achieve $v_2 > 3V$, but we cannot get a delay in v_o dropping from $+12V$ to $-12V$.

case IV: $a=L$ and $b=R$

Since $L=\text{wire}$ and we can pick R , we can achieve $v_2 > 3V$. When switch moves, the L continues to carry same current initially. Thus, $v_2 > v_1$ is sustained for delay. Should work.


sol'n: 2.a) cont. When switch closes, we have RL circuit that determines v_2 . Time constant $\tau = L/R$. Output v_0 drops when v_2 drops below 3V.

As $t \rightarrow \infty$, the L in 'a' acts like a wire and the switch is closed $\Rightarrow v_2(t \rightarrow \infty) = 0V$

Without additional constraints, we may choose any v_2 between 3V and 12V. One choice is

$$v_2(0^-) = 6V. \text{ Using } v\text{-divider of } 12k\Omega \text{ and 'b', } b = 12k\Omega.$$

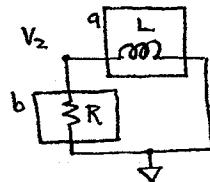We want $v_2(t=10\mu s) = 3V$ so v_0 drops at time $t_0 + 10\mu s$. (Assume $t_0 = 0s$)




$$\begin{aligned} v_2(t > 0) &= v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/\tau} \\ &= 0V + [v_2(0^+) - 0V] e^{-t/\tau} \\ &= v_2(0^+) e^{-t/\tau}, \text{ Now find } v_2(0^+). \end{aligned}$$

Consider $t=0^-$: $L = \text{wire}$ $R = 12k\Omega$

$$i_L(0^-) = \frac{12V}{12k\Omega + 12k\Omega} = \frac{1}{2} mA$$

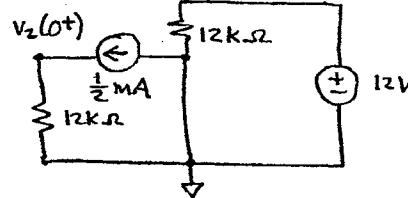$t=0^+$: $L = i$ src where $i_L(0^+) = i_L(0^-) = \frac{1}{2} mA$



$$\begin{aligned} v_2(0^+) &= \frac{1}{2} mA \cdot 12k\Omega \\ v_2(0^+) &= 6V \end{aligned}$$

$$v_2(t > 0) = 6V e^{-t/\tau}$$

We want $v_2(10\mu s) = 3V = 6V e^{-10\mu s/\tau}$


$$\frac{3V}{6V} = \frac{1}{2} = e^{-10\mu s/\tau}, \quad \ln \frac{1}{2} = -10\mu s / \tau$$

$$\tau = \frac{-10\mu s}{\ln \frac{1}{2}} = \frac{10\mu s}{\ln 2} = 14.4\mu s = \frac{L}{R} = \frac{L}{12k\Omega}$$

$$L = 14.4\mu s \cdot 12k\Omega = 173 mH$$


Summary:	$a = L = 173 mH$
	$b = R = 12k\Omega$

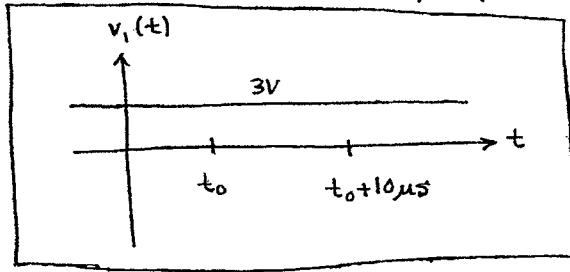Sol'n: 2.b) As shown in sol'n for (a), $v_1(t) = 3V$. It never changes.




c) From sol'n to (a), we have $v_2(t>0) = 6Ve^{-t/14.4\mu s}$



For $v_2(t<0)$, we have $v_2(t<0) = 6V$.

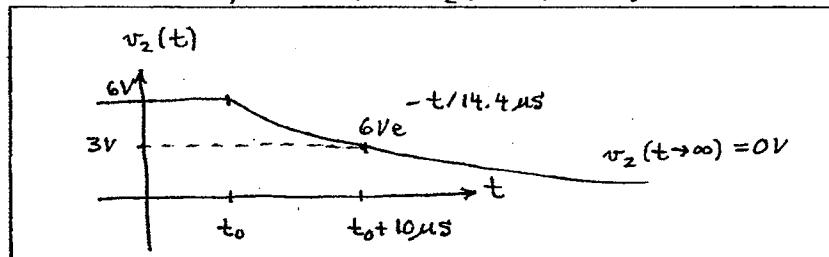

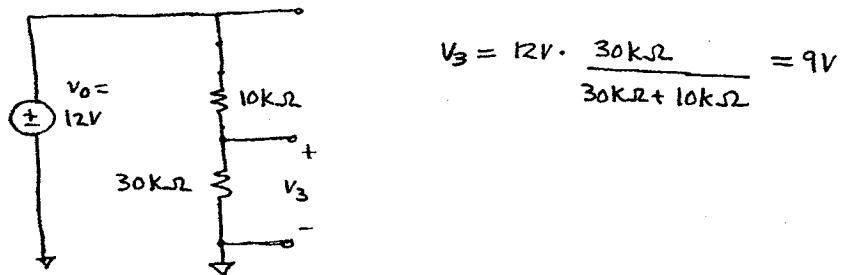d) When $v_o > 0V$, top diode = wire, bottom diode = open.




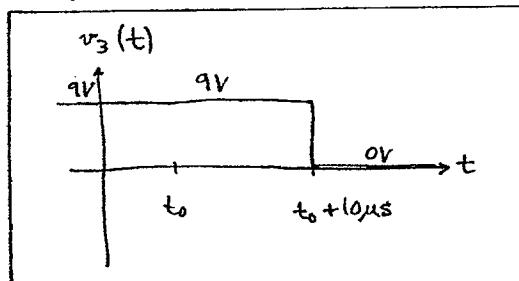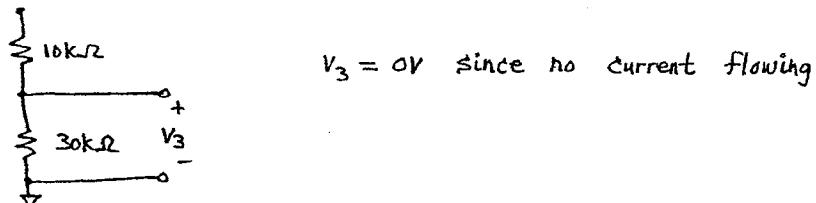When $v_o < 0V$, top diode = open, bottom diode doesn't matter since no current



HW #10 Cont.

3.

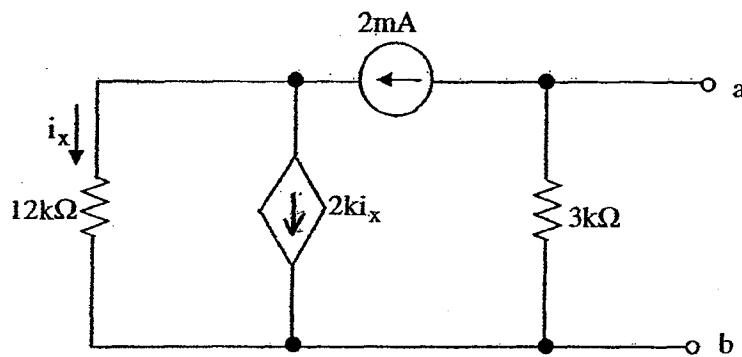

- a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- c. Calculate the value of that maximum power absorbed by R_L .

HW#10 Cont.

ECE 1000


Su 05

$$\text{sol'n: 3.9) } V_{Th} = V_{a,b \text{ open circ}} = -2\text{mA} \cdot 3\text{k}\Omega = -6\text{V}$$

The current source is between a, b
and the $12\text{k}\Omega$ and dependent source.

The current source thus isolates behavior
at a, b from the $12\text{k}\Omega$ and dependent source.

Use i_{sc} to find R_{Th} :

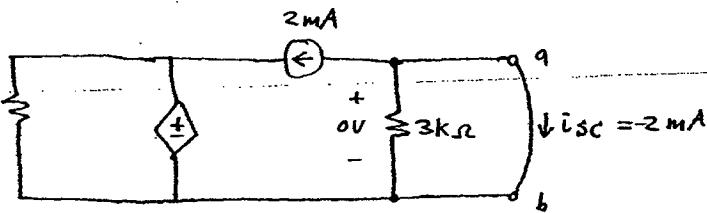

we short a, b so no v-drop across $3\text{k}\Omega$.

so $i_{3k\Omega} = 0$ and $i_{sc} = -2\text{mA}$.

$$R_{Th} = \frac{V_{Th}}{i_s} = \frac{-6\text{V}}{-2\text{mA}} = 3\text{k}\Omega$$

$V_{Th} = -6\text{V}$	$R_{Th} = 3\text{k}\Omega$
-----------------------	----------------------------


Comments: 1) we could also just turn off
the 2mA source and look into a, b
to see $R_{Th} = 3\text{k}\Omega$.

2) we really just started with
a Norton equivalent that we converted
to Thevenin equivalent.

b) max pwr when $R_L = R_{Th} = 3\text{k}\Omega = R_L$


c) max pwr $P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(-6\text{V})^2}{4 \cdot 3\text{k}\Omega} = 3\text{mW} = P_{max}$

3.

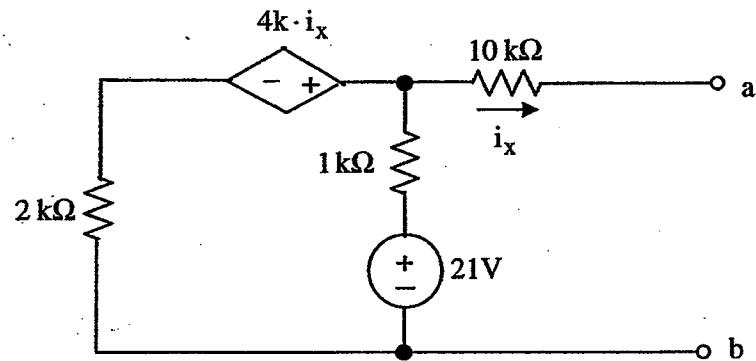

- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .


sol'n: 3.a)

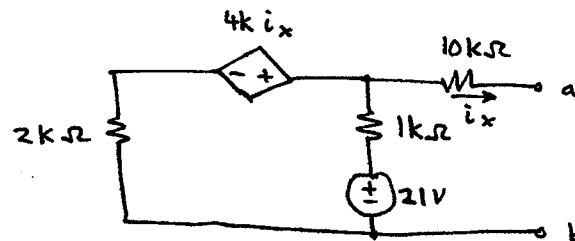

$$V_{Th} = V_{ab} \text{ open circuit}$$

$$i_x = 0 \text{ for open circuit } a, b. \therefore 4k_i_x = 0V$$

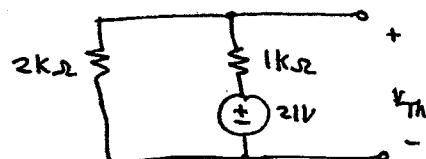No $i_x \Rightarrow$ no v drop across $10k\Omega \Rightarrow$ ignore $10k\Omega$




This is V-divider.

$$V_{Th} = 21V \cdot \frac{2k\Omega}{2k\Omega + 1k\Omega} = 14V$$

$$\boxed{V_{Th} = 14V}$$

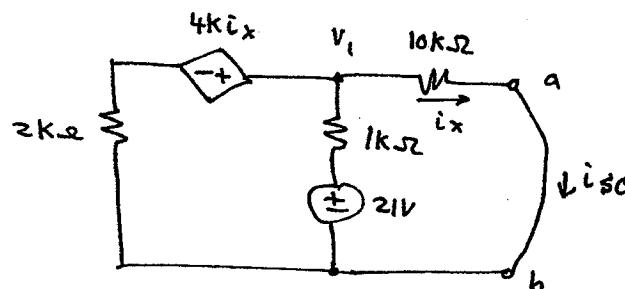To find R_{Th} we can use the i_{sc} method:



$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

Need to find
 $i_{sc} \therefore$ Find V_1

Find V_1 by node-voltage method:

$$i_x = \frac{V_1}{10k\Omega} \text{ so we can eliminate } i_x$$

$$\frac{V_1 - 4k\frac{V_1}{10k\Omega}}{2k\Omega} + \frac{V_1 - 21V}{1k\Omega} + \frac{V_1}{10k\Omega} = 0A$$

mult everything by $10k\Omega$

$$V_1 \cdot 5 - V_1 \cdot 2 + V_1 \cdot 10 + V_1 \cdot 1 = 210V$$

$$V_1(5 - 2 + 10 + 1) = 210V \quad V_1 - 14 = 210V \quad V_1 = 15V$$

$$i_{sc} = i_x = \frac{V_1}{10k\Omega} = 1.5mA \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{14V}{1.5mA}$$

$$\boxed{R_{Th} = 9.33k\Omega}$$


Sol'n: 3.b) max pwr when

$$R_L = R_{Th} = 9.33 \text{ k}\Omega$$

c) max pwr $P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(14V)^2}{4 \cdot \frac{14}{1.5} \text{ k}\Omega} = \frac{14(1.5)}{4} \text{ mW}$

$$P_{\max} = \frac{21}{4} \text{ mW} = 5.25 \text{ mW}$$

3. (30 points)

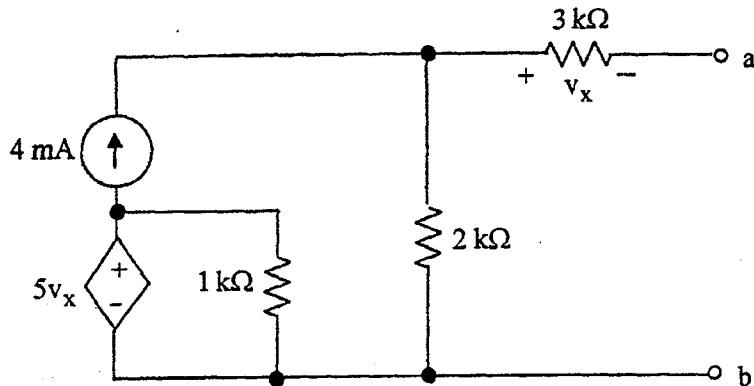

Pts

- 20 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.
 5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
 5 c. Calculate the value of that maximum power absorbed by R_L .


$$\text{sol'n: a)} \quad V_{Th} = V_{ab, \text{open circuit}}$$

open circuit $\Rightarrow v_x = 0$ since no current in $3\text{k}\Omega$.

$\therefore 5v_x \text{ src} = 0V = \text{wire}$

$1\text{k}\Omega$ across v_x shorted so can be ignored.

So we have:

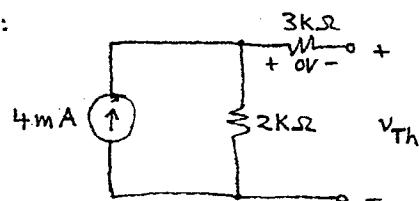

$$V_{Th} = 4\text{mA} \cdot 2\text{k}\Omega = 8\text{V}$$

$$\boxed{V_{Th} = 8\text{V}}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} \quad \text{If we short a,b we have current divider. } i_{sc} = 4\text{mA} \cdot \frac{2\text{k}\Omega}{2\text{k}\Omega + 3\text{k}\Omega} = \frac{8}{5} \text{mA}$$

$$R_{Th} = \frac{8\text{V}}{\frac{8}{5} \text{mA}} = 5\text{k}\Omega$$

$$\boxed{R_{Th} = 5\text{k}\Omega}$$


Note: Easier sol'n is to say $5v_x$ and $1\text{k}\Omega$ don't matter because they are in series with current source. Then $R_{Th} = 2\text{k}\Omega + 3\text{k}\Omega$ seen from a,b with 4mA off.

sol'n: 3.b) max pwr when $R_L = R_{Th} = 5\text{ k}\Omega$

$$3.c) \text{max pwr} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8V)^2}{4 \cdot 5\text{k}\Omega} = \frac{64}{20} \text{ mW} = 3.2 \text{ mW}$$

$$\boxed{\text{max pwr} = 3.2 \text{ mW}}$$

3. (35 points)

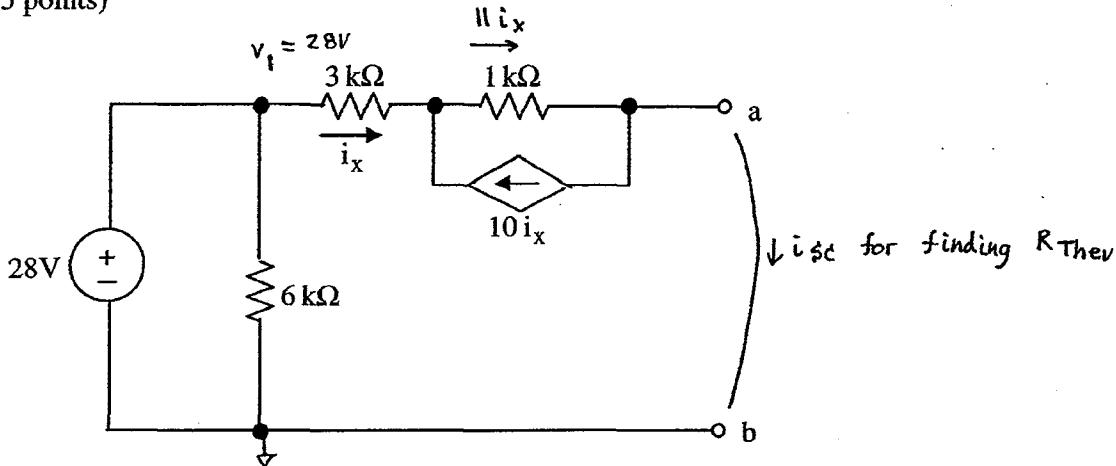

Pts

25 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.

5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.

5 c. Calculate the value of that maximum power absorbed by R_L .

Sol'n: a) The $6\text{k}\Omega$ resistor is across the 28V source, so it may be ignored.

For V_{Thev} we use $V_{a,b}$ with no load. Since no current flows out of the 'a' terminal, $i_x = 0$.

$\therefore 10i_x = 0\text{A}$ and v drop across $3\text{k}\Omega$ and $1\text{k}\Omega$ is zero.

$$\therefore V_{a,b} = 28\text{V} \text{ from v src} \quad \therefore V_{\text{Thev}} = 28\text{V}$$

Now find i_{sc} flowing in wire connected from a to b.


From current sum at node on left end of $1\text{k}\Omega$, we have current $11i_x$ flowing in $1\text{k}\Omega$ resistor.

Using v drops for $3\text{k}\Omega$ and $1\text{k}\Omega$, we must have

$$i_x \cdot 3\text{k}\Omega + 11i_x \cdot 1\text{k}\Omega = 28\text{V} \quad \text{or} \quad 14\text{k}\Omega \cdot i_x = 28\text{V}$$

$$\text{or } i_x = 2\text{ mA. Since } i_{sc} = i_x \text{ and } R_{\text{Th}} = \frac{V_{\text{Th}}}{i_{sc}},$$
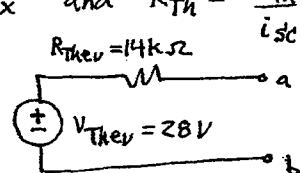
$$R_{\text{Th}} = \frac{28\text{V}}{2\text{mA}} = 14\text{k}\Omega$$



Sol'n: 3.b) Max pwr when $R_L = R_{Ther} = 14\text{k}\Omega$


$$3.c) \text{Max pwr} = \frac{V_{Ther}^2}{4R_{Ther}} = \frac{(28V)^2}{4 \cdot 14\text{k}\Omega} = 7(2)\text{W/k}$$

$$\boxed{\text{Max pwr} = 14\text{mW}}$$

(40)

HW #10 Cont.

4.

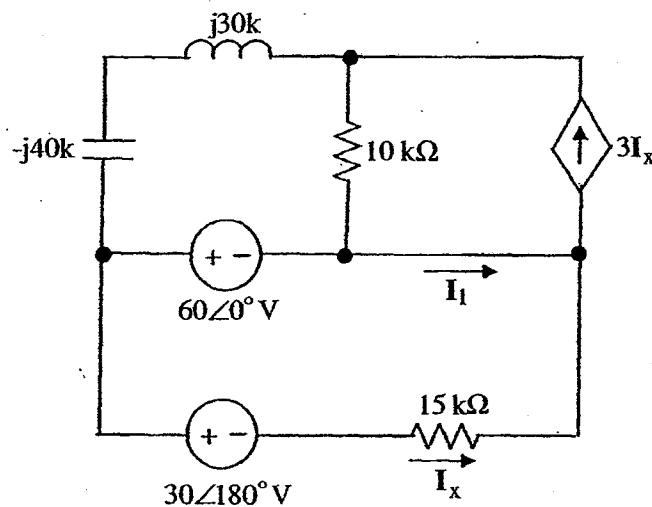


- A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.
- Given $\omega = 53.13 \text{ rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

HW #10 Cont.

SW 05

ECE 1000

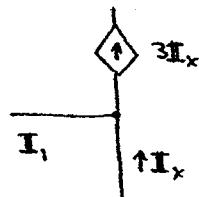
sol'n: 4. a) Sum of currents for node on right side:



$$\text{we see that } I_1 = 2I_x$$

from sum of currents
out of node = 0.

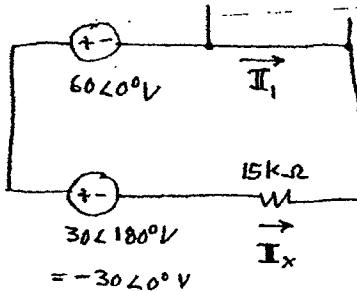From the bottom half of the circuit, we
can compute I_x directly:



From v-loop we have

$$I_x = \frac{60L0^\circ V - 30L0^\circ V}{15k\Omega}$$

$$I_x = \frac{30L0^\circ V}{15k\Omega}$$

$$I_x = 6 \text{ mA } L 0^\circ$$

$$\text{So, } I_1 = 2I_x = 12 \text{ mA } L 0^\circ$$


$$I_1 = 12 L 0^\circ \text{ mA}$$

b)

$$i_1(t) = 12 \cos(53.13t) \text{ mA}$$


or πt

3.

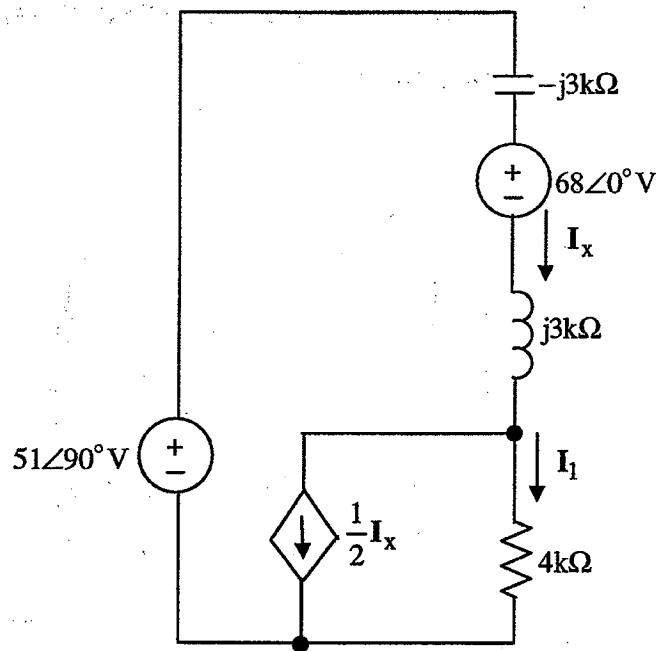

- A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.
- Given $\omega = \pi \text{ rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

4. (25 points)

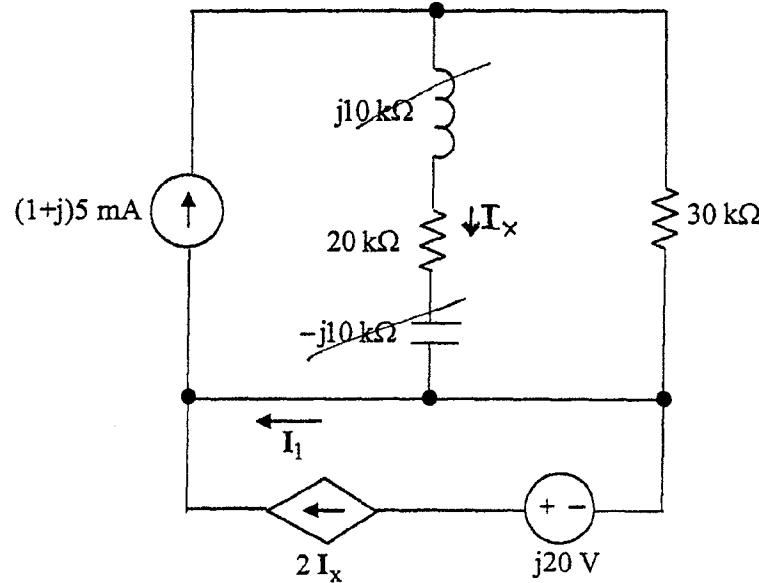

20 pts a. A frequency-domain circuit is shown above. Write the value of I_1 in polar form.

5 pts b. Given $\omega = 100 \text{ k rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

sol'n: 4.a) $j10\text{k}\Omega - j10\text{k}\Omega = 0\Omega$ so L and C cancel.

Current divider for $20\text{k}\Omega$ and $30\text{k}\Omega$.

$$\therefore I_x = (1+j) 5 \text{ mA} \cdot \frac{30\text{k}\Omega}{20\text{k}\Omega + 30\text{k}\Omega} = (1+j) 3 \text{ mA}$$

Find I_1 from sum of currents at node
on left side:

$$(1+j) 5 \text{ mA} - 2 \underbrace{(1+j) 3 \text{ mA}}_{I_x} - I_1 = 0$$

$$I_1 = (1+j) 5 \text{ mA} - 2 (1+j) 3 \text{ mA} = (1+j)(5-6) \text{ mA}$$


$$I_1 = (1+j)(-1) \text{ mA} = -(1+j) \text{ mA}$$

$I_1 = -\sqrt{2} \angle 45^\circ \text{ mA}$	$= \sqrt{2} \angle -135^\circ \text{ mA}$
--	---

or 225°

b) $i_1(t) = \sqrt{2} \cos(100kt - 135^\circ) \text{ mA}$


3. (30 points)

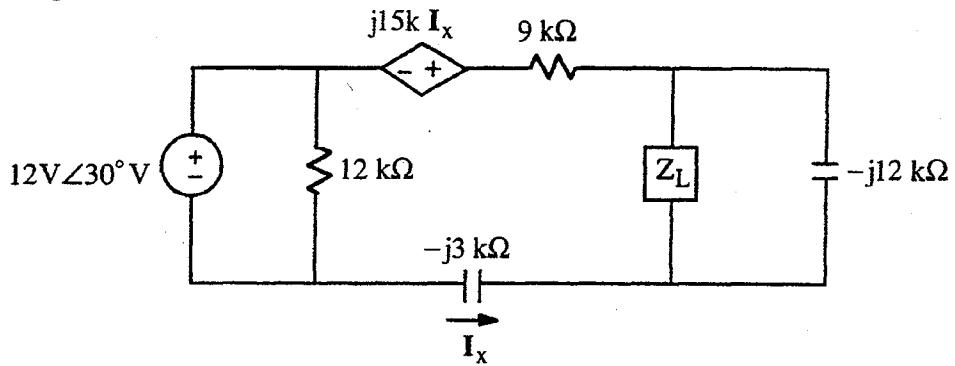

Pts

- 15 a. Choose the value of Z_L that will absorb maximum average power.
15 b. Calculate the value of that maximum average power absorbed by Z_L .

(46)

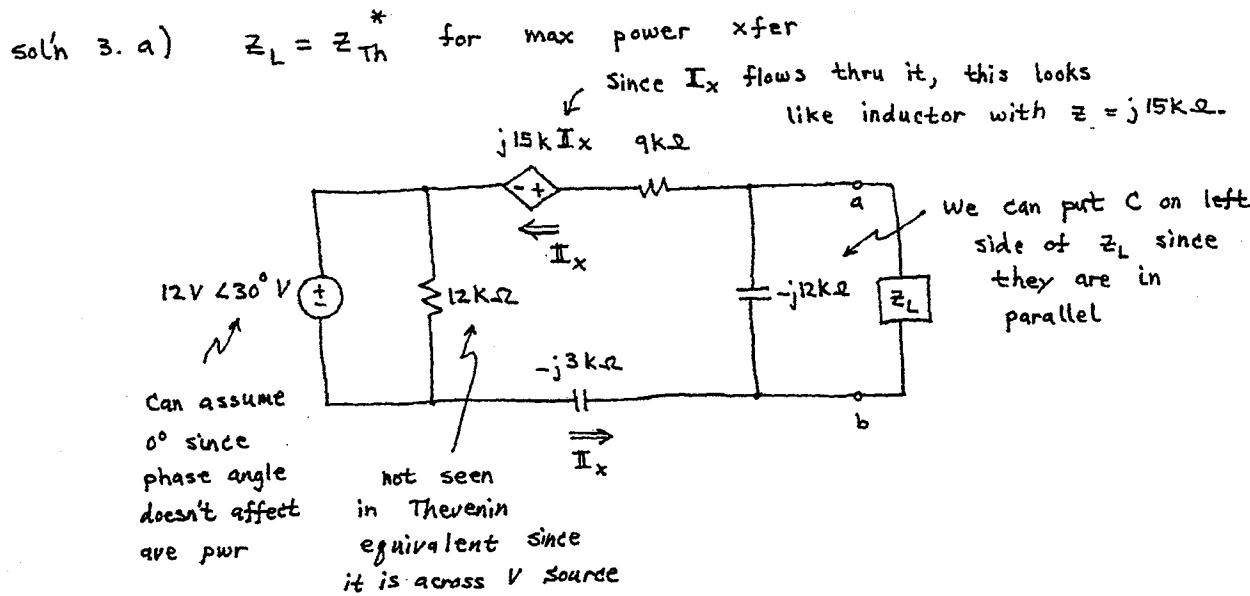

Circuit for determining Thvenin equivalent:

$$z_L = z_{Th}^* = 16k\Omega + j12k\Omega$$


$$\therefore z_{Th} = -j12k\Omega \parallel (-j3k\Omega + j15k\Omega + 9k\Omega)$$

$$= -j12k\Omega \parallel (9k\Omega + j12k\Omega)$$

$$= -j12k\Omega \frac{(9k\Omega + j12k\Omega)}{-j12k\Omega + 9k\Omega + j12k\Omega}$$

$$= -j \frac{12k\Omega (9k\Omega + j12k\Omega)}{9k\Omega}$$

$$= -j12k\Omega + 16k\Omega$$

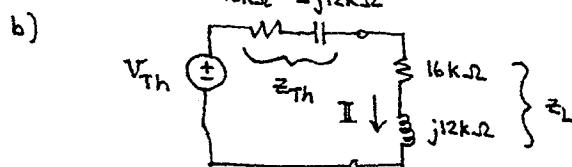


$$P \equiv (\text{ave pwr in } z_L) = \frac{|I|^2}{2} R \quad \text{where } R = 16k\Omega \text{ in } z_L$$

$$I = \frac{V_{Th}}{16k\Omega - j12k\Omega + 16k\Omega + j12k\Omega} = \frac{V_{Th}}{32k\Omega}$$

$$V_{Th} = 12V \cdot \frac{-j12k\Omega}{-j12k\Omega + -j3k\Omega + j15k\Omega + 9k\Omega} = 12V \left(\frac{-j12k\Omega}{9k\Omega} \right) = -j16V$$

$$\therefore P = \frac{|-j16V|^2}{32k\Omega} \cdot 16k\Omega = \frac{|-j|^2 V^2}{|12k\Omega|^2} \cdot \frac{16k\Omega}{2} = \frac{1V^2 \cdot 8}{4k\Omega} \text{ or } P = 2mW$$

4. (25 points)

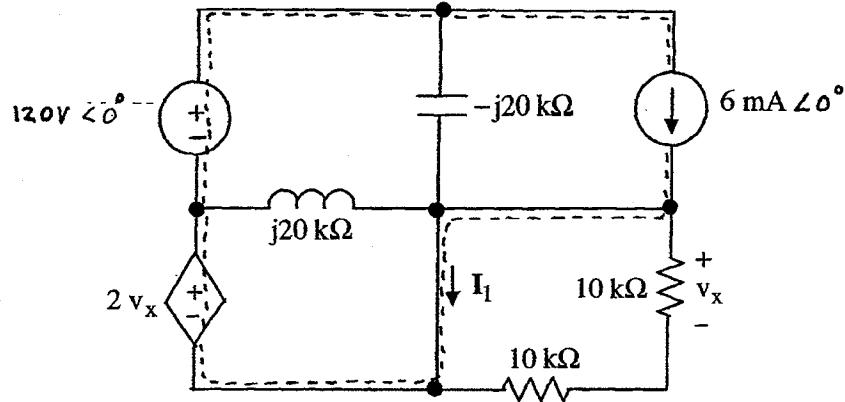

Pts

- 20 a. A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.
- 5 b. Given $\omega = \pi$ rad/s, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

Sol'n: a) Since the two $10\text{k}\Omega$ resistors are shorted by wires.

\therefore There is no v drop across the $10\text{k}\Omega$ resistors,
and $v_x = 0\text{V}$.

Thus, the $2v_x$ dependent source = 0V = wire
Superposition Case I: 6mA on, 120V off = wire.
It follows that all of the 6mA from the independent current source flows in the wires (shown as dashed lines above).

$$\therefore I_{11} = 6\text{mA} < 0^\circ$$

Case II: 120V on, 6mA off = open circuit
we observe that the $-j20\text{k}\Omega$ is directly across the 120V source, given the wires shown as dashed lines.

$$\therefore I_{12} = \frac{120\text{V} < 0^\circ}{-j20\text{k}\Omega} = j6\text{mA} = 6\text{mA} < 90^\circ$$

$$\text{Thus, } I_1 = I_{11} + I_{12} = 6\text{mA} \cdot (1+j)$$

or $I_1 = \sqrt{2} \cdot 6\text{mA} < 45^\circ$

b) $i_1(t) = \sqrt{2} \cdot 6\text{mA} \cos(\pi t + 45^\circ)$