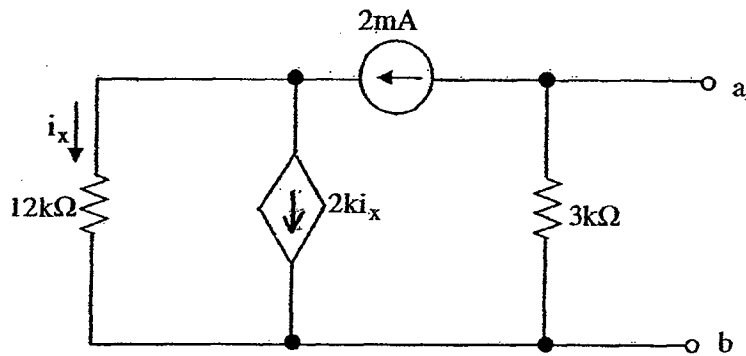


HW #10 Cont.

3.



- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .

HW#10 Cont.

ECE 1000


Su 05

sol'n: 3. a) $V_{Th} = V_{a,b} \text{ open circ} = -2 \text{ mA} \cdot 3 \text{ k}\Omega = -6 \text{ V}$

The current source is between a,b and the $12 \text{ k}\Omega$ and dependent source.

The current source thus isolates behavior at a,b from the $12 \text{ k}\Omega$ and dependent source.

Use i_{sc} to find R_{Th} :

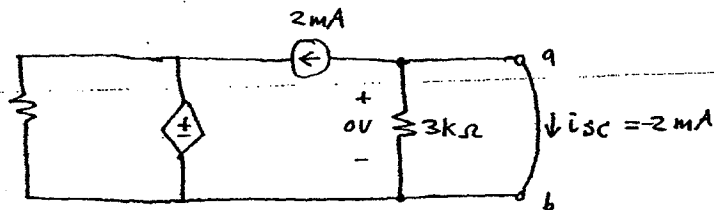

we short a,b so no v-drop across $3 \text{ k}\Omega$.

So $i_{3 \text{ k}\Omega} = 0$ and $i_{sc} = -2 \text{ mA}$.

$$R_{Th} = \frac{V_{Th}}{i_s} = \frac{-6 \text{ V}}{-2 \text{ mA}} = 3 \text{ k}\Omega$$

$V_{Th} = -6 \text{ V} \quad R_{Th} = 3 \text{ k}\Omega$


Comments: 1) We could also just turn off the 2 mA source and look into a,b to see $R_{Th} = 3 \text{ k}\Omega$.

2) We really just started with a Norton equivalent that we converted to Thevenin equivalent.

b) max pwr when $R_L = R_{Th} = 3 \text{ k}\Omega = R_L$


c) max pwr $P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(-6 \text{ V})^2}{4 \cdot 3 \text{ k}\Omega} = 3 \text{ mW} = P_{max}$

3.

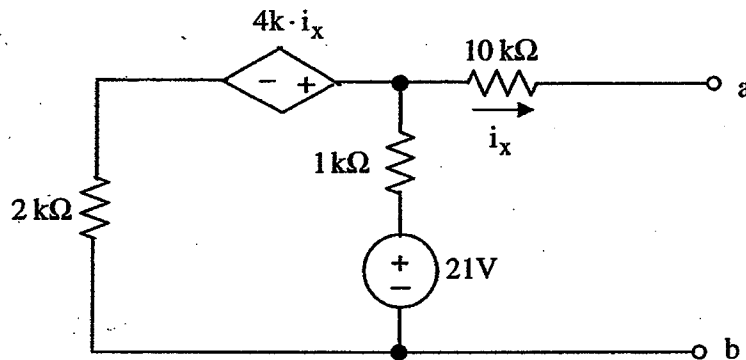

- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .


soln: 3.a)

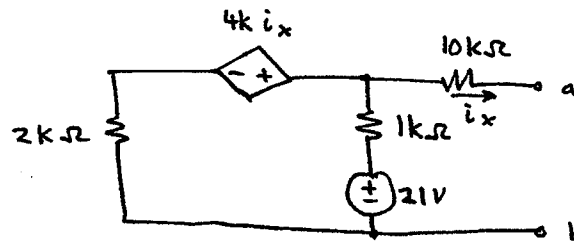

$$V_{Th} = V_{ab} \text{ open circuit}$$

$$i_x = 0 \text{ for open circuit } a, b. \therefore 4k i_x = 0V$$

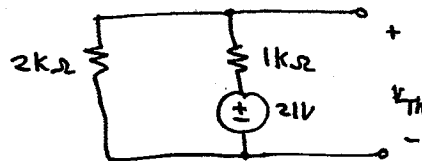No $i_x \Rightarrow$ no V drop across $10k\Omega \Rightarrow$ ignore $10k\Omega$




This is V -divider.

$$V_{Th} = 21V \cdot \frac{2k\Omega}{2k\Omega + 1k\Omega} = 14V$$

$$V_{Th} = 14V$$

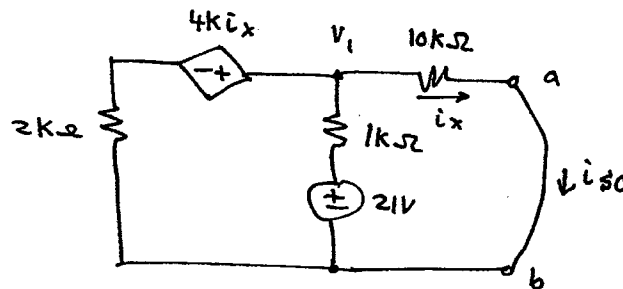To find R_{Th} we can use the i_{sc} method:



$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

Need to find i_{sc} . \therefore Find v_1

Find v_1 by node-voltage method:

$$i_x = \frac{v_1}{10k\Omega} \text{ so we can eliminate } i_x$$

$$\frac{v_1 - 4k \frac{v_1}{10k\Omega}}{2k\Omega} + \frac{v_1 - 21V}{1k\Omega} + \frac{v_1}{10k\Omega} = 0A$$

mult everything by $10k\Omega$

$$v_1 \cdot 5 - v_1 \cdot 2 + v_1 \cdot 10 + v_1 \cdot 1 = 210V$$

$$v_1 (5 - 2 + 10 + 1) = 210V \quad v_1 \cdot 14 = 210V \quad v_1 = 15V$$

$$i_{sc} = i_x = \frac{v_1}{10k\Omega} = 1.5mA$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{14V}{1.5mA}$$

$$R_{Th} = 9.33k\Omega$$

35


sol'n: 3.b) max pwr when

$$R_L = R_{Th} = 9.33 \text{ k}\Omega$$

$$c) \text{ max pwr } P_{\text{max}} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(14V)^2}{4 \cdot \frac{14 \text{ k}\Omega}{1.5}} = \frac{14(1.5)}{4} \text{ mW}$$

$$P_{\text{max}} = \frac{21}{4} \text{ mW} = 5.25 \text{ mW}$$

3. (30 points)

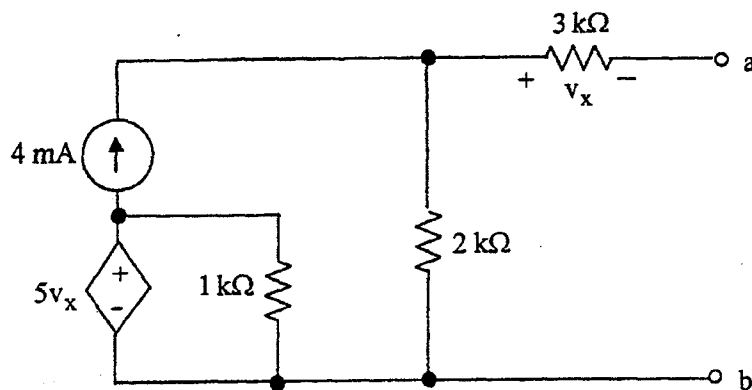

Pts

- 20 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- 5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- 5 c. Calculate the value of that maximum power absorbed by R_L .

sol'n: a)


$$V_{Th} = V_{a,b} \text{ open circuit}$$

open circuit $\Rightarrow V_x = 0$ since no current in $3k\Omega$.

$\therefore 5V_x$ src = $0V$ = wire

$1k\Omega$ across V_x shorted so can be ignored.

So we have:

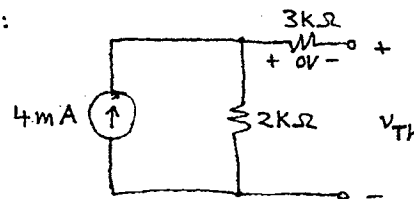

$$V_{Th} = 4mA \cdot 2k\Omega = 8V$$

$$V_{Th} = 8V$$

$R_{Th} = \frac{V_{Th}}{i_{sc}}$ If we short a,b we have current divider. $i_{sc} = 4mA \cdot \frac{2k\Omega}{2k\Omega + 3k\Omega} = \frac{8}{5} mA$

$$R_{Th} = \frac{8V}{8/5 mA} = 5k\Omega$$

$$R_{Th} = 5k\Omega$$


Note: Easier sol'n is to say $5V_x$ and $1k\Omega$ don't matter because they are in series with current source. Then $R_{Th} = 2k\Omega + 3k\Omega$ seen from a,b with $4mA$ off.

sol'n: 3.b) max pwr when $R_L = R_{Th} = 5\text{ k}\Omega$

$$3.c) \quad \text{max pwr} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8V)^2}{4 \cdot 5\text{ k}\Omega} = \frac{64}{20} \text{ mW} = 3.2 \text{ mW}$$

$$\text{max pwr} = 3.2 \text{ mW}$$

3. (35 points)

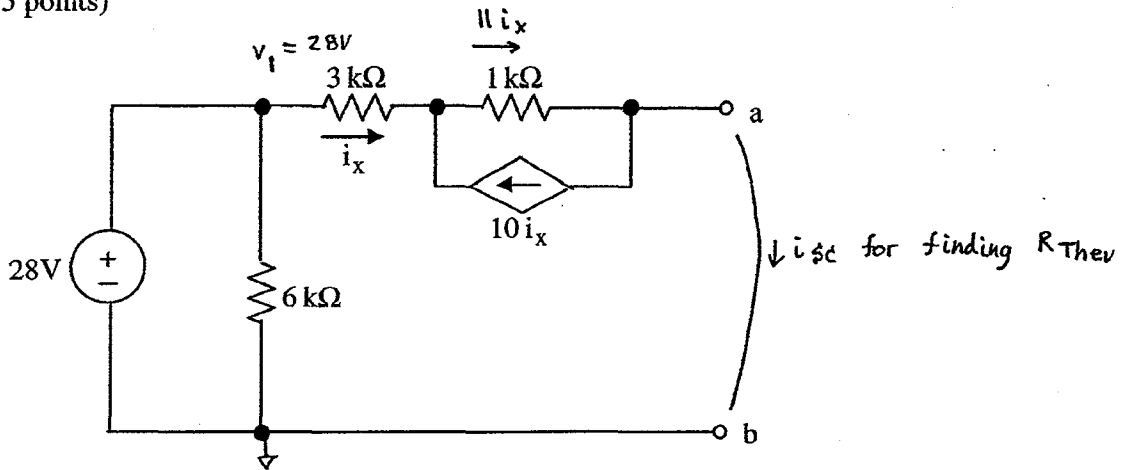

Pts

- 25 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- 5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- 5 c. Calculate the value of that maximum power absorbed by R_L .

sol'n: a) The $6k\Omega$ resistor is across the $28V$ source, so it may be ignored.

For V_{Thev} we use $V_{a,b}$ with no load. Since no current flows out of the 'a' terminal, $i_x = 0$.

$\therefore 10i_x = 0A$ and v drop across $3k\Omega$ and $1k\Omega$ is zero.

$\therefore V_{a,b} = 28V$ from v src $\therefore V_{Thev} = 28V$

Now find i_{sc} flowing in wire connected from a to b.


From current sum at node on left end of $1k\Omega$, we have current $11i_x$ flowing in $1k\Omega$ resistor.

Using v drops for $3k\Omega$ and $1k\Omega$, we must have

$$i_x \cdot 3k\Omega + 11i_x \cdot 1k\Omega = 28V \quad \text{or} \quad 14k\Omega \cdot i_x = 28V$$

or $i_x = 2mA$. Since $i_{sc} = i_x$ and $R_{Th} = \frac{V_{Th}}{i_{sc}}$,

$$R_{Th} = \frac{28V}{2mA} = 14k\Omega$$

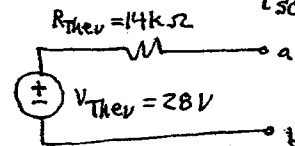

sol'n: 3. b) Max pwr when $R_L = R_{Thev} = 14k\Omega$

$$3. c) \text{ Max pwr} = \frac{V_{Thev}^2}{4 R_{Thev}} = \frac{(28V)^2}{4 \cdot 14k\Omega} = 7(2)W/k$$

$$\text{Max pwr} = 14mW$$