


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000

HOMEWORK #9

Spring 2005

1.

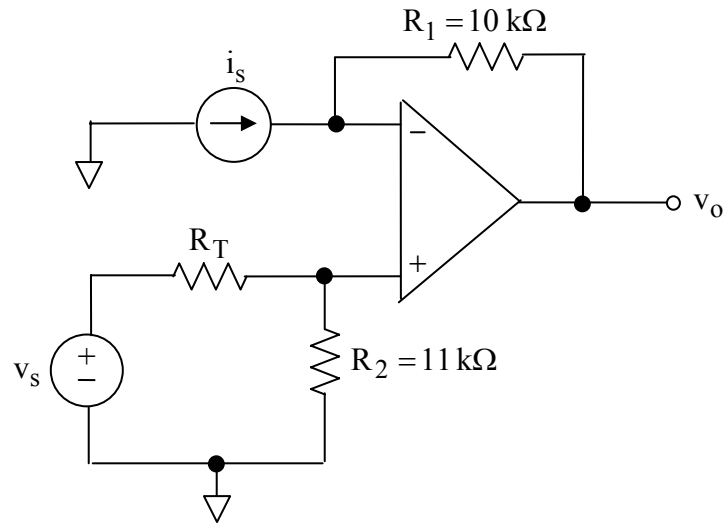


Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermistor with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 12.25 \text{ k}\Omega$, $\beta = 170^\circ \text{K}$, and T is temperature in $^\circ \text{K}$. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . **Hint: Use superposition.**

2.
 - a. Calculate the numerical values of R_T (273°K) and R_T (373°K).
 - b. Determine a value for v_s such that $v_o(T = 373^\circ \text{K}) - v_o(T = 273^\circ \text{K}) = 1 \text{V}$
 - c. Using your answer to (b), determine a value of i_s such that $v_o(T = 273^\circ \text{K}) = 0 \text{ V}$.
 - d. Using the component values you chose above, calculate v_o when $T = 323^\circ \text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ \text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

3.

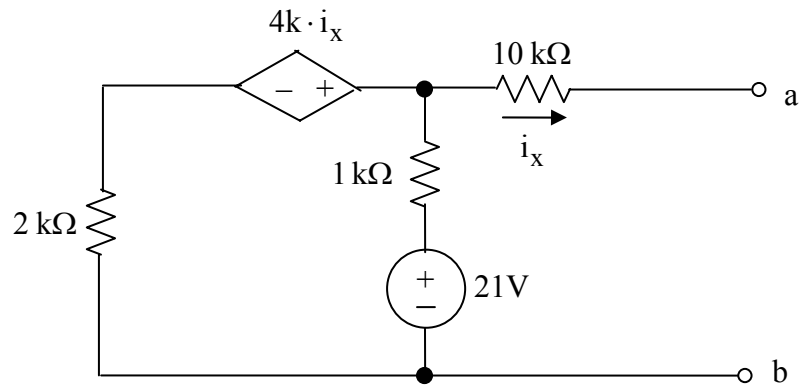

- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000

HOMEWORK #9

Spring 2005

1.

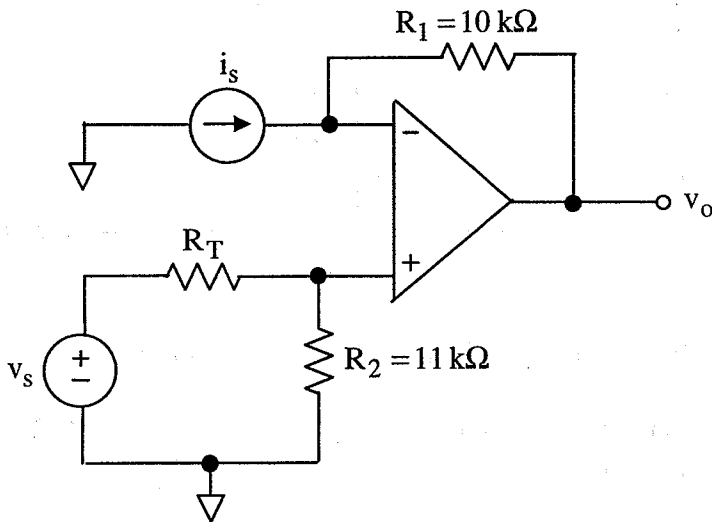

Rail voltage = ± 15 V


Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermistor with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 12.25 \text{ k}\Omega$, $\beta = 170^\circ \text{K}$, and T is temperature in $^\circ \text{K}$. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . **Hint: Use superposition.**

2.
 - a. Calculate the numerical values of R_T (273°K) and R_T (373°K).
 - b. Determine a value for v_s such that $v_o(T = 373^\circ \text{K}) - v_o(T = 273^\circ \text{K}) = 1\text{V}$
 - c. Using your answer to (b), determine a value of i_s such that $v_o(T = 273^\circ \text{K}) = 0 \text{ V}$.
 - d. Using the component values you chose above, calculate v_o when $T = 323^\circ \text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ \text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

sol'n: 1.

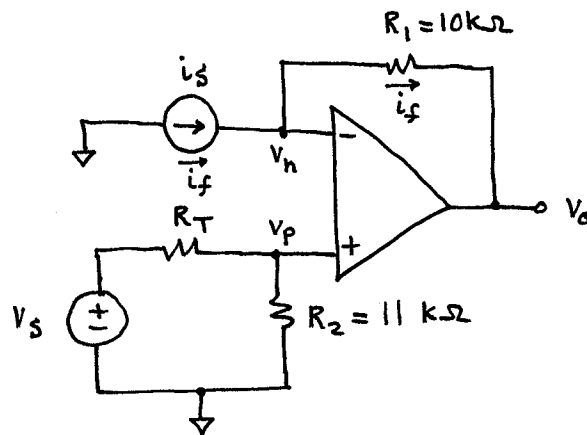Find v_p :

$$v_p = v_s \frac{R_2}{R_2 + R_T} \quad \text{V-divider}$$

$$v_n = v_p$$

Find i_f on left: $i_f = i_s$ Find i_f on right: $i_f = \frac{v_n - v_o}{R_1}$ Set i_f 's equal and use $v_n = v_p$

$$i_s = \frac{v_n - v_o}{R_1} \quad \text{or} \quad v_o = v_n - i_s R_1$$

$$v_o = v_s \frac{R_2}{R_2 + R_T} - i_s R_1$$

$$2. a) \quad R_T(273^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{170^\circ\text{K} \left(\frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 13 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{170^\circ\text{K} \left(\frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 11 \text{ k}\Omega$$

$$R_T(273^\circ\text{K}) = 13 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 11 \text{ k}\Omega$$

$$b) \quad IV = v_o(373^\circ\text{K}) - v_o(273^\circ\text{K}) = v_s \frac{R_2}{R_2 + R_T(373^\circ\text{K})} - \cancel{i_s R_1} \\ - \left(v_s \frac{R_2}{R_2 + R_T(273^\circ\text{K})} - \cancel{i_s R_1} \right)$$

$$IV = v_s \cdot 11 \text{ k}\Omega \cdot \left(\frac{1}{11 \text{ k}\Omega + 11 \text{ k}\Omega} - \frac{1}{11 \text{ k}\Omega + 13 \text{ k}\Omega} \right)$$

$$v_s = \frac{IV}{11 \text{ k}\Omega} \frac{22 \text{ k}\Omega \cdot 24 \text{ k}\Omega}{24 \text{ k}\Omega - 22 \text{ k}\Omega} = 24 \text{ V}$$

sol'n: 2.c) $0V = v_o(273^\circ K) = v_s \frac{R_2}{R_2 + R_T(273^\circ K)} - i_s R_1$


$$i_s = \frac{1}{R_1} v_s \frac{R_2}{R_2 + R_T(273^\circ K)} = \frac{1}{10k\Omega} \cdot 24V \cdot \frac{11k\Omega}{11k\Omega + 13k\Omega}$$

$$i_s = \frac{11}{10k} A = 1.1 mA$$


$$i_s = 1.1 mA$$

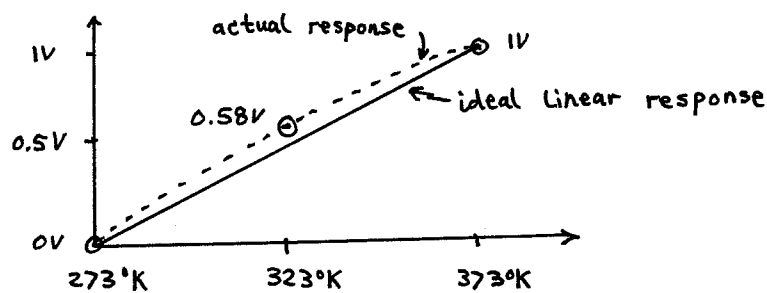d) $R_T(323^\circ K) = 12.25k\Omega \cdot e^{170^\circ K \left(\frac{1}{323^\circ K} - \frac{1}{300^\circ K} \right)} = 11.8k\Omega$

$$v_o(323^\circ K) = 24V \frac{11k\Omega}{11k\Omega + 11.8k\Omega} - 1.1mA \cdot 10k\Omega = 0.58V$$




3.

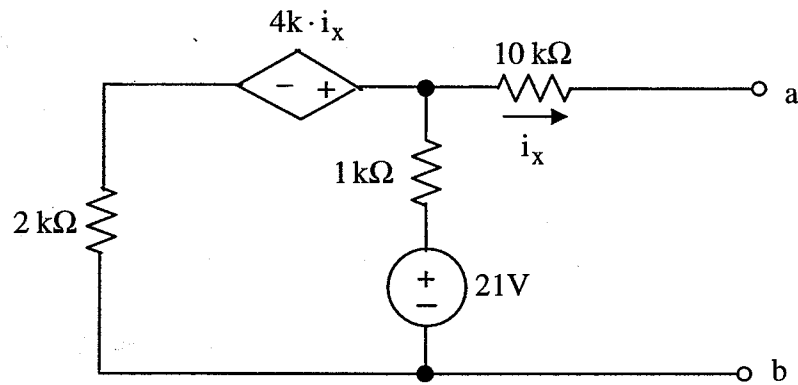

- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .


sol'n: 3. a)

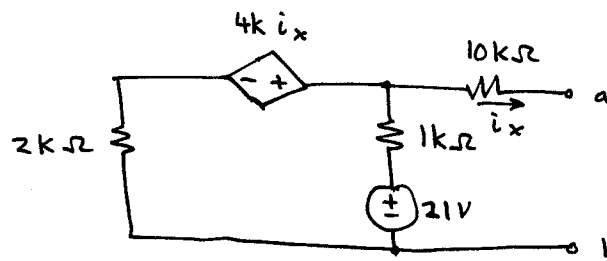

$$V_{Th} = V_{ab} \text{ open circuit}$$

$$i_x = 0 \text{ for open circuit } a, b. \therefore 4k \cdot i_x = 0V$$

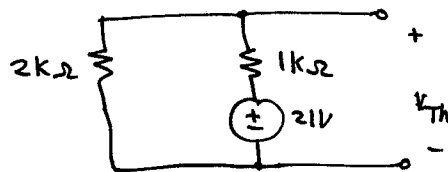No $i_x \Rightarrow$ no V drop across $10k\Omega \Rightarrow$ ignore $10k\Omega$




This is V -divider.

$$V_{Th} = 21V \cdot \frac{2k\Omega}{2k\Omega + 1k\Omega} = 14V$$

$$V_{Th} = 14V$$

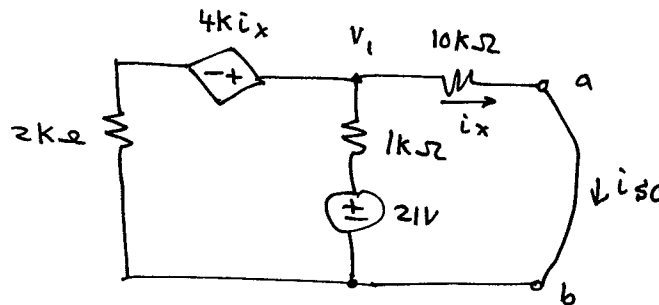To find R_{Th} we can use the i_{sc} method:



$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

Need to find i_{sc} . \therefore Find v_1

Find v_1 by node-voltage method:

$$i_x = \frac{v_1}{10k\Omega} \text{ so we can eliminate } i_x$$

$$\frac{v_1 - 4k \frac{v_1}{10k\Omega}}{2k\Omega} + \frac{v_1 - 21V}{1k\Omega} + \frac{v_1}{10k\Omega} = 0A$$

mult everything by $10k\Omega$

$$v_1 \cdot 5 - v_1 \cdot 2 + v_1 \cdot 10 + v_1 \cdot 1 = 210V$$

$$v_1 (5 - 2 + 10 + 1) = 210V \quad v_1 \cdot 14 = 210V \quad v_1 = 15V$$

$$i_{sc} = i_x = \frac{v_1}{10k\Omega} = 1.5mA \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{14V}{1.5mA}$$

$$R_{Th} = 9.33k\Omega$$

sol'n: 3.b) max pwr when

$$R_L = R_{Th} = 9.33 \text{ k}\Omega$$

$$c) \quad \text{max pwr} \quad P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(14V)^2}{4 \cdot \frac{14}{1.5} \text{ k}\Omega} = \frac{14(1.5)}{4} \text{ mW}$$

$$P_{\max} = \frac{21}{4} \text{ mW} = 5.25 \text{ mW}$$


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000


HOMEWORK #10

Spring 2005

1.

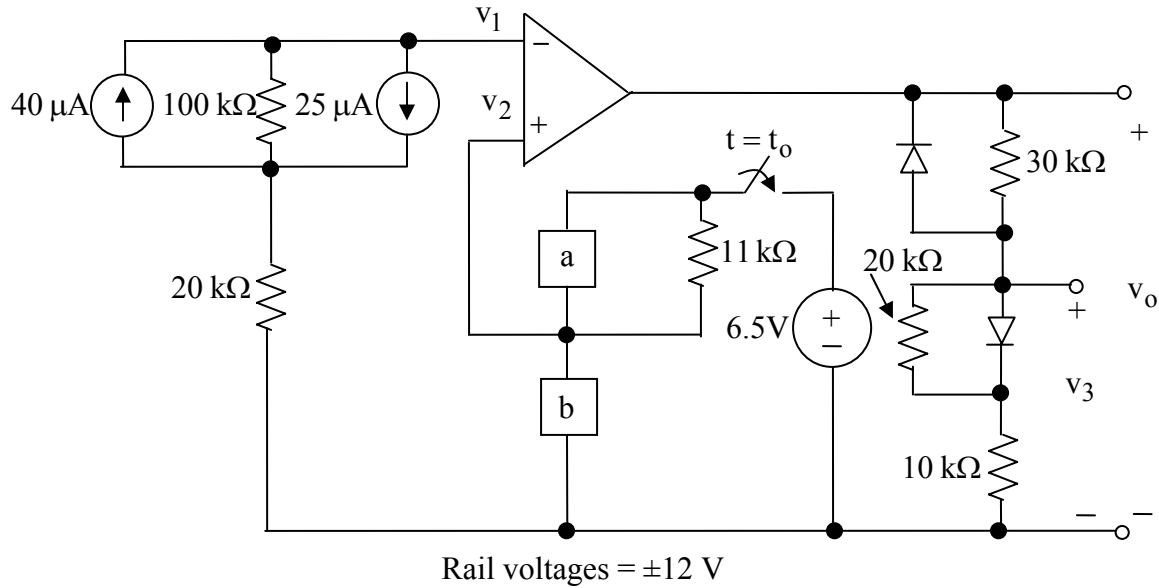

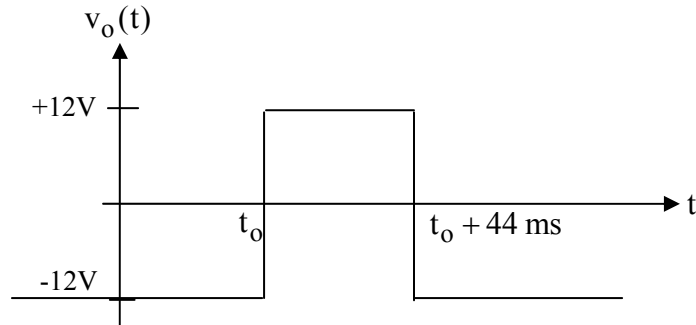
After being open for a long time, the switch closes at $t = t_0$.



- a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value. **Hint:** Use $v_2(t \rightarrow \infty) = 1$ V
 - b. Sketch $v_1(t)$, showing numerical values appropriately.
2. a. Sketch $v_2(t)$, showing numerical values appropriately.
 - b. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 44$ ms, and for $t_0 + 44$ ms $< t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

3.

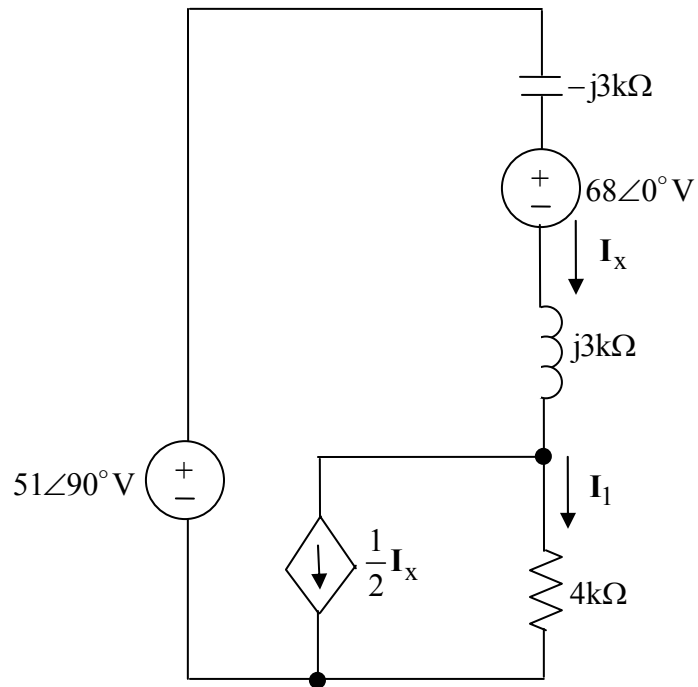

- A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.
- Given $\omega = \pi$ rad/s, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000


HOMEWORK #10

Spring 2005

1.

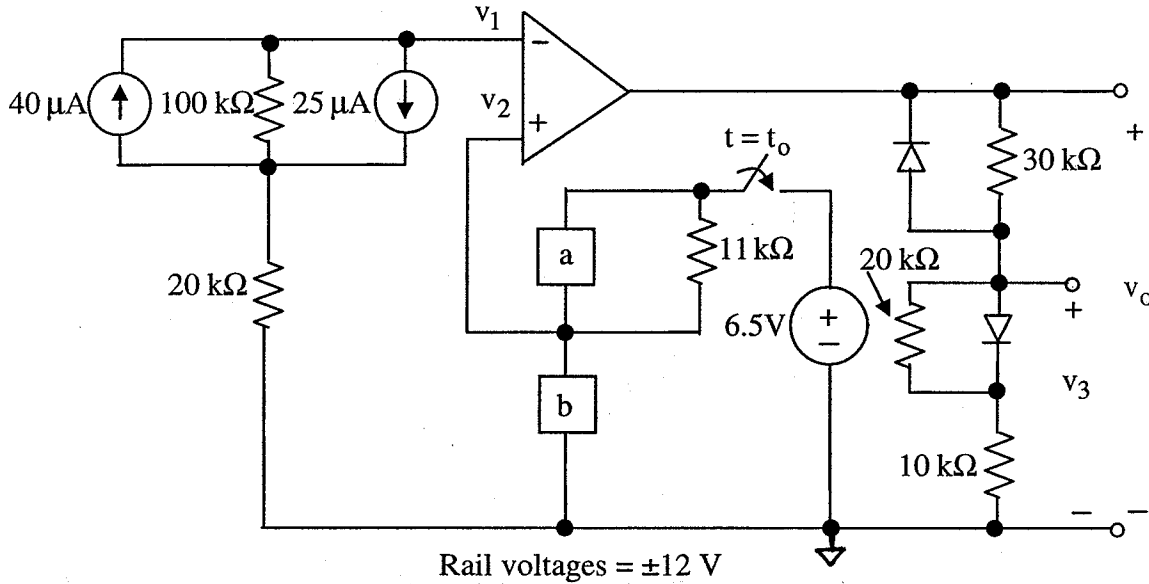

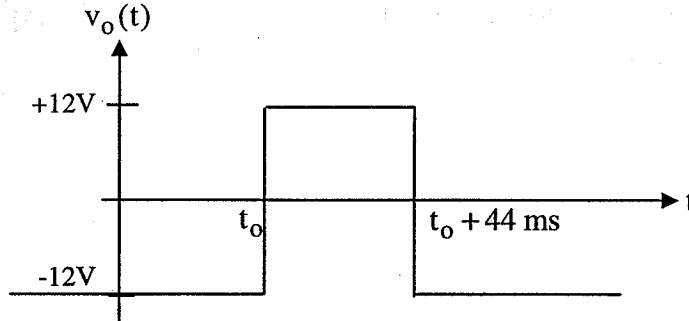After being open for a long time, the switch closes at $t = t_0$.



- a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value. **Hint:** Use $v_2(t \rightarrow \infty) = 1V$
 - b. Sketch $v_1(t)$, showing numerical values appropriately.
2. a. Sketch $v_2(t)$, showing numerical values appropriately.
 - b. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 44 \text{ ms}$, and for $t_0 + 44 \text{ ms} < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n: 1.a) Consider possibilities.

$a=R$ and $b=R$: v_2 would change at time $t=t_0$ but never change again. Thus, v_0 could not go high and then low again.

$a=C_1$ and $b=C_2$: Before $t=t_0$, there would be no path for C_2 in b to discharge. Thus, we would need to know $v_{C_2}(t=t_0^-)$.

We would also have $v_{C_1}(t=t_0^-) = 0V$ since C_1 will discharge thru the R in parallel with it.

When the switch closes, we have an invalid circuit if $v_{C_2}(t_0^+) + v_{C_1}(t_0^+) \neq 6.5V$. This means we must have

$v_{C_2}(t_0^+) = v_{C_2}(t_0^-) = 6.5V$ since

$v_{C_1}(t_0^+) = v_{C_1}(t_0^-) = 0V$.

But if $v_{C_2}(t_0^+) = 6.5$, nothing changes when the switch closes. Thus, we could not get a waveform that goes high and then low again.

$a=R$ and $b=C$: As in the case of $a=C_1$ and $b=C_2$, we would have some value of $v_C(t_0^-) = v_C(t_0^+)$. Since $v_2 = v_C(t_0^+)$ at $t=t_0^+$, v_0 would not change at t_0 .

Thus, this will not work.

$a=C$ and $b=R$:

The C in a will discharge thru the R in parallel with it. $\therefore v_C(t_0^-) = 0V$.

Also, no current flows in R for $t < t_0$ because there is no closed circuit path in which current could flow.

Thus, $v_2(t_0^-) = i \cdot R = 0V$.

sol'n: 1.a) cont.

At $t = t_0^+$, we have $v_2(t_0^+) = 6.5V - v_C(t_0^+)$
 or $v_2(t_0^+) = 6.5V$ since $v_C(t_0^+) = v_C(t_0^-) = 0V$.

Thus, v_2 jumps from $0V$ to $6.5V$ at t_0 .

If $v_2(t_0^+) > v_1$, then v_o would go high,
 (assuming $v_1 > 0V$ and $v_1 < 6.5V$).

After t_0 , C will charge and v_2 will
 start to drop. If v_2 eventually drops
 below v_1 , then v_o will go low again.

Thus, this will work.

Now find values of R and C :


v_1 : Since no current flows into the $-$ input
 of the op amp, no current flows thru
 the $20k\Omega$ resistor (lower left).

Combining the parallel current sources, we
 have $40\mu A - 25\mu A = 15\mu A$. This current
 flows thru the $100k\Omega$ to produce voltage

$$15\mu A \cdot 100k\Omega = 1.5V.$$

$$\therefore v_1 = 2.5V \text{ (constant)}$$

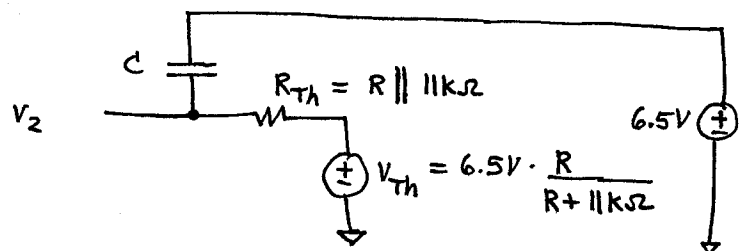v_2 : For $t > t_0$, we use a Thevenin equivalent
 circuit for the $6.5V$ source, the $11k\Omega$, and
 R in b .



sol'n: 1.a) cont.


We use the general RC sol'n for $v_2(t)$:

$$v_2(t) = v_2(t \rightarrow \infty) + [v_2(t_0^+) - v_2(t \rightarrow \infty)] e^{-t/R_{TH}C}$$

To find $v_2(t \rightarrow \infty)$, we observed that, when C is charged, no current flows in R_{TH} .

$$\text{Thus } v_2(t \rightarrow \infty) = V_{TH} = 6.5V \frac{R}{R+11k\Omega} < 6.5V.$$

From earlier, $v_2(t_0^+) = 6.5V$.

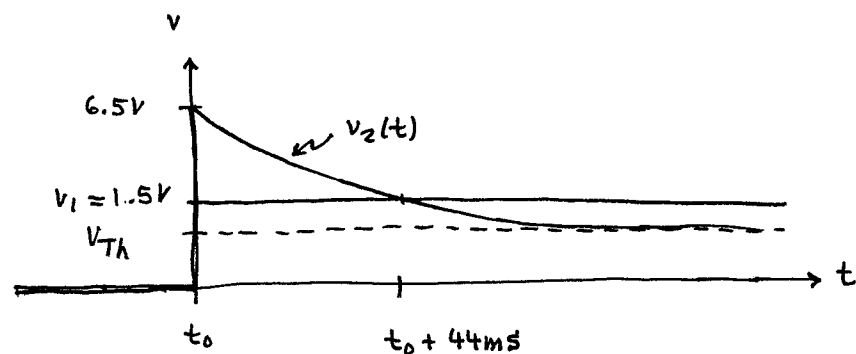

Any $V_{TH} < v_1$ will suffice. For convenience,

$$\text{let } V_{TH} = 1V = 6.5V \cdot \frac{R}{R+11k\Omega} \Rightarrow \boxed{R = 2k\Omega}$$

Assume $t_0 = 0$. For v_0 to switch at $t = 44ms$,

$$\text{we have } v_2(44ms) = v_1 = 1.5V$$

$$\text{or } 1V + [6.5V - 1V] e^{-44ms/R_{TH}C} = 0.5V$$

$$\text{or } 5.5V e^{-44ms/R_{TH}C} = 0.5V \quad \text{where}$$

$$R_{TH} = R \parallel 11k\Omega = 2k \parallel 11k\Omega = \frac{22}{13} k\Omega.$$


Take \ln of both sides of exponential RC eq'n:

$$-\frac{44ms}{\frac{22}{13} k\Omega \cdot C} = \ln \frac{0.5V}{5.5V} = -2.39$$


$$C = \frac{2}{\frac{2.39}{13}} \mu F = 10.9 \mu F$$

$$\boxed{C = 11 \mu F}$$

sol'n: 1.b) $v_1(t) = 1.5V$ constant

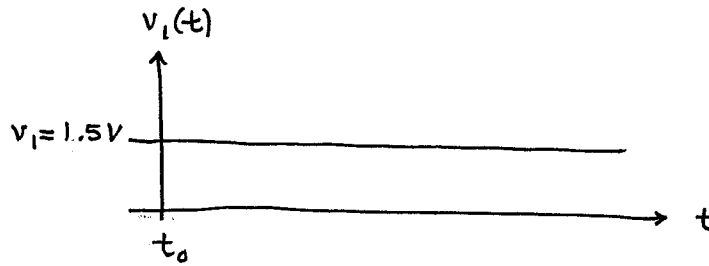


2.a)

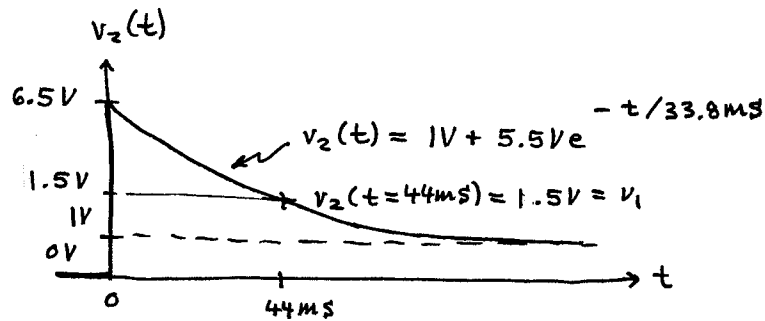

Note: $R_{TH} C = \frac{22 k\Omega \cdot 20 \mu F}{13} \doteq 33.8ms$


Note: Assume $t_0 = 0$.

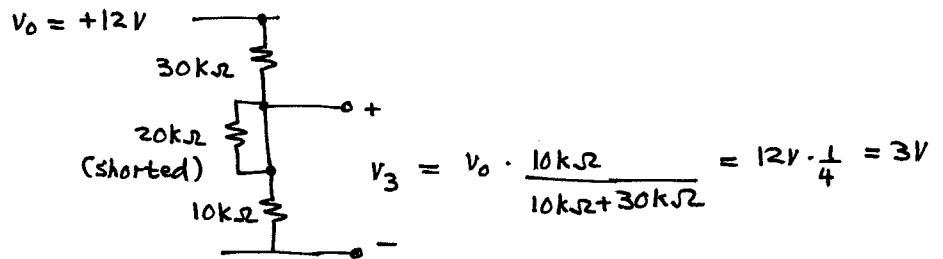b) When $v_0 = +12V$, top diode is reverse biased = open.
The bottom diode is forward biased = wire.




when $v_0 = -12V$, top diode is forward biased = wire.

Thus, v_0 is shorted to $-12V$.

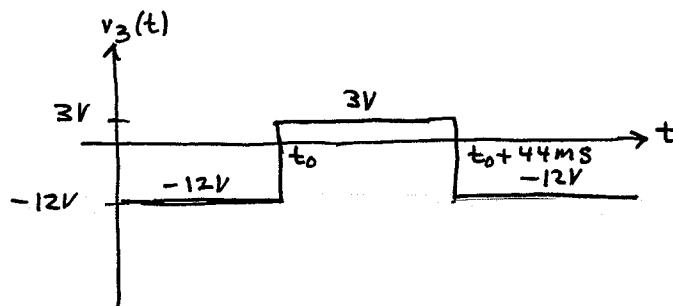


3.

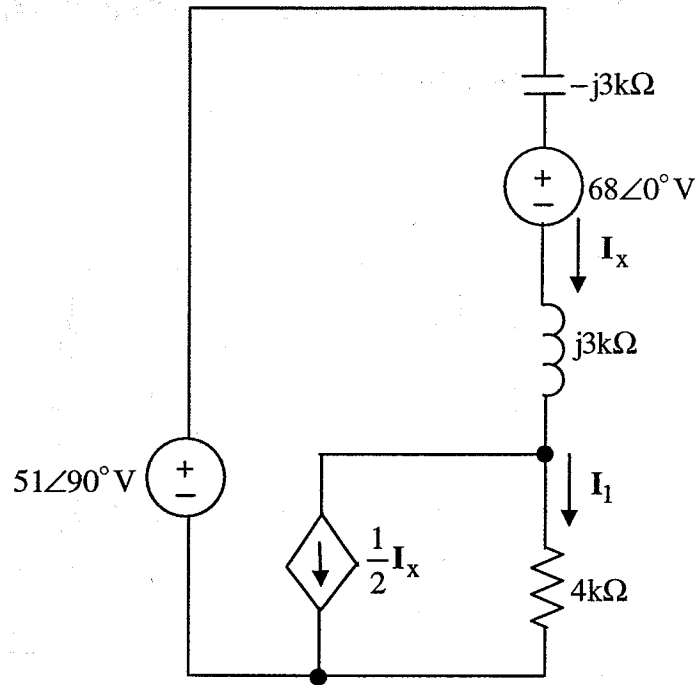

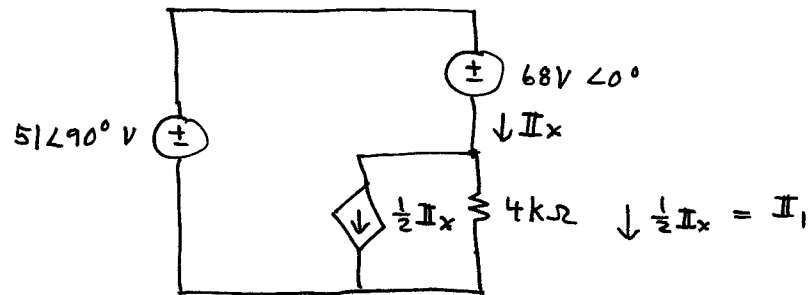- a. A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.
- b. Given $\omega = \pi \text{ rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

sol'n: 3.a) The $-j3k\Omega$ and $j3k\Omega$ sum to zero and act like a wire. Thus, they do not affect I_x .
So we have:



Clearly, $\frac{1}{2} I_x$ flows thru the $4k\Omega$ (for sum of currents at node above $4k\Omega = 0$).

But the current thru $4k\Omega$ is $\frac{51\angle 90^\circ V - 68\angle 0^\circ V}{4k\Omega}$

$$\text{or } \frac{1}{2} I_x = I_1 = \frac{17.3\angle 90^\circ - 17.4\angle 0^\circ V}{4k\Omega}$$

$$I_1 = 17 \frac{j3 - 4}{4k\Omega} = \frac{17}{4} (-4 + j3) = \frac{17.5V}{4} \angle 143^\circ \text{ mA}$$

$$I_1 = -17 + j12.75 \text{ mA} = 21.25 \angle 143^\circ \text{ mA}$$

b)

$$i_1(t) = 17 \cos(\pi t + 180^\circ) - 12.75 \sin(\pi t) \text{ mA}$$

$$= 21.25 \cos(\pi t + 143^\circ) \text{ mA}$$