
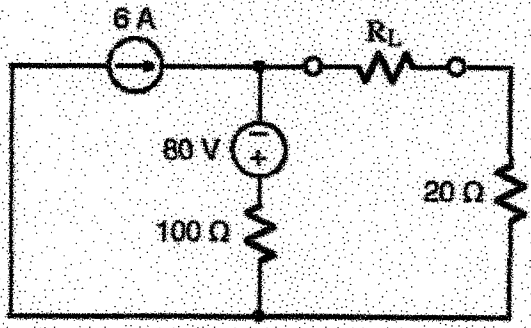


Homework #6/Review Examples

3.

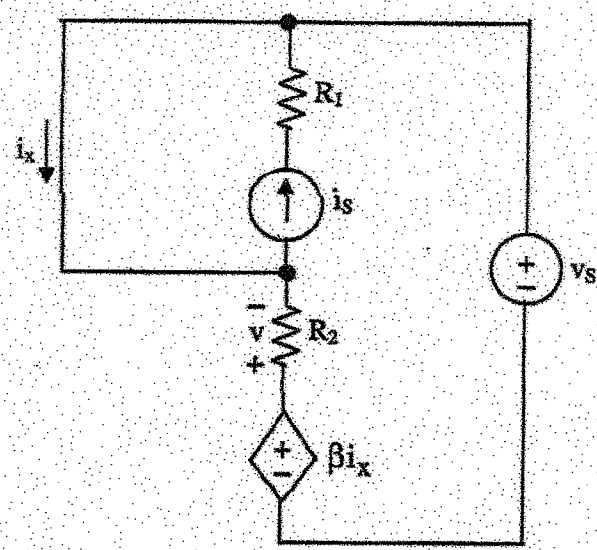


- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.



Using superposition, derive an expression for v that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and β . Note: $\beta > 0$.

sol'n: case I: i_s on, v_s off = wire

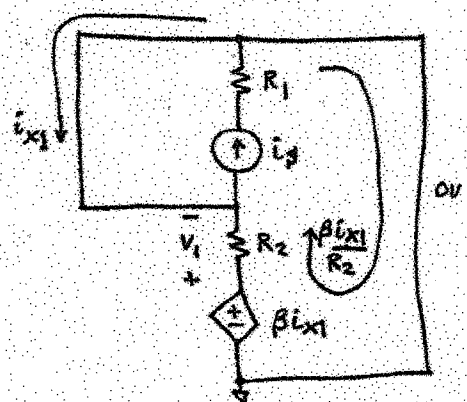

$v_1 = \beta i_{x1}$ from outer v loop

Current summation at center node gives


$$-i_s + i_{x1} + \frac{\beta i_{x1}}{R_2} = 0A$$

$$\text{or } i_{x1} \left(1 + \frac{\beta}{R_2}\right) = i_s$$

$$i_{x1} = \frac{i_s}{1 + \frac{\beta}{R_2}} = i_s \cdot \frac{R_2}{R_2 + \beta}$$

$$v_1 = \beta i_{x1} = \beta i_s \frac{R_2}{R_2 + \beta} = i_s \cdot R_2 \parallel \beta$$

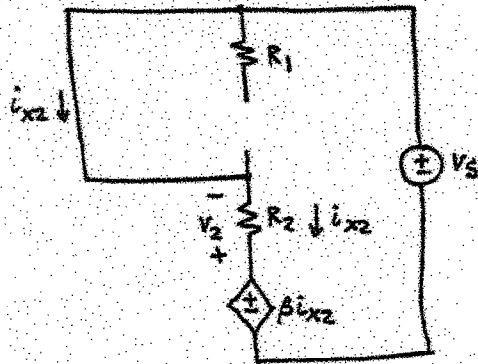soln: 5. cont. case I: i_3 off, V_3 on
= open



V loop around outside gives

$$\beta i_{x2} - i_{x2} \cdot R_2 - V_3 = 0V$$

$$i_{x2} (\beta + R_2) = V_3$$

$$i_{x2} = \frac{V_3}{\beta + R_2}$$

$$v_2 = -i_{x2} R_2 = -\frac{V_3 R_2}{\beta + R_2} = -\frac{V_3 R_2}{R_2 + \beta}$$


$$v = v_1 + v_2 = \beta i_3 \frac{R_2}{R_2 + \beta} - \frac{V_3 R_2}{R_2 + \beta} = (\beta i_3 - V_3) \frac{R_2}{R_2 + \beta}$$

$$v = (\beta i_3 - V_3) \frac{R_2}{R_2 + \beta}$$

Homework #6/Review Examples


125

4.

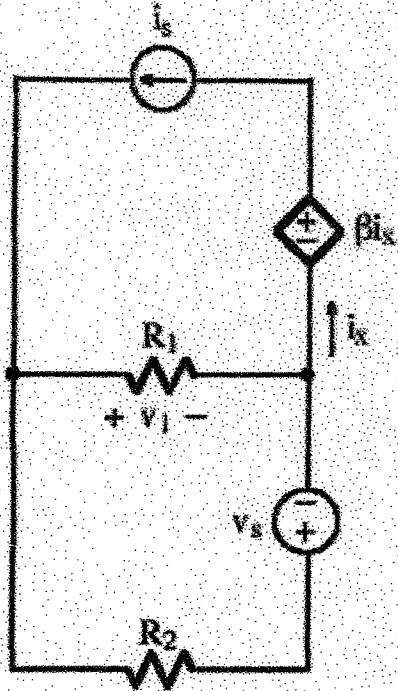

Using superposition, derive an expression for v_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and β , where $\beta > 0$.


EX:

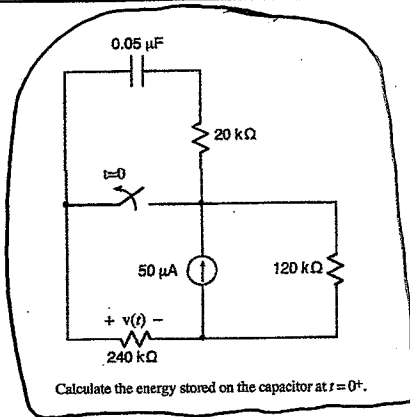Calculate the energy stored on the capacitor at $t=0^+$.

Sol'n: Energy $w_C = \frac{1}{2} C v_C^2(t=0^+)$

Since capacitor voltage cannot change instantly, $v_C(0^+) = v_C(0^-)$.

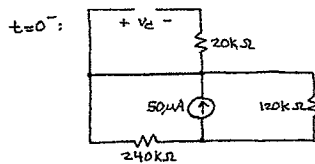At $t=0^-$, C acts like open circuit and switch is closed.




The short created by the switch creates a voltage loop on top left with 0V across C and across the 20kΩ resistor.

$$\text{Thus } v_C(0^-) = 0V = v_C(0^+)$$

$$\therefore w_C(0^+) = 0J$$

Note: The units for energy are Joules.

EX:

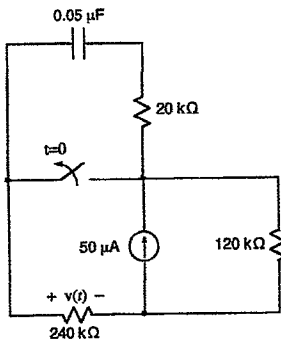Write a numerical expression for $v(t)$ for $t > 0$.

Sol'n: We use general form of solution for RC circuits.

$$v(t > 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

We find $v(0^+)$, $v(t \rightarrow \infty)$, and R_{Th} .


We start at $t=0^-$ to find voltage on C at $t=0^+$.

$t=0^-$: C acts like open circuit. Switch is closed.

Switch creates a short circuit, and $v_C(0^-) = 0V$.

$t=0^+$: $v_C(0^+) = v_C(0^-) = 0V$ since v_C can't change instantly.

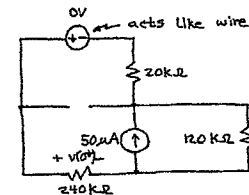We model C as voltage source of 0V. Thus, it acts like a wire.



This is a current-divider circuit with $20k\Omega + 240k\Omega = 260k\Omega$ on one side and $120k\Omega$ on the other side.

The current thru the 240kΩ is

$$i(0^+) = 50\mu A \cdot \frac{120k\Omega}{20k\Omega + 240k\Omega + 120k\Omega}$$


$$i(0^+) = 50\mu A \cdot \frac{120k\Omega}{380k\Omega}$$

$v(0^+)$ from Ohm's Law is

$$v(0^+) = 50\mu A \cdot \frac{120k\Omega}{380k\Omega} \cdot 240k\Omega$$

$$v(0^+) = 6V \cdot \frac{12}{19}$$

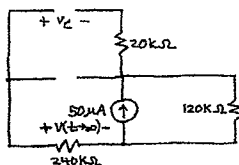
$t \rightarrow \infty$: Switch is open. C = open circuit.



No current can flow thru the 240kΩ resistor.

$$\therefore v(t \rightarrow \infty) = 0V$$

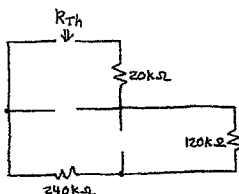R_{Th} : We look in from the terminals where C is connected, and we turn off the current source.



$$R_{Th} = 20k\Omega + 120k\Omega + 240k\Omega = 380k\Omega$$

127

The time constant is $R_{Th}C$.

$$\tau = 380k\Omega \cdot 0.05\mu F = 19ms$$


Putting results together:

$$v(t > 0) = 0V + \left(6V \cdot \frac{12}{19} - 0V\right) e^{-t/19ms}$$

or

$$v(t > 0) = 6V \cdot \frac{12}{19} e^{-t/19ms} \approx 3.8V e^{-t/19ms}$$


Ex:

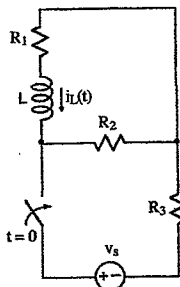

- Write an expression for $i_L(t=0^+)$
- Write an expression for $i_L(t>0)$ in terms of R_1, R_2, R_3, v_s , and L .

Sol'n: a) $i_L(0^+) = i_L(0^-)$

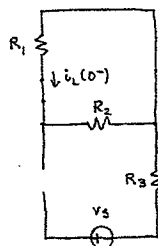At $t=0^-$, L acts like wire.
Switch is open at $t=0^-$.



There is no power source in the R_1, R_2 loop, and v_s is disconnected.
 $\therefore i_L(0^-) = 0A$


Thus, $i_L(0^+) = i_L(0^-) = 0A$

b) For $i_L(t>0)$, we use the general form of sol'n for RL problems:

$$i_L(t > 0) = i(t \rightarrow \infty) + [i_L(0^+) - i_L(t \rightarrow \infty)] e^{-t/L/R_{Th}}$$


$t=0^+$: We model L as i-src with value $i_L(0^+) = i_L(0^-) = 0A$.

Switch is closed.

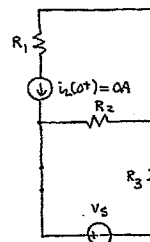

Since the quantity we are looking for is $i_L(0^+)$, we do not have to solve the circuit, but this is the circuit we would use.

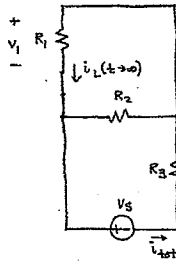$t \rightarrow \infty$: L acts like wire
Switch is closed



We can calculate i_{tot} as

$$i_{tot} = \frac{-V_s}{R_1 \parallel R_2 + R_3}$$

Then we can use a current divider to find $i_L(t \rightarrow \infty)$:

$$i_L(t \rightarrow \infty) = i_{tot} \cdot \frac{R_2}{R_1 + R_2}$$

$$i_L(t \rightarrow \infty) = \frac{-V_s}{R_1 \parallel R_2 + R_3} \cdot \frac{R_2}{R_1 + R_2}$$

Another way to calculate i_{tot} is to write $R_1 \parallel R_2$ in a different way:

$$R_1 \parallel R_2 = \frac{R_1}{1 + \frac{R_1}{R_2}}$$

Then we use a voltage divider formula:

$$V_1 = -V_s \frac{R_1}{1 + R_1/R_2} \cdot \frac{R_1}{R_1 + R_3}$$


$$V_1 = -V_s \frac{R_1}{R_1 + R_3 (1 + R_1/R_2)}$$

We divide V_1 by R_1 to find $i_L(t \rightarrow \infty)$:

$$i_L(t \rightarrow \infty) = \frac{-V_s}{R_1 + R_3 (1 + R_1/R_2)}$$


This answer is equivalent to our previous answer

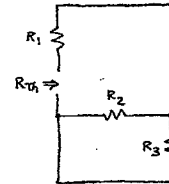R_{Th} : We turn off the V_s source and look in from the terminals where L is connected. Switch is closed.



$$R_{Th} = R_1 + R_2 \parallel R_3$$


EX:

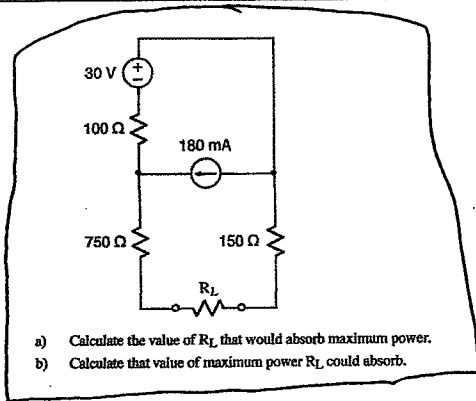

- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

Sol'n: a) $R_L = R_{Th}$ for max power transfer

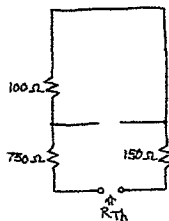We find R_{Th} by looking into the terminals where R_L is connected (but without R_L) with the two independent sources turned off.



$$R_{Th} = 750 \Omega + 100 \Omega + 150 \Omega$$

$$R_{Th} = 1k\Omega$$


$$\therefore R_L = 1k\Omega$$

$$b) \max pwr = \left(\frac{V_{Th}}{2} \right)^2 \frac{1}{R_{Th}}$$

We find V_{Th} as the open circuit voltage across the terminals where R_L is connected.

We find V_{Th} by using superposition.

case I: 30V on, 180 mA off

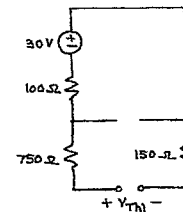


Since no current flows, there is no v -drop across the R 's.

$$\therefore V_{Th} = -30V \quad (-v \text{ src})$$

Note: Since we will square V_{Th} , the polarity we choose for measuring V_{Th} doesn't matter.

case II: 30V off, 180 mA on

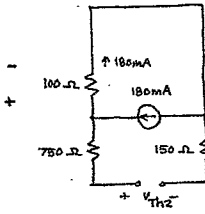

No current flows in the 750 ohm and 150 ohm. Thus, there is no v-drop across these R's.

The v-drop across the 100 ohm is equal to V_{Th2} .

$$V_{Th2} = 180 \text{ mA} \cdot 100 \Omega = 18 \text{ V}$$

We sum results to find V_{Th} .

$$V_{Th} = V_{Th1} + V_{Th2}$$

$$V_{Th} = -30 \text{ V} + 18 \text{ V} = -12 \text{ V}$$

$$\text{max pwr} = \frac{(V_{Th})^2}{R_{Th}} = \frac{6^2}{1k} = 36 \text{ mW}$$

$$\text{or } i_{12} = i_s \frac{R_2 / \alpha}{R_2 + 1/\alpha}$$

$$\text{or } i_{12} = i_s \frac{R_2 / \alpha}{R_2 / \alpha + R_1 (R_2 + 1/\alpha)}$$

$$\text{or } i_{12} = i_s \frac{R_2}{R_2 + R_1 (\alpha R_2 + 1)}$$


We sum i_{11} and i_{12} to get i_1 :

$$i_1 = i_{11} + i_{12}$$

$$\text{or } i_1 = -\frac{V_s}{R_1 + R_2 \parallel \frac{1}{\alpha}} + i_s \frac{R_2}{R_2 + R_1 (\alpha R_2 + 1)}$$

Note: When a current source is off it becomes an open circuit.
When a voltage source is off it becomes a wire.


Ex:

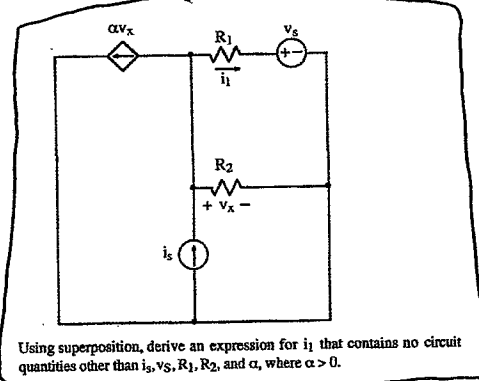

Using superposition, derive an expression for i_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and α , where $\alpha > 0$.

Sol'n: We turn on one source at a time. (Never turn off dependent source.)

case I: v_s on, i_s off

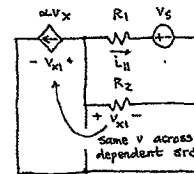

The dependent source is equivalent to $R_{eq} = \frac{v}{i} = \frac{v_{x1}}{\alpha v_{x1}} = \frac{1}{\alpha}$.