

Unit 3



Capacitor (C in Farads)

$$i(t) = C \frac{dV(t)}{dt}$$

- Parallel plates dielectric between V causes i to flow
- stores charge on plates like a small battery

V can not change instantly for C

V constant $\Rightarrow i=0$ ($\frac{dV}{dt}=0$)

$$\text{Energy} = \frac{1}{2} CV^2$$

General Equation:

$$x(t) = \text{Final} + [\text{Initial} - \text{Final}] e^{-(t-t_0)/\tau}$$

procedure:

1. Find Initial value on cap / inductor before switch ($t=0^-$)
 $\{ i_c(t=0^-) \text{ OR } V_c(t=0^-) \}$

\Rightarrow Note: voltage in C cannot change instantaneously

$$V_c(t=0^-) = V_c(t=0^+) \quad \{ V \text{ src.} \}$$

\Rightarrow Note: current in L cannot change instantaneously

$$i_L(t=0^-) = i_L(t=0^+) \quad \{ I \text{ src.} \}$$

2. Find final value on C/L ($t \rightarrow \infty$)

\Rightarrow Note: use $V_c(t) = 0$ (wire), $i_L(t) = 0$ (open)


3. Find τ (use switch in FINAL position)

$$\tau = \text{Req. } C$$

OR $\tau = \frac{L}{\text{Req.}}$, where Req is R seen by element

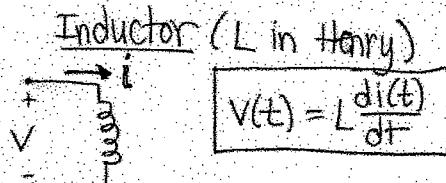4. Plug into general equation

Note: If finding other variables, relate to $V_c(t)$ or $i_L(t)$ eq.



Inductor (L in Henry)

$$V(t) = L \frac{di(t)}{dt}$$

(95)

i cannot change instantly for L


i constant $\Rightarrow V=0$ ($\frac{di}{dt}=0$)

$$\text{Energy} = \frac{1}{2} Li^2$$

<u>Cap</u> Series: $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$ parallel: $C_{eq} = C_1 + C_2$	<u>Ind</u> Series: $\frac{1}{L_{eq}} = L_1 + L_2$ parallel: $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$
--	--

start time at switch (usually set to zero)

Derivation

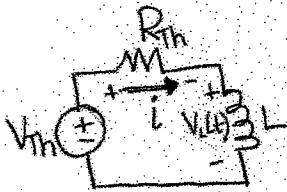

$$\begin{aligned} \text{V-loop} \\ +V_m - iR_m - V_c(t) = 0 \\ V_m - iR_m - L \frac{di(t)}{dt} = 0 \\ L \frac{di(t)}{dt} = +V_m - iR_m \end{aligned}$$

$$i(t) = \frac{dI}{dt} = \frac{-i(R_m - V_m)}{L}$$

$$\int_{i(t_0)}^{i(t)} \frac{di(t)}{dt} dt = \int_{t_0}^t -\frac{1}{L} (R_m - V_m) dt$$

$$\frac{1}{R_m} \left[\ln(R_m i(t) - V_m) - \ln(R_m i(t_0) - V_m) \right] = -\frac{(t-t_0)}{L}$$

$$\ln \left[\frac{R_m i(t) - V_m}{R_m i(t_0) - V_m} \right] = -\frac{(t-t_0)}{L} R_m$$

$$R_m i(t) - V_m = (R_m i(t_0) - V_m) e^{-\frac{(t-t_0)}{L} R_m}$$

$$i(t) = \frac{V_m}{R_m} + \left(i(t_0) - \frac{V_m}{R_m} \right) e^{-\frac{(t-t_0)}{L} R_m}$$

Note: after a long time ($t \rightarrow \infty$)

V_m = constant and so $V_c(t \rightarrow \infty) = 0$ (wire)
so $i_c(t \rightarrow \infty) = \frac{V_m}{R_m}$ (final value)

$i(t_0)$ = initial value

$$\gamma = \frac{1}{L} R_m$$

$$i(t) = \text{Final} + (\text{initial} - \text{final}) e^{-\frac{(t-t_0)}{T}}$$

Recall #1

$$\int \frac{du}{a+bu} = \frac{1}{b} \ln|au+b| + C$$

Recall #2

$$\ln a - \ln b = \ln \left(\frac{a}{b} \right)$$

(9b)

$$\begin{aligned} & \text{V-loop} \\ & +V_m - i_c(t) R_m - V_c(t) = 0 \\ & V_m - i_c(t) R_m - C \frac{dv_c(t)}{dt} = 0 \end{aligned}$$

$$\frac{dv_c(t)}{dt} = \frac{V_m - V_c(t)}{R_m C}$$

$$\int_{V_c(t_0)}^{V_c(t)} \frac{dv_c(t)}{dt} dt = \int_{t_0}^t \frac{1}{R_m C} dt$$

$$\ln(V_c(t) - V_m) - \ln(V_c(t_0) - V_m) = -\frac{(t-t_0)}{R_m C}$$

$$\ln \left[\frac{(V_c(t) - V_m)}{V_c(t_0) - V_m} \right] = -\frac{(t-t_0)}{R_m C}$$

$$V_c(t) - V_m = (V_c(t_0) - V_m) e^{-\frac{(t-t_0)}{R_m C}}$$

$$V_c(t) = V_m + (V_c(t_0) - V_m) e^{-\frac{(t-t_0)}{R_m C}}$$

Note: After a long time ($t \rightarrow \infty$)

V_m = constant and so $i_c(t) = 0$ (open)
so $V_c(t \rightarrow \infty) = V_m$ (final value)

$V_c(t_0)$ = initial value


$$\gamma = R_m \cdot C$$

$$\therefore V_c(t) = \text{Final} + [\text{initial} - \text{final}] e^{-\frac{(t-t_0)}{\gamma}}$$


Homework #5 Examples

(97)


1.

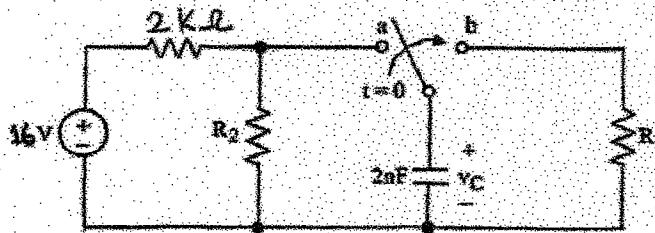

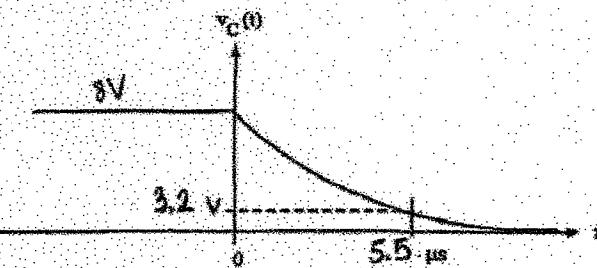After being in position a for a long time, the switch moves to position b at $t = 0$. Find R_2 and R_3 that give the following plot for $v_C(t)$:



1. ($t=0^+$) \Rightarrow

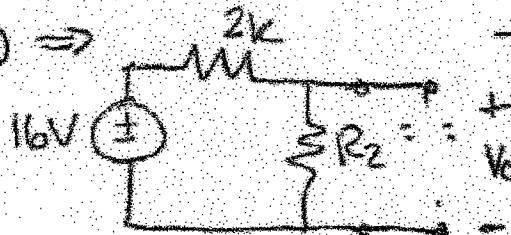

$$v_C = \frac{16(R_2)}{R_2 + 2k}$$

$(t=0^+)$ \Rightarrow because cap v can not change instantaneously

$$V_C(t=0^+) = V_C(t=0^+) = \frac{16(R_2)}{R_2 + 2k}$$

From graph \rightarrow

$$V_C(t=0^+) = 8V$$

$$8 = \frac{16(R_2)}{R_2 + 2k} \Rightarrow 8R_2 + 16k = 16R_2 - 8R_2$$

$$\boxed{R_2 = 2k\Omega}$$

$(t=\infty)$:



$$V_C = 0$$

$$\gamma = R_3(2n)$$

$$V_C(t) = 8 + (0-8)(1-e^{-t/(2n)}) = +8e^{-t/(2n)}$$

From graph $V(5.5\mu s) = 3.2V$


$$3.2 = 8e^{-5.5\mu s / (2n)}$$

$$\ln \frac{3.2}{8} = -\frac{5.5\mu s}{R_3(2n)} \Rightarrow R_3 = \frac{-5.5\mu s}{2n(\ln(\frac{3.2}{8}))} \approx \boxed{3k\Omega}$$


Homework #5 Example

(98)

1.

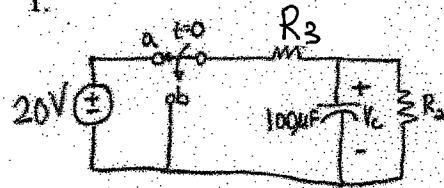


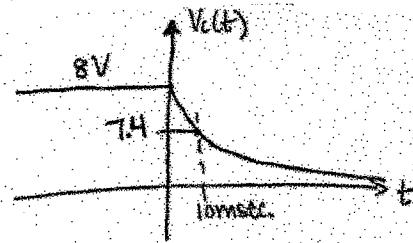After being in position a for a long time, the switch moves to position b at $t=0$. Find R_2 and R_3 that gives the plot below for $V_c(t)$.




Homework #5 Examples

2

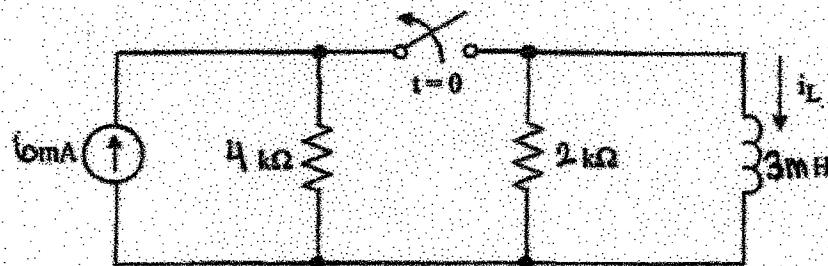

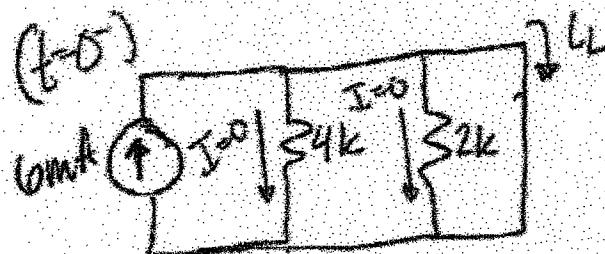After being closed for a long time, the switch opens at $t = 0$. Find $i_L(t)$ for $t > 0$.



$$i_L = 6\text{mA}$$

$(t=0^+)$: • inductor current remains the same
 $i_L(t=0) = i_L(t=0^+) = 6\text{mA} \leftarrow (\text{initial value})$


$(t=\infty)$:



$$i_L = 0$$

$$i_L(t) = 6\text{mA} + (0 - 6\text{mA})(1 - e^{-t/\tau})$$

(switch at $t = \infty$):

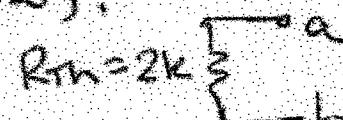


$$\therefore i_L(t) = +6\text{mA} e^{-t/3m/2k} \text{ A}$$

Homework #5 Example

100

2.

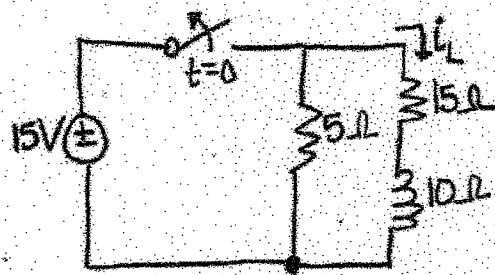


After being closed for a long time, the switch opens at $t = 0$. Find $i_L(t)$ for $t > 0$.

Homework #5 Examples


101

3.

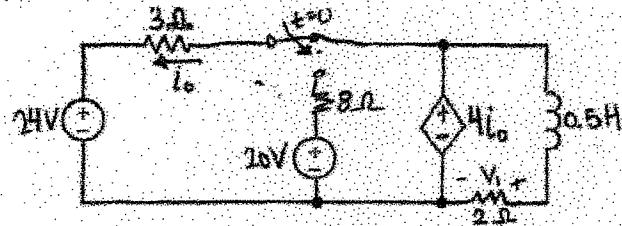

After being in the above position for a long time, the switch changes at $t=0$. Find $v_L(t)$ for $t > 0$.

$(t=0^-)$:

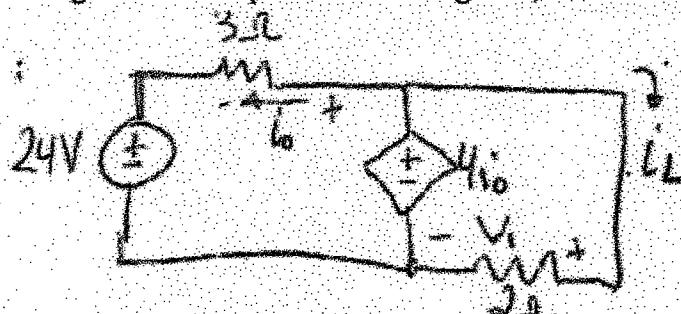


$$+4i_o - 3i_o - 24 = 0$$

$$i_o = +24V/2$$

$$i_L = \frac{4i_o}{2} = \frac{4(24)}{2} = 48A$$



$(t=0^+)$: Inductor current stays the same $\Rightarrow i_L(t=0^+) = i_L(t=0^-) = 48A$ ← initial value

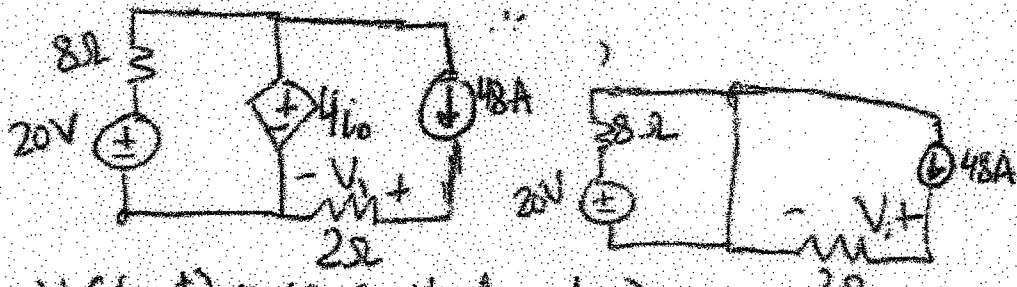Note that
 V_L changes
from $t=0^-$
to $t=0^+$.



$$V_L(t=0^+) = 48(2) \text{ (initial value)}$$

$(t=\infty)$:

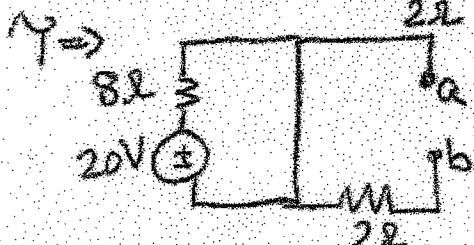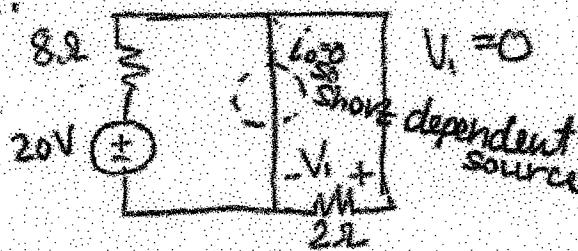


$$\frac{L}{R_m} = \frac{0.5}{2} = 0.25$$

$$V_L(t) = 96 + (0.96)(1 - e^{-t/0.25}) = 96e^{-4t} V$$

Homework #5 Example

3.

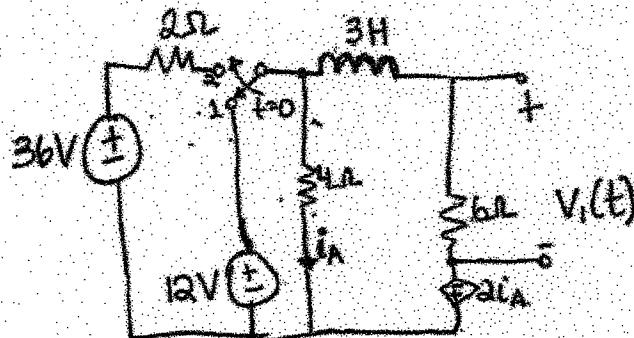


After being at position 1 for a long time, the switch moves to position 2 at $t=0$. Find $v_1(t)$ for $t > 0$.


Homework #5 Examples

103

4.

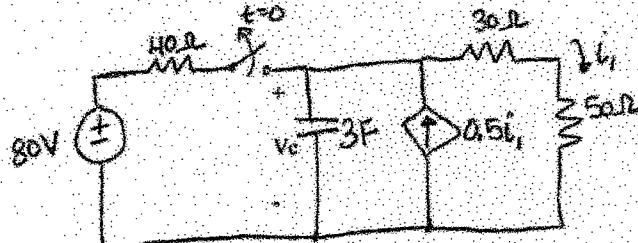

After being closed for a long time, the switch opens at $t=0$. Find $V_c(t)$ for $t > 0$.

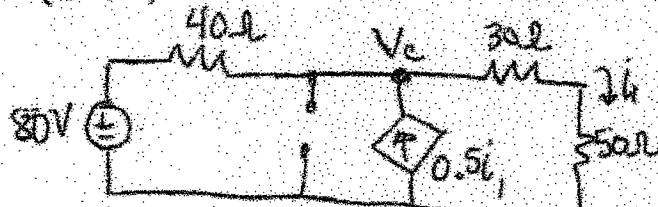 $(t=0^-)$


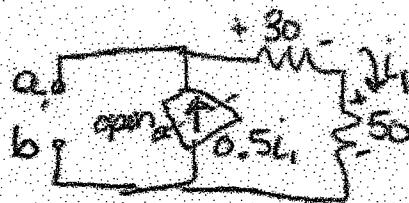
$$\frac{V_c - 80}{40} - 0.5i_1 + \frac{V_c}{80} = 0$$

$$i_1 = \frac{V_c}{80}$$

$$\frac{V_c}{40} - 0.5\left(\frac{V_c}{80}\right) + \frac{V_c}{80} = \frac{80}{40}$$

$$V_c \left(\frac{4}{160} - \frac{1}{160} + \frac{2}{160} \right) = \frac{80}{40}$$


$$V_c = 2 \cdot \frac{1}{(5/160)} = \frac{2(160)}{5}$$

 $(t \rightarrow \infty)$


$$0.5i_1 - i_1 = 0 \Rightarrow i_1 = 0$$

 $V_c = 0V \leftarrow \text{final}$

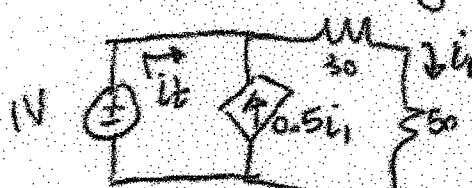Need to use a test supply since $V_{Th}=0$ and $R_{Th} \neq 0$ or the capacitor will not discharge. It must though since $V_c=0$ as a final value and it started with 64V initially.



$$i_t + 0.5i_1 - i_1 = 0$$

$$i_t = 0.5i_1$$

$$i_1 = \frac{1}{80}$$

$$i_t = 0.5\left(\frac{1}{80}\right) = \frac{1}{160}$$


$$R_{Th} = \frac{1}{160} = 160/2$$

$$V_c(t) = 64e^{-t/480} V$$

Homework #5 Example

104

4.

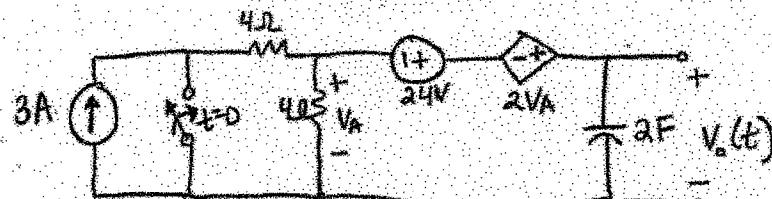

After being open for a long time, the switch closes at $t=0$. Find $V_o(t)$ for $t > 0$.

Examples


Dr. Cotter

UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT



ECE 1000

Spring 2005

1.

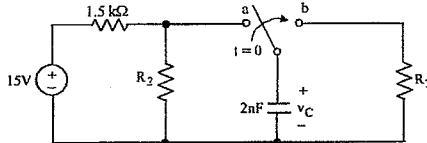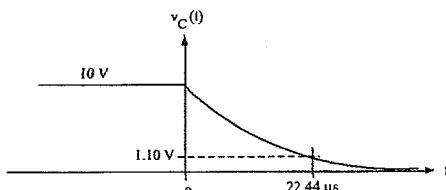
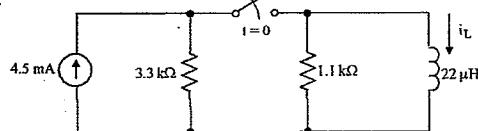
ERC²

After being in position a for a long time, the switch moves to position b at $t = 0$. Find R_2 and R_3 that give the following plot for $v_C(t)$:

ERL²

After being closed for a long time, the switch opens at $t = 0$. Find $i_L(t)$ for $t > 0$.

ECE 1000

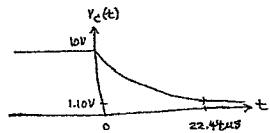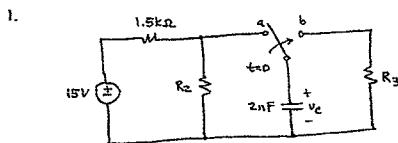


Find R_2 and R_3 to give above plot.

Soln: R_2 determines init voltage on C.

From plot, $v_C(t=0^-) = 10V$.

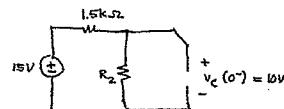Circuit model at $t=0^-$: C acts like open circuit.



$$\text{Use } V\text{-divider: } v_C(0^-) = 15V \cdot \frac{R_2}{R_2 + 1.5k\Omega} = 10V$$

$$\therefore \frac{R_2}{R_2 + 1.5k\Omega} = \frac{2}{3} \quad \text{or} \quad 3R_2 = 2(R_2 + 1.5k\Omega)$$

$$R_2 = 3k\Omega$$

R_3 determines the time constant = $R_3 C$

using the general soln for $v_C(t)$ we have:

ECE 1000

$$\text{Soln: 1. cont. } v_C(t>0) = v_C(t=0^-) + [v_C(t=0^+) - v_C(t=0^-)] e^{-t/R_3 C}$$

0V	0V	0V
10V	10V	10V

$$v_C(t>0) = 10V e^{-t/R_3 C} \quad \text{where } C = 2nF$$

From the plot, we have $v_C(22.44 \mu s) = 1.10V$.

$$\therefore 1.10V = 10V e^{-22.44 \mu s / R_3 C}$$


Solve for R_3 :

$$\ln \frac{1.10V}{10V} = -22.44 \mu s / R_3 C$$

$$R_3 = -\frac{22.44 \mu s / 2nF}{\ln \frac{1.10V}{10V}}$$

$$R_3 \approx 5.1 k\Omega$$

2.

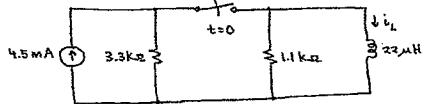
Find $i_L(t)$ for $t > 0$.

sol'n: We use general sol'n:

$$i_L(t > 0) = i_L(t \rightarrow \infty) + [i_L(t=0^+) - i_L(t \rightarrow \infty)] e^{-t/L/R_{Th}}$$

To find $i_L(t=0^+)$, we start at $t=0^-$.

$t=0^-$: Treat L as wire when circuit has been sitting for a long time, (so $\frac{di_L}{dt} = 0 \Rightarrow V_L = L \frac{di_L}{dt} = 0$).

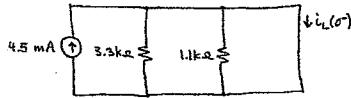Find $i_L(0^-)$ because $i_L(0^+) = i_L(0^-)$.Switch is closed at $t=0^-$.

All the current will flow thru the wire.

$$i_L(0^-) = 4.5 \text{ mA}$$

Since the energy stored by the inductor cannot change instantly, $i_L(0^+) = i_L(0^-)$.
 $\therefore i_L(0^+) = 4.5 \text{ mA}$

sol'n 2. cont.


To find $i_L(t \rightarrow \infty)$, we again treat L as wire. $t \rightarrow \infty$: Switch open. 4.5mA and 3.3kΩ not connected.

$$i_L(t \rightarrow \infty) = 0 \text{ A}$$

No power source
so current = 0A.

$$i_L(t \rightarrow \infty) = 0 \text{ A}$$

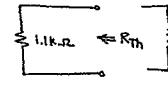The time constant is $\frac{L}{R_{Th}}$ where R_{Th} is from the Thevenin equivalent of circuit (for $t > 0$) where L is connected.



$$R_{Th} = 1.1 \text{ k}\Omega$$


$$\frac{L}{R_{Th}} = \frac{22\mu\text{H}}{1.1 \text{ k}\Omega} = 20 \text{ ns}$$

Plug quantities into general sol'n:


$$i_L(t > 0) = 0 \text{ A} + [4.5 \text{ mA} - 0 \text{ A}] e^{-t/20 \text{ ns}}$$

$$\text{or } i_L(t > 0) = 4.5 \text{ mA} e^{-t/20 \text{ ns}}$$

3.

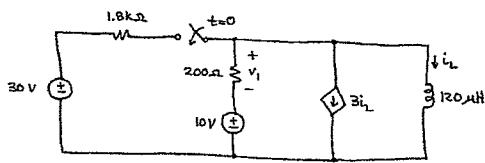Find $v_i(t)$ for $t > 0$.sol'n: Find i_L for $t=0^-$.

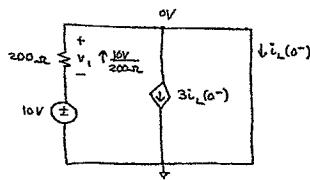$t=0^-$: Switch is open. L = wire.
 30V and 1.8kΩ not connected.



Because L = wire, we have 10V across 200Ω (so 10V src + $v_{200\Omega} = 0 \text{ V}$).


Thus, current $\frac{10V}{200\Omega}$ flows upward thru 200Ω .

This current equals $3i_L(0^-) + i_L(0^-)$.

$$\therefore \frac{10V}{200\Omega} = 3i_L(0^-) + i_L(0^-) = 4i_L(0^-)$$

$$50 \text{ mA} = 4i_L(0^-)$$

$$i_L(0^-) = \frac{50 \text{ mA}}{4} = 12.5 \text{ mA}$$

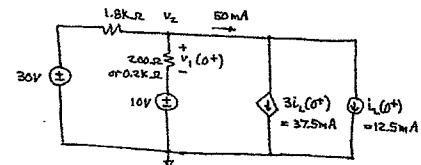sol'n 3. cont. Now find $v_1(t=0^+)$. $t=0^+$: Switch is closed:L = current source at $t=0^+$
 $i_L(0^+) = i_L(0^-)$ since i_L doesn't
 " = 12.5 mA change instantlyUse node voltage to find v_2 .

$$\frac{v_2 - 30V}{1.8k\Omega} + \frac{v_2 - 10V}{0.2k\Omega} + 50 \text{ mA} = 0 \text{ A}$$

$$v_2 \left(\frac{1}{1.8k\Omega} + \frac{1}{0.2k\Omega} \right) = \frac{30V}{1.8k\Omega} + \frac{10V}{0.2k\Omega} - 50 \text{ mA}$$

$$v_2 \left(\frac{1}{1.8k\Omega} + \frac{1}{0.2k\Omega} \right) \cdot 1.8k\Omega = 30V$$

$$v_2 (1 + 9) = 30V$$

$$v_2 = \frac{30V}{10} = 3V$$


$$10V + v_1(0^+) = v_2 = 3V$$

$$v_1(0^+) = -7V$$

Sol'n: 3. cont. Now find $v_i(t \rightarrow \infty)$.


$t \rightarrow \infty$: Switch is closed.

L = wire

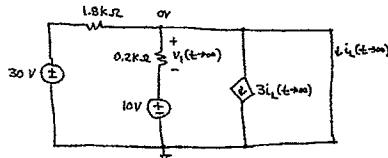

The voltage across 10V src and 0.2kΩ is 0V. $\therefore v_i(t \rightarrow \infty) = -10V$

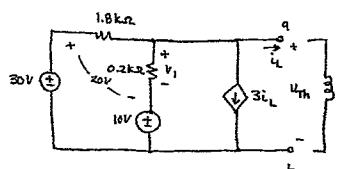Now find time constant $\frac{L}{R_{Th}}$. R_{Th} is for circuit where L is connected.



$$V_{Th} = V_{ab} \text{ open circ}$$


$i_L = 0$ so we treat $3i_L$ src as open circuit.

We could use node voltage method to find V_{ab} , but a simpler approach is to observe that we have 20V across 1.8kΩ and 0.2kΩ in series.

Sol'n: 3. cont. Using a voltage divider, $v_i = 20V \cdot \frac{0.2k\Omega}{0.2k\Omega + 1.8k\Omega} = 2V$.

$$\therefore V_{Th} = V_{ab} \text{ open circ} = 10V + v_i = 12V$$

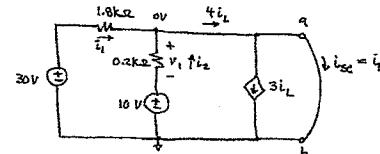Now short a, b terminals to find i_{sc} .



This is the same circuit as for $t \rightarrow \infty$. Using the value of 0V on the top node, we can find i_1 and i_2 :

$$i_1 = \frac{30V}{1.8k\Omega} \quad i_2 = \frac{10V}{0.2k\Omega}$$

Summing currents, we have

$$-i_1 - i_2 + 4i_L = 0A$$

$$\text{or } i_L = i_{sc} = \frac{i_1 + i_2}{4} = \frac{30V + 10V}{4 \cdot 1.8k\Omega} = \frac{120V}{4 \cdot 1.8k\Omega}$$

$$i_{sc} = \frac{30V}{1.8k\Omega} + \frac{10V}{1.8k\Omega} = \frac{120V}{4 \cdot 1.8k\Omega}$$

$$i_{sc} = \frac{30V}{1.8k\Omega}$$

$$R_{Th} = V_{Th}/i_{sc} = \frac{12V}{30V/1.8k\Omega} = 1.8k\Omega \frac{12V}{30V}$$

$$R_{Th} = 1.8k\Omega \cdot \frac{5}{5} = \frac{3.6k\Omega}{5} = 720\Omega$$

Sol'n: 3. cont. Our time constant is $\frac{L}{R_{Th}} = \frac{120\mu H}{720\Omega} = \frac{1}{6} \mu s$.


Plug values into general soln:

$$v_i(t=0) = v_i(t \rightarrow \infty) + [v_i(0^+) - v_i(t \rightarrow \infty)] e^{-t/L/R_{Th}}$$

$$v_i(t=0) = -10V + [-7V - -10V] e^{-t/1/6 \mu s}$$

$$v_i(t=0) = -10V + 3V e^{-t/1/6 \mu s}$$

4.

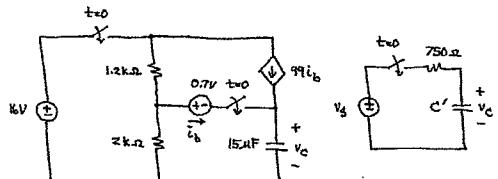

a. Find $v_c(t)$ for $t > 0$ for circuit on left


b. Find v_b and C' values that make circuit on right have same v_c as circuit on left.

Assume $v_c(0^-) = 0V$.

Sol'n: a) $v_c(0^+) = v_c(0^-) = 0V$ since v_c can't change instantly

Now find $v_c(t \rightarrow \infty)$.

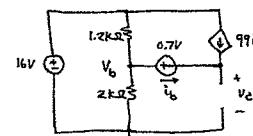$t \rightarrow \infty$: C = open
switches closed



If we sum currents at node above C, we have $-i_b - 99i_b = 0A \Rightarrow i_b = 0$.

Thus, $99i_b$ src is open.

$$\therefore v_c = v_b - 0.7V$$

Sol'n: 4.a) cont. We use v-divider formula to find V_b :

$$V_b = 16V \cdot \frac{2k\Omega}{1.2k\Omega + 2k\Omega} = 16V \cdot \frac{2k\Omega}{3.2k\Omega}$$

$$V_b = 16V \cdot \frac{20k\Omega}{32k\Omega} = \frac{1}{2} \cdot 20V$$

$$V_b = 10V$$

$$V_c(t \rightarrow \infty) = 10V - 0.7V = 9.3V$$


Now we find $R_{Th}C$. First, we find

$V_{Th} = V$ across terminals where C connected but with C removed

But this is the same as $V_c(t \rightarrow \infty)$.

$$V_{Th} = 9.3V$$

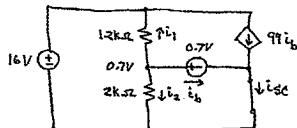Now short the terminals where C connected and find i_{sc} .



From current summation at node above C , $i_{sc} = i_b + 99i_b = 100i_b$.

Because of 0.7V src, we 0.7V at center node. We get i_b from current summation at this node.

Sol'n: 4.a) cont.

$$i_1 = \frac{0.7V - 16V}{1.2k\Omega} = -\frac{15.3V}{1.2k\Omega}$$

$$i_2 = \frac{0.7V}{2k\Omega}$$

$$i_1 + i_2 + i_b = 0A$$


$$i_b = -(i_1 + i_2) = \frac{15.3V}{1.2k\Omega} - \frac{0.7V}{2k\Omega}$$

$$i_{sc} = 100i_b = 100 \left(\frac{15.3V}{1.2k\Omega} - \frac{0.7V}{2k\Omega} \right)$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{9.3V}{100 \left(\frac{15.3V}{1.2k\Omega} - \frac{0.7V}{2k\Omega} \right)}$$

$$R_{Th} = 7.5\Omega$$

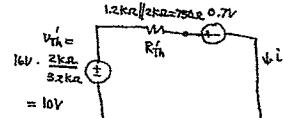This worked, but a better approach is to use a Thévenin equivalent of 16V, $1.2k\Omega$, and $2k\Omega$.



$$\text{We have } i_b = \frac{V_{Th}' - 0.7V}{R_{Th}'} = \frac{9.3V}{750\Omega}$$

$$i_{sc} = 100i_b = \frac{9.3V}{750\Omega} \cdot 100$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{9.3V}{\frac{9.3V \cdot 100}{750\Omega}} = \frac{750\Omega}{100} = 7.5\Omega$$

Sol'n: 4.b) cont. Plug values into general soln.

$$V_c(t > 0) = V_c(t \rightarrow \infty) + [V_c(0^+) - V_c(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

$$R_{Th}C = 7.5\Omega \cdot 15\mu F = 112.5\mu s$$

$$V_c(t > 0) = 9.3V [1 - e^{-t/112.5\mu s}]$$

For circuit on right, we have $V_c(0^+) = V_c(0^-) = 0V$ (given). We also have $V_c(t \rightarrow \infty) = V_s$ and $RC' = 750\Omega \cdot C'$.

To make the V_c 's the same for the two circuits, we use $V_s = 9.3V$ and


$$C' = \frac{RC}{750\Omega} = \frac{7.5\Omega \cdot 15\mu F}{750\Omega} = 150\text{nF}$$

$$C' = 150\text{nF}$$

Superposition Example


109

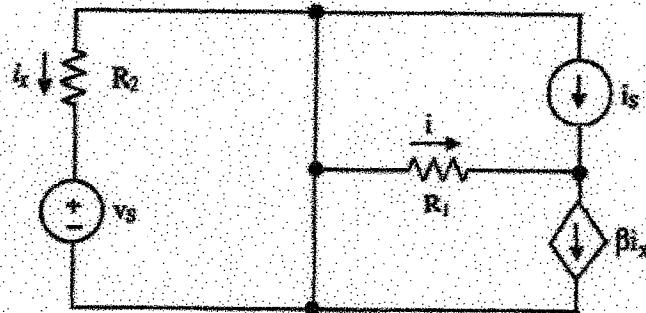- if $V=0$, treat as a wire.
- if $I=0$, treat as an open.



Using superposition, derive an expression for i that contains no circuit quantities other than i_s , V_s , R_1 , R_2 , and β .

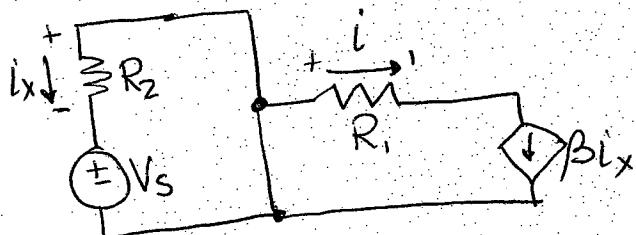- Turn on only 1 independent source, all others off.
< Dependent sources always stay in circuit >
- Redraw circuit (V_s on, i_s off (open))




$$V\text{-loop: } +V_s + i_x R_2 = 0$$

$$i_x = -\frac{V_s}{R_2}$$

$$i = \beta i_x = -\frac{\beta V_s}{R_2} //$$

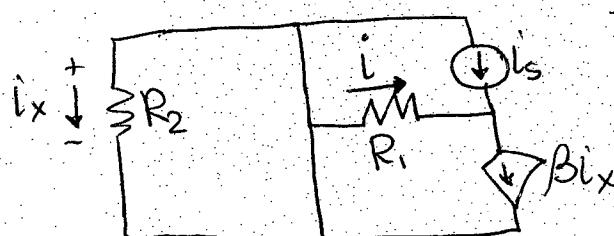- Redraw circuit (V_s off (wire), i_s on)



$$+i_x R_2 = 0 \Rightarrow i_x = 0$$

$$\beta i_x = 0 \rightarrow \text{open}$$


$$i = -i_s //$$

- Sum results of partials for total:

$$i = -\frac{\beta V_s}{R_2} - i_s$$

Max Power Example


(110)

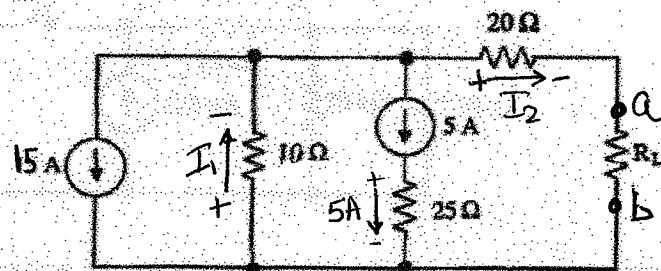

Calculate the value of R_L that would absorb maximum power, and calculate that value of maximum power R_L could absorb.

- Maximum power is absorbed in element when R_L value = R_{Th} (equivalent resistance seen by R_L)

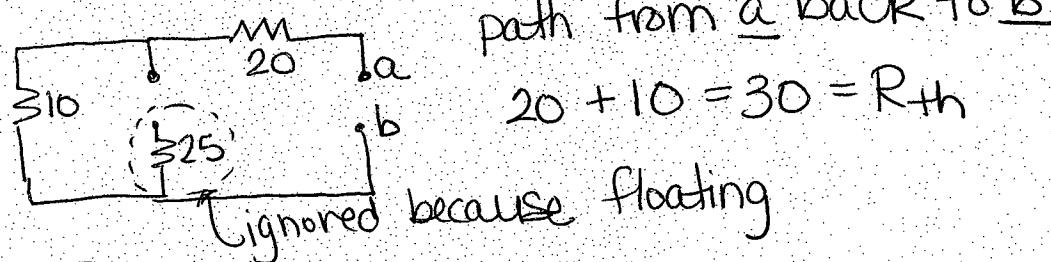
- Independent sources only in circuit. $R_{Th} = \text{Req.}$
- Set $V=0$, $I=0$ and redraw \Rightarrow



$$R_L = 30\Omega$$

$$\text{power} = \frac{(V_{Th})^2}{4(R_{Th})}$$


- Find V_{Th} (redraw circuit)

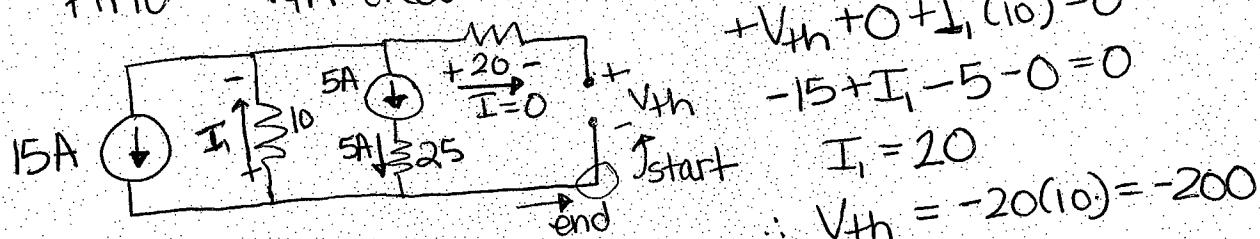

$$\text{power} = \frac{(-200)^2}{4(30)} = 333\text{W}$$

Energy Example

(1)

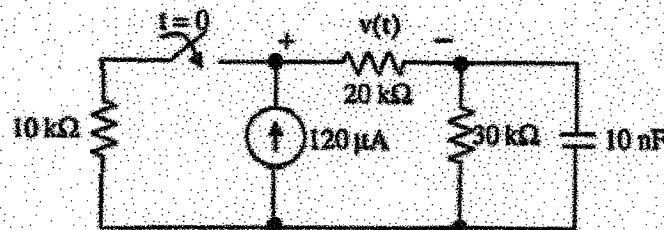


Cap \Rightarrow becomes open after a long time
 • Stays V value at $t=0^+$ (V_{src})
 $\gamma = R_{eq} \cdot C$

After being open for a long time, the switch is closed at $t=0$. Calculate the energy stored on the capacitor at $t \rightarrow \infty$.

Write a numerical expression for $v(t)$, $t > 0$.

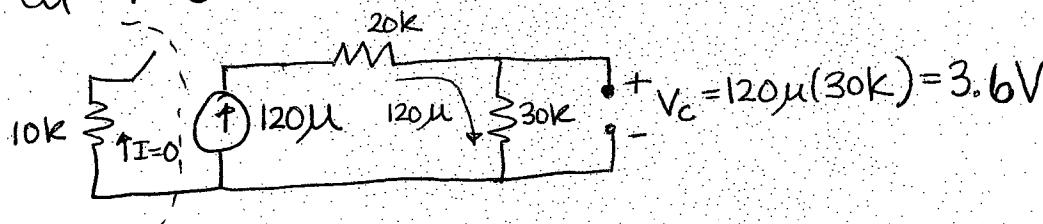at $t=0^-$: (redraw circuit - cap acts as open)



at $t=0^+$: (redraw circuit - voltage on cap cannot change instantaneously: use V_{source})


$$\text{node-voltage: } \frac{V_2}{10k} - 120\mu + \frac{V_2 - 3.6}{20k} = 0$$

$$V_2 \left(\frac{1}{10k} + \frac{1}{20k} \right) = +120\mu + \frac{3.6}{20k}$$

$$V_2 = \frac{300\mu}{150\mu} = 2V$$

$$V(t)_{t=0^+} = V_2 - 3.6 = -1.6V \quad \begin{matrix} \text{Initial} \\ \text{value} \end{matrix}$$

at $t=\infty$: (redraw, cap open)

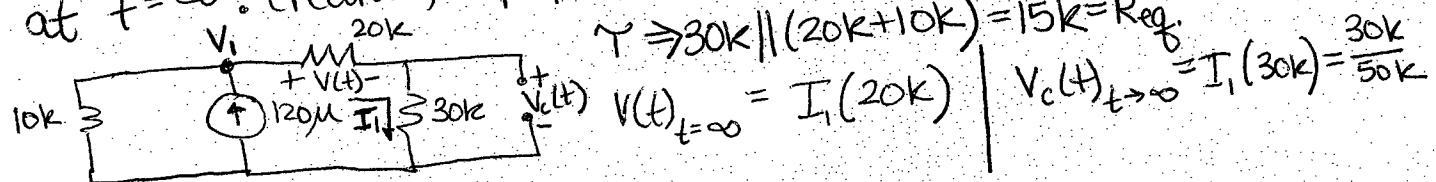

node-voltage:

$$\frac{V_1}{10k} - 120\mu + \frac{V_1}{50k} = 0 \Rightarrow V_1 \left(\frac{1}{10k} + \frac{1}{50k} \right) = 120\mu \Rightarrow V_1 = 1V$$

$$I_1 = \frac{V_1}{50k} = \frac{1}{50k} \Rightarrow V(t)_{t=\infty} = \frac{20k}{50k} = 0.4V \quad \begin{matrix} \text{Final Value} \\ -t/(15k \cdot 10n) \end{matrix}$$

for $t > 0$, $V(t) = 0.4 + (-1.6 - 0.4)e^{-(t/(15k \cdot 10n))}$


$$V(t) = 0.4 - 2e^{-t/150\mu\text{sec}} \quad \boxed{V}$$

$$W_c(t \rightarrow \infty) = \frac{1}{2}(C)(V_c(t \rightarrow \infty))^2$$

$$W_c(t \rightarrow \infty) = \frac{1}{2}(10n)(\frac{3}{5})^2 = 1.8nJ$$

Switch RL Example

112



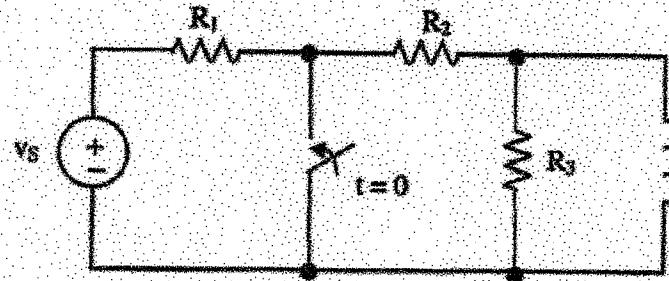


$L \Rightarrow$ becomes wire after a long time.

• I stays same at $t = 0^+$ (I_{src})

$$\gamma = \frac{L}{R_{eq}}$$

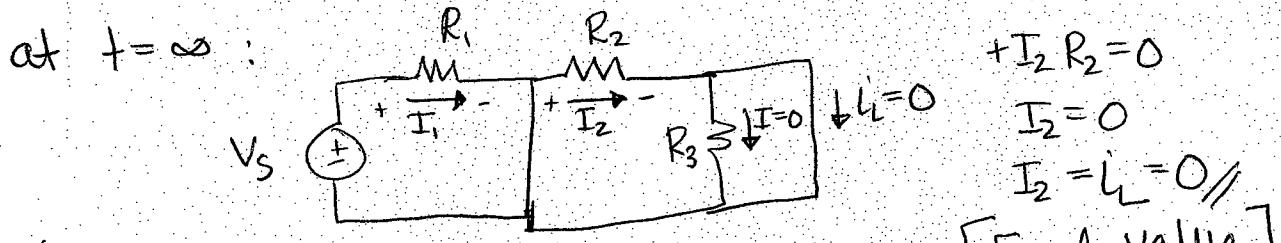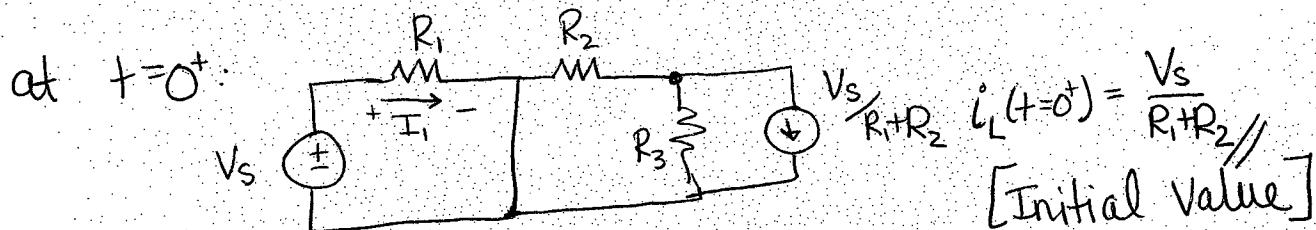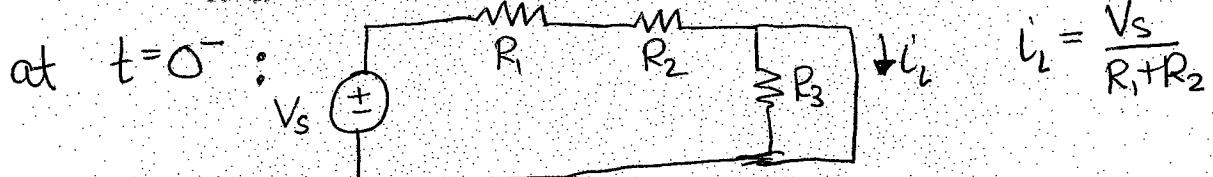After being open for a long time, the switch is closed at $t = 0$. Write an expression for $i_L(t)$.
 $t > 0$.




$t > 0$

$$i_L(t) = 0 + \left[\left(\frac{V_s}{R_1 + R_2} \right) - 0 \right] e^{-t/\gamma}$$

$\gamma \Rightarrow R_{eq} = R_3 // R_2$ (redraw)

$t > 0$

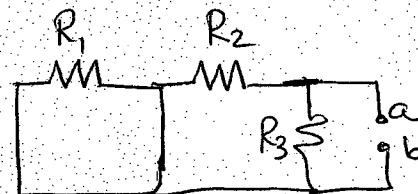
$$i_L(t) = \left(\frac{V_s}{R_1 + R_2} \right) e^{-t/(R_2 // R_3)}$$



HW #6 Examples

Dr. Gitter
113

1.

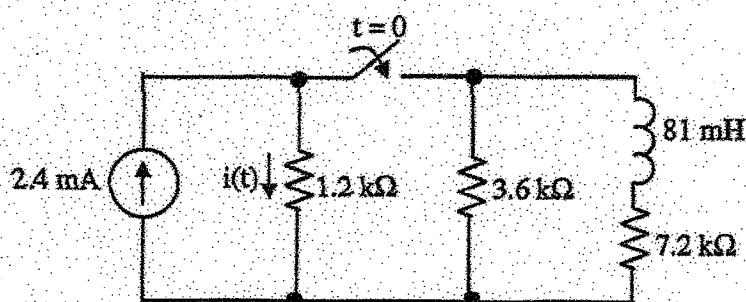


After being open for a long time, the switch is closed at $t = 0$.

Calculate the energy stored on the inductor at $t \rightarrow \infty$.

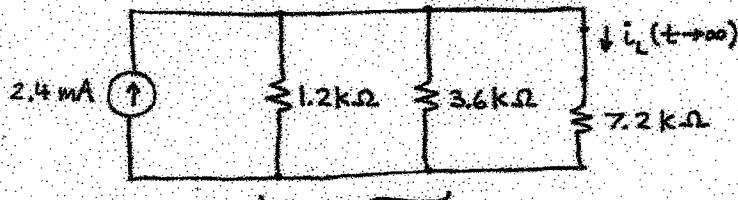2. Write a numerical expression for $i(t)$, $t > 0$.

Sol'n: 1. For $t \rightarrow \infty$, L acts like wire, switch is closed.

Find $i_L(t \rightarrow \infty)$. Energy, $w = \frac{1}{2} L i_L^2$.



$$R_{\text{eq}} = 1.2 \text{ k}\Omega \parallel 3.6 \text{ k}\Omega = 1.2 \text{ k}\Omega \cdot \frac{1}{1+3} = 1.2 \text{ k}\Omega \cdot \frac{3}{4}$$

$$R_{\text{eq}} = 0.9 \text{ k}\Omega$$

We have current divider.

$$i_L(t \rightarrow \infty) = 2.4 \text{ mA} \cdot \frac{R_{\text{eq}}}{R_{\text{eq}} + 7.2 \text{ k}\Omega} = 2.4 \text{ mA} \cdot \frac{0.9 \text{ k}\Omega}{8.1 \text{ k}\Omega}$$

$$i_L(t \rightarrow \infty) = \frac{2.4 \text{ mA}}{9} = \frac{24}{90} \text{ mA} = \frac{12}{45} \text{ mA} = \frac{4}{15} \text{ mA}$$

$$w = \frac{1}{2} 81 \text{ mH} \left(\frac{4}{15} \text{ mA} \right)^2 = \frac{1}{2} 81 \cdot \frac{16}{25 \cdot 9} \text{ nJ}$$

$$w = \frac{9(8)}{25} \text{ nJ} = \frac{72 \cdot 40}{25 \cdot 40} \text{ nJ} = 2.88 \text{ nJ}$$


$$w_L(t \rightarrow \infty) = 2.88 \text{ nJ}$$

114


sol'n: 2. We want to find $i(t=0^+)$. We start by finding $i_L(t=0^-)$ so we will know $i_L(t=0^+)$, since $i_L(t=0^+) = i_L(t=0^-)$.

$t=0^-$: L acts like wire, switch is open.

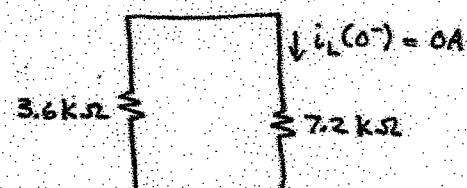No pur src for L, so L discharges to give $i_L(0^-) = 0A$.



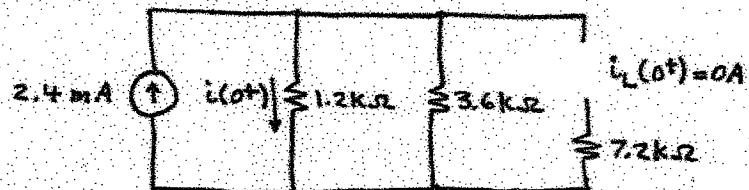
$t=0^+$: L acts like current src of value $i_L(0^+) = i_L(0^-) = 0A = \text{open circuit}$
Switch is closed.



This is a current divider.

$$i(0^+) = 2.4 \text{ mA} \cdot \frac{3.6 \text{ k}\Omega}{1.2 \text{ k}\Omega + 3.6 \text{ k}\Omega} = 1.8 \text{ mA}$$

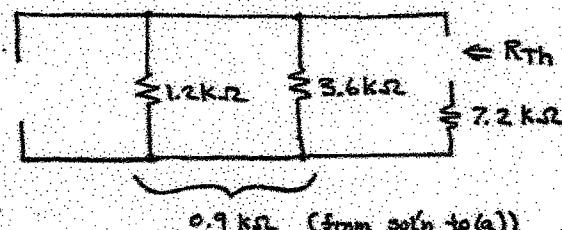For time constant $\frac{L}{R_{Th}}$, we look into the terminals where L is connected. We turn off independent 2.4 mA src which becomes open circuit.



115

sol'n: 2. cont.

$$R_{Th} = 7.2k\Omega + 0.9k\Omega = 8.1k\Omega$$

Our time constant is $\frac{L}{R_{Th}} = \frac{81mH}{8.1k\Omega} = 10\mu s$.

Find $i(t \rightarrow \infty)$ [see below].

Plug values into general solution.


$$i(t > 0) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)] e^{-t/\frac{L}{R_{Th}}}$$

$$i(t > 0) = 1.6mA + [1.8mA - 1.6mA] e^{-t/10\mu s}$$

$$i(t > 0) = 1.6mA + 0.2mA e^{-t/10\mu s}$$

$t \rightarrow \infty$: L acts like wire, switch closed

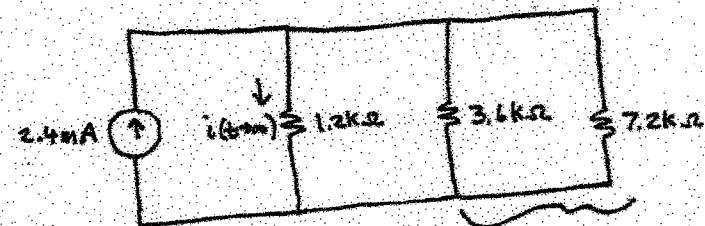Find $i(t \rightarrow \infty)$ (not i_L).




$$\begin{aligned} 3.6k\parallel 7.2k\Omega &= 3.6k\Omega \parallel 2 \\ &= 3.6k\Omega \cdot \frac{2}{3} \\ &= 2.4k\Omega \end{aligned}$$

$$i\text{-divider: } i(t \rightarrow \infty) = 2.4mA \cdot \frac{2.4k\Omega}{2.4k\Omega + 1.2k\Omega} = 1.6mA$$

Homework #6/Review Examples

116

1.

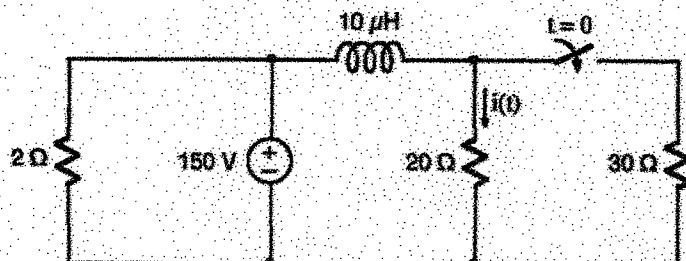


After being closed for a long time, the switch closes at $t = 0$.

Calculate the energy stored on the inductor as $t \rightarrow \infty$.

find $i(t)$ for $t > 0$.

3.

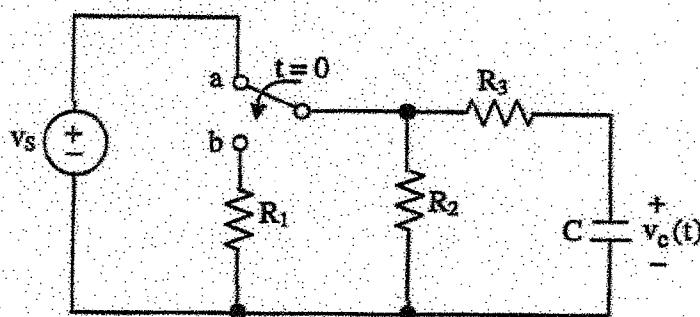

After being at position a for a long time, the switch moves to position b at time $t = 0$.


a. Write an expression for $v_c(t = 0^+)$.

b. Write an expression for $v_c(t)$, $t > 0$.

$$\text{sol'n: a) } v_c(t=0^+) = v_c(t=0^-)$$

At $t=0^-$, switch is in position a.

C acts like open circuit.

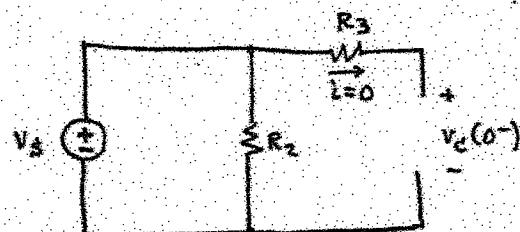

No current in R_3 means no v-drop for R_3 .

$$\therefore v_c(0^-) = V_s$$

$$v_c(0^+) = V_s$$

b) Find $v_c(t \rightarrow \infty)$ and $R_{Th}C = \text{time constant}$.


$t \rightarrow \infty$: Switch is in position b. No pur src.

C discharges thru R's

$$\therefore v_c(t \rightarrow \infty) = 0V$$

R_{Th} is resistance seen looking into terminals where C connected with switch in position b.

Sol'n: 3.6) cont.

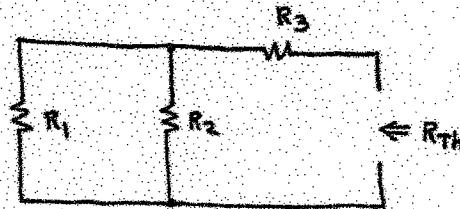

$$R_{Th} = (R_1 \parallel R_2) + R_3$$

Now plug values into general sol'n.

$$v_c(t>0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/R_{Th}C}$$


$$v_c(t>0) = ov + [v_s - ov] e^{-t/(R_1 \parallel R_2 + R_3)C}$$

$$v_c(t>0) = v_s e^{-t/(R_1 \parallel R_2 + R_3)C}$$

Homework #6/Review Examples


(119)

2.

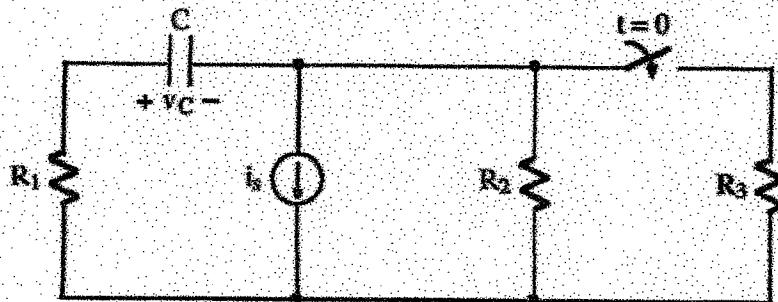

After being open for a long time, the switch closes at $t = 0$. Write an expression for $v_C(t \geq 0)$ in terms of R_1 , R_2 , R_3 , i_s , and C .


(120)

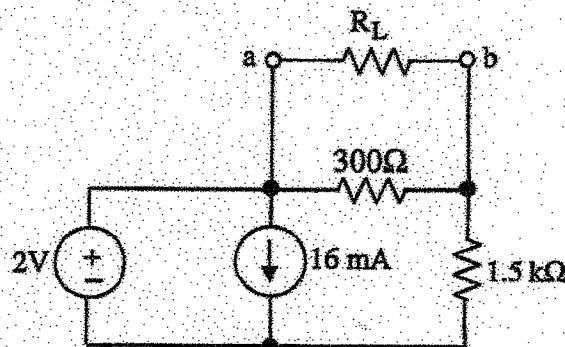

- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

Soln: a) $R_L = R_{Th}$ yields max pwr transfer

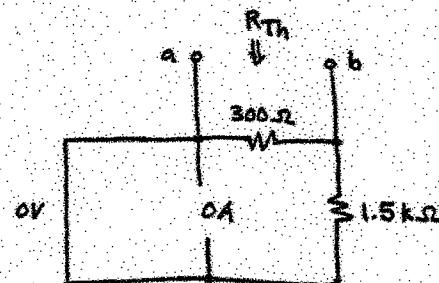We find R_{Th} by removing R_L , turning independent src's off, and seeing what resistance we have looking into terminals a,b.



$$R_{Th} = 300\Omega \parallel 1.5k\Omega = 300\Omega \cdot 1 \parallel 5 = 300\Omega \cdot \frac{5}{6}$$

$$R_{Th} = 250\Omega$$

$$\therefore R_L = 250\Omega$$


(12)

Sol'n: 4.b) Find Thevenin equivalent of circuit where R_L connected.

$$V_{Th} = V_{ab} \text{ with } R_L \text{ removed.}$$

use superposition (or other method such as node-voltage) to find V_{Th} .

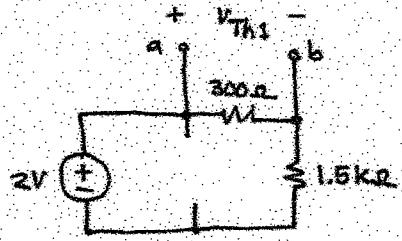case I: 2V src on, 16mA src off (open circuit)




We have v-divider.

$$V_{Th1} = 2V \cdot \frac{300\Omega}{300\Omega + 1.5k\Omega}$$

$$V_{Th1} = \frac{2V}{6}$$

case II: 2V src off, 16 mA src on
= wire

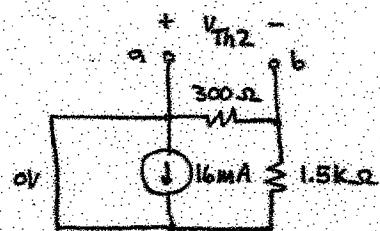

We have i-divider.

All current flows thru wire.
 $\therefore V_{Th2} = 0V$

$$V_{Th} = V_{Th1} + V_{Th2} = \frac{2V}{6} + 0V = \frac{2V}{6} = \frac{1}{3}V$$

$$\text{max pwr} = \frac{V^2}{4R_{Th}} = \frac{\left(\frac{1}{3}V\right)^2}{4 \cdot 250\Omega} = \frac{1}{q} \text{ mW}$$

$$\boxed{\text{max pwr} = \frac{1}{q} \text{ mW}}$$