

EX: If $f(t) = 2\sin(\omega t + \pi/3)$ find $P[f(t)]$, (i.e., find the phasor)

ANS: $P[f(t)] = F = 2e^{-j\pi/6} = 2\angle\pi/6$

SOL'N: If we have a cosine, we use the standard identity for phasors:

$$P[A\cos(\omega t + \phi)] = Ae^{j\phi} = A\angle\phi$$

For a sine, we multiply the standard identity by $-j$ (which is the phasor for a sine of magnitude one and zero phase shift):

$$P[\sin(\omega t)] = -j = 1\angle -90^\circ$$

Thus, we have

$$P[f(t)] = F = -2je^{j\pi/3}$$

The above is mathematically correct and works properly in solving problems, but we will apply identities to express the answer in standard form:

$$-1 = e^{j180^\circ} = e^{-j180^\circ} = e^{j\pi} = e^{-j\pi}$$

NOTE: (We use whichever of $+180^\circ$ or -180° is most convenient.)

$$j = e^{j90^\circ} = e^{j\pi/2}$$

Applying the identities:

$$F = -2je^{j\pi/3} = 2e^{-j\pi}e^{j\pi/2}e^{j\pi/3} = 2e^{-j\pi/6} = 2\angle -\pi/6.$$

EX: If $F = (2.5 + j3.2)$ find $P^{-1}[F]$, (i.e., find the inverse phasor)

ANS: $P^{-1}[F] = 4.06 \cos(\omega t + 52^\circ)$

SOL'N: We convert to polar form:

$$2.5 + j3.2 = \sqrt{2.5^2 + 3.2^2} e^{j \tan^{-1}\left(\frac{3.2}{2.5}\right)} = 4.06 e^{j52^\circ}$$

Now use the standard inverse phasor identity:

$$P^{-1}[Ae^{j\phi}] = A \cos(\omega t + \phi)$$

NOTE: There is no math to do here—we just substitute the values of A and ϕ into the $\cos(\)$.

NOTE: We don't know the value of ω for this problem. Thus, we just use a symbolic variable for ω . The value of ω is *not* part of a phasor. (The value of ω must be kept track of separately.)

Using the identity gives the answer:


$$P^{-1}[F] = 4.06 \cos(\omega t + 52^\circ)$$

NOTE: Mathematically, it is also correct to invert the given phasor in two pieces, with the real part giving a cosine term having no phase shift and the imaginary part giving a (negative) sine term having no phase shift:

$$P^{-1}[2.5 + j3.2] = 2.5 \cos(\omega t) - 3.2 \sin(\omega t).$$

Although this answer is correct, it is usually easier to visualize a single sinusoid with a phase shift. The sum of the cos and sin terms is equal to the single cos with a phase shift given above. This follows from the observation that the sum of any number of sinusoids of the same frequency may be expressed as a single sinusoid of that frequency. (The challenging part is determining the magnitude and phase shift of the single sinusoid.)

EX:

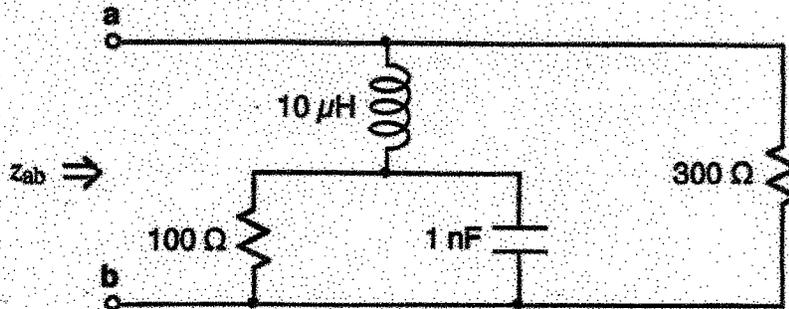


Given $\omega = 10 \text{ M rad/s}$, find z_{ab} .

Sol'n: $z_L = j\omega L = j 10 \text{ M r/s} \cdot 10 \mu\text{H} = j 100 \Omega$

$$z_C = \frac{-j}{\omega C} = \frac{-j}{10 \text{ M r/s} \cdot 1 \text{ nF}} = \frac{-j \Omega}{10 \text{ m}} = -j 100 \Omega$$

frequency domain (or s-domain) model:

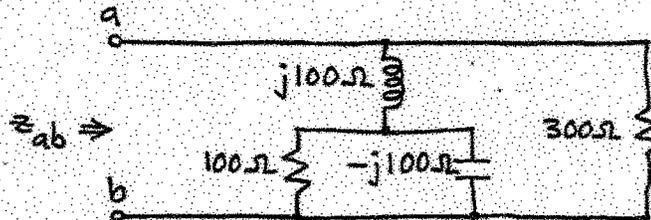

We first consider the R and C in parallel.

$$100 \Omega \parallel -j 100 \Omega = 100 \Omega \cdot \frac{1}{1 - j} = 100 \Omega \cdot \frac{-j}{1 - j}$$

Rationalizing this expression, we have

$$100 \Omega \parallel -j 100 \Omega = 100 \Omega \cdot \frac{-j}{1 - j} \cdot \frac{1 + j}{1 + j}$$

or

$$100\ \Omega \parallel -j100\ \Omega = 100\ \Omega \cdot \frac{1-j}{2} = 100\ \Omega \cdot \left(\frac{1}{2} - \frac{j}{2}\right)$$

Now we add $z_L = j100\ \Omega$

$$\begin{aligned} 100\ \Omega \parallel -j100\ \Omega + j100\ \Omega &= 100\ \Omega \left(\frac{1-j}{2} + j\right) \\ &= 100\ \Omega \left(\frac{1}{2} + \frac{j}{2}\right) \end{aligned}$$

To find z_{ab} , we use conductance $g_{ab} = \frac{1}{z_{ab}}$:

$$\begin{aligned} g_{ab} &= \frac{1}{100\ \Omega \parallel -j100\ \Omega + j100\ \Omega} + \frac{1}{300\ \Omega} \\ &= \frac{1}{100\ \Omega \left(\frac{1}{2} + \frac{j}{2}\right)} + \frac{1}{100\ \Omega} \cdot \frac{1}{3} \\ &= \frac{1}{100\ \Omega} \cdot \frac{2}{1+j} \cdot \frac{1-j}{1-j} + \frac{1}{100\ \Omega} \cdot \frac{1}{3} \\ &= \frac{1}{100\ \Omega} \cdot \frac{2-j2}{2} + \frac{1}{100\ \Omega} \cdot \frac{1}{3} \\ &= \frac{1}{100\ \Omega} (1-j) + \frac{1}{100\ \Omega} \cdot \frac{1}{3} \\ &= \frac{1}{100\ \Omega} \left(\frac{4}{3} - j\right) \end{aligned}$$

Now we calculate $\frac{1}{g_{ab}} = z_{ab}$.




$$\begin{aligned} z_{ab} &= \frac{1}{g_{ab}} = 100 \Omega \frac{1}{\frac{4}{3} - j} \\ &= 100 \Omega \frac{3}{4 - j3} \\ &= 100 \Omega \frac{3}{4 - j3} \cdot \frac{4 + j3}{4 + j3} \\ &= 100 \Omega \frac{12 + j9}{4^2 + 3^2} \\ &= 100 \Omega \frac{12 + j9}{25} \\ &= 4 \cdot (12 + j9) \\ z_{ab} &= 48 + j36 \end{aligned}$$

Homework #7 Examples

155


1.

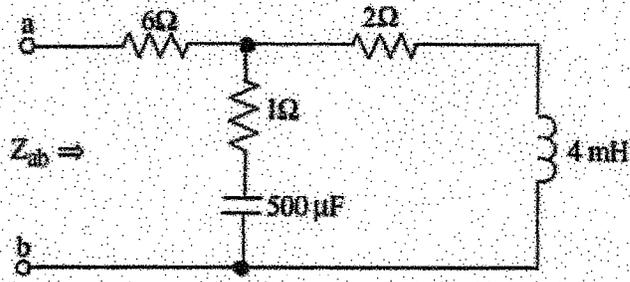

Given $\omega = 1\text{ k rad/sec}$, find Z_{ab} .

156

EX:

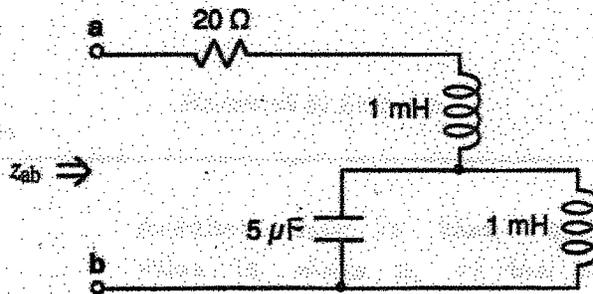

Find a frequency, ω , that causes z_{ab} to be real, (i.e., imaginary part equals zero).

Sol'n: $z_{ab} = 20 \Omega + z_{L1} + z_C \parallel z_{L2}$

For z_{ab} to be real, we must have

$$z_{L1} + z_C \parallel z_{L2} = \text{real}$$

One simple sol'n is to let $\omega = 0$ so both L's act like wires and C acts like open circuit.

Other potential sol'ns are $\omega = \infty$, (so L's act like opens, resulting in $z_{ab} = \infty$), and $\omega = \text{frequency where } z_C = -z_{L2}$, (so C and L in parallel have equal but opposite impedances).

The latter case, where $z_C = -z_{L2}$ gives

the interesting result that $z_C \parallel z_{L2} = \frac{L/C}{0} = \infty$

This means $z_{ab} = \infty \Omega$. In this case, (unlike $\omega \rightarrow \infty$), $z_{ab} \rightarrow \infty$ along real axis as $z_C \parallel z_{L2} \rightarrow \infty$.

or $\omega = 20 \text{K rad/s}$

Another soln is that $z_c \parallel z_L$ has a value is minus z_L of the top inductor.

In that case, $z_L + z_c \parallel z_L = 0$ and $z_{ab} = 0 = \text{wire}$.

$$z_L = j\omega L$$

$$\begin{aligned} z_c \parallel z_L &= \frac{-j}{\omega C} \parallel j\omega L = \frac{-j - j\omega L}{-j + j\omega L} = \frac{L/C}{j(\omega L - \frac{1}{\omega C})} \\ &= -\frac{j L/C}{\omega L - \frac{1}{\omega C}} \end{aligned}$$

$$\text{Thus, we want } j\omega L - \frac{jL/C}{\omega L - \frac{1}{\omega C}} = 0$$

$$\text{or } \omega L = \frac{L/C}{\omega L - \frac{1}{\omega C}}$$

$$\text{or } \omega L \left(\omega L - \frac{1}{\omega C} \right) = L/C$$

$$\text{or } \omega^2 L^2 - \frac{L}{C} = \frac{L}{C}$$

$$\text{or } \omega^2 L^2 = \frac{2L}{C} \quad \text{or } \omega^2 = \frac{2}{LC}$$

$$\text{or } \omega = \sqrt{\frac{2}{LC}} \quad \text{or } \omega = \sqrt{\frac{2}{5\mu\text{F} \cdot 1\text{mH}}}$$


$$\text{or } \omega = \sqrt{\frac{2}{5}} \text{ r/s} = \sqrt{400\text{M}} \text{ r/s}$$

$$\text{or } \omega = 20\text{k} \text{ r/s}$$

Homework #7 Examples


158

2.

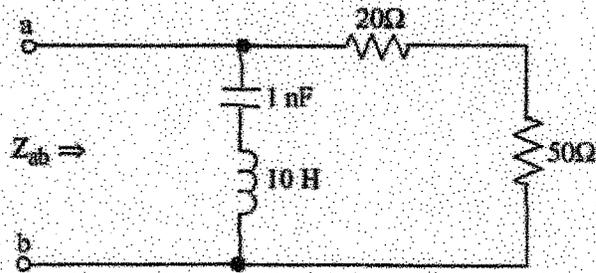

Find a frequency, ω , that causes Z_{ab} to be real (i.e. imaginary part equals zero).
 $\omega \neq 0$ or $\omega \neq \infty$.

EX:

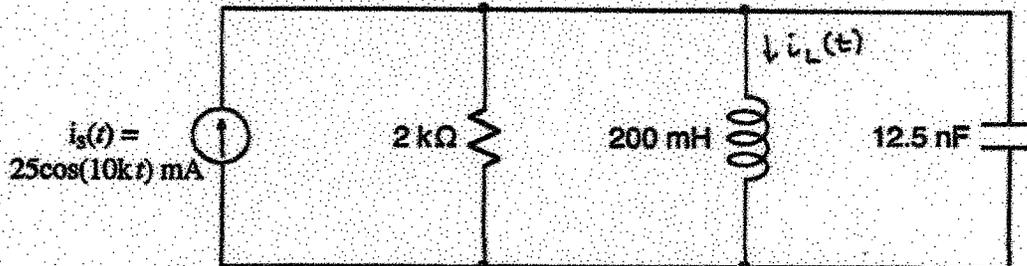

- Find the phasor value for $i_s(t)$.
- Draw the frequency-domain circuit diagram, including the phasor value for $i_s(t)$ and impedance values for components.
- Find the phasor value for $i_L(t)$.

Sol'n: a) The phasor for $A\cos(\omega t + \phi)$ is $Ae^{j\phi}$.


$$\therefore \mathbb{I}_s = 25 e^{j0^\circ} \text{ mA or } 25 \angle 0^\circ \text{ mA}$$

b) From $i_s(t)$, we see that $\omega = 10\text{krad/s}$.

$$\text{Impedance } z_L = j\omega L = j 10\text{k} 200\text{mH} = j2\text{k}\Omega$$

$$z_C = \frac{-j}{\omega C} = \frac{-j}{10\text{k} 12.5\text{nF}} = \frac{-j}{125\mu}$$
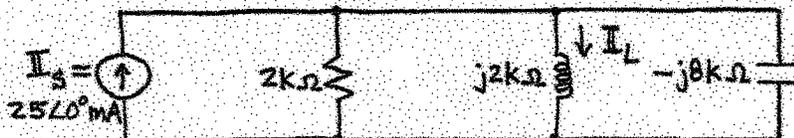
$$z_C = \frac{-j 8\text{k}\Omega}{8\text{k} \cdot 125\mu} = -j8\text{k}\Omega$$




c) The value for I_L is given by the current divider formula:

$$\begin{aligned}
 I_L &= I_s \cdot \frac{R \parallel z_c}{R \parallel z_c + z_L} \\
 &= I_s \frac{1}{1 + \frac{z_L}{R \parallel z_c}} \\
 &= I_s \frac{1}{1 + z_L \left(\frac{1}{R} + \frac{1}{z_c} \right)} \\
 &= 25 \angle 0^\circ \text{ mA} \frac{1}{1 + j2k\Omega \left(\frac{1}{2k\Omega} + \frac{1}{-j8k\Omega} \right)} \\
 &= 25 \angle 0^\circ \text{ mA} \frac{4}{4} \frac{1}{1 + j - \frac{1}{4}} \\
 &= 25 \angle 0^\circ \text{ mA} \frac{4}{3 + j4} \\
 &= 25 \angle 0^\circ \text{ mA} \frac{4}{3 + j4} \cdot \frac{3 - j4}{3 - j4} \\
 &= 25 \angle 0^\circ \text{ mA} \frac{12 - j16}{3^2 + 4^2} \\
 &= 1 \angle 0^\circ \text{ mA} \cdot 20 \angle -53.1^\circ \\
 I_L &= 20 \text{ mA} \angle -53.1^\circ
 \end{aligned}$$



Homework #7 Examples

3.

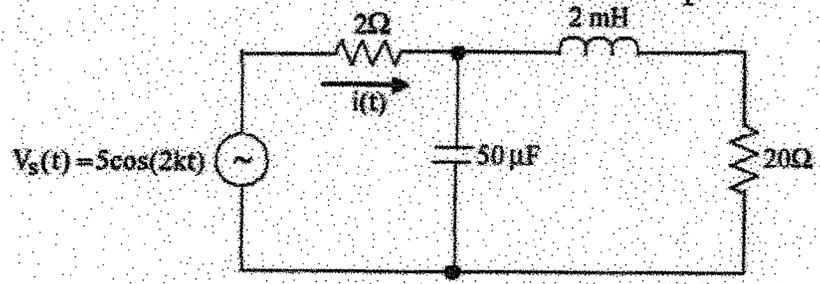

- a. Find the phasor value for $V_s(t)$.
- b. Draw the frequency-domain circuit diagram, including the phasor value for $V_s(t)$ and impedance values for components.
- b. Find the phasor value for $i(t)$.

EX:

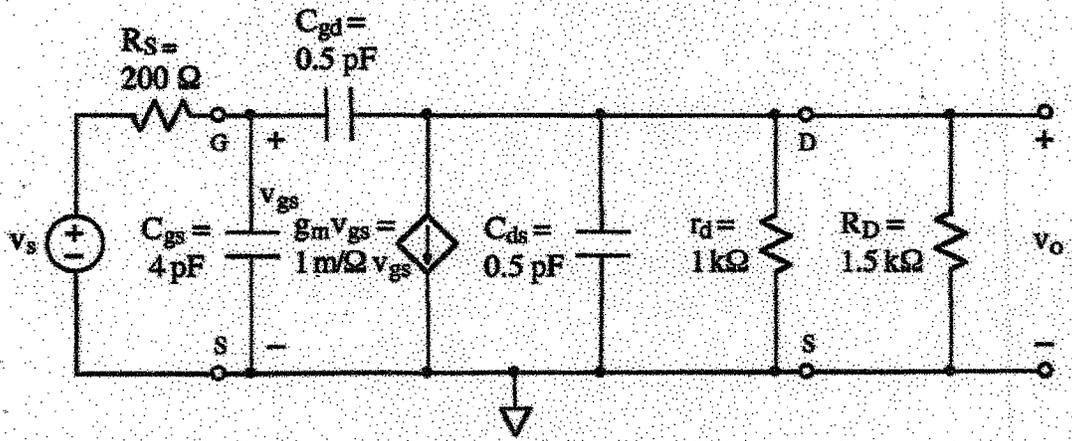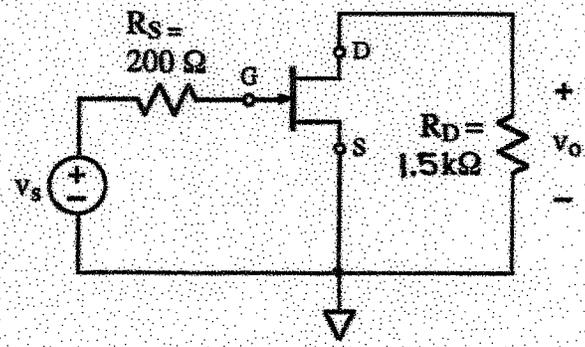

$$v_s(t) = 2 \cos(10kt) \text{ V}$$

The above circuit diagrams show a common-source JFET amplifier and its high-frequency equivalent circuit. Find $v_o(t)$.

Sol'n: In this practical circuit, we have circuit values that allow us to make simplifying approximations.

We first calculate impedance values.

$$\omega = 10k \text{ r/s} \text{ from } v_s(t) = 2 \cos(10kt) \text{ V}$$

163


$$Z_{Cgs} = \frac{-j}{\omega C_{gs}} = \frac{-j \Omega}{10k \cdot 4p} = -j 25M \Omega$$

$$Z_{Cgd} = \frac{-j}{\omega C_{gd}} = \frac{-j}{10k \cdot \frac{1}{2} p} = -j 200M \Omega$$

$$Z_{Cds} = \frac{-j}{\omega C_{ds}} = \frac{-j}{10k \cdot \frac{1}{2} p} = -j 200M \Omega$$

The phasor for $v_s(t)$ is $V_s = 2 \angle 0^\circ V$.

Frequency domain (or s-domain) model:

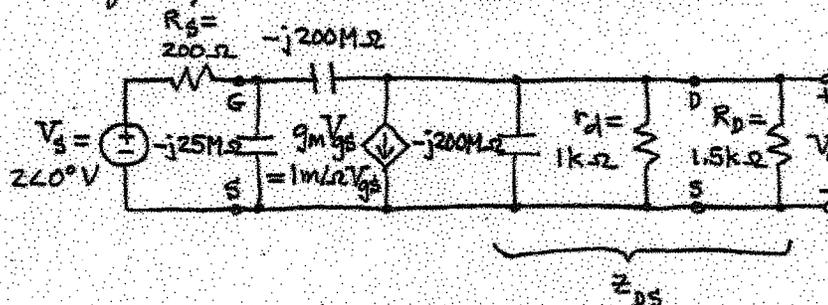

$$Z_{DS} = -j 200M \parallel 1k \parallel 1.5k \Omega$$

Starting with $1k \parallel 1.5k \Omega$ we have

$$1k \parallel 1.5k \Omega = 500 \Omega \cdot 2 \parallel 3 = 500 \cdot \frac{6}{5}$$

$$= 600 \Omega$$

$$\text{Thus, } Z_{DS} = -j 200M \parallel 600 \Omega = \frac{1}{\frac{1}{600} - \frac{1}{j 200M}}$$

Using $-\frac{1}{j} = j$ and rationalizing gives

$$z_{DS} = \frac{1}{\frac{1}{600} + \frac{j}{200M}} \frac{1}{\frac{1}{600} - \frac{j}{200M}} \Omega$$

$$= \frac{\frac{1}{600} - \frac{j}{200M}}{\left(\frac{1}{600}\right)^2 + \left(\frac{1}{200M}\right)^2} \Omega$$

$$\approx \frac{1}{600} - \frac{j}{200M} \Omega \quad \text{Since } \frac{1}{200M} \ll \frac{1}{600}$$


$$z_{DS} \approx \frac{1}{\left(\frac{1}{600}\right)^2} \Omega = 600 \Omega$$

In retrospect, we could have made the approximation that $-j200M \parallel 600 \Omega \approx 600 \Omega$.


We may make this approximation despite the j in one of the quantities. In general, we may make the following approximations of complex values:

$$a + jb \approx a \quad \text{when } |b| \ll |a|$$


$$a + jb \approx jb \quad \text{when } |a| \ll |b|$$

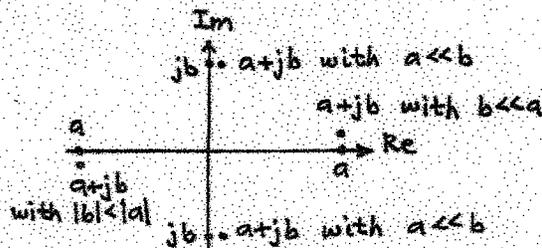

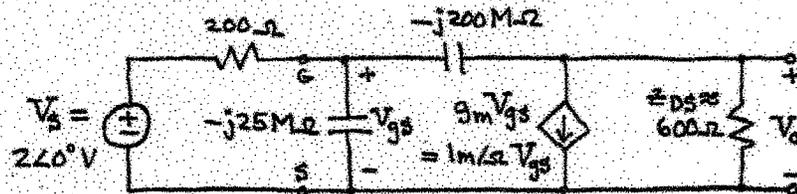With our z_{DS} value, we have a simplified model:



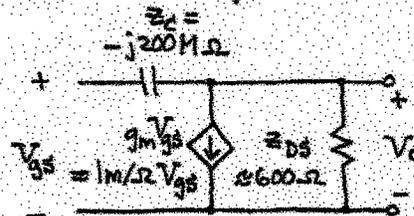We now analyze the dependent source so we can replace it with an impedance, z_{eg} .



$$z_{eg} = \frac{V_o}{g_m V_{gs}} \quad \text{using Ohm's law to write } z_{eg} = V/I$$

Now we find a way to write V_o in terms of V_{gs} . We use a V-divider:

$$V_o = V_{gs} \frac{z_{eg} \parallel z_{DS}}{z_{eg} \parallel z_{DS} + z_c}$$

Substituting for V_o in our z_{eg} eq'n, we have

$$z_{eg} = \frac{V_{gs} \frac{z_{eg} \parallel z_{DS}}{z_{eg} \parallel z_{DS} + z_c}}{V_{gs} \cdot g_m}$$

$$z_{eg} = \frac{1}{g_m} \frac{\frac{z_{eg} z_{DS}}{z_{eg} + z_{DS}}}{\frac{z_{eg} z_{DS}}{z_{eg} + z_{DS}} + z_c}$$

166

$$z_{eg} = \frac{1}{g_m} \frac{z_{eg} z_{Ds}}{z_{eg} z_{Ds} + z_c (z_{eg} + z_{Ds})}$$

Dividing top and bottom by z_{eg} gives the following:

$$z_{eg} = \frac{1}{g_m} \frac{z_{Ds}}{z_{Ds} + z_c + \frac{z_c z_{Ds}}{z_{eg}}}$$

$$z_{eg} \left(z_{Ds} + z_c + \frac{z_c z_{Ds}}{z_{eg}} \right) = \frac{1}{g_m} z_{Ds}$$

$$z_{eg} (z_{Ds} + z_c) + z_c z_{Ds} = \frac{1}{g_m} z_{Ds}$$

$$z_{eg} \frac{(z_{Ds} + z_c)}{z_{Ds}} = \frac{1}{g_m} \frac{z_{Ds} - z_c z_{Ds}}{z_{Ds}}$$

$$z_{eg} = \frac{1}{g_m} - z_c = \frac{1\Omega - j200M\Omega}{1 + \frac{z_c}{z_{Ds}}} = \frac{1\Omega - j200M\Omega}{1 + \frac{-j200M\Omega}{600\Omega}}$$

$$z_{eg} = \frac{1k + j200M\Omega}{1 - j\frac{1}{3}M}$$

The imaginary parts of the numerator and denominator are much larger than the real parts. Thus, we ignore the real parts.

$$z_{eg} \approx j200M\Omega / -j\frac{1}{3}M \approx -600\Omega$$

Now we have a problem: $z_{eg} \parallel z_{DS} = -\frac{600^2}{0} \Omega$.

That means $z_{eg} \parallel z_{DS} = \infty \Omega$.

It is a good idea to try a more exact calculation to be sure that $z_{eg} \parallel z_{DS}$ is much larger than $z_c = -j200M\Omega$.

We use conductance to simplify calculations.

$$\frac{1}{z_{eg} \parallel z_{DS}} = \frac{1}{z_{eg}} + \frac{1}{z_{DS}} = \frac{1 + \frac{z_c}{z_{DS}}}{\frac{1}{g_m} - z_c} + \frac{1}{z_{DS}}$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + z_c}{\frac{1}{g_m} - z_c} + 1 \right)$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + z_c}{\frac{1}{g_m} - z_c} + \frac{\frac{1}{g_m} - z_c}{\frac{1}{g_m} - z_c} \right)$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + \frac{1}{g_m}}{\frac{1}{g_m} - z_c} \right)$$

$$= \frac{g_m + \frac{1}{z_{DS}}}{1 - g_m z_c}$$

$$= \frac{1m + \frac{1}{600}}{1 - 1m(-j200M)} / \Omega$$


$$z_{eg} \parallel z_{DS} = \frac{1 + j200k}{\frac{1}{1k} + \frac{1}{600}} \Omega$$

$$z_{eg} \parallel z_{DS} = \frac{1 + j200k \Omega}{\frac{3+5}{3k}} = \frac{3k}{8} (1 + j200k) \Omega$$

$$= \frac{3k}{8} + j75M \Omega$$

We see that the value is smaller than $z_c = -j200M \Omega$.

Our new, simplified model:

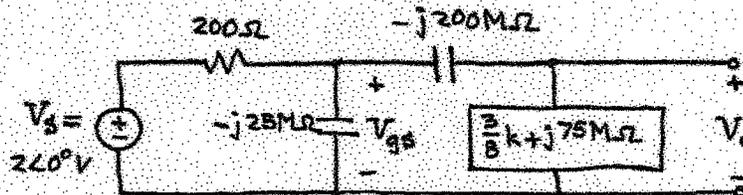

We use V-dividers to find V_o .

$$V_{gs} = V_s \cdot \frac{-j25M \Omega \parallel (-j200M + \frac{3k}{8} + j75M \Omega)}{200 + -j25M \Omega \parallel (-j200M + \frac{3k}{8} + j75M \Omega)}$$

$$V_{gs} \approx \frac{V_s \cdot (-j25M \Omega \parallel -j125M \Omega)}{200 - j25M \Omega \parallel -j125M \Omega}$$

$$\text{where } -j25M \Omega \parallel -j125M \Omega = -j25M \Omega \cdot \frac{1}{5}$$

$$= -j25M \Omega \cdot \frac{5}{6}$$

$$= -j \frac{125}{6} M \Omega$$

$$V_{gs} = V_s \cdot \frac{\left(-j \frac{125}{6} M \Omega\right)}{200 - j \frac{125}{6} M \Omega} \approx V_s$$

$$V_o = V_{gs} \frac{\frac{3}{8} k + j 75 M\Omega}{\frac{3}{8} k + j 75 M\Omega - j 200 M\Omega}$$

$$V_o \approx V_{gs} \frac{j 75 M\Omega}{-j 125 M\Omega} = V_{gs} \left(-\frac{3}{5} \right)$$

$$V_o \approx 2 \angle 0^\circ V \left(-\frac{3}{5} \right) = -\frac{6}{5} \angle 0^\circ V = \frac{6}{5} \angle 180^\circ V$$


Note: a minus sign is the same as 180° of phase shift.

$$v_o(t) = \frac{6}{5} \cos(10kt + 180^\circ) V$$

Homework #7 Examples

170


4.

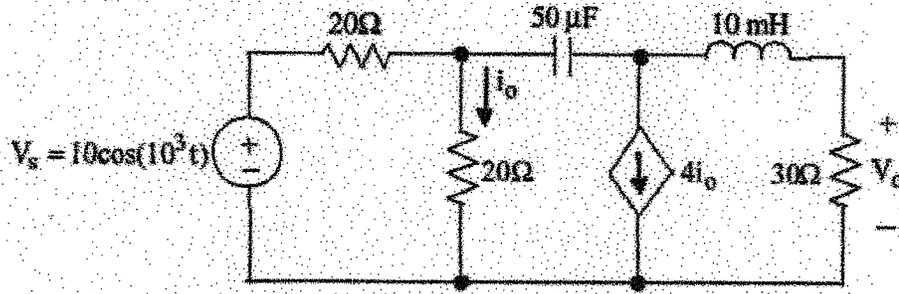

Find $V_o(t)$.

HW #7

EXAMPLE

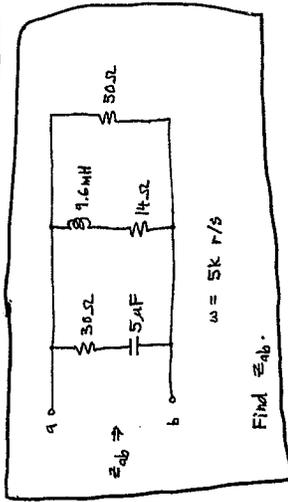

Find Z_{ab} .

Sol'n: Convert C value to impedance $Z_C = \frac{-j}{\omega C}$.


$$Z_C = \frac{-j}{5kr/s \cdot 5\mu F} = \frac{-j}{25m} = -j40 \Omega$$

Convert L value to impedance $Z_L = j\omega L$.

$$Z_L = j 5kr/s \cdot 1.6mH = j48 \Omega$$

R values are the same as Z_R values.

Frequency-domain Model:

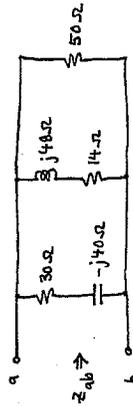

$$Z_{ab} = (30 - j40) \parallel (j48) \parallel 50 \Omega$$

For parallel Z 's, it is often easier to use conductance, $\frac{1}{Z}$.

$$\frac{1}{Z_{ab}} = \frac{1}{30 - j40 \Omega} + \frac{1}{j48 \Omega} + \frac{1}{50 \Omega}$$

Sol'n: 1. cont.

Rationalize the $\frac{1}{Z}$ values and sum them.

$$\frac{1}{Z_{ab}} = \frac{30 + j40}{30^2 + 40^2 \Omega} + \frac{j48}{j48^2 \Omega} + \frac{1}{50 \Omega}$$

$$\frac{1}{Z_{ab}} = \frac{30 + j40}{50^2 \Omega} + \frac{j48}{50^2 \Omega} + \frac{50}{50^2 \Omega}$$


Conveniently, we have the same denominator for every term. (Not typical!)

$$\frac{1}{Z_{ab}} = \frac{30 + j40 + 50 + j(40 - 48)}{50^2 \Omega} = \frac{94 - j8}{50^2 \Omega}$$

$$Z_{ab} = \frac{50^2 \Omega}{94 - j8} = \frac{50^2 (94 + j8)}{(94 - j8)(94 + j8)} = \frac{50^2 (94 + j8)}{8900}$$


$$Z_{ab} = \frac{25 \cdot (94 + j8) \Omega}{89} = 26.4 + j2.25 \Omega$$

sol'n: 3.c) cont.

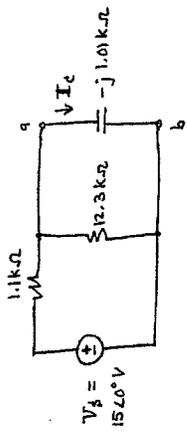

We take the Thevenin equivalent of the circuit to the left of the a,b terminals. Notice that the above circuit is the same as the original since the $12.3k\Omega$ and $-j1.01k\Omega$ are still in parallel.

Using Thevenin equivalent, we have

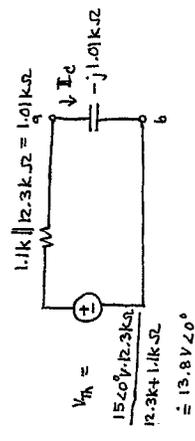

Now we can calculate I_c from V_{TH}/Z_{Tot} :

$$I_c = \frac{13.8\angle 0^\circ V}{1.01k - j1.01k\Omega} = \frac{13.8\angle 0^\circ V}{1.01k\Omega (1-j)} (1+j)$$

$$= \frac{13.8\angle 0^\circ V (1+j)}{1.01k\Omega \cdot 2} = 6.83 \text{ mA} \cdot \sqrt{2} \angle 45^\circ$$

$$I_c = 9.66 \angle 45^\circ \text{ mA}$$

d) $i_c(t) = P^{-1} [I_c] = P^{-1} [9.66 \angle 45^\circ \text{ mA}]$

$$i_c(t) = 9.66 \cos(3kt + 45^\circ) \text{ mA}$$

3.


a. Find phasor for $v_s(t)$.
 b. Draw frequency domain circuit diagram.
 c. Find phasor for $i_c(t)$.
 d. Find $i_c(t)$.

sol'n: a) $P [v_s(t)] = P [15 \cos(3kt) V] = 15 \angle 0^\circ V \equiv V_s$

b) From $v_s(t)$, $\omega = 3k \text{ r/s}$.


Impedance $Z_C = \frac{-j}{\omega C} = \frac{-j \Omega}{3k \cdot 330n} = \frac{-j \text{ M}\Omega}{990}$

$Z_C = -j1.01k\Omega \approx -j1k\Omega$

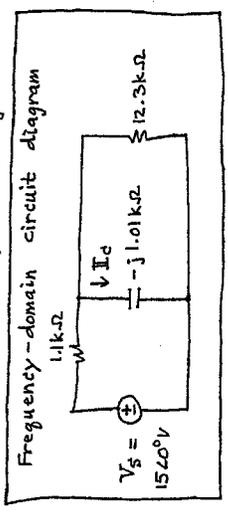


c) We could use the node-voltage method or mesh currents, but we can rearrange the circuit and use a Thevenin equivalent involving only R's. This reduces the number of calculations with complex quantities.

soln: 4. cont.

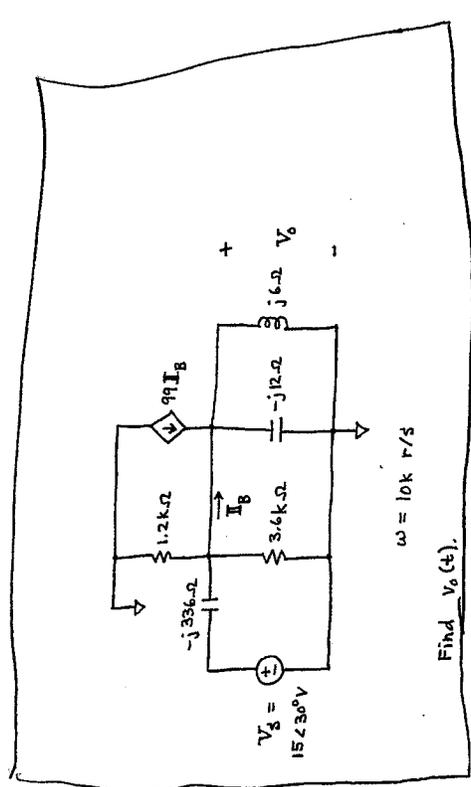

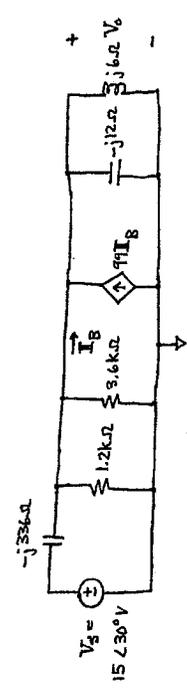
soln: Redraw circuit, being careful to preserve I_B .



Combine parallel z's, again preserving I_B .

$$1.2k\Omega \parallel 3.6k\Omega = 1.2k\Omega \parallel \frac{1}{\frac{1}{3} + \frac{1}{3.6}} = 1.2k\Omega \parallel \frac{3}{4} = 0.9k\Omega$$
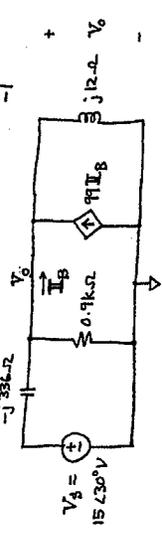
$$-j12\Omega \parallel j6\Omega = j6(-2\parallel 1) = j6 \cdot \frac{-2}{-1} = j12\Omega$$



If we try to use node-voltage to find V_0 , we must express I_B in terms of V_0 . We use a current sum at the node above the $99I_B$ src.

$$-I_B - 99I_B + \frac{V_0}{j12\Omega} = 0A$$

$$100 I_B = \frac{V_0}{j12\Omega}$$

$$I_B = \frac{V_0}{j1.2k\Omega}$$

Now we can write node-voltage eqn for V_0 :

$$\frac{V_0 - 15\angle 30^\circ V}{-j336\Omega} + \frac{V_0}{0.9k\Omega} - 99 \frac{V_0}{j1.2k\Omega} + \frac{V_0}{j12\Omega} = 0A$$

$$V_0 \left(\frac{1}{-j336\Omega} + \frac{1}{0.9k\Omega} - \frac{99}{j1.2k\Omega} + \frac{100}{j1.2k\Omega} \right) = \frac{15\angle 30^\circ V}{j336\Omega}$$

$$V_0 \left(\frac{j}{336\Omega} + \frac{1}{0.9k\Omega} - j \frac{82.5}{1.2k\Omega} \right) = \frac{j15\angle 30^\circ V}{336\Omega}$$

$$V_0 = \frac{j15\angle 30^\circ V (-j336\Omega \parallel 0.9k\Omega \parallel j1.2k\Omega)}{336\Omega}$$

$$-j336\Omega \parallel j1.2k\Omega = j12 \cdot 28 \parallel 100 = j48 - j12.5 \Omega$$

$$= j35.5 \parallel \frac{175}{183} = -j \frac{1400}{3} \Omega$$

$$0.9k\Omega \parallel -j \frac{1400}{3} \Omega = 100 \cdot 9 \parallel -j \frac{14}{3} \Omega$$

$$= 100 \frac{(-j42)}{9-j14} = 100 \frac{(-j42) \cdot 3}{27-j14}$$

$$= -j4(25) \frac{6(7) \cdot 3}{27-j14} = -j \frac{28 \cdot 12 \cdot 25 \cdot 3/2}{27-j14}$$

$$\therefore V_0 = \frac{15\angle 30^\circ V (j) 25 \cdot 3/2}{27-j14} \cdot \frac{27+j14}{27+j14}$$

Sol'n: 4. cont.


$$V_o = \frac{15 \angle 30^\circ (25)(3/2)}{92.5} \cdot (27 + j14) \text{ V}$$

$$V_o \approx \frac{15 \angle 30^\circ}{2.37} 30.4 \angle 30^\circ + 27.4^\circ \text{ V}$$

$$V_o \approx 18.5 \angle 57.4^\circ \text{ V}$$


$$V_o(t) \approx 18.5 \cos(10kt + 57.4^\circ) \text{ V}$$

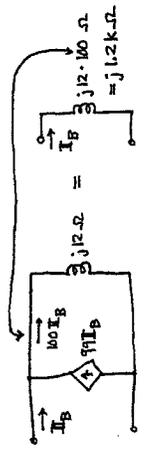An alternate approach is to use the idea of impedance multiplication.



The current thru the $j12\Omega$ causes a voltage drop equivalent to I_B flowing thru $j12\Omega \cdot 100$.

Now our circuit is simpler:

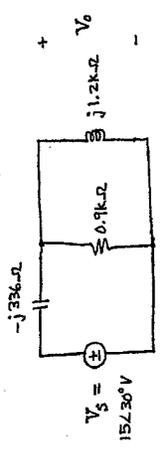

$$V_o = \frac{15.230 \text{ V}}{(0.9k \parallel j1.2k\Omega) - j336\Omega}$$

$$0.9k \parallel j1.2k\Omega = 0.3k\Omega - j1.4 = 0.3k\Omega \cdot \frac{j12}{3+j4}$$

$$0.9k \parallel j1.2k\Omega = \frac{300 \cdot j12}{3+j4} = j144(3-j4)\Omega$$

$$= 576 + j432$$

$$V_o = \frac{15 \angle 30^\circ \text{ V} \cdot (576 + j432)\Omega}{576 + j432 - j336\Omega}$$

$$= \frac{15 \angle 30^\circ \text{ V} (576 + j432)}{576 + j96}$$

$$= \frac{15 \angle 30^\circ \text{ V} \cdot 720 \angle 36.9^\circ}{584 \angle 9.5^\circ}$$

$$= \frac{15(720)}{584} \angle 30^\circ + 36.9^\circ - 9.5^\circ \text{ V}$$

$$V_o = 18.5 \angle 57.4^\circ \text{ V}$$

$$V_o(t) = 18.5 \cos(10kt + 57.4^\circ) \text{ V}$$

as before