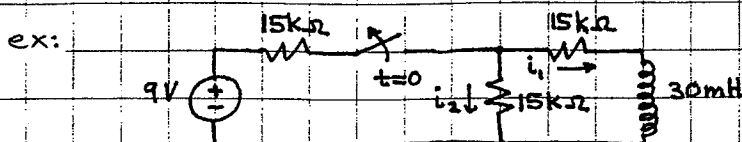


Problem  
Set #5

Ref: Nilsson & Riedel, Rev 6, Prob 7.5

Rev. 8, Prob. 7.2



The switch has been closed for a long time before opening at time  $t=0$ .


Note: Whenever a circuit configuration has existed "for a long time" it means forever — from  $t=-\infty$  to  $t=0$ . Thus, all currents and voltages have achieved final values. In other words,  
 $\frac{di}{dt} = 0$  for all currents,  $\frac{dv}{dt} = 0$  for all voltages.

a) Find  $i_1(t=0^-)$  and  $i_2(t=0^-)$ .

sol'n: At  $t=0^-$  the circuit has had the same configuration "for a long time", and  $\frac{di_1}{dt} = 0$   $\frac{di_2}{dt} = 0$ .

For the L we have  $v_L = L \frac{di}{dt} = L \cdot 0 = 0V$ .

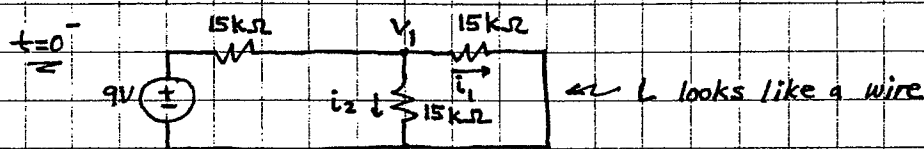Thus, the 30mH L looks like a wire (as L's always do for their final values), and our circuit model is:




We get  $V_1$  from V-divider:  $V_1 = 9V \cdot \frac{15k\Omega // 15k\Omega}{15k\Omega + 15k\Omega // 15k\Omega}$

$\therefore V_1 = 3V$

$i_1(t=0^-) = i_2(t=0^-) = V_1 / 15k\Omega = \frac{3V}{15k\Omega} = 0.2mA$

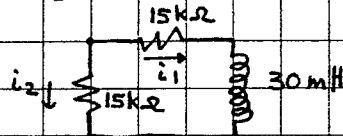b) Find  $i_1(t=0^+)$  and  $i_2(t=0^+)$ .

sol'n: With the switch open, the 9V and 15k $\Omega$  before the switch no longer affect  $i_1$  and  $i_2$ . Our model (for  $i_1$  and  $i_2$ ) becomes:



Since the current through the L cannot change instantly, we must have  $i_1(t=0^+) = i_1(t=0^-)$ .


But now we also have the two 15k $\Omega$  R's in series. Thus,  $i_2 = -i_1 = -i_1(t=0^-)$ .

$$\therefore i_1(t=0^+) = 0.2 \text{ mA} \quad i_2(t=0^+) = -0.2 \text{ mA}$$

Note: The current in an R can change instantly, as happens here (with  $i_2$  changing sign).

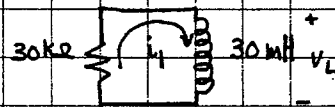c) Find  $i_1(t)$  for  $t \geq 0$

sol'n: Our circuit model (with 15k $\Omega$  R's summed) is:



$$V_L = L \frac{di_1}{dt} \quad \text{and} \quad V_L = -i_1 \cdot 30k\Omega \quad \text{by Ohm's law}$$

$$\therefore -i_1 \cdot \frac{30k\Omega}{R} = L \frac{di_1}{dt} \quad \text{or} \quad i_1 \cdot R + L \frac{di_1}{dt} = 0 \text{ V}$$

Note: we used sum of V's around loop = 0V

$$\text{From text p. 279, } i_1(t) = i_1(0^+) e^{-t/R/L} = 0.2 \text{ mA} e^{-t \cdot 30k\Omega / 30 \text{ mH}}$$

$$\therefore i_1(t) = 0.2 \text{ mA} \cdot e^{-t \cdot 10^6 / \text{s}}$$

d) Find  $i_2(t)$  for  $t \geq 0^+$

sol'n: From part (b) we have  $i_2(t) = -i_1(t)$  for  $t \geq 0^+$


$$\therefore i_2(t \geq 0^+) = -0.2 \text{ mA} \cdot e^{-t \cdot 10^6/\text{s}}$$

e) Explain why  $i_2(0^-) \neq i_2(0^+)$ .

answer: As noted in the solution to (b), the current in an R can change instantly. It does so here to keep  $i_1(t)$  the same when the switch opens.

Note: The R current can change instantly because an R stores no energy. It takes time to change the energy stored in an L, and energy =  $\frac{1}{2} Li^2$ .

ex:

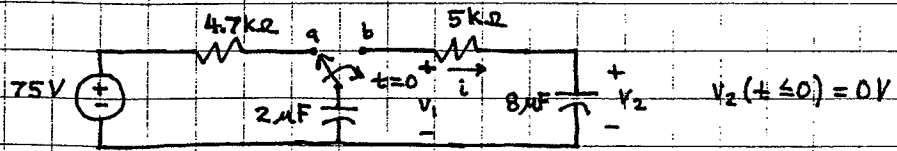


The switch in the circuit has been in position 'a' for a long time before it changes to position 'b' at  $t=0$ .

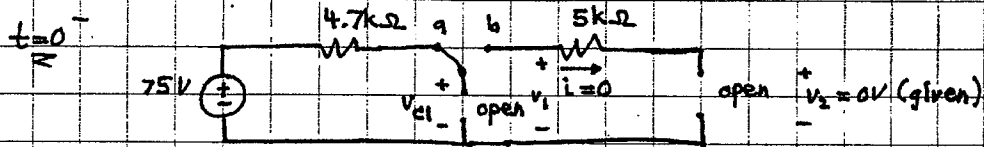a) Find  $i$ ,  $v_1$ , and  $v_2$  for  $t \geq 0^+$ .


At  $t=0^-$  we have  $\frac{dv_c}{dt} = 0$  both C's.

$\therefore i_c = 0$  for both C's.  $\therefore$  C's look like open circuits



Since no current flows on the left side, there is no  $V$ -drop across the  $4.7k\Omega$  R. Thus,  $v_{c1} = 75V$ .

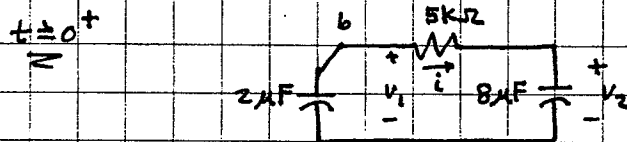When we throw the switch at  $t=0$ , the left side 75V and  $4.7k\Omega$  no longer affect  $i$ ,  $v_1$ , and  $v_2$ :




We combine the two C's in series into one  $C_{eq} = 2\mu F // 8\mu F$ ;

$$C_{eq} = \frac{2\mu F \cdot 8\mu F}{2\mu F + 8\mu F} = \frac{16\mu F}{10} = 1.6\mu F.$$

The initial voltage on  $C_{eq}$  is  $v_1(0^+) - v_2(0^+) = v_1(0^-) - v_2(0^-)$ , since  $V$  across C's cannot change instantly.

Now our equivalent circuit is an RC

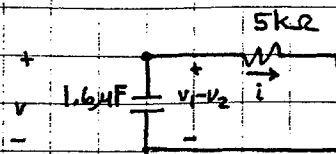with initial voltage  $v_{c1} - v_{c2} = 75V - 0 = 75V$ ;



We sum currents flowing out of node between R & C, (instead of summing V's around loop as we did for RL problems).

In other words, we equate the  $i$  in the R & C.

$$-i = C \frac{dv_1 - v_2}{dt} \equiv C \frac{dv}{dt} \quad \text{and} \quad i = \frac{v_2 - v_1}{R} \equiv \frac{v}{R}$$

$$\therefore \frac{v}{R} = -C \frac{dv}{dt} \quad \text{or} \quad \frac{v}{R} + C \frac{dv}{dt} = 0$$

As shown on p.287 of text, the solution is

$$v(t) = v(t=0^+) e^{-t/RC_{eq}} = 75V \cdot e^{-t/5k\Omega \cdot 1.6\mu F} = 75V \cdot e^{-t/8ms}$$

$$i(t) = \frac{v(t)}{R} = \frac{75V}{5k\Omega} e^{-t/8ms} = 15mA e^{-t/8ms}$$

Now that we have  $i(t)$ , we can integrate  $i(t)$  to find  $v_1(t)$  and  $v_2(t)$ .

$$-i(t) = C_1 \frac{dv_1}{dt}$$

$$-\int_{t=0^+}^{t=t} i(t') dt' = C_1 \int_{v_1(t=0^+)}^{v_1(t)} dv_1$$

$$i(t) = C_2 \frac{dv_2}{dt}$$

$$\int_{t=0^+}^{t=t} i(t') dt' = C_2 \int_{v_2(t=0^+)}^{v_2(t)} dv_2$$


$$60V \cdot \left( \frac{-8ms \cdot 15mA}{2\mu F} \right) e^{-t/8ms} \Big|_{t=0}^{t=t} = v_1(t) - v_1(0^+)$$

$$-15 \cdot \left( \frac{-8ms \cdot 15mA}{8\mu F} \right) e^{-t/8ms} \Big|_{t=0}^{t=t} = v_2(t) - v_2(0^+)$$

$$v_1(t) = 60V \left( e^{-t/8ms} - 1 \right) + 75V$$

$$v_2(t) = -15V \left( e^{-t/8ms} - 1 \right)$$


ex:

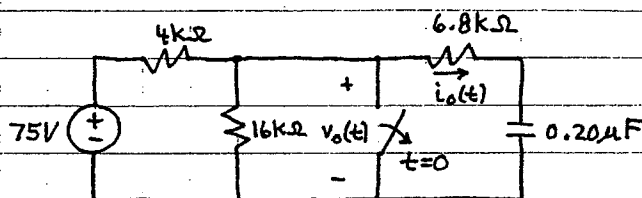

Switch has been closed for a long time before opening at time  $t=0$ .

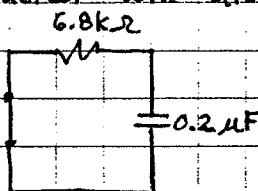a) Find initial value of  $i_o(t)$ .

sol'n: If switch was closed for a long time, then the capacitor will discharge through  $6.8k\Omega$ :




(Right side of circuit, see 'note' below.)

Note: The closed switch creates a short circuit. The left and right sides of the circuit may then be treated as though they are totally independent. Why? Because the currents flowing through the short create no  $V$  drop. Thus, the mesh currents on the <sup>two</sup> sides of the short do not interact.

Thus, at  $t=0^-$  the  $C$  has no charge, and  $v_c = 0$ .  
 $\therefore C$  acts like short at  $t=0^-$ . Since  $v_c$  cannot change instantly,  $v_c(t=0^+) = 0V$ , too.

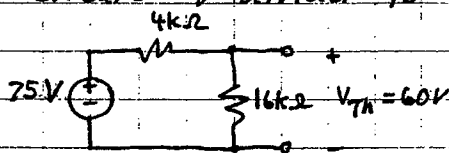
Also, we replace the  $75V$  and  $4k\Omega$  and  $16k\Omega$  with a Thevenin equivalent.  $V_{TH}$  from open-circuit  $V$ -divider is  $75V \cdot \frac{16k\Omega}{4k\Omega + 16k\Omega} = 60V = V_{TH}$



Turn  $75V$  down to  $0V$  and connect  $1V$  source to output to get  $R_{TH} = 1V / [1V / (4k\Omega \parallel 16k\Omega)] = 4k\Omega \parallel 16k\Omega$

$$R_{TH} = 4k\Omega \parallel 4 = \frac{4k\Omega \cdot 4}{5} = 3.2k\Omega$$

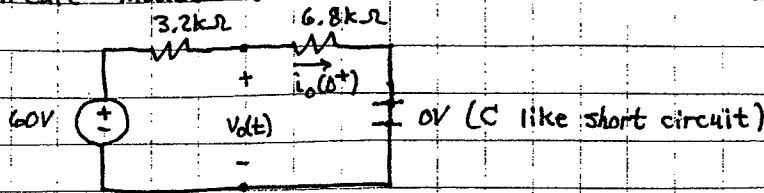$\therefore$  Circuit model for  $t=0^+$  is:



$$i_o(t=0^+) = \frac{60V}{3.2k\Omega + 6.8k\Omega} = \frac{60V}{10k\Omega} = \frac{6V}{1k\Omega} = 6mA$$

b) Find  $i_o(t \rightarrow \infty)$ .

sol'n: When the C is charged, it looks like open circuit.

Note:  $i_c(t \rightarrow \infty) = 0A$  for all C's in all switching probs.

$v_c(t=0^-) = v_c(t=0^+)$  " " " " " " " "

But  $v_c(t=0^-) = 0V$  only if circuit discharges C completely for  $t < 0$ . Otherwise,  $v_c(t=0^-)$  is some nonzero value.

If C is open circuit, then  $i_o(t \rightarrow \infty) = 0A$ .

c) Find time constant for  $t \geq 0$ .

$$\begin{aligned} \text{sol'n: } \tau &= R_{eq} \cdot C & R_{eq} &= 10k\Omega = 3.2k\Omega + 6.8k\Omega \\ &= 10k\Omega \cdot 0.2\mu F & C &= 0.2\mu F \\ &= 2ms \end{aligned}$$

d) Find expression for  $i_o(t)$  when  $t \geq 0^+$

sol'n: General sol'n for  $i_o(t)$  is:


$$\begin{aligned} i_o(t) &= i_o(t=0^+) + [i_o(t \rightarrow \infty) - i_o(t=0^+)] [1 - e^{-t/RC}] \\ &= 6mA + [0 - 6mA] [1 - e^{-t/2ms}] \\ &= 6mA e^{-t/2ms} \quad t \geq 0^+ \end{aligned}$$

e) Find expression for  $v_o(t)$  when  $t \geq 0^+$

$$\begin{aligned} \text{sol'n: } v_o(t) &= 60V - i_o(t) \cdot 3.2k\Omega = 60V - 6mA \cdot e^{-t/2ms} \cdot 3.2k\Omega \\ &= 60V - 19.2V e^{-t/2ms} \quad t \geq 0^+ \end{aligned}$$



ex:

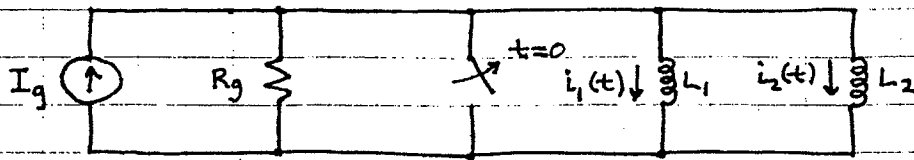


No energy stored in  $L_1$  and  $L_2$  when switch opens.

- a) Find  $i_1(t \geq 0)$  and  $i_2(t \geq 0)$ .      b) Find  $i_1(t \rightarrow \infty)$  and  $i_2(t \rightarrow \infty)$

ans: a)  $i_1(t \geq 0) = I_g \frac{L_2}{L_1 + L_2} (1 - e^{-t/\tau})$       where  $\tau \equiv L_1 \parallel L_2$   
 $i_2(t \geq 0) = I_g \frac{L_1}{L_1 + L_2} (1 - e^{-t/\tau})$       "      "

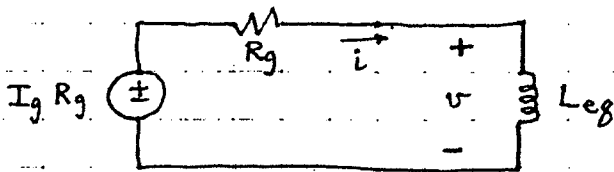b)  $i_1(t \rightarrow \infty) = I_g \frac{L_2}{L_1 + L_2}$        $i_2(t \rightarrow \infty) = I_g \frac{L_1}{L_1 + L_2}$

sol'n: a) Take Thevenin equiv. of  $I_g$  and  $R_g$  on left. Solve for  $v$  across  $L$ 's by replacing  $L$ 's with equivalent  $L$ :



circuit for  $t \geq 0$

$L$ 's in parallel give  $L_{eq} = L_1 \parallel L_2 = \frac{L_1 L_2}{L_1 + L_2}$

( $L$ 's in parallel are like  $R$ 's in parallel in terms of the formula we use.)

Now we use the general solution for  $v(t \geq 0)$ :

$$v(t \geq 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t / \tau}$$

$\tau = L_{eq} / R_g$   
 time constant

To find  $v(0^+)$ , we use  $i_1(0^+) = i_1(0^-)$  and  $i_2(0^+) = i_2(0^-)$ . But  $i_1(0^-) = i_2(0^-) = 0$  since no energy is stored in  $L_1$  and  $L_2$  at  $t=0$ .

a) cont.

Since  $i_1(0^+)$  and  $i_2(0^+) = 0$ , we must have no current through  $R_g$  at  $t = 0^+$ .

$\therefore$  At  $t = 0^+$ , we have no  $v$  drop across  $R_g$ .

$$\therefore v(t=0^+) = V_{TH} = I_g R_g$$

For  $v(t \rightarrow \infty)$  we observe that the  $L$ 's act like wires, and  $v(t \rightarrow \infty) = 0$ .

Plugging into the general sol'n gives

$$v(t \geq 0) = I_g R_g e^{-t/(L_{eq}/R_g)}$$

Note: The time constant for circuit with  $L$  and  $R$  is  $L_{eq}/R_{Ther}$ . Taking the Thevenin equivalent always gives the needed  $R$ .

Now we can also write down a formula for  $i(t) = i_1(t) + i_2(t)$  for  $t \geq 0$ :

$$i(t \geq 0) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)] e^{-t/(L_{eq}/R_g)}$$

Note: All  $i$ 's and  $v$ 's have same time constant.

We know  $i(0^+) = i_1(0^+) + i_2(0^+) = i_1(0^-) + i_2(0^-) = 0$ .

At  $t \rightarrow \infty$ , the  $L$ 's act like wires, giving  $i = I_g$ .

$$\therefore i(t \geq 0) = I_g \left[ 1 - e^{-t/(L_{eq}/R_g)} \right]$$

Now we determine how  $i(t \geq 0)$  is divided between the two  $L$ 's to give  $i_1(t \geq 0)$  and  $i_2(t \geq 0)$ .

a) cont.

Since both  $L$ 's have same  $V$  across them, we have

$$v = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} \quad \therefore \frac{di_1}{dt} = \frac{L_2}{L_1} \frac{di_2}{dt}$$

Now we calculate currents:

$$i_1(t) = \int \frac{di_1}{dt} dt = \int \frac{L_2}{L_1} \frac{di_2}{dt} dt = \frac{L_2}{L_1} \int di_2$$

$$\text{or } i_1(t) = \frac{L_2}{L_1} i_2(t)$$

$$\text{Also, } i_1(t) + i_2(t) = i(t).$$

$$\text{Solving these two eqns gives } i_1(t) = \frac{L_2}{L_1 + L_2} i(t)$$

$$i_2(t) = \frac{L_1}{L_1 + L_2} i(t)$$

$$\text{Thus, } i_1(t \geq 0) = I_g \frac{L_2}{L_1 + L_2} \left( 1 - e^{-t/(L_{eq}/R_g)} \right)$$

$$i_2(t \geq 0) = I_g \frac{L_1}{L_1 + L_2} \left( 1 - e^{-t/(L_{eq}/R_g)} \right)$$

$$b) \quad \text{At } t \rightarrow \infty \text{ we have } e^{-t/(L_{eq}/R_g)} \rightarrow 0.$$

$$\therefore i_1(t \rightarrow \infty) = I_g \frac{L_2}{L_1 + L_2}$$

$$i_2(t \rightarrow \infty) = I_g \frac{L_1}{L_1 + L_2}$$