
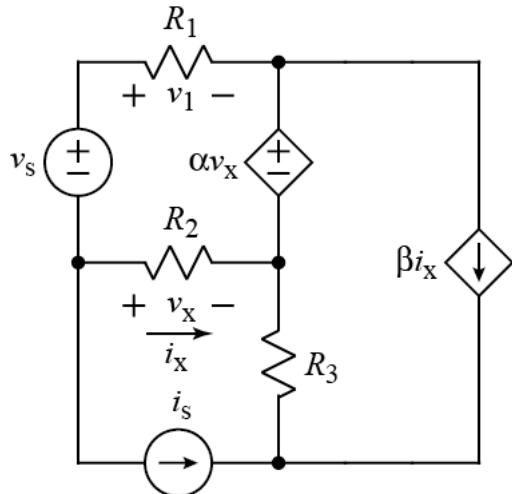


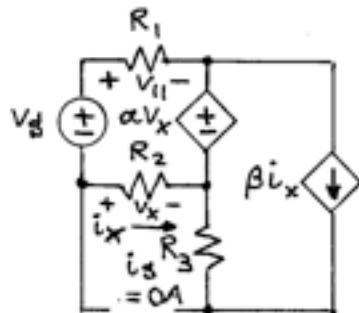**Ex:** Using superposition, find an expression for  $v_1$  in the circuit shown below.




**Sol'n:** We turn on one independent source at a time. Dependent sources stay on.

**case I:**  $v_s$  on,  $i_s$  off = open



If we examine where  $i_x$  goes, we discover that  $i_x$  flows thru  $R_1$ . Thus, a  $v$ -loop around the upper left yields a value for  $i_x$ .

Note that  $v_{x1} = i_{x1}R_2$ .

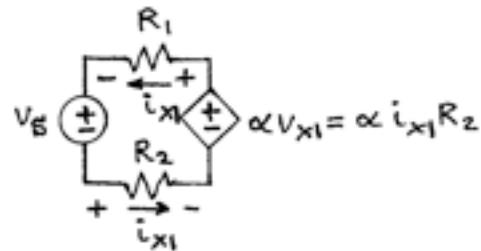

$$V\text{-loop: } V_S + i_{x1}R_1 - i_{x1}\alpha R_2 + i_{x1}R_2 = 0 \text{ V}$$


$$\text{or } i_{x1}(R_1 + R_2 - \alpha R_2) = -V_S$$

$$\text{or } i_{x1} = \frac{-V_S}{R_1 + R_2 - \alpha R_2}$$


Using Ohm's law to find  $V_{11}$  we have

$$V_{11} = -i_{x1}R_1 = V_S \frac{R_1}{R_1 + R_2 - \alpha R_2}$$

case II:  $V_S$  off = wire,  $i_g$  on

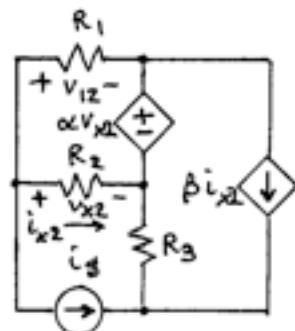

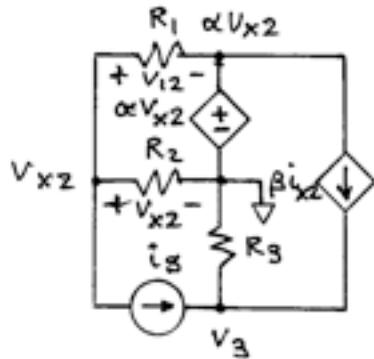We can always use node-voltage.  
 Putting a reference in the center  
 is convenient.



Consider the  $V_{x2}$  node:

$$\frac{V_{x2} - \alpha V_{x2}}{R_1} + \frac{V_{x2}}{R_2} + i_S = 0A$$

$$\text{or } V_{x2} \left( \frac{1}{R_1} - \frac{\alpha}{R_1} + \frac{1}{R_2} \right) = -i_S$$

$$\text{or } V_{x2} (R_2 - \alpha R_2 + R_1) = -i_S R_1 R_2$$

$$\text{or } V_{x2} = \frac{-i_S R_1 R_2}{R_1 + R_2 (1 - \alpha)}$$

$$V_{12} = V_{x2} - \alpha V_{x2} = (1 - \alpha) V_{x2}$$


$$\text{or } V_{12} = -\frac{i_S R_1 R_2 (1 - \alpha)}{R_1 + R_2 (1 - \alpha)}$$

Now we sum the results from the two cases.

$$V_1 = V_{11} + V_{12} = \frac{v_S R_1 - i_S R_1 R_2 (1 - \alpha)}{R_1 + R_2 (1 - \alpha)}$$

We perform some consistency checks. We set some component values to zero to create a circuit with an obvious solution. Then we see if our above expression for  $v_1$  gives the correct answer.

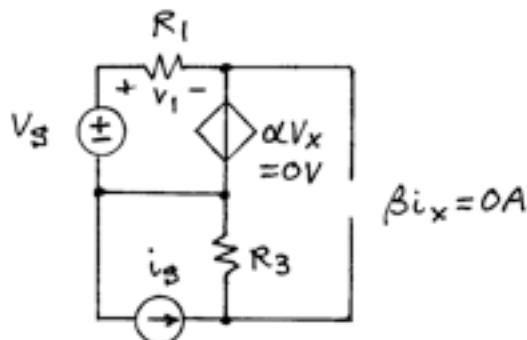Check 1: Set  $R_2 = 0$  so  $v_x = 0V$ .  
Set  $\beta = 0$  so  $\beta i_x = 0A$ .



From the v-loop in the upper left we have  $v_1 = V_S$ .

Our answer above gives


$$v_1 = \frac{V_S R_1 - i_S R_1 (0)(1-\alpha)}{R_1 + 0(1-\alpha)} = V_S \quad \checkmark$$

Check 2: Set  $R_1 = 0$ , then  $v_1 = 0V$ .

Our answer for  $v_1$  gives

$$v_1 = \frac{V_S (0) - i_S (0) R_2 (1-\alpha)}{0 + R_2 (1-\alpha)} = 0V \quad \checkmark$$

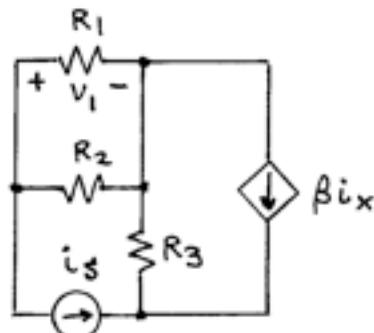Check 3: Set  $v_g = 0V$  and  $\alpha = 0$ .



Careful inspection reveals that  $R_1$  and  $R_2$  are in parallel and  $i_s$  flows thru  $R_1$  and  $R_2$ .

So we have a current divider, and voltage  $v_i$  is given by

$$v_i = -i_s \frac{R_2}{R_1 + R_2} \cdot R_1$$

Our answer above gives

$$v_i = \cancel{\alpha R_1}^0 - i_s R_1 R_2 (1 - \alpha) \over R_1 + R_2 (1 - \alpha)$$

$$\text{or } v_i = -\frac{i_s R_1 R_2}{R_1 + R_2} \quad \checkmark$$

All checks thus far are satisfied.