

**Stuff**

Labs start Wednesday. Bring an old video camera with power supply & audio / video connections if you want to do those parts of lab 1.

**Decibels etc.**

Start with lecture notes 1/10/03, p.4 & 5

**Problem Sessions:**

W, 11:50 - 12:40 am, WBB 212 (tall brick geology building)

F, 10:45 - 11:35 am, MEB 1208 (by SW entrance)

**Desirable characteristics of amplifiers**


Want  $R_{in} \rightarrow \infty$  High input resistance means the amplifier will not load down the source or previous stage.

Want  $R_o \rightarrow 0$  Low output resistance means the amplifier supply lots of current to the load or next stage.

High  $R_{in}$  and low  $R_c$  means good current gain. In fact these terms are used much more often than "current gain".

At higher frequencies it may become more important to match impedances than to maximize  $R_{in}$  & minimize  $R_o$ .

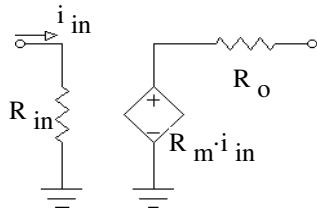**Other amplifier models** Note correction from last lecture notes,  $G_m$  &  $R_m$  were reversed




Transresistance amplifier


Instead of  $A_{vo} = \frac{v_o}{v_{in}}$  (unloaded)

This amp has  $R_m = \frac{v_o}{i_{in}}$  (unloaded)

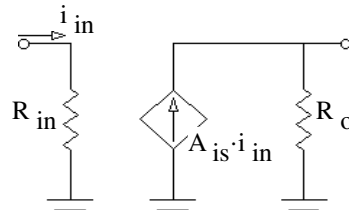$\frac{V}{I} = \Omega$ , that's why it's called transresistance



Current amplifier

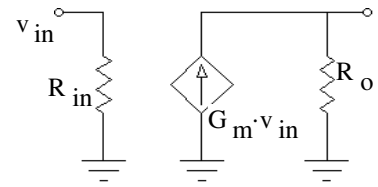

Transconductance amplifier

Instead of  $A_{vo} = \frac{v_o}{v_{in}}$  (unloaded)


This amp has  $G_m = \frac{i_o}{v_{in}}$  (unloaded)

$\frac{I}{V} = \text{conductance}$ , that's why it's called transconductance, units mho or seimen

See p.24 in text for more details

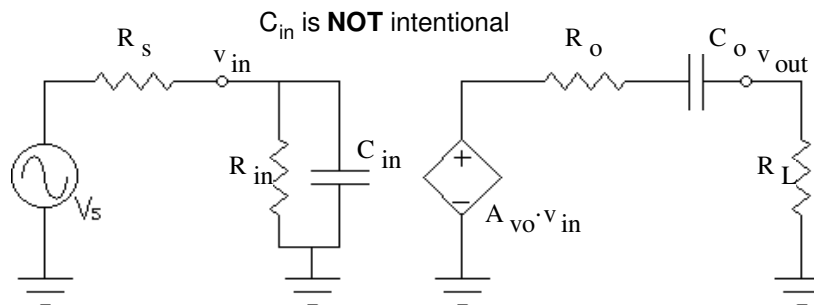**$Z_{in}$  &  $Z_{out}$**

$C_{in}$  is inevitable. All points in the circuit will exhibit some capacitance to all others. Because  $R_{in}$  is often quite high, and because this is a sensitive spot in the circuit, the "stray" capacitance at  $C_{in}$  is a big deal. Also,  $C_{in}$  can actually appear much larger due to something called the "Miller effect".



$$Z_{in} = \frac{1}{\frac{1}{R_{in}} + j \cdot \omega \cdot C_{in}}$$

= input impedance

$$Z_o = R_o + \frac{1}{j \cdot \omega \cdot C_o}$$

= output impedance

Coupling capacitors like  $C_o$  are very common in amplifiers. They isolate the DC from stage to stage while allowing the signals to go through.

**Frequency Response**

$C_{in}$  will cause a high-frequency roll-off &  $C_o$  will cause a low-frequency roll-off, so we'd better review filters and Bode plots.

Continue to **Frequency Response & Bode Plot Examples**