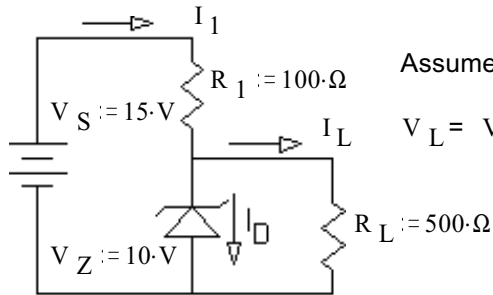


### Shunt Regulators

The purpose of a voltage regulator is to keep the voltage at the "load" as constant as possible. Two separate things can cause the load voltage to change -- changes (including ripple) in the source voltage and changes in the load resistance. A simple voltage regulator can be made with a zener diode.



Shunt regulator


Assume zener is conducting in breakdown region

$$V_L = V_D = V_Z \quad I_L := \frac{V_Z}{R_L} \quad I_L = 20 \text{ mA}$$

$$I_1 := \frac{V_S - V_Z}{R_1} \quad I_1 = 50 \text{ mA}$$

Check If you assumed conducting, then check current.
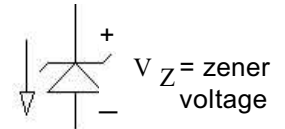
$$I_D := I_1 - I_L \quad I_D = 30 \text{ mA} > 0, \text{ so assumption OK}$$



What is the smallest  $V_S$  for which  $V_L$  remains "regulated"? Figure  $V_L$  and  $I_L$  and as above, now assume  $I_D = 0$ . Anything less than this and the regulator "drops out" of regulation.

$$I_{1\text{min}} := I_L \quad I_{1\text{min}} = 20 \text{ mA}$$

$$V_{R1\text{min}} := I_{1\text{min}} \cdot R_1 \quad V_{R1\text{min}} = 2 \text{ V}$$

$$V_{S\text{min}} := V_D + V_{R1\text{min}} \quad V_{S\text{min}} = 12 \text{ V}$$

Assuming  $V_S = 15\text{V}$  again, what is the smallest  $R_L$  for which the remains "in regulation".  $I_1$  is as calculated before.



$$I_{D\text{min}} := 0 \text{ mA} \quad I_{L\text{max}} := I_1 \quad R_{L\text{min}} := \frac{V_D}{I_{L\text{max}}} \quad R_{L\text{min}} = 200 \text{ } \Omega$$

Of course these calculation assume an **ideal** zener diode which holds exactly the same reverse voltage regardless of the current, right down to 0 current. Oh, would that it were so easy...
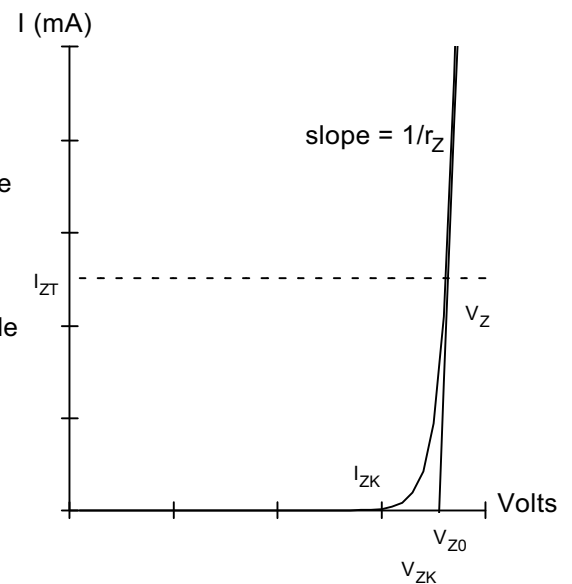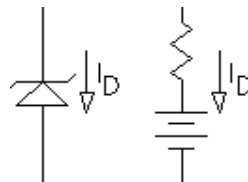
### Non-ideal zener


- $V_Z$  = Specified zener voltage
- $I_{ZT}$  = The current required to get the specified zener voltage
- $r_Z$  = The diode resistance, defined by the slope of the diode curve
- $V_{Z0}$  = The smallest zener voltage due to  $r_Z$  if there were no "knee"
- $V_{Z0} = V_Z - r_Z \cdot I_{ZT}$
- $I_{ZK}$  = The knee current, the minimum current under which the diode voltage no longer considered "regulated"
- $V_{ZK}$  = The knee voltage at  $I_{ZK}$ .

Above the knee, we can model the diode as:



# ECE 2100 Lecture Notes 2/19/03 p2

## Non-ideal shunt regulator

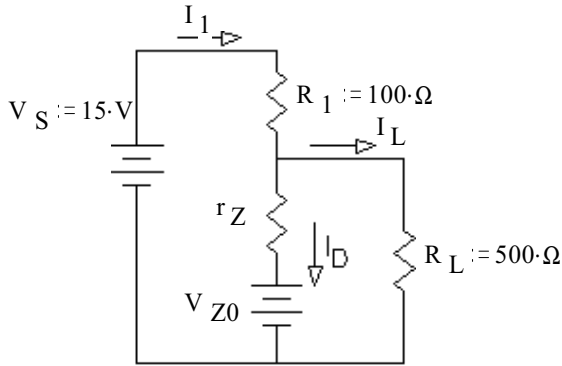

Shunt regulator

Let's say we have the specs for the diode:

$$V_Z := 10 \cdot V \text{ at } 50 \text{ mA, which means: } I_{ZT} := 50 \cdot \text{mA}$$

$$r_Z := 4 \cdot \Omega \quad I_{ZK} := 5 \cdot \text{mA}$$

We need  $V_{Z0}$  to complete our model of the diode. This number is rarely given. Usually you'll have to calculate it.

$$V_{Z0} := V_Z - I_{ZT} \cdot r_Z \quad V_{Z0} = 9.8 \cdot V$$

This circuit can now be analyzed by superposition, Thevenin equivalent, or by nodal analysis. But we'll put that off for a minute and find the limit cases first, because they are a little easier.

What is the smallest  $V_S$  for which  $V_L$  remains "regulated"?

$$V_{Dmin} := V_{Z0} + I_{ZK} \cdot r_Z \quad V_{Dmin} = 9.82 \cdot V$$

$$I_{Dmin} := I_{ZK} \quad I_{Lmin} := \frac{V_{Dmin}}{R_L} \quad I_{Lmin} = 19.64 \cdot \text{mA}$$

$$I_{1min} := I_{ZK} + I_{Lmin} \quad I_{1min} = 24.64 \cdot \text{mA}$$

$$V_{Smin} := V_{Dmin} + I_{1min} \cdot R_1 \quad V_{Smin} = 12.284 \cdot V$$

Assuming  $V_S = 15V$  again, what is the smallest  $R_L$  for which the remains "in regulation".


$$V_{Dmin} := V_{Z0} + I_{ZK} \cdot r_Z \quad V_{Dmin} = 9.82 \cdot V$$

$$I_{Dmin} := I_{ZK} \text{ again} \quad I_{1max} := \frac{V_S - V_{Dmin}}{R_1} \quad I_{1max} = 51.8 \cdot \text{mA}$$


$$I_{Lmax} := I_{1max} - I_{Dmin} \quad I_{Lmax} = 46.8 \cdot \text{mA}$$

$$R_{Lmin} := \frac{V_{Dmin}}{I_{Lmax}} \quad R_{Lmin} = 209.8 \cdot \Omega$$

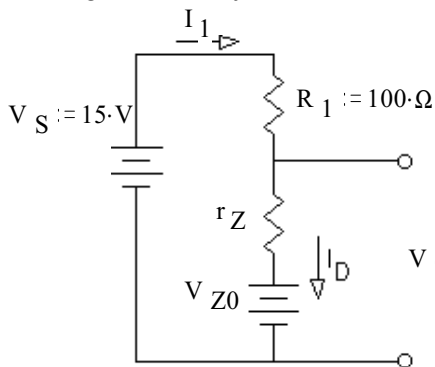
For the general analysis, make a Thevenin's equivalent


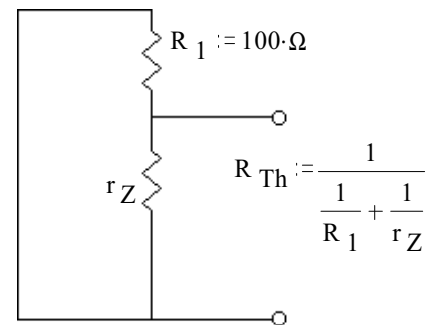
$$V_{Th} := (V_S - V_{Z0}) \cdot \frac{r_Z}{R_1 + r_Z} + V_{Z0}$$


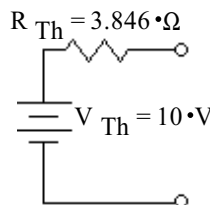
$$R_{Th} := \frac{1}{\frac{1}{R_1} + \frac{1}{r_Z}}$$



If  $R_1 \gg r_Z$ , then  $R_{Th} \sim r_Z$

Now you can find the voltage across almost any load very quickly

## Regulation

$$\text{Load Regulation} = \frac{V_{nL} - V_{fL}}{I_{fL} - I_{nL}} = \frac{\Delta V_L}{\Delta I_L} = \frac{-V_{RTh}}{I_L} = -R_{Th} = -\frac{1}{\frac{1}{R_1} + \frac{1}{r_Z}}$$


$$\text{Line Regulation} = \frac{V_{Lmax} - V_{Lmin}}{V_{Smax} - V_{Smin}} = \frac{\Delta V_L}{\Delta V_S} = \frac{\Delta V_{Th}}{\Delta V_S} = \frac{d}{dV_S} \left[ (V_S - V_{Z0}) \cdot \frac{r_Z}{R_1 + r_Z} + V_{Z0} \right] = \frac{r_Z}{R_1 + r_Z}$$

no load current, or constant load current

# ECE 2100 Lecture Notes 2/19/03 p3
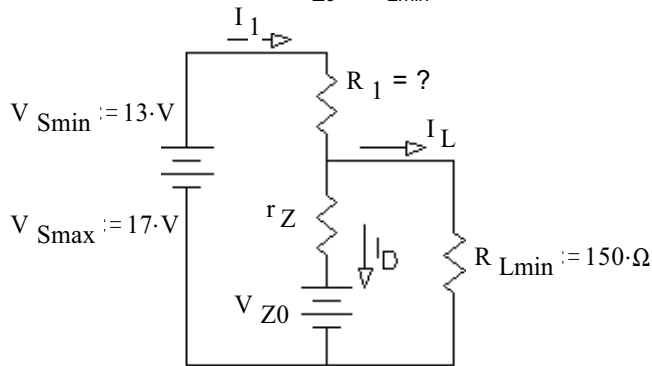
## Design

Select a diode such the  $V_{Z0} > V_{Lmin}$  required. Now design  $R_1$  for the minimum  $R_L$  and minimum  $V_S$ .



Let's say we select the diode:

$$V_Z := 10 \cdot V \quad \text{at } 50 \text{ mA, which means: } I_{ZT} := 50 \cdot \text{mA}$$

$$r_Z := 4 \cdot \Omega \quad I_{ZK} := 5 \cdot \text{mA}$$

We need  $V_{Z0}$  to complete our model of the diode. This number is rarely given. Usually you'll have to calculate it.

$$V_{Z0} := V_Z - I_{ZT} \cdot r_Z \quad V_{Z0} = 9.8 \cdot V$$

$$I_{Dmin} := I_{ZK}$$

$$V_{Dmin} := V_{Z0} + I_{ZK} \cdot r_Z \quad V_{Dmin} = 9.82 \cdot V$$

$$I_{Lmax} := \frac{V_{Dmin}}{R_{Lmin}} \quad I_{Lmax} = 65.47 \cdot \text{mA}$$

$$I_1 := I_{Lmax} + I_{Dmin} \quad I_1 = 70.47 \cdot \text{mA}$$

$$R_1 := \frac{V_S - V_{Dmin}}{I_1} \quad R_1 = 73.5 \cdot \Omega$$

Select the standard value of  $72 \Omega$   $105\% \cdot 72 \cdot \Omega = 75.6 \cdot \Omega$   
won't work in worst case

Select the standard value of  $R_1 := 68 \cdot \Omega$   $105\% \cdot R_1 = 71.4 \cdot \Omega$  OK

Must check some power dissipations.  $P_{R1} = \frac{(V_{Smax} - V_{Dmin})^2}{R_1} = 0.758 \cdot W$  need a 1 watt  $R_1$ . Can be a combination of lower wattage resistors

What if  $R_L$  were removed?  $I_{Zmax} := \frac{V_{Smax} - V_{Z0}}{R_1 + r_Z} \quad I_{Zmax} = 100 \cdot \text{mA}$

$$P_{Zmax} = I_{Zmax} \cdot V_{Z0} + I_{Zmax}^2 \cdot r_Z = 1.02 \cdot W$$

need better than a 1 W zener

Can be two or more in series, but not in parallel, one  $V_Z$  will always be a little smaller and that diode will take the most current.

## Diode Equation section 3.2 in book

Actually diode characteristic is a curve

## Diode Equation

diode voltage

$$\text{Diode current: } I_d = I_s \cdot \left( e^{\frac{V_d}{n \cdot V_T}} - 1 \right)$$

Usually drop this 1 in forward bias


Saturation current  
(AKA scale current)

$$\text{Thermal voltage } = \frac{k \cdot T}{q} \approx 25 \cdot \text{mV}$$

Fudge factor, assume  $n = 1$  in ICs  
and  $n = 2$  for discrete parts
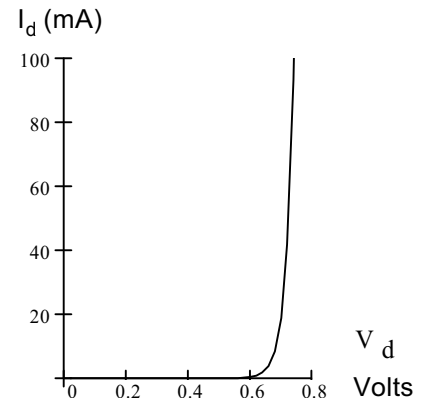
## Other permutations of the diode equation:

$$V_d = n \cdot V_T \cdot \ln \left( \frac{I_d}{I_s} \right) \quad I_s = \frac{I_d}{\left( e^{\frac{V_d}{n \cdot V_T}} - 1 \right)}$$



Absolute temperature:  $T = ^\circ C + 273$

Electron volt:  $eV := 1.60 \cdot 10^{-19} \cdot \text{joule}$

Boltzmann's constant:  $k := 8.63 \cdot 10^{-5} \cdot \frac{eV}{K}$

Electron charge:  $q := 1.60 \cdot 10^{-19} \cdot \text{coul}$