

Stuff



Interested in research at the "U"? Check out a series of talks in EMCB 112, Thursdays 2-3pm. These talks are geared for undergraduates.

Friday Reed Harrison will be here for a few minutes to talk about ECE 3110 and IC design classes.

Finish up BJT Bias Design


A couple of other bias schemes

Base bias, p280

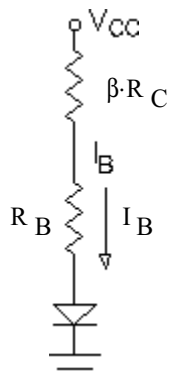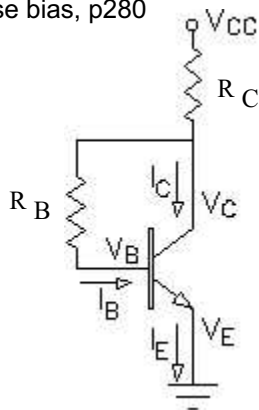

$$I_B = \frac{V_{CC} - 0.7\text{V}}{R_B + \beta R_C}$$

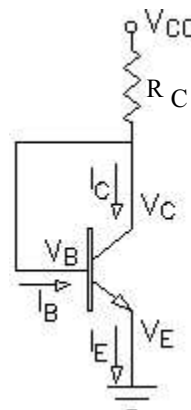The bigger R_C is with respect to R_B , the more stable I_C is



Taken to extremes, I_C is now very stable at:


$$I_C = \frac{V_{CC} - 0.7\text{V}}{R_C}$$

Seems like a useless circuit, but...

Current source bias: We could make the bias current very stable if we had a current source



If we can make current sources (drains), then...

Current source bias, p281

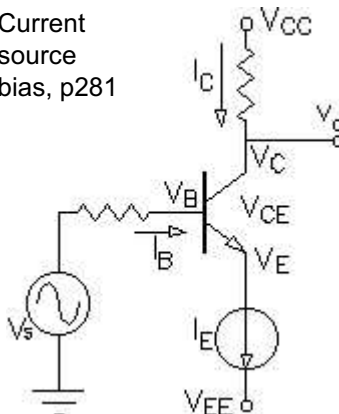

For a perfect current source, $R_E = \infty$

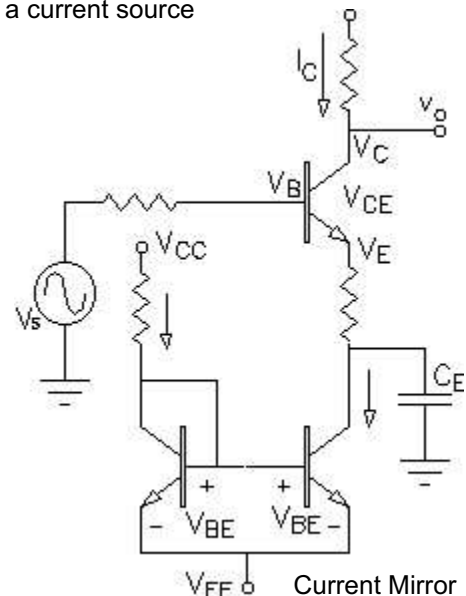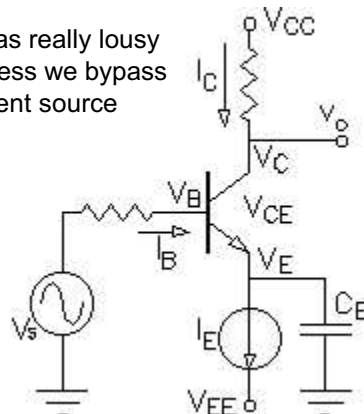which has really lousy gain unless we bypass the current source



Current Mirror

Current mirrors A way to make a current source (drain)


$$I_{C1} = \frac{V_{CC} - V_{EE} - 0.7\text{V}}{R_C} = I_{\text{ref}}$$

Recall that v_{BE} is really not exactly 0.7V, from Ebers-Moll eq.: $I_C = I_S e^{\frac{v_{BE}}{V_T}}$

Because $V_{BE1} = V_{BE2}$, $I_{C1} = I_{C2}$

We can get a current source (usually called a current drain in this type of configuration). I could make a positive source if I used PNP transistors.

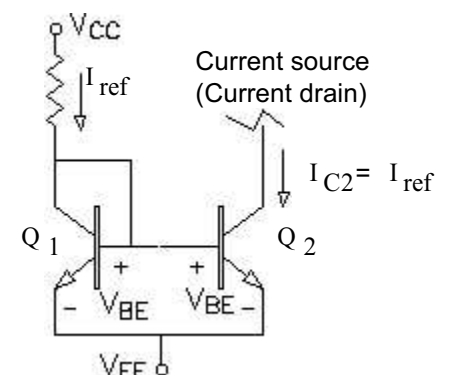But, the transistors must be identical, and at the same temperature, like in an IC.




DC in the active region (not bias)

I said early on that few DC circuits use the transistor in its active region, but there are some...

How about an adjustable current source to power multiple LEDs with a non-stable voltage source (like car power). Q_1 and Q_2 work together to maintain the voltages shown (This is negative feedback). So the current through the LEDs can be set by R_1 as $0.7V/R_1$. Select R_2 so that in the worst case the current through it is more than $I_{LED}/100$.

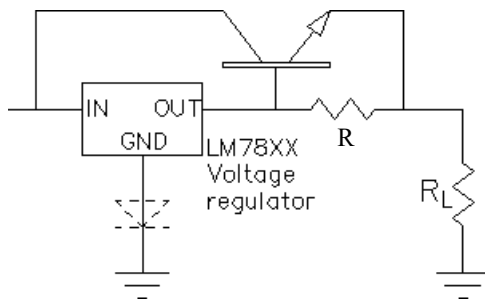
Or perhaps a way to make a 1A voltage regulator handle more current.



When enough current flows through R to get $0.7V$ across it, then the transistor will start to turn on to supply more current to the load. You could put a diode in the ground connection of the regulator to make up for the lost $0.7V$ across R .

Or, you could make the whole regulator from scratch.

Make sure that R_1 is small enough to handle I_L/β_1

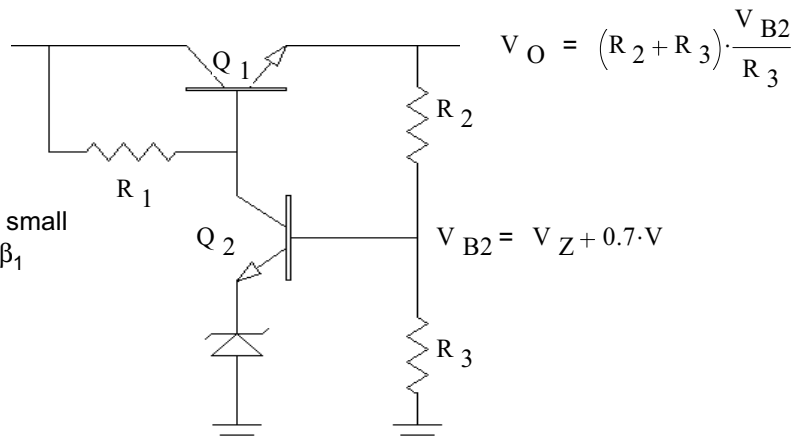**Adding Signals to the analysis****DC Bias or Quiescent-point (Q-point) Analysis**

Variation of superposition for circuits with DC power supply(s) and AC signals.

- 1) Zero all signal sources.
- 2) Consider all coupling and bypass capacitors as open.
- 3) Use special DC models for non-linear parts and/or active elements ($0.7V$ drop for base-emitter diode).
- 4) Compute the DC voltages or currents.
- 5) Check your assumptions and models.

AC Small-Signal Analysis

Variation of superposition for circuits with DC power supply(s) and AC signals.

- 1) Zero all DC sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 2) Consider all coupling and bypass capacitors as shorts.
- 3) Use special small-signal models for non-linear parts and/or active elements. Some may depend on Q-point values.

small-signal emitter resistance: $r_e = \frac{V_T}{I_C}$ $V_T \approx 25mV$

- 4) Compute the signal voltages or currents of interest.
- 5) Check your assumptions and models.

Common collector (CC)

The circuits shown are typical arrangements. Note that V_{EE} is often 0 V (ground). The equations below are for these circuits, adapt them as necessary to fit your actual circuit.

Voltage gain about 1. Good for current gain, or to match a high impedance source to a low impedance load.

The small-signal emitter resistance is right in the emitter of the transistor (where the arrow is).

Recall that the emitter resistor looks β times as big from the base's point-of-view. That's also true for signals

$$\text{Input impedance: } R_i = R_{B1} \parallel R_{B2} \parallel \beta(r_e + R_E \parallel R_L)$$

The opposite effect also works, resistors at the base look β times smaller from the emitter's point-of-view.

$$\text{Output impedance: } R_o = R_E \parallel r_e + R_{B1} \parallel R_{B2} \parallel R_S \quad \beta$$

Low frequency corner frequencies

$$f_{CL1} = \frac{1}{2 \cdot \pi \cdot (R_S + R_i) \cdot C_{in}} \quad f_{CL2} = \frac{1}{2 \cdot \pi \cdot (R_L + R_o) \cdot C_{out}}$$




From the signal analysis, the only thing between the base signal and the output signal is r_e . To find the output, just use the voltage divider equation.

$$\text{Voltage gain: } A_v = \frac{v_o}{v_b} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L} \approx 1$$

$$\text{OR: } \frac{v_o}{v_s} = \frac{R_i}{R_S + R_i} \cdot \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L}$$



You could think of the output as simply 0.7V DC less than the input, which doesn't make the AC signal any less. Of course this doesn't account for the r_e effects.
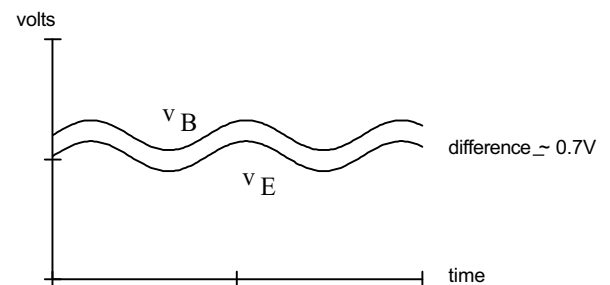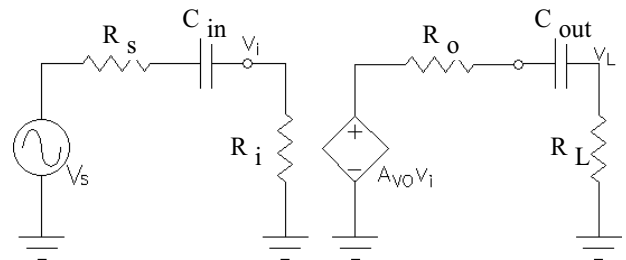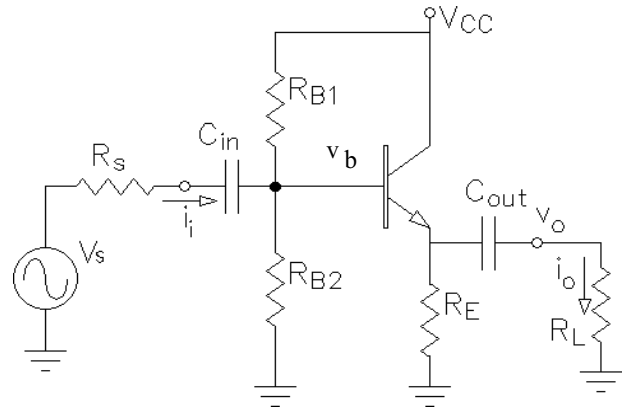
$$\text{Current gain: } A_i = \frac{i_o}{i_i} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L} \cdot \frac{R_i}{R_L} = A_v \cdot \frac{R_i}{R_L} \approx \frac{R_i}{R_L}$$



Common emitter (CE)

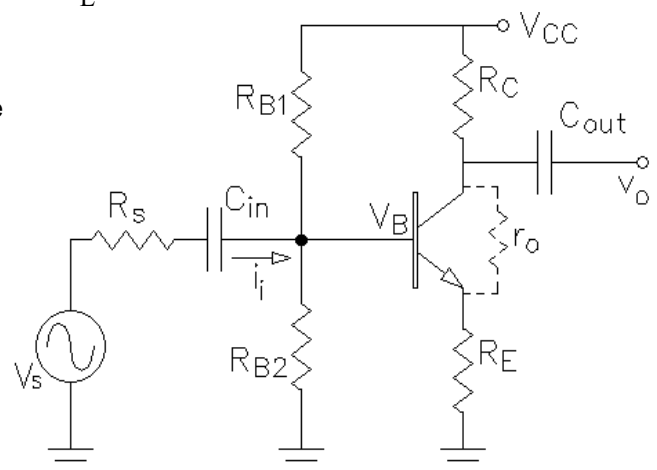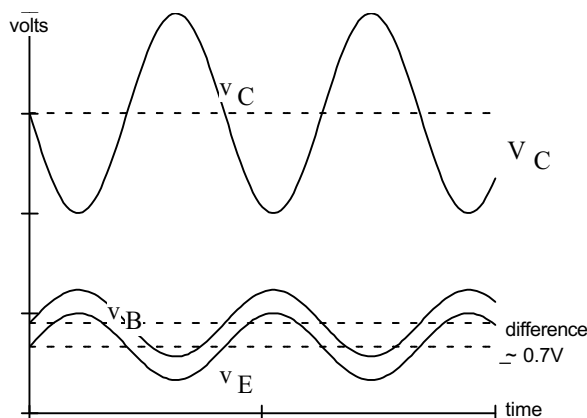Now let's add a resistor in the collector (R_C). Nearly the same current that flows through R_E flows through R_C .



$$v_c = -i_c \cdot R_C \quad v_e = i_e \cdot R_E \approx v_b$$

$$i_c \approx i_e \quad \text{so: } \frac{v_c}{v_b} \approx -\frac{R_C}{R_E} \quad \text{gain}$$