

Stuff

Interested in research at the "U"? Check out a series of talks in EMCB 112, Thursdays 2-3pm. These talks are geared for undergraduates.

Dr. Harrison will be here for a few minutes today to talk about ECE 3110 and IC design classes.

Finish up Common collector (CC)

Common emitter (CE)

Common Emitter amplifier, example:


Bias:

$$V_{BB} := \frac{R_{B2}}{R_{B2} + R_{B1}} \cdot V_{CC} \quad V_{BB} = 1.782 \cdot V$$

$$R_{BB} := \frac{1}{\left(\frac{1}{R_{B2}} + \frac{1}{R_{B1}}\right)} \quad R_{BB} = 1.479 \cdot k\Omega$$

$$I_B := \frac{V_{BB} - 0.7 \cdot V}{R_{BB} + \beta \cdot R_E} \quad I_B = 0.056 \cdot mA$$
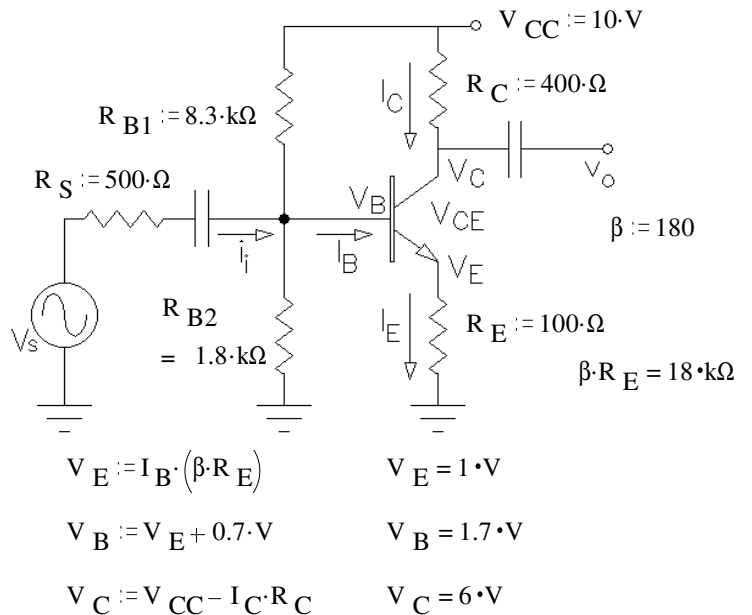
$$I_E := \frac{V_E}{R_E} \quad I_C := I_E \quad I_C = 10 \cdot mA$$



$$V_E := I_B \cdot (\beta \cdot R_E) \quad V_E = 1 \cdot V$$

$$V_B := V_E + 0.7 \cdot V \quad V_B = 1.7 \cdot V$$

$$V_C := V_{CC} - I_C \cdot R_C \quad V_C = 6 \cdot V$$

What if we put in an AC input signal:  $v_B(t) := V_B + 0.5 \cdot V \cdot \cos\left(6280 \cdot \frac{rad}{sec} \cdot t\right)$   $v_E(t) := v_B(t) - 0.7 \cdot V$

$$i_C(t) := \frac{v_E(t)}{R_E}$$

$$v_C(t) := V_{CC} - i_C(t) \cdot R_C$$

$$\frac{R_C}{R_E} = \frac{400 \cdot \Omega}{100 \cdot \Omega} = 4$$



$v_C$  is 4 times bigger and inverted

Actually, to be more correct, we should account for the small-signal resistance of the base-emitter junction.

$$r_e := \frac{V_T}{I_C} \quad r_e = 2.5 \cdot \Omega$$

gain is really:

$$\frac{R_C}{R_E + r_e} = 3.902$$

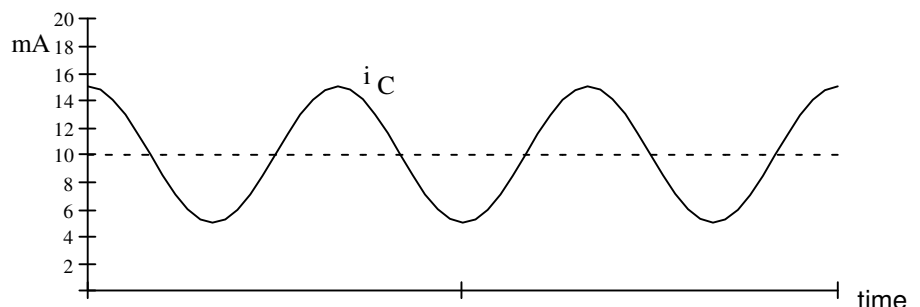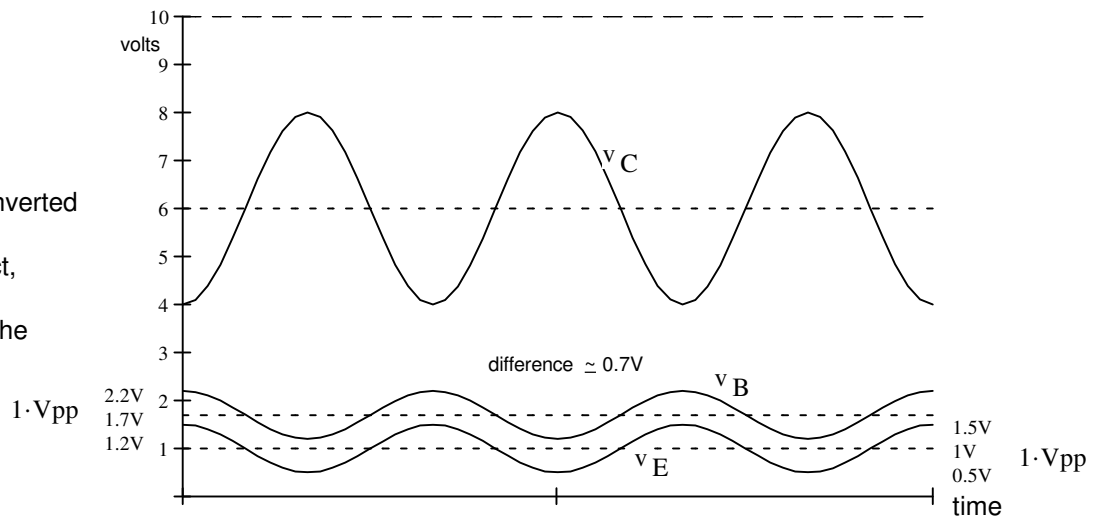

**Common emitter (CE), continued**

Input impedance:  $R_i = R_{B1} \parallel R_{B2} \parallel \beta \cdot (r_e + R_E)$

Output impedance:  $R_o = R_C \parallel r_o$

Often neglected  $r_o = \frac{V_A}{I_C}$  Early voltage. (guess  $V_A \approx 100$  V if no data)

AC collector resistance:  $r_c = R_C \parallel R_L \parallel r_o$

More correct, use:  $r_o \cdot \frac{A_v}{A_v + 1}$

instead of  $r_o$  very rarely done.

Voltage gain:  $A_v = \frac{v_o}{v_b} = \frac{r_c}{r_e + R_E}$

Current gain:  $A_i = \frac{i_o}{i_i} = \frac{r_c}{r_e + R_E} \cdot \frac{R_i}{R_L} = A_v \cdot \frac{R_i}{R_L}$

Low frequency corner frequencies

$$f_{CL1} = \frac{1}{2 \cdot \pi \cdot (R_S + R_i) \cdot C_{in}}$$

$$f_{CL2} = \frac{1}{2 \cdot \pi \cdot (R_L + R_o) \cdot C_{out}}$$

**With bypass capacitor (C<sub>E</sub>)**

This basically makes the  $R_E$  disappear at signal frequencies (If the cap is big enough).

Input impedance:  $R_i = R_{B1} \parallel R_{B2} \parallel \beta \cdot r_e$  Much lower

Output impedance:  $R_o = R_C \parallel r_o$  Same as above, but no  $r_o$  correction needed

AC collector resistance:  $r_c = R_C \parallel R_L \parallel r_o$

Voltage gain:  $A_v = \frac{v_o}{v_b} = \frac{r_c}{r_e}$


Current gain:  $A_i = A_v \cdot \frac{R_i}{R_L}$

Another low frequency corner frequency:

$$f_{CL3} = \frac{1}{2 \cdot \pi \cdot C_E} \cdot \left( \frac{1}{r_e} + \frac{1}{R_E} \right)$$




Because  $r_e$  is so small, this will usually dominate, even when  $C_E$  is big.

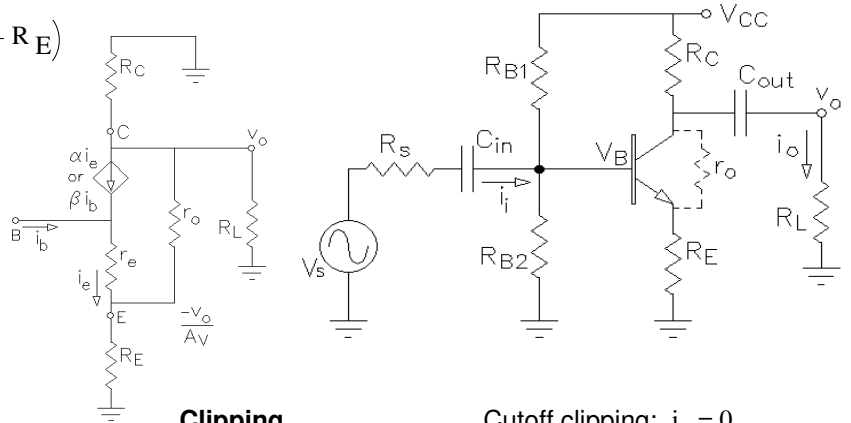Have a good & a safe Spring Break, see you in a week & a half. Go find some sun....



**Clipping**

Cutoff clipping:  $i_E = 0$

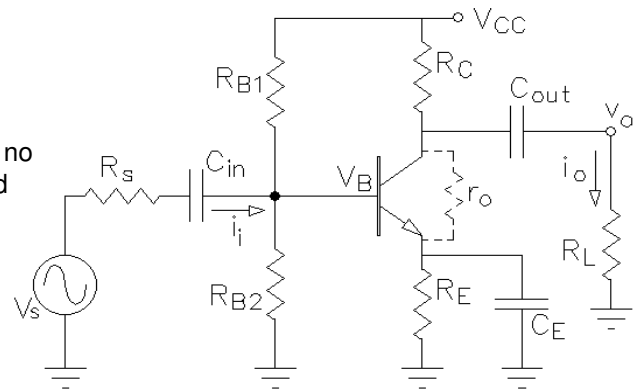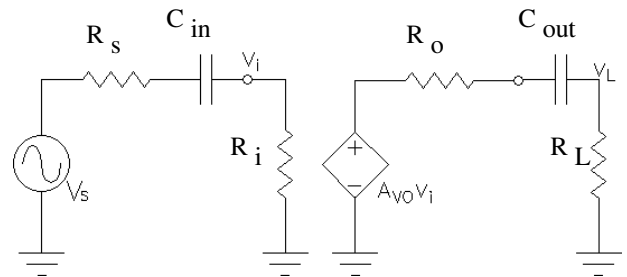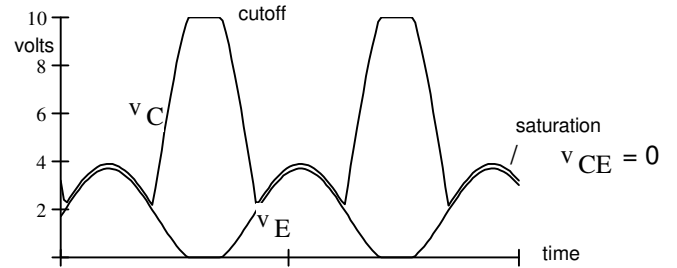

If the output swing is too big you'll get distortion because  $r_e$  varies with  $i_c$

