

Stuff Review for Final: Fri, 4/25 3:30 pm  
Final: Mon, 4/28 8:00 am

Spice #S3, due: F, 4/18 handout

HW # 23, due: F 4/18 Ex5.17 - Ex5.23  
May be handed in Monday because I screwed up


HW # 24, due: M 4/21 Ex5.24 - Ex5.34  
Ex 5.28 Book answers are OK  
May need for Ex5.33:  $V_{DD} = 5V, V_{tn} = 0.8V$

HW # 25, due: W 4/23 Ex5.35 - Ex5.39

HW # 26, due: W 4/23 Ex5.40 - Ex5.48  
May be handed in with the final

N-channel MOSFETs as  $R_D$  in CS amp p.419

Basic CS Amp



 


Last time we replaced the  $R_D$  with a current source made with P-channel devices and got a good amplifier, But PMOS devices take up a lot of space on an IC.

Try a new configuration using an NMOS with the drain connected to the gate.

$Q_2$  is guaranteed to be in saturation because  $V_D = V_G$ . Also, it's  $V_{GS} = V_{DS}$ , so we can draw the following familiar curve with a new x-axis variable:

 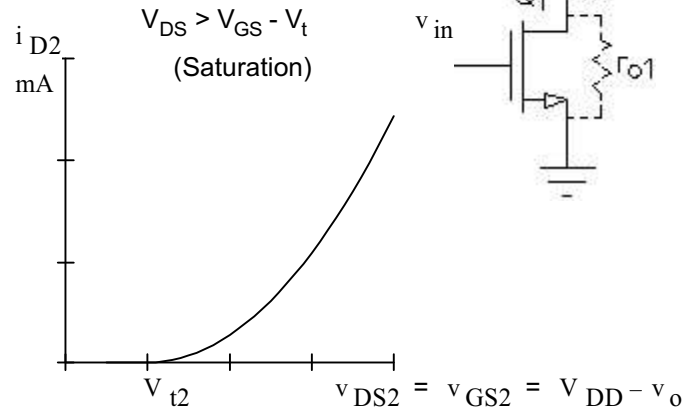 If I draw the curve with respect to  $V_{DD} - V_{DS2} = V_{DS1}$ , it will go backwards and can now be drawn on top of the  $Q_1$  curves:



Notice that the new "load line" curves up. Its non-linearity will nicely offset the inherent  $i_D$  vs  $v_{GS}$  non-linearity of the  $Q_1$ . This results in a very linear transfer characteristic and an unexpected square root in the gain term. Too bad the gain stinks.

$$i_{D1} = \frac{1}{2} \cdot k'_n \cdot \frac{W_1}{L_1} \cdot (V_{GS} + v_{in} - V_{t1})^2 = i_{D2} = \frac{1}{2} \cdot k'_n \cdot \frac{W_2}{L_2} \cdot (V_{DD} - V_D - v_o - V_{t2})^2$$

$$\sqrt{\frac{W_1}{L_1}} \cdot (V_{GS} + v_{in} - V_{t1})^2 = \sqrt{\frac{W_2}{L_2}} \cdot (V_{DD} - V_D - v_o - V_{t2})^2$$

$$\sqrt{\frac{W_1}{L_1} \cdot \frac{L_2}{W_2}} \cdot (V_{GS} + v_{in} - V_{t1}) = (V_{DD} - V_D - v_o - V_{t2})$$

Subtract off the constant, bias values from both sides:  $A_v = \frac{v_o}{v_{in}} \approx - \sqrt{\frac{W_1 \cdot L_2}{L_1 \cdot W_2}}$

If you account for the body effects of  $C_2$ :  $A_v = - \sqrt{\frac{W_1 \cdot L_2}{L_1 \cdot W_2}} \cdot \left( \frac{1}{1 + \chi} \right)$


## Depletion-type MOSFET as $R_D$ p.421

The connection of  $Q_2$ 's drain to its gate insured that it was in the saturation region.




The same connection will not have the same effect on a depletion-type NMOS. Because these parts have a negative  $V_t$ ,  $V_D$  must be  $-V_t$  volts higher than the gate. This is not a bad thing, because now we'll get a current flow even with  $v_{GS} = 0$ . That means that we can tie the gate to the source and simply operate on the  $v_{GS} = 0$  curve.

If I draw the  $v_{GS} = 0$  curve with respect to  $V_{DD} - V_{DS2} = V_{DS1}$ , it will go backwards and can now be drawn on top of the  $Q_1$  curves:

 This looks an awful lot like the PMOS load, but it's much different because of  $Q_2$  body effects.





## ECE 2100 Lecture Notes 4/18/03 p2

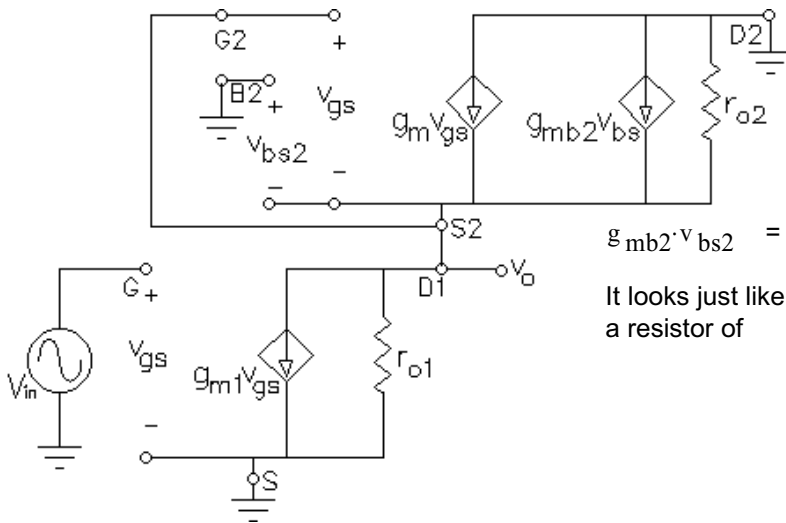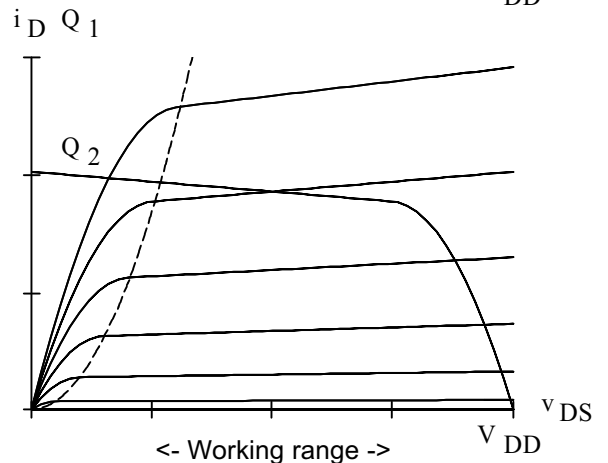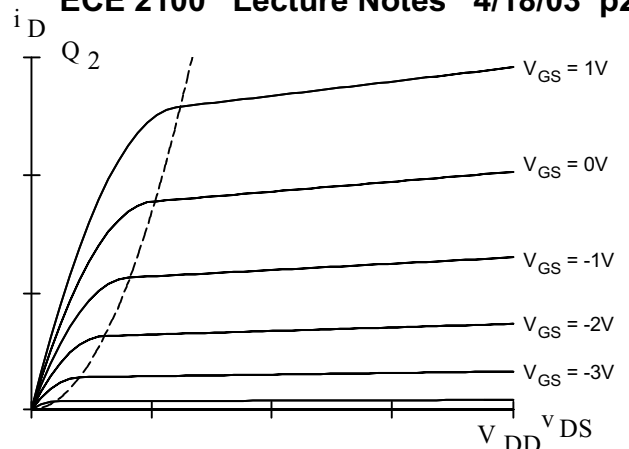

$$g_{mb2} v_{bs2} = g_{mb2} (-v_o)$$

  It looks just like a resistor of  $\frac{1}{g_{mb2}}$




$$A_v = -g_{m1} \cdot \frac{1}{g_{mb2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} \approx -\frac{g_{m1}}{g_{mb2}} = -\frac{g_{m1}}{\chi \cdot g_{m2}}$$



Since:  $g_m = \sqrt{k'_n \cdot \frac{W}{L} \cdot 2 \cdot I_D}$  and both transistors share the same  $i_D$ ,

$$A_v = -\frac{W_1 \cdot L_2}{L_1 \cdot W_2} \cdot \left(\frac{1}{\chi}\right)$$

 Which is about 3 times higher than the previous circuit.



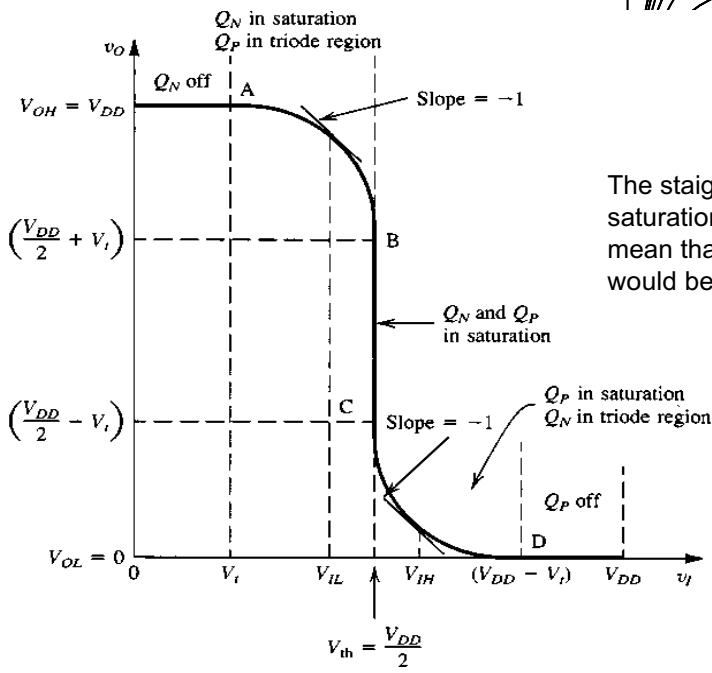 $V_{DD} = V_{GS2} + V_{GS1}$  If I draw the  $v_{GS} = 0$  curve with respect to  $V_{DD} - V_{DS2} = V_{DS1}$ , it will go backwards and can now be drawn on top of the  $Q_1$  curves:



The straight-line region, where both transistors are in saturation would only be vertical if  $\lambda = 0$ , that would mean that the saturation part of the curves above would be flat. Not a real possibility.

As a digital inverter, when the output is high,  $v_{ds}$  for the p-channel part is small and the output resistance looks like the  $r_{ds}$  for that transistor.


When the output is low,  $v_{ds}$  for the n-channel part is small and the output resistance looks like the  $r_{ds}$  for that transistor.

$$r_{ds} = \frac{1}{k' \cdot \frac{W}{L} \cdot (V_{DD} - |V_t|)}$$

Right in the center ( $V_{th}$ )

$$i_{Dn} = i_{Dp}$$


$$i_{Dn} = \frac{1}{2} \cdot k'_n \cdot \frac{W_n}{L_n} \cdot (V_{th} - V_{tn})^2 = i_{Dp} = \frac{1}{2} \cdot k'_p \cdot \frac{W_p}{L_p} \cdot (V_{DD} - V_{th} - |V_{tp}|)^2$$

 

CMOS Digital circuits are usually hooked to other MOS parts, so the load they see is usually a capacitor.

The text goes into some detail about how the capacitor is charged and discharged to find the rise and fall times. These times set the speed limits of the digital circuitry.

 A full on-off cycle results in a finite amount of charge flowing first from  $V_{DD}$  into the capacitor and then from the capacitor to ground. This means a certain amount of energy is used for each cycle.



Also makes a good linear amplifier, with the right bias: