

ECE 2100 Lecture Notes 4/23/03

A. Stolp
4/22/03,

Stuff Review for Final: Fri, 4/25 3:30 pm
Final: Mon, 4/28 8:00 am

To avoid a 5% grade penalty:

DO NOT blow off the Spice assignment

Make sure you've done all the labs.

If you're retaking the class, do lab 13.




HW # 24, due: M 4/21 Ex5.24 - Ex5.34

Ex 5.28 Book answers are OK

May need for Ex5.33: $V_{DD} = 5V$, $V_{tn} = 0.8V$

HW # 25, due: W 4/23 Ex5.35 - Ex5.39

HW # 26, Cancelled

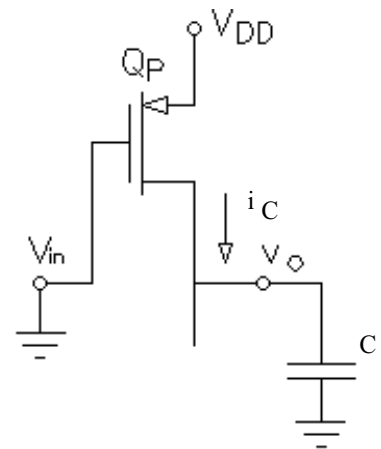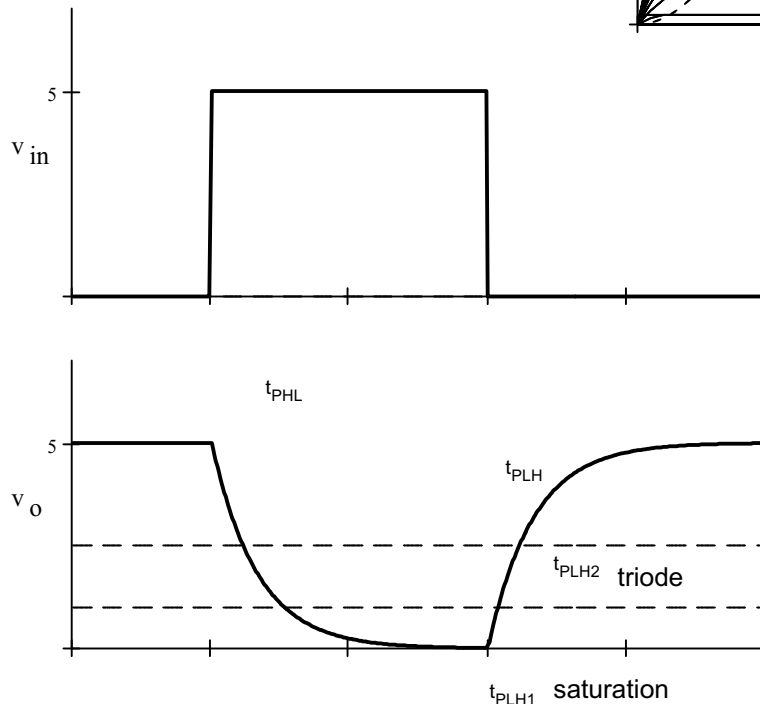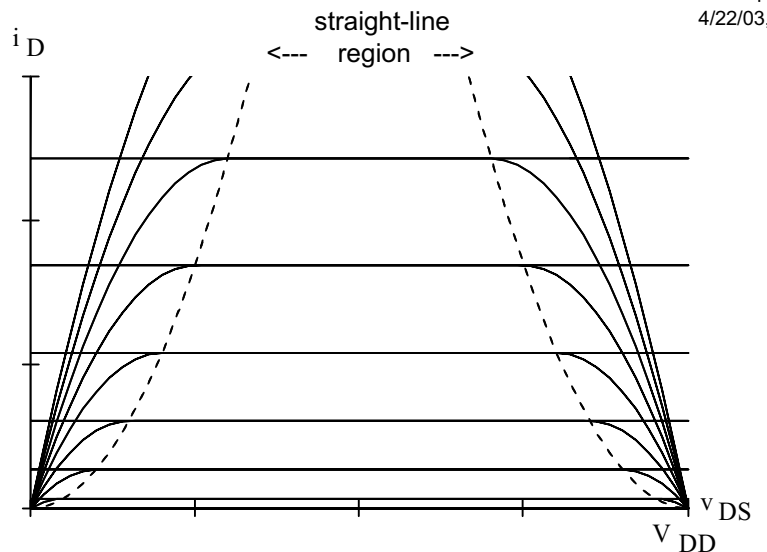

$$t_{PLH} = \frac{2 \cdot C}{k'_p \cdot \frac{W}{L}_p \cdot (V_{DD} - |V_{tp}|)} \cdot \left(\frac{|V_{tp}|}{V_{DD} - |V_{tp}|} + \frac{1}{2} \cdot \ln \left(\frac{3 \cdot V_{DD} - 4 \cdot |V_{tp}|}{V_{DD}} \right) \right)$$

Or, if $V_t \approx \frac{V_{DD}}{5}$ then this simplifies to:

$$t_{PLH} = \frac{1.6 \cdot C}{k'_p \cdot \frac{W}{L}_p \cdot V_{DD}}$$

Energy used to charge cap: $E = V_{DD} \cdot \int i_C dt$ but, when fully charged: $\frac{1}{C} \cdot \left(\int i_C dt \right) = V_{DD}$

so: $E = C \cdot V_{DD}^2$ This is the energy used per on-off cycle per CMOS pair

If you switch the gate at f cycles per second, then the power dissipated is: $P_D = f \cdot C \cdot V_{DD}^2$

ECE 2100 Lecture Notes 4/23/03

Well, That's ECE2100, Good Luck on the Final, and see you next year (hopefully not in an official capacity). Arn