


Review Notes

A. Stolp 1/14/03

Thévenin equivalent

To calculate the Thévenin equivalent:

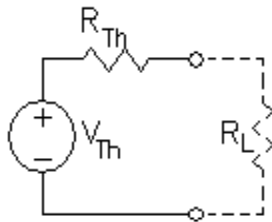- 1) Disregard the load and calculate the open-circuit voltage. This is the Thévenin voltage (V_{Th}).
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Thévenin source resistance (R_{Th}).
- 4) Draw the Thévenin equivalent circuit and add your values.



NOTE: Same procedure for impedances, but V_{Th} may have a phase angle and R_{Th} will be Z_{Th} .

Superposition

For circuits with more than 1 source.

- 1) Zero all but one source. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 2) Compute your wanted voltage or current due to the remaining source. Careful, some may be negative.
- 3) Repeat the first two steps for all the sources.
- 4) Sum all the contributions from all the sources to find the actual voltage or current. **Watch your signs!**

Q-point Analysis


Variation of superposition for circuits with DC power supply(s) and AC signals.

- 1) Zero all signal sources.
- 2) Consider all coupling and bypass capacitors as open.
- 3) Use special DC models for non-linear parts and/or active elements.
- 4) Compute the DC voltages or currents.
- 5) Check your assumptions and models.

Norton equivalent

To calculate the Norton equivalent:

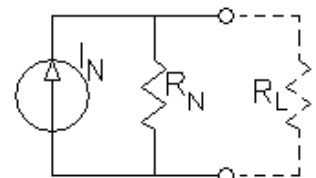- 1) Disregard the load and calculate the short-circuit current. This is the Norton current (I_N).
- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals. (DO NOT include the load in this resistance.) This is the Norton source resistance (R_N). (Exactly the same Thévenin source resistance (R_{Th})).
- 4) Draw the Norton equivalent circuit and add your values.



OR...

- 1) Find the Thévenin equivalent circuit.
- 2) Convert to Norton circuit, $R_N = R_{Th}$ and $I_N = V_{th}/R_{Th}$.

NOTE: Same procedure for impedances, but I_N may have a phase angle and R_N will be Z_N .

Small-Signal Analysis

Variation of superposition for circuits with DC power supply(s) and AC signals.

- 1) Zero all DC sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 2) Consider all coupling and bypass capacitors as shorts.
- 3) Use special small-signal models for non-linear parts and/or active elements. Some may depend on Q-point values.
- 4) Compute the signal voltages or currents of interest.
- 5) Check your assumptions and models.