

ECE 2100 homework # 15 Due: Wed, 3/12/03

Microelectronic Circuits, 4th Ed. Ch. 4
 prob. 4.2 (ans: $\beta = 368, 122, 24.2$), Ex. 4.1 - 4.7

Assume thermal voltage: $V_T = 25\text{mV}$

Note for Fig. 4.8: i_B should flow out of transistor.


A.Stolp
 3/17/02,
 2/27/03

ECE 2100 homework # 16 Due: Fri, 3/14/03 Name: _____


On separate paper, do: Microelectronic Circuits, 4th Ed. Ch. 4 Ex. 4.8 - 4.9, prob. 4.21, 4.22 (ans: 28k, 28.3k)

1. Fill in the blanks in the circuit below. You may neglect the base bias current (I_B).


a)

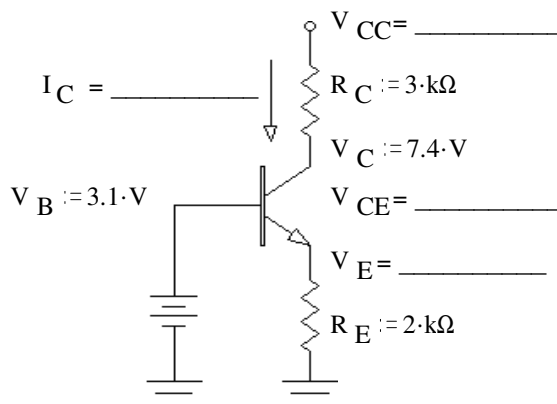

b)

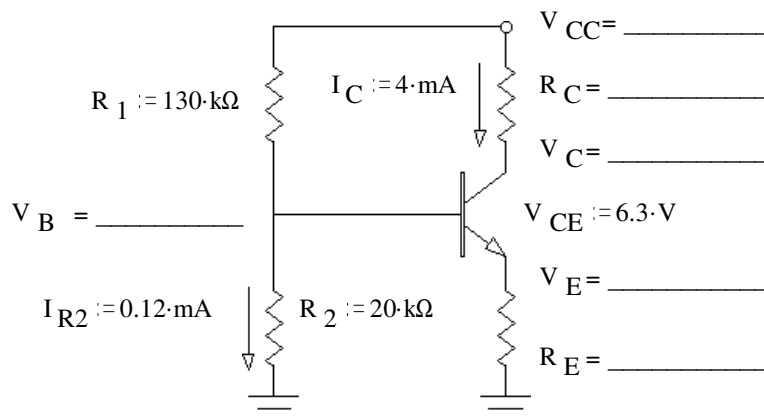


c)

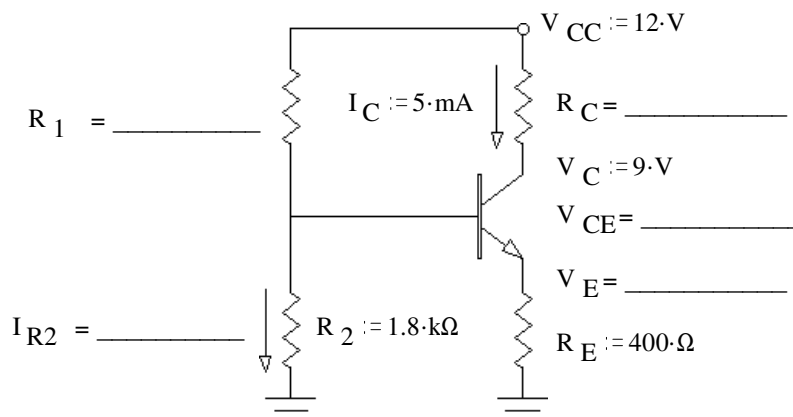

2. a) Fill in the blanks in the circuit. Neglect I_B .

ECE 2100 homework # 16, p2

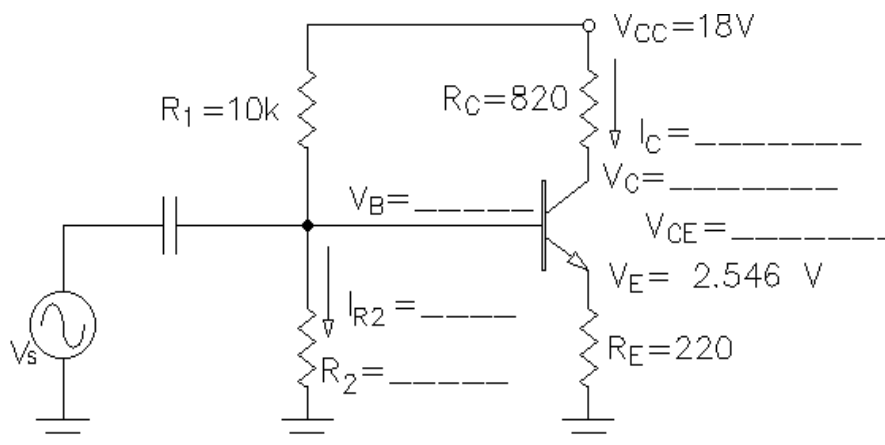

Note: You'll probably want to add a sheet of paper in order to work out the rest of this problem.

b) Is the transistor operating in the active region? Show your evidence. Yes No

c) If $\beta = 150$, how big is that I_B that we neglected?

d) Compare this value to I_{R2} . Was it reasonable to neglect I_B ? (is $I_B < 10\%$ of I_{R2})

e) If we actually built this circuit, what effect would the actual I_B have on I_C ? That is would I_C be lower, higher or the same as you found earlier? Hint: would V_B be higher or lower? Would V_E be higher or lower? Would I_E be higher or lower?

I_C would be: lower higher same
(circle one)

f) Considering only I_C and V_{CE} , how much power does this transistor dissipate or contribute?

g) Does it dissipate or contribute power? dissipate contribute (circle one)

h) If the v_s signal were applied at the base, an AC signal would also appear at the collector. How much larger would it be. (Voltage gain).

Answers

1 a) $V_E = 2.4 \text{ V}$, $V_{CE} = 5 \text{ V}$, $I_C = 1.2 \text{ mA}$, and $V_{CC} = 11 \text{ V}$ b) $V_B = 2.4 \text{ V}$, $V_{CC} = 18 \text{ V}$, $V_E = 1.7 \text{ V}$, $R_E = 425$, $V_C = 8 \text{ V}$, $R_C = 2.5 \text{ k}$ c) $V_E = 2.0 \text{ V}$, $V_{CE} = 7 \text{ V}$, $R_C = 600$, and $V_B = 2.7 \text{ V}$, $I_{R2} = 1.5 \text{ mA}$, $R_1 = 6.2 \text{ k}$

2. a) $I_E := 11.57 \text{ mA}$ $V_C := 8.51 \text{ V}$ $V_{CE} := 5.96 \text{ V}$ $V_B := 3.246 \text{ V}$ $I_{R2} := 1.475 \text{ mA}$ $R_2 := 2.2 \text{ k}\Omega$

b) Yes, $V_{CE} > 0.2 \text{ V}$ c) $I_B := 0.077 \text{ mA}$ d) OK to neglect e) lower f) 69 mW g) dissipate h) 3.73