

Common Collector

1. Find the following, do not neglect I_B .

Bias:

a) The Thevenin equivalent of the base bias circuit

$V_{BB} = ? \quad R_{BB} = ?$

b) $I_B = ? \quad I_C = ?$


Small signal characteristics

You may assume that the coupling capacitors are adequately sized, meaning that you can neglect them in your small signal calculations.

c) $r_e = ?$ don't neglect r_e in the following calculations

d) Input resistance, R_{in} , include R_L in this calculation

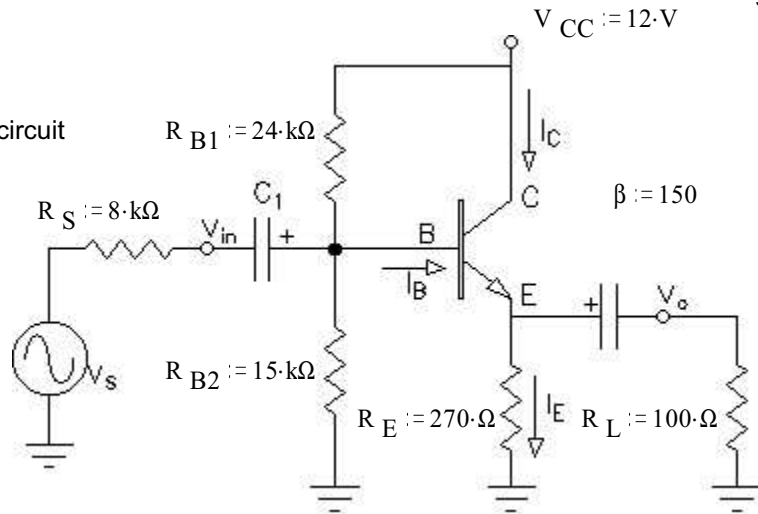e) Output resistance, R_o , include R_s in this calculation





Common Collector Bias (The circuits in the following problems were designed for good bias at $\beta = 150$)

2. at $\beta = 150$, $I_B = 69 \mu A$, $I_C = 10.3 \text{ mA}$, $V_C = 5.9 \text{ V}$,

a) Calculate I_B , I_C , and V_C for $\beta = 100$

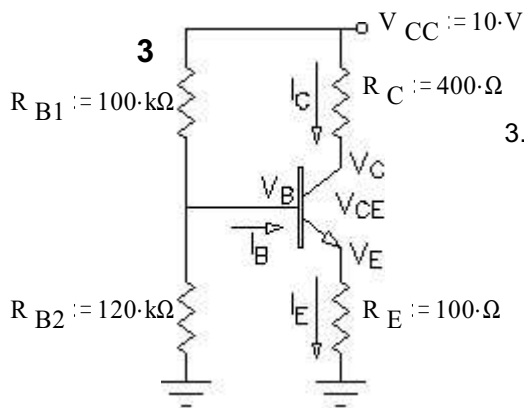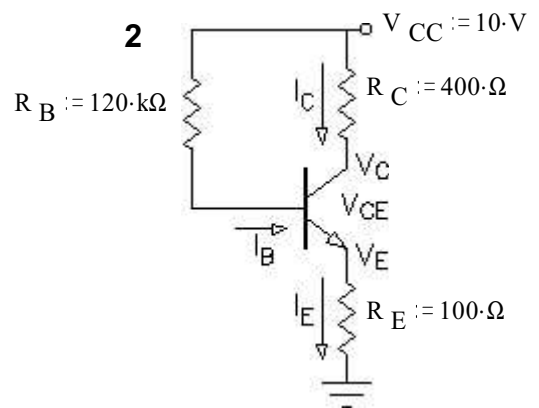b) Calculate I_B , I_C , and V_C for $\beta = 400$. Check V_{CE} to make sure the transistor is not in saturation. Recalculate I_B , I_C , and V_C if it is.



3. at $\beta = 150$, $I_B = 68.4 \mu A$, $I_C = 10.3 \text{ mA}$, $V_C = 5.9 \text{ V}$


a) Calculate I_B , I_C , and V_C for $\beta = 100$

b) Calculate I_B , I_C , and V_C for $\beta = 400$. Check V_{CE} to make sure the transistor is not in saturation. Recalculate I_B , I_C , and V_C if it is.

4. at $\beta = 150$, $I_B = 74 \mu A$, $I_C = 11 \text{ mA}$, $V_C = 5.6 \text{ V}$

a) Calculate I_B , I_C , and V_C for $\beta = 100$

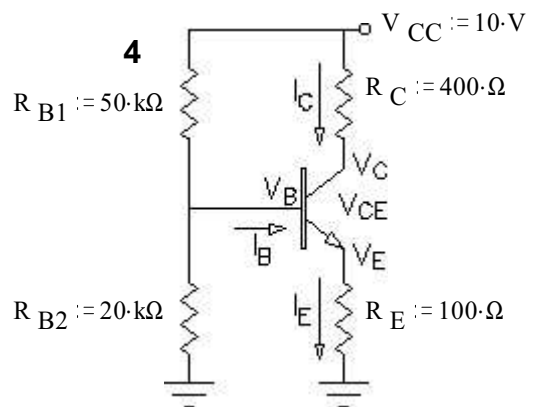b) Calculate I_B , I_C , and V_C for $\beta = 400$. Check V_{CE} to make sure the transistor is not in saturation. Recalculate I_B , I_C , and V_C if it is.



Answers

1.a) 4.62 V 9.23 kΩ b) 79 μA 11.8 mA c) 2.12 Ω d) 5.07 kΩ e) 27.6 Ω

2. a) at $\beta = 100$, $I_B = 71.5 \mu A$, $I_C = 7.15 \text{ mA}$, $V_C = 7.14 \text{ V}$

b) at $\beta = 400$, $I_B = 61.2 \mu A$, $I_C = 19.6 \text{ mA}$, $V_C = 2.16 \text{ V}$

3. a) at $\beta = 100$, $I_B = 73.7 \mu A$, $I_C = 7.37 \text{ mA}$, $V_C = 7.05 \text{ V}$

b) at $\beta = 400$, $I_B = 51.2 \mu A$, $I_C = 19.6 \text{ mA}$, $V_C = 2.16 \text{ V}$

4. a) at $\beta = 100$, $I_B = 89 \mu A$, $I_C = 8.9 \text{ mA}$, $V_C = 6.45 \text{ V}$

b) at $\beta = 400$, $I_B = 40 \mu A$, $I_C = 16 \text{ mA}$, $V_C = 3.6 \text{ V}$