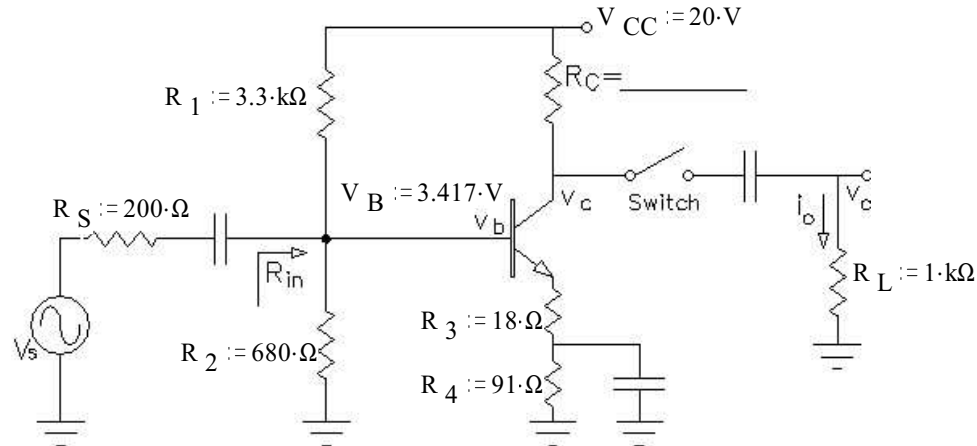


ECE 2100 homework # 18 Due: Fri, 3/28/03

A.Stolp
4/12/02
3/13/03

1. Consider the circuit below. You may neglect the base bias current (I_B) and the Early effect (r_o).



a) When the switch is open, the peak-to-peak output signal voltage at the collector is 4 Vpp. When the switch is closed this voltage drops to 2.88 Vpp. What is the output resistance of this amplifier?

no load collector signal: $v_{c,nl} := 4 \cdot V$

loaded collector signal: $v_{c,l} := 2.88 \cdot V$

b) What is the value of R_C ?

c) What is the peak-to-peak voltage at the base? $v_b = ?$

d) The input resistance (R_{in}) has been measured as 452Ω . What is the peak-to-peak voltage at the source?


e) The input resistance (R_{in}) has been measured as 452Ω . Find β . $R_1 := 452 \Omega$ $\beta = ?$

f) When the switch is closed, what is the maximum peak-to-peak output voltage you can get from this amplifier without clipping? $V_{oppmax} = ?$

ECE 2100 homework # 18 p.2

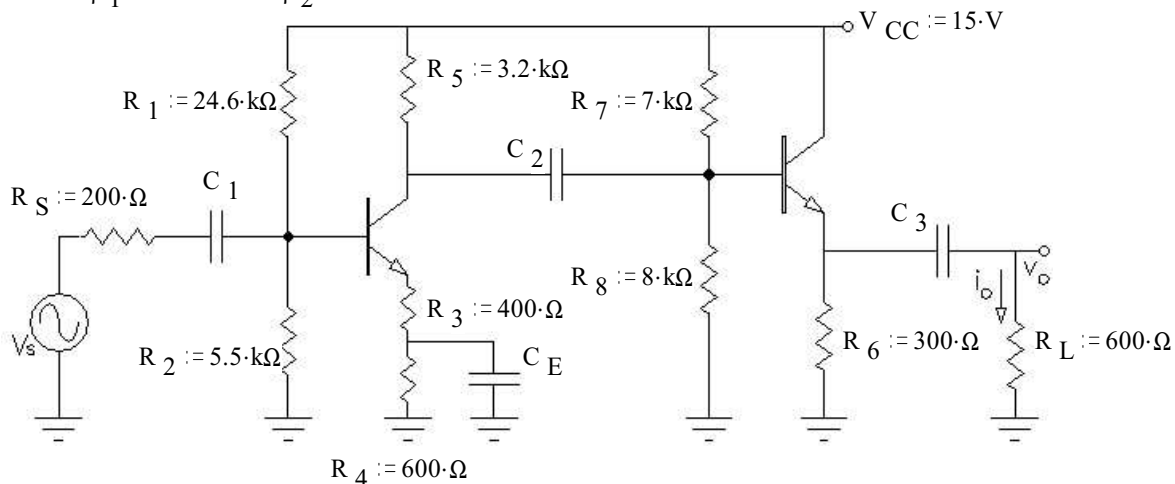2. Consider the circuit below. You may neglect the base bias currents (I_B) and the Early effects (r_c).

Assume that $\beta_1 := 112$ and $\beta_2 := 112$



a) What is the output resistance of the first stage? $R_{o1} = ?$

b) What is the output resistance of the second stage? $R_{o2} = ?$ You may neglect r_e for this stage

c) What is the approximate voltage gain of the second stage? $A_{v2} = ?$ You may neglect r_e for this stage

d) This amplifier should have a low corner frequency of 40 Hz. What is the minimum allowable value of C_3 ?

$f_{CL} := 40 \cdot \text{Hz}$ $C_3 = ?$ You may neglect r_e for the second stage

Answers

1a) $R_{o1} := 389 \cdot \Omega$ b) $R_{o2} := 389 \cdot \Omega$ c) $v_b := 195 \cdot \text{mV}$ d) $v_s := 282 \cdot \text{mV}$ e) $\beta := 120$ f) $V_{oppmax} := 13.3 \cdot \text{V}$

2a) $R_{o1} := 3.2 \cdot \text{k}\Omega$ b) $R_{o2} := 14.6 \cdot \Omega$ c) $A_{v2} = 1$ d) $C_3 := 6.47 \cdot \mu\text{F}$