

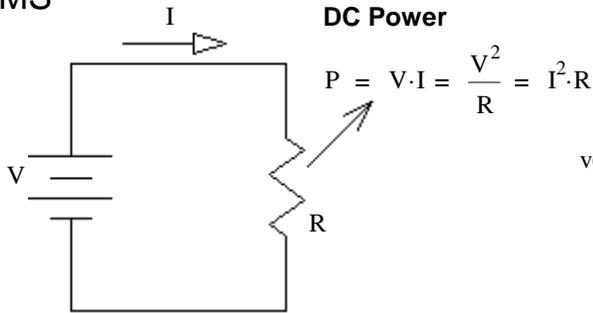
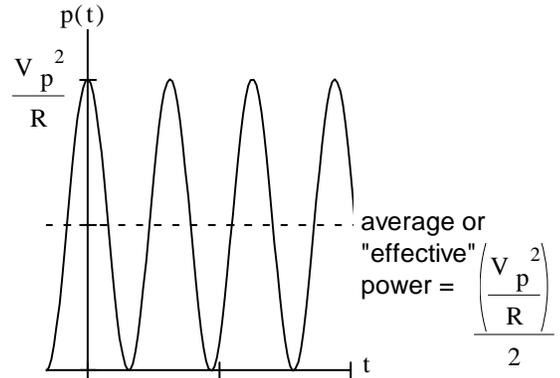


RMS

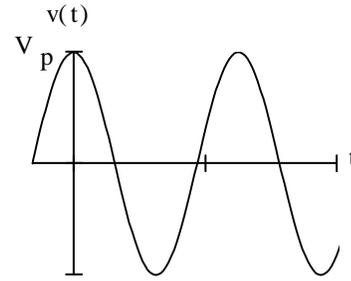
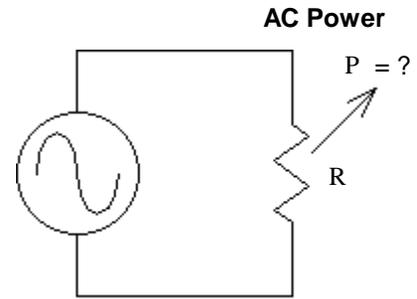
$$v(t) = V_p \cdot \cos(\omega \cdot t)$$




Couldn't we define an "effective" voltage that would allow us to use the same relationships for AC power as used for DC power?

$$P_{ave} = \frac{\left(\frac{V_p^2}{R}\right)}{2} = \frac{\left(\frac{V_p^2}{2}\right)}{R} = \frac{\left(\frac{V_p}{\sqrt{2}}\right)^2}{R}$$

$$V_{eff} = \sqrt{\left(\frac{V_p}{\sqrt{2}}\right)^2} = \frac{V_p}{\sqrt{2}} = V_{rms} = \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt}$$

Root Mean (average) Square

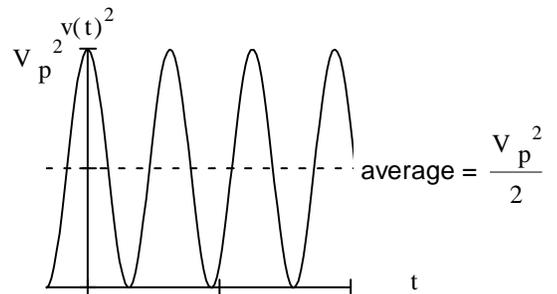

RMS Root of the **M**ean of the **S**quare
Use RMS in power calculations

Sinusoids


$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt} = \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega \cdot t))^2 dt} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \cdot \left(\frac{1}{2} + \frac{1}{2} \cos(2 \cdot \omega \cdot t)\right) dt} \\ &= \frac{V_p}{\sqrt{2}} \cdot \sqrt{\frac{1}{T} \int_0^T (1) dt + \frac{1}{T} \int_0^T \cos(2 \cdot \omega \cdot t) dt} = \frac{V_p}{\sqrt{2}} \cdot \sqrt{1 + 0} \end{aligned}$$

Common household power

$$f = 60\text{-Hz}$$

$$\omega = 377 \frac{\text{rad}}{\text{sec}}$$

$$T = 16.67\text{-ms}$$




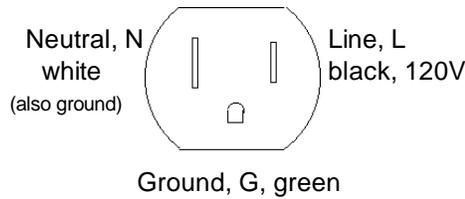


ECE 2210 AC Power p2


$$V_{\text{rms}} := 120\text{-V}$$

$$V_p = V_{\text{rms}} \cdot \sqrt{2} = 170\text{-V}$$

What about other wave shapes??

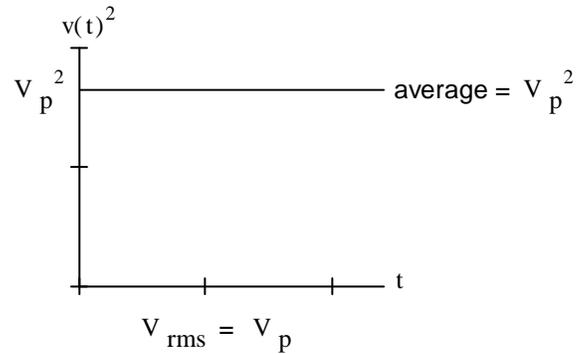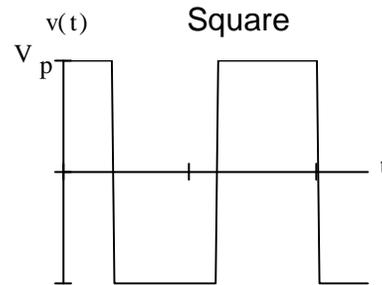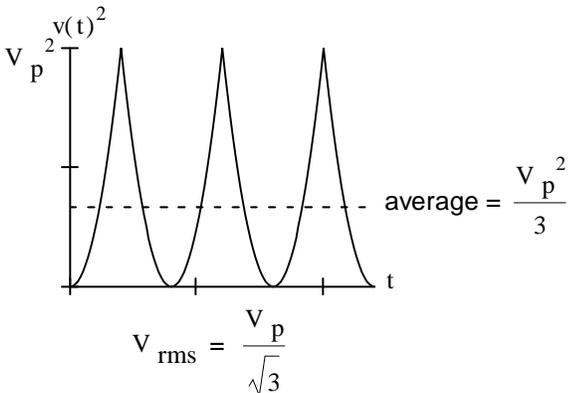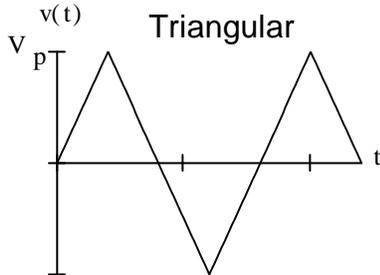

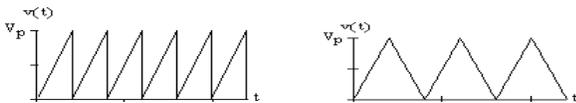Works for all types of triangular and sawtooth waveforms



Same for DC

How about AC + DC ?

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt}$$


$$= \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega t) + V_{\text{DC}})^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T [(V_p \cdot \cos(\omega t))^2 + 2 \cdot (V_p \cdot \cos(\omega t)) \cdot V_{\text{DC}} + V_{\text{DC}}^2] dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega t))^2 dt + \frac{1}{T} \int_0^T 2 \cdot (V_p \cdot \cos(\omega t)) \cdot V_{\text{DC}} dt + \frac{1}{T} \int_0^T V_{\text{DC}}^2 dt}$$

--- zero over one period ---
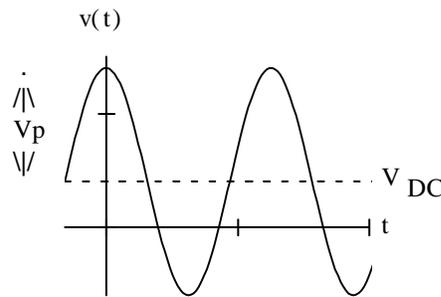
$$= \sqrt{V_{\text{rmsAC}}^2 + 0 + V_{\text{DC}}^2} = \sqrt{V_{\text{rmsAC}}^2 + V_{\text{DC}}^2}$$



ECE 2210 AC Power p3


 sinusoid: $V_{rms} = \frac{V_p}{\sqrt{2}}$ $I_{rms} = \frac{I_p}{\sqrt{2}}$


 triangular: $V_{rms} = \frac{V_p}{\sqrt{3}}$ $I_{rms} = \frac{I_p}{\sqrt{3}}$


 square: $V_{rms} = V_p$ $I_{rms} = I_p$


 waveform + DC $V_{rms} = \sqrt{V_{rmsAC}^2 + V_{DC}^2}$

rectified average $V_{ra} = \frac{1}{T} \int_0^T |v(t)| dt$


 $V_{ra} = \frac{2}{\pi} \cdot V_p$ $I_{ra} = \frac{2}{\pi} \cdot I_p$


 $V_{ra} = \frac{1}{2} \cdot V_p$ $I_{ra} = \frac{1}{2} \cdot I_p$


 $V_{ra} = V_{rms} = V_p$ $I_{ra} = I_{rms} = I_p$

Most AC meters don't measure true RMS. Instead, they measure V_{ra} , display $1.11V_{ra}$, and call it RMS. That works for sine waves but not for any other waveform.


Use RMS in power calculations

Some waveforms don't fall into these forms, then you have to perform the math from scratch

For waveform shown

The average DC (V_{DC}) value
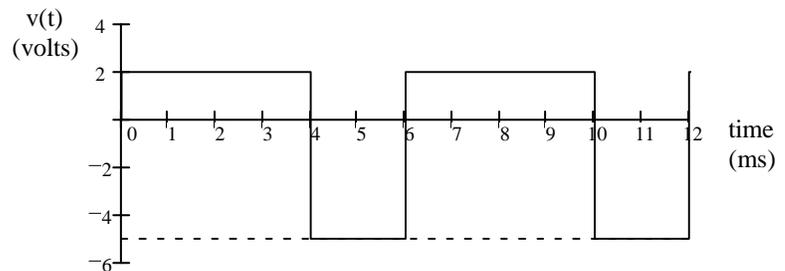
$$\frac{2 \cdot V \cdot (4 \cdot \text{ms}) + (-5 \cdot V) \cdot (2 \cdot \text{ms})}{6 \cdot \text{ms}} = -0.333 \cdot V$$




The RMS (effective) value

Graphical way

$$\frac{4 \cdot V^2 \cdot (4 \cdot \text{ms}) + 25 \cdot V^2 \cdot (2 \cdot \text{ms})}{6 \cdot \text{ms}} = 11 \cdot V^2$$
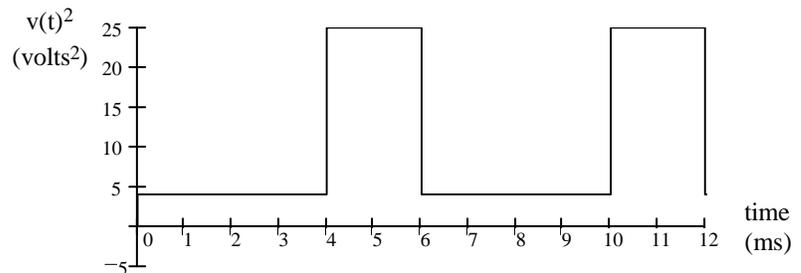
$$V_{RMS} := \sqrt{11 \cdot V^2} \quad V_{RMS} = 3.32 \cdot V$$



OR...

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt}$$


$$= \sqrt{\frac{1}{6 \cdot \text{ms}} \left[\int_{0 \cdot \text{ms}}^{4 \cdot \text{ms}} (2 \cdot V)^2 dt + \int_{4 \cdot \text{ms}}^{6 \cdot \text{ms}} (-5 \cdot V)^2 dt \right]} = \sqrt{\frac{1}{6 \cdot \text{ms}} \cdot [4 \cdot \text{ms} \cdot (2 \cdot V)^2 + 2 \cdot \text{ms} \cdot (-5 \cdot V)^2]} = 3.32 \cdot V$$

The voltage is hooked to a resistor, as shown, for 6 seconds.

The energy is transferred to the resistor during that 6 seconds:

$$P_L := \frac{V_{RMS}^2}{R_L} \quad P_L = 0.22 \cdot W$$






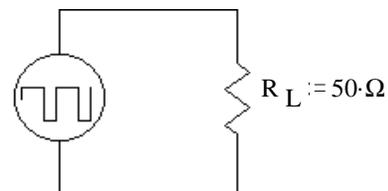
$$W_L := P_L \cdot 6 \cdot \text{sec} \quad W_L = 1.32 \cdot \text{joule} \quad \text{All converted to heat}$$



Use RMS in power calculations

$$P = I_{Rms}^2 \cdot R = \frac{V_{Rms}^2}{R} \quad \text{for Resistors ONLY !!}$$

Capacitors and Inductors

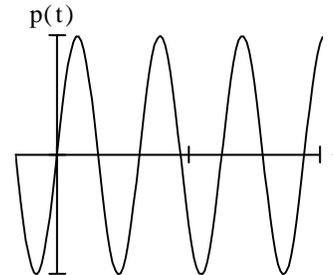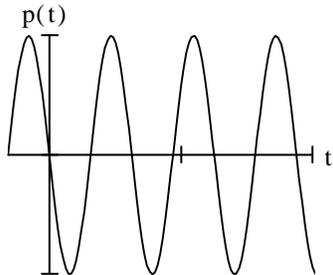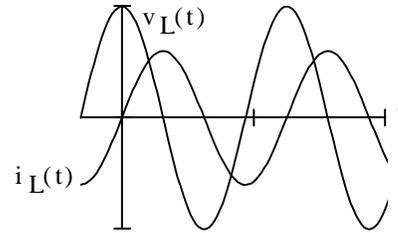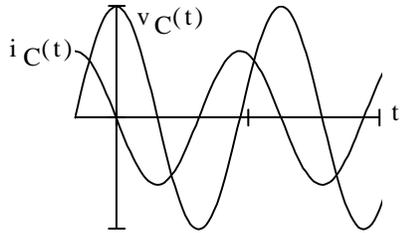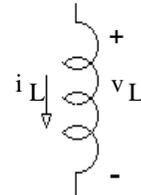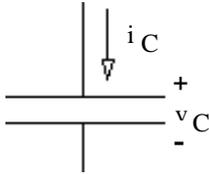

Average power is ZERO $P = 0$

Average power is ZERO $P = 0$

Capacitors and Inductors DO NOT dissipate (real) average power.


Reactive power is negative

$$Q_C = -I_{Crms} \cdot V_{Crms} \\ = -I_{Crms}^2 \cdot \frac{1}{\omega \cdot C} = -V_{Crms}^2 \cdot \omega \cdot C$$


Reactive power is positive

$$Q_L = I_{Lrms} \cdot V_{Lrms} \\ = I_{Lrms}^2 \cdot \omega \cdot L = \frac{V_{Lrms}^2}{\omega \cdot L}$$

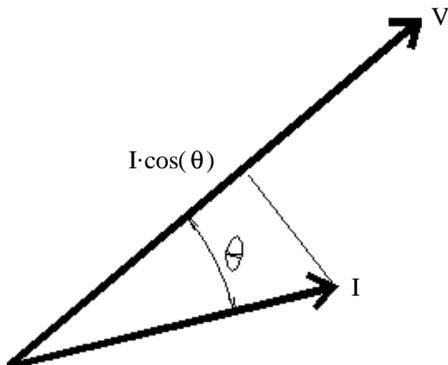If current and voltage are not in phase, only the in-phase part of the current matters for the power-- DOT PRODUCT



"Lagging" power
Inductor dominates

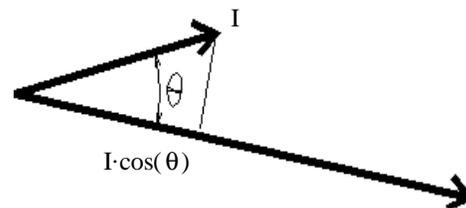

"Leading" Power
Capacitor dominates

All voltages and currents shown are RMS

Real Power

$$P = V \cdot I \cdot \cos(\theta) = I^2 \cdot |Z| \cdot \cos(\theta) = \frac{V^2}{|Z|} \cdot \cos(\theta)$$


BOLD is a complex number

$$P = \text{"Real" Power (average)} = V \cdot I \cdot \text{pf} = I^2 \cdot |Z| \cdot \text{pf} = \frac{V^2}{|Z|} \cdot \text{pf}$$

units: watts, kW, MW, etc.

pf = cos(θ) = power factor

otherwise....

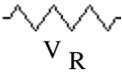I_R  V_R for resistors only part that uses real average power
 $P = I_R^2 \cdot R = \frac{V_R^2}{R}$

Reactive Power

$$Q = \text{Reactive "power"} = V \cdot I \cdot \sin(\theta)$$

units: VAR, kVAR, etc. "volt-amp-reactive"

otherwise....

I_C  V_C capacitors -> - Q $Q_C = I_C^2 \cdot X_C = \frac{V_C^2}{X_C}$ $X_C = -\frac{1}{\omega \cdot C}$ and is a negative number

I_L  V_L inductors -> + Q $Q_L = I_L^2 \cdot X_L = \frac{V_L^2}{X_L}$ $X_L = \omega \cdot L$ and is a positive number

Complex and Apparent Power

$$S = \text{Complex "power"} = P + jQ = VI / \theta = \mathbf{V \cdot I} = I^2 \cdot \mathbf{Z}$$

complex conjugate

units: VA, kVA, etc. "volt-amp"

NOT $V \cdot I$ **NOR** $\frac{V^2}{Z}$

$$S = \text{Apparent "power"} = |S| = \sqrt{P^2 + Q^2} = V \cdot I$$

units: VA, kVA, etc. "volt-amp"

Power factor

$$\text{pf} = \cos(\theta) = \text{power factor (sometimes expressed in \%)} \quad 0 \leq \text{pf} \leq 1$$

θ is the **phase angle** between the voltage and the current or the phase angle of the impedance. $\theta = \theta_Z$



θ < 0 Load is "Capacitive", power factor is "leading". This condition is very rare

θ > 0 Load is "Inductive", power factor is "lagging". This condition is so common you can assume any power factor given is lagging unless specified otherwise. Transformers and motors make most loads inductive.

Industrial users are charged for the reactive power that they use, so power factor < 1 is a bad thing.

Power factor < 1 is also bad for the power company. To deliver the same power to the load, they have more line current (and thus more line losses).

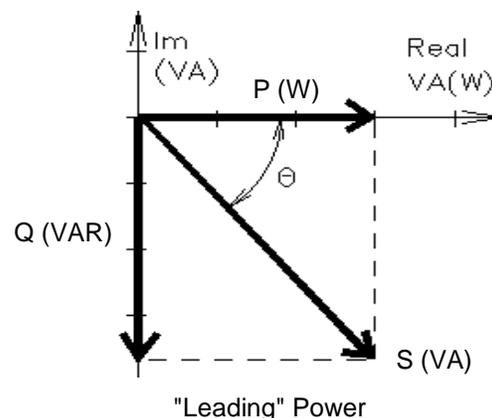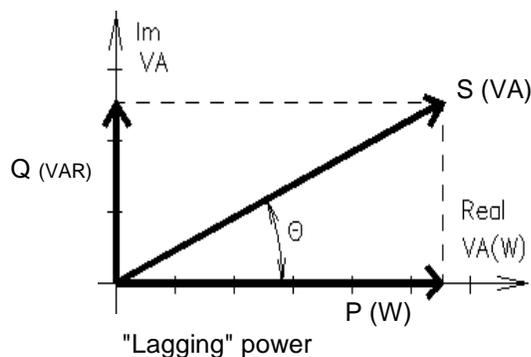Power factors are "corrected" by adding capacitors (or capacitive loads) in parallel with the inductive loads which cause the problems. (In the rare case that the load is capacitive, the pf would be corrected by an inductor.)



A Transformer is two coils of wire that are magnetically coupled.

Transformers are only useful for AC, which is one of the big reasons electrical power is generated and distributed as AC.

Transformer turns and turns ratios are rarely given, V_p/V_s is much more common where V_p/V_s is the rated primary over rated secondary voltages. You may take this to be the same as N_1/N_2 although in reality N_2 is usually a little bit bigger to make up for losses. Also common: $V_p : V_s$.



Both RMS

Transformers are rated in VA Transformer Rating (VA) = (rated V) x (rated I) , on either side.

Don't allow voltages over the rated V , regardless of the actual current.

Don't allow currents over the rated I , regardless of the actual voltage.

Ideal Transformers

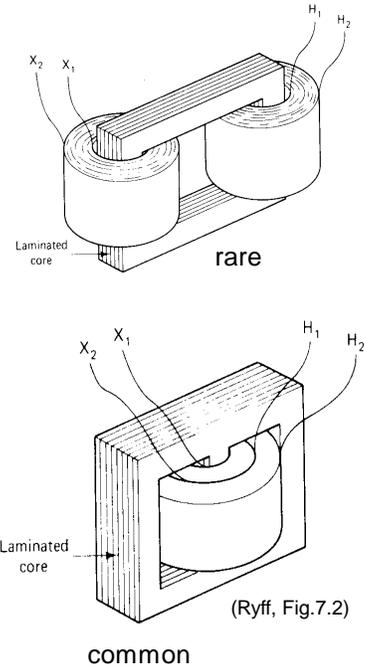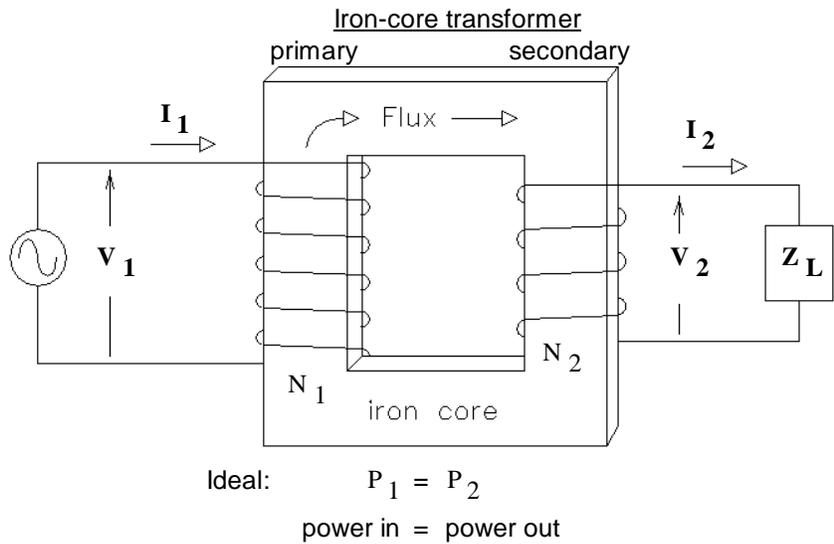

Transformation of voltage and current


$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

Turns ratio

Turns ratio as defined in most books: $N = \frac{N_1}{N_2}$

Note: some other texts define the turns ratio as: $\frac{N_2}{N_1}$ Be careful how you and others use this term.

Transformation of impedance

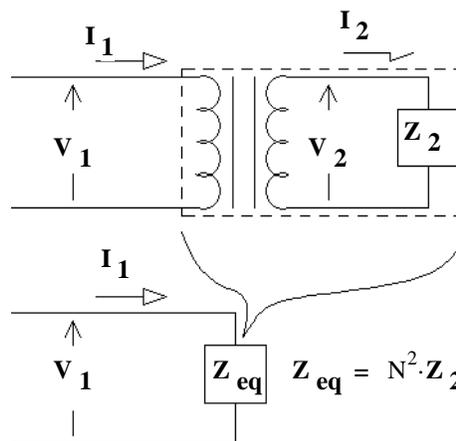

You can replace the entire transformer and load with (Z_{eq}). This "impedance transformation" can be very handy.

Transformers can be used for "impedance matching"

$$Z_{eq} = N^2 \cdot Z_2 = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$$

This also works the opposite way, to move an impedance from the primary to the secondary, multiply by: $\left(\frac{N_2}{N_1}\right)^2$

Other Transformers


- Multi-tap transformers: Many transformers have more than two connections to primary and/or the secondary. The extra connections are called "taps" and may allow you to select from several different voltages or get more than one voltage at the same time.
- Isolation Transformers: Almost all transformers isolate the primary from the secondary. An Isolation transformer has a 1:1 turns ratio and is just for isolation.
- Auto Transformers: Auto transformers have only one winding with taps for various voltages. The primary and secondary are simply parts of the same winding. These parts may overlap. Any regular transformer can be wired as an auto transformer. Auto transformers DO NOT provide isolation.
- Vari-AC: A special form of auto transformer with an adjustable tap for an adjustable output voltage.
- LVDT: A Linear-Variable-Differential-Transformers has moveable core which couples the primary winding to the secondary winding(s) in such a way the the secondary voltage is proportional to the position of the core. LVDTs are used as position sensors.

Home power

Standard 120 V outlet connections are shown at right.

The 3 lines coming into your house are **NOT** 3-phase. They are +120 V, Gnd, -120 V

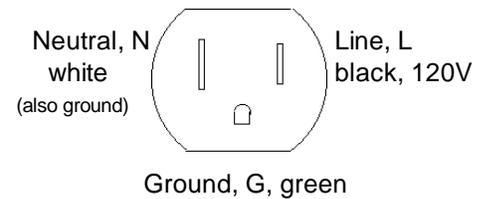(The two 120s are 180° out-of-phase, allowing for 240 V connections)




3-Phase Power (FYI ONLY)

Single phase power pulses at 120 Hz. This is not good for motors or generators over 5 hp.


Three phase power is constant as long as the three loads are balanced.

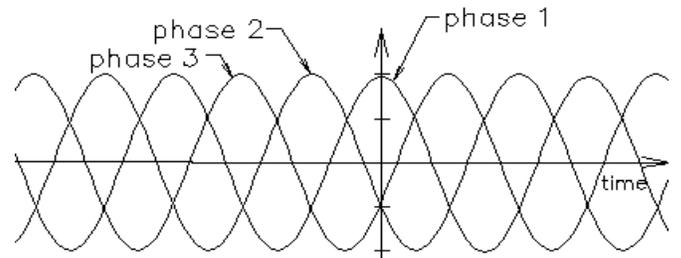Three lines are needed to transmit 3-phase power. If loads are balanced, ground return current will be zero.



Wye connection:

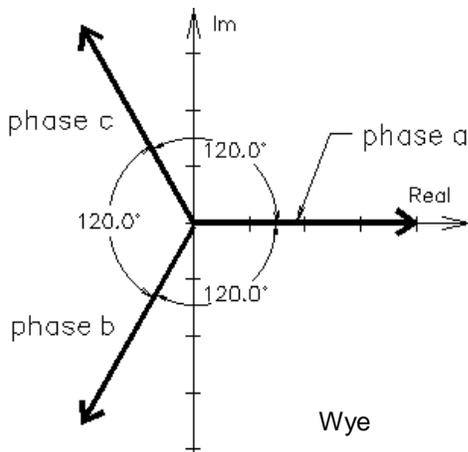Connect each load or generator phase between a line and ground.




$$V_{LN} = \frac{V_{LL}}{\sqrt{3}}$$

$$I_L = \sqrt{3} \cdot I_{LL}$$

Delta connection:

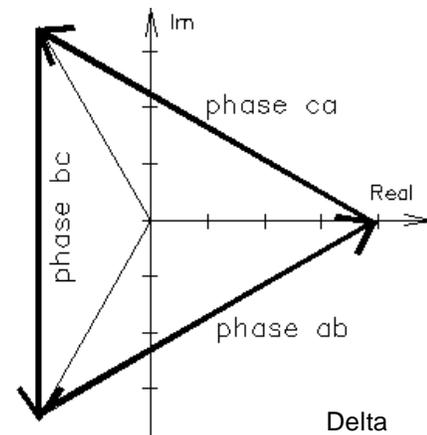Connect each load or generator phase between two lines.





$$V_{LL} = \sqrt{3} \cdot V_{LN}$$

$$I_{LL} = \frac{I_L}{\sqrt{3}}$$

3-Phase Power (FYI ONLY)


Common 3-phase voltages:

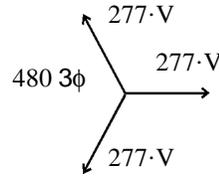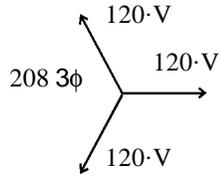

Apparent Power: $|S_{3\phi}| = 3 \cdot V_{LN} \cdot I_L = 3 \cdot V_{LL} \cdot I_{LL} = \sqrt{3} \cdot V_{LL} \cdot I_L$



Power: $P_{3\phi} = 3 \cdot V_{LN} \cdot I_L \cdot \text{pf} = 3 \cdot V_{LL} \cdot I_{LL} \cdot \text{pf} = \sqrt{3} \cdot V_{LL} \cdot I_L \cdot \text{pf} = S_{3\phi} \cdot \text{pf} \quad \text{pf} = \cos(\theta)$

Reactive power: $Q_{3\phi} = 3 \cdot V_{LN} \cdot I_L \cdot \sin(\theta) \text{ etc...} = \sqrt{(|S_{3\phi}|)^2 - P_{3\phi}^2}$

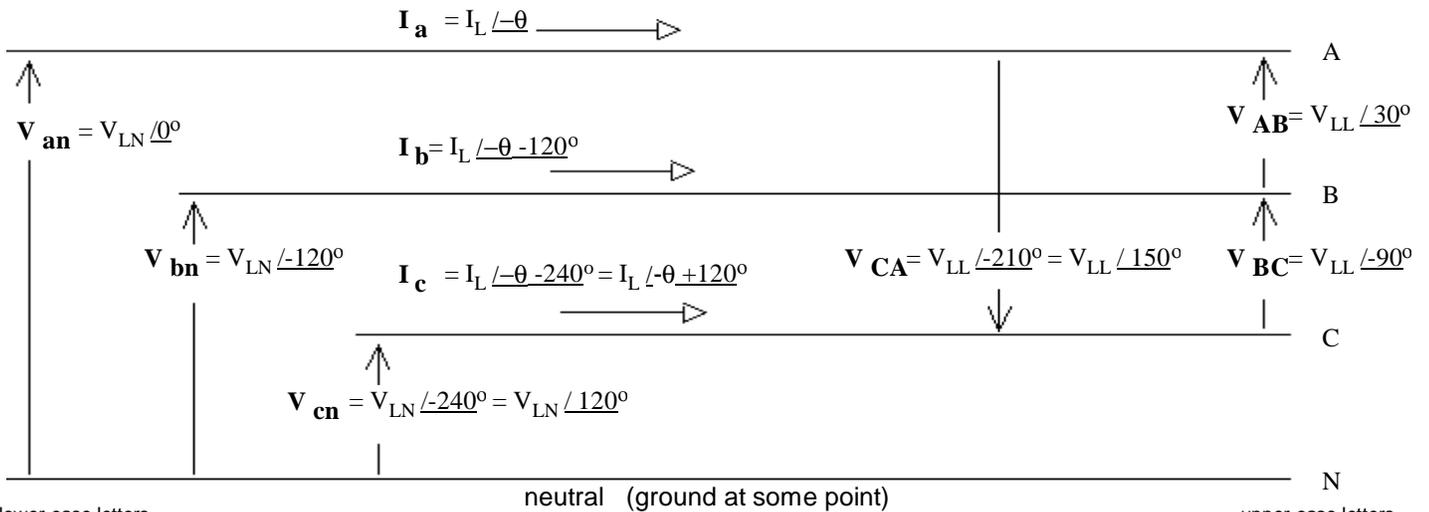

lower-case letters at source end

upper-case letters at load end

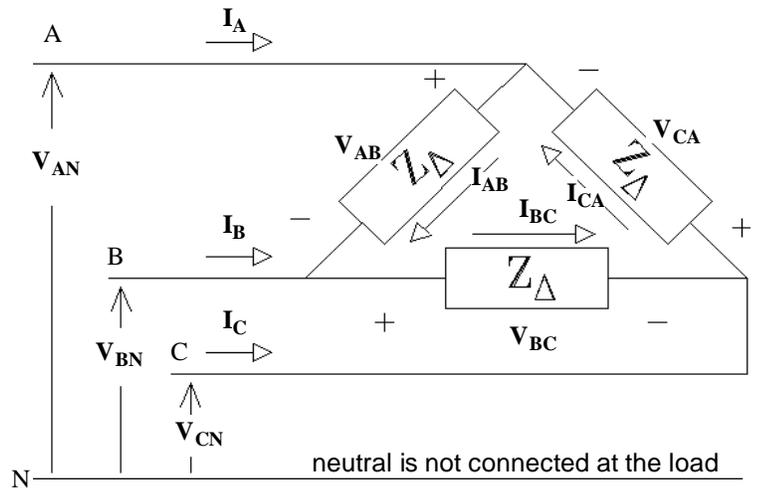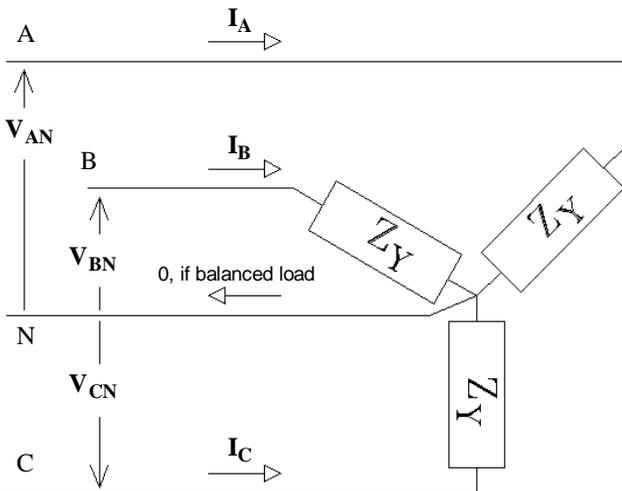

$|V_{AN}| = |V_{BN}| = |V_{CN}| = V_{LN} = \frac{V_{LL}}{\sqrt{3}}$

$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_{LL} = \sqrt{3} \cdot V_{LN}$

$|I_A| = |I_B| = |I_C| = I_L = \sqrt{3} \cdot I_{LL}$


$|I_{AB}| = |I_{BC}| = |I_{CA}| = I_{LL} = \frac{I_L}{\sqrt{3}}$

To get equivalent line currents with equivalent voltages

$Z_Y = \frac{Z_{\Delta}}{3}$

$Z_{\Delta} = 3 \cdot Z_Y$

Ex. 1 R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.

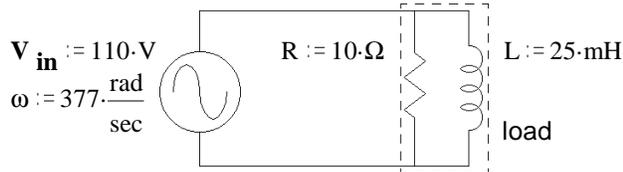

$$Z := \frac{1}{\left(\frac{1}{R} + \frac{1}{j\omega L}\right)} = \frac{1}{0.1458 \cdot \frac{1}{\Omega} \cdot e^{-j \cdot 46.7 \cdot \text{deg}}}$$

$$Z = 4.704 + 4.991j \cdot \Omega \quad |Z| = 6.859 \cdot \Omega \quad \theta := \arg(Z) \quad \theta = 46.7 \cdot \text{deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.686$$

$$I := \frac{V_{in}}{Z} \quad I = 11 - 11.671j \cdot A \quad |I| = 16.038 \cdot A \quad \arg(I) = -46.7 \cdot \text{deg}$$

$$P := |V_{in}| \cdot |I| \cdot \text{pf} \quad P = 1.21 \cdot \text{kW}$$

$$Q := |V_{in}| \cdot |I| \cdot \sin(\theta) \quad Q = 1.284 \cdot \text{kVAR} \quad \text{OR...} \quad Q := |V_{in}| \cdot |I| \cdot \sqrt{1 - \text{pf}^2} \quad Q = 1.284 \cdot \text{kVAR}$$

$$S := V_{in} \cdot \bar{I} \quad \text{OR..} \quad S := P + j \cdot Q \quad S = 1.21 + 1.284j \cdot \text{kVA} = 1.764 \text{kVA} / 46.7^\circ \quad \text{atan}\left(\frac{\text{Im}(S)}{\text{Re}(S)}\right) = 46.696 \cdot \text{deg} \quad \text{same angle as } Z$$

$$S := \sqrt{P^2 + Q^2} = |S| = 1.764 \cdot \text{kVA} = |V_{in}| \cdot |I| = 1.764 \cdot \text{kVA}$$

OR, since we know that the voltage across each element of the load is $V_{in} \dots$
Real power is dissipated only by resistors

$$P := \frac{(|V_{in}|)^2}{R} \quad P = 1.21 \cdot \text{kW} \quad Q := \frac{(|V_{in}|)^2}{\omega L} \quad Q = 1.284 \cdot \text{kVAR}$$


$$S := P + j \cdot Q$$

$$S = |S| = \sqrt{P^2 + Q^2} = 1.764 \cdot \text{kVA} \quad \text{pf} = \frac{P}{|S|} = 0.686$$

What value of C in parallel with R & L would make $\text{pf} = 1$ ($Q = 0$) ?


$$Q_C := -Q = \frac{(110 \cdot V)^2}{X_C} \quad X_C := \frac{(110 \cdot V)^2}{-Q} \quad X_C = -9.425 \cdot \Omega$$

$$\frac{1}{|X_C| \cdot \omega} = 281 \cdot \mu\text{F} \quad \text{OR..} \quad Q_C := -Q = (110 \cdot V)^2 \cdot \omega \cdot C \quad C = \frac{-Q}{(110 \cdot V)^2 \cdot \omega} = -281.434 \cdot \mu\text{F}$$

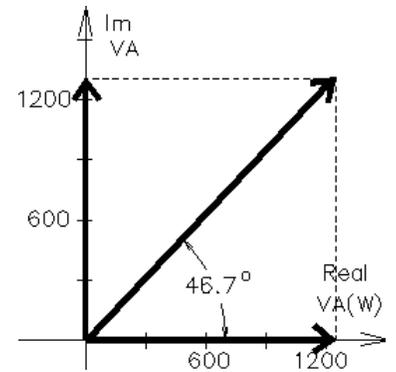

Ex. 2 R & L together are the load. Find the real power P, the reactive power Q, the complex power S, the apparent power |S|, & the power factor pf. Draw phasor diagram for the power.

Series R & L

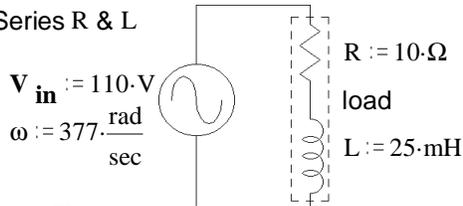

$$Z := R + j \cdot \omega L \quad Z = 10 + 9.425j \cdot \Omega \quad |Z| = 13.742 \cdot \Omega \quad \theta := \arg(Z) \quad \theta = 43.304 \cdot \text{deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.728$$

$$I := \frac{V_{in}}{Z} \quad I = 5.825 - 5.49j \cdot A$$


$$|I| = 8.005 \cdot A \quad \arg(I) = -43.304 \cdot \text{deg}$$

$$P := |V_{in}| \cdot |I| \cdot \text{pf} \quad P = 0.641 \cdot \text{kW}$$

$$Q := |V_{in}| \cdot |I| \cdot \sin(\theta) \quad Q = 0.604 \cdot \text{kVAR}$$

$$S := V_{in} \cdot \bar{I} \quad S = 0.641 + 0.604j \cdot \text{kVA}$$

$$|S| = 0.881 \cdot \text{kVA} \quad \arg(S) = 43.304 \cdot \text{deg} \quad S = 881 \text{VA} / 43.3^\circ$$

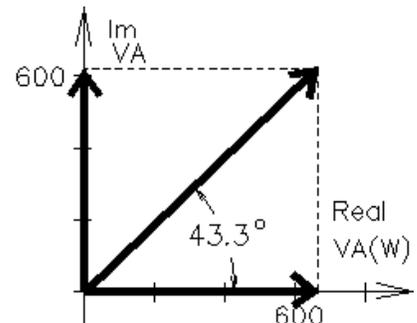

ECE 2210 AC Power Examples, p.2

OR, if we first find the magnitude of the current which flows through each element of the load...

$$|\mathbf{I}| = \frac{V_{in}}{\sqrt{R^2 + (\omega \cdot L)^2}} = 8.005 \cdot A$$

$$P := (|\mathbf{I}|)^2 \cdot R \quad P = 0.641 \cdot kW \quad Q := (|\mathbf{I}|)^2 \cdot (\omega \cdot L) \quad Q = 0.604 \cdot kVAR$$

$$\mathbf{S} := P + j \cdot Q \quad |\mathbf{S}| = \sqrt{P^2 + Q^2} = 0.881 \cdot kVA \quad pf = \frac{P}{|\mathbf{S}|} = 0.728$$

What value of C in parallel with R & L would make $pf = 1$ ($Q = 0$) ?


$$Q = 603.9 \cdot VAR \quad \text{so we need: } Q_C := -Q \quad Q_C = -603.9 \cdot VAR = \frac{V_{in}^2}{X_C}$$

$$X_C := \frac{V_{in}^2}{Q_C} \quad X_C = -20.035 \cdot \Omega = \frac{-1}{\omega \cdot C} \quad C := \frac{1}{|X_C| \cdot \omega} \quad C = 132 \cdot \mu F$$

$$\text{Check: } \frac{1}{\frac{1}{R + j \cdot \omega \cdot L} + j \cdot \omega \cdot C} = 18.883 \cdot \Omega \quad \text{No } j \text{ term, so } \theta = 0^\circ$$

Ex. 3 R, & C together are the load in the circuit shown.

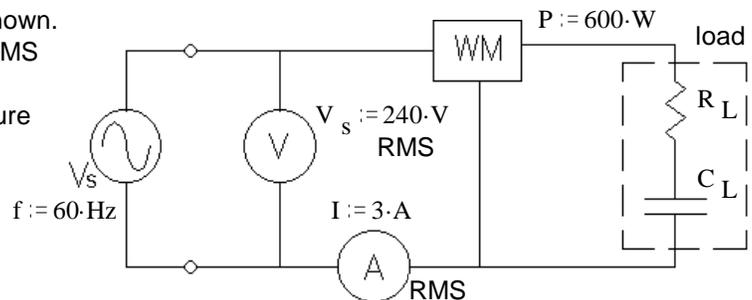The RMS voltmeter measures 240 V, the RMS ammeter measures 3 A, and the wattmeter measures 600 W. Find the following: Be sure to show the correct units for each value.



a) The value of the load resistor. $R_L = ?$

$$P = I^2 \cdot R_L$$

$$R_L := \frac{P}{I^2} \quad R_L = 66.7 \cdot \Omega$$

b) The apparent power. $|\mathbf{S}| = ?$ $\mathbf{S} := V_s \cdot I$ $S = 720 \cdot VA$

c) The reactive power. $Q = ?$ $Q := -\sqrt{S^2 - P^2}$ $Q = -398 \cdot VAR$

d) The complex power. $\mathbf{S} = ?$ $\mathbf{S} := P + j \cdot Q$ $\mathbf{S} = 600 - 398j \cdot VA$

e) The power factor. $pf = ?$ $pf := \frac{P}{V_s \cdot I}$ $pf = 0.833$

f) The power factor is leading or lagging? leading (load is capacitive, Q is negative)

g) The two components of the load are in a box which cannot be opened. Add (draw it) another component to the circuit above which can correct the power factor (make $pf = 1$). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.


Add an inductor in parallel with load

$$f = 60 \cdot Hz \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 376.991 \cdot \frac{rad}{sec}$$

$$Q = -398 \cdot VAR \quad \text{so we need: } Q_L := -Q \quad Q_L = 398 \cdot VAR = \frac{V_s^2}{X_L}$$

$$X_L := \frac{V_s^2}{Q_L} \quad X_L = 144.725 \cdot \Omega = \omega \cdot L \quad L := \frac{|X_L|}{\omega} \quad L = 384 \cdot mH$$

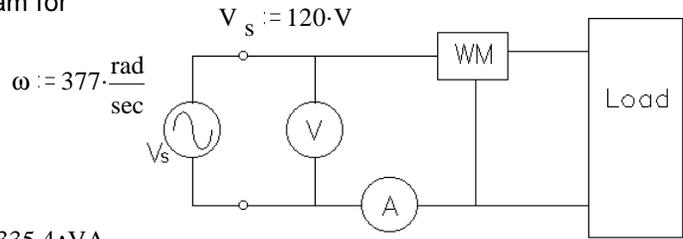Ex. 4 For the 60 Hz load shown in the figure, the RMS voltmeter measures 120 V. The phasor diagram for the power is also shown. Find the following:



a) The complex power. $S = ?$

$$P := 300 \cdot \text{W} \quad Q := -150 \cdot \text{VA}$$

$$S := P + j \cdot Q \quad S = 300 - 150j \cdot \text{VA}$$

b) The apparent power. $|S| = ? \quad |S| = \sqrt{P^2 + Q^2} = 335.4 \cdot \text{VA}$


c) The power factor. $\text{pf} = ? \quad \text{pf} := \frac{P}{|S|} \quad \text{pf} = 0.894$

d) The item marked "WM" in the figure is a wattmeter, what does it read? (give a number) $P = 300 \cdot \text{W}$

e) The item marked "A" in the figure is an RMS ammeter, what does it read? (give a number)

$$I := \frac{|S|}{V} \quad I = 2.795 \cdot \text{A} \quad I = 2.8 \cdot \text{A}$$

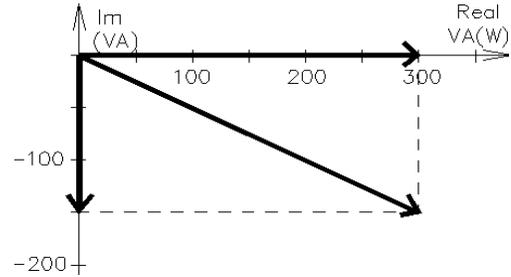f) The power factor is leading or lagging? leading (Q is negative)



g) The 3 components of the load are in a box which cannot be opened. Add another component to the circuit above which can correct the power factor (make $\text{pf} = 1$). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

Add an inductor in parallel with load

$$Q = -150 \cdot \text{VAR} \quad \text{need: } Q_L := -Q \quad Q_L = 150 \cdot \text{VAR} = \frac{V_s^2}{\omega \cdot L} \quad L := \frac{V_s^2}{\omega \cdot Q_L} \quad L = 255 \cdot \text{mH}$$


Ex. 5 R, L, & C together are the load in the circuit shown

The RMS voltmeter measures 120 V. $V_s := 120 \cdot \text{V}$

The wattmeter measures 270 W. $P := 270 \cdot \text{W}$

The RMS ammeter measures 3.75 A. $I := 3.75 \cdot \text{A}$

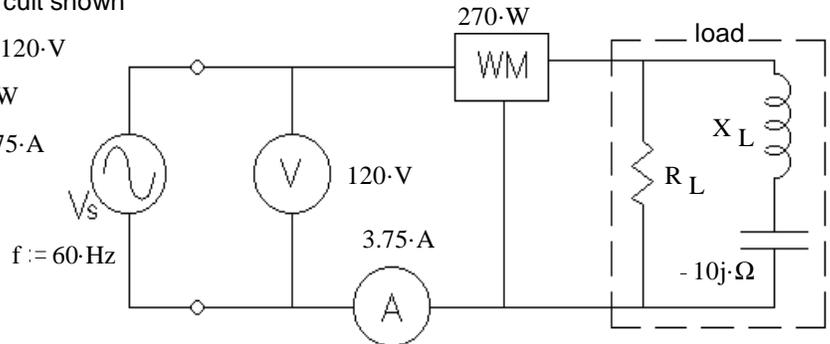Find the following: Be sure to show the correct units for each value.



a) The value of the load resistor. $R_L = ?$

$$P = \frac{V_s^2}{R_L} \quad R_L := \frac{V_s^2}{P} \quad R_L = 53.3 \cdot \Omega$$

b) The magnitude of the impedance of the load inductor (reactance). $|Z_L| = X_L = ?$

$$I_R := \frac{V_s}{R_L} \quad I_R = 2.25 \cdot \text{A} \quad I_L := \sqrt{I^2 - I_R^2} \quad I_L = 3 \cdot \text{A} \quad X := \frac{V_s}{I_L} \quad X = 40 \cdot \Omega$$

$$\text{OR: } S := V_s \cdot I \quad S = 450 \cdot \text{VA} \quad Q := \sqrt{S^2 - P^2} \quad Q = 360 \cdot \text{VAR} = \frac{V_s^2}{X} \quad X = \frac{V_s^2}{Q} = 40 \cdot \Omega$$

$$\text{either way: } X_C := -10 \cdot \Omega \quad X_L := X - X_C \quad X_L = 50 \cdot \Omega$$

c) The reactive power. $Q = ? \quad Q := \sqrt{(V_s \cdot I)^2 - P^2} \quad Q = 360 \cdot \text{VAR} \quad \text{positive, because the load is primarily inductive}$

d) The power factor is leading or lagging? lagging (load is inductive, Q is positive)

ECE 2210 AC Power Examples, p.4

- e) The 3 components of the load are in a box which cannot be opened. Add another component to the circuit above which can correct the power factor (make $pf = 1$). Show the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

Add a capacitor in parallel with load

$$f = 60 \cdot \text{Hz} \quad \omega := 377 \cdot \frac{\text{rad}}{\text{sec}}$$

$$Q = 360 \cdot \text{VAR} \quad \text{so we need: } Q_C := -Q \quad Q_C = -360 \cdot \text{VAR} = -\frac{V_s^2}{\omega \cdot C} = -\omega \cdot C \cdot V_s^2$$

$$C := \frac{Q_C}{-\omega \cdot V_s^2} \quad C = 66.3 \cdot \mu\text{F}$$

Ex. 6 A step-down transformer has an output voltage of 220 V (rms) when the primary is connected across a 560 V (rms) source.

- a) If there are 280 turns on the primary winding, how many turns are required on the secondary? $280 \cdot \frac{220 \cdot \text{volt}}{560 \cdot \text{volt}} = 110 \text{ turns}$
- b) If the current in the primary is 2.4 A, what current flows in the load connected to the secondary? $2.4 \cdot \text{amp} \cdot \frac{280}{110} = 6.11 \cdot \text{A}$
- c) If the transformer is rated at 700/275 V, 2.1 kVA, what are the rated primary and secondary currents? $\text{pri: } \frac{2.1 \cdot \text{kVA}}{700 \cdot \text{V}} = 3 \cdot \text{A} \quad \text{sec: } \frac{2.1 \cdot \text{kVA}}{275 \cdot \text{V}} = 7.636 \cdot \text{A}$

Ex. 7 The transformer shown in the circuit below is ideal. Find the following:

a) $|I_1| = ?$

$$V_s := 120 \cdot \text{V} \quad \omega := 377 \cdot \frac{\text{rad}}{\text{sec}}$$

$$R_1 := 20 \cdot \Omega \quad R_2 := 15 \cdot \Omega \quad C := 40 \cdot \mu\text{F}$$

$$N_1 := 150 \cdot \text{turns} \quad N_2 := 50 \cdot \text{turns}$$

$$Z_L := \frac{1}{\frac{1}{R_2} + j \cdot \omega \cdot C}$$

Make an equivalent circuit:

$$Z_{eq} := \left(\frac{N_1}{N_2}\right)^2 \cdot Z_L \quad Z_{eq} = 128.429 - 29.051j \cdot \Omega$$

$$R_1 + Z_{eq} = 148.429 - 29.051j \cdot \Omega \quad \sqrt{148.429^2 + 29.051^2} = 151.245$$

$$|I_1| = \frac{V_s}{|R_1 + Z_{eq}|} = \frac{V_s}{151.245 \cdot \Omega} = 0.793 \cdot \text{A}$$

b) $|I_2| = ? = \left(\frac{N_1}{N_2}\right) \cdot |I_1| = \frac{150}{50} \cdot 0.793 \cdot \text{A} = 2.379 \cdot \text{A}$

c) $|V_1| = ? = V_s \cdot \left| \frac{Z_{eq}}{R_1 + Z_{eq}} \right| \quad \text{OR.. } |V_1| = |I_1| \cdot |Z_{eq}| = 0.793 \cdot \text{A} \cdot \sqrt{128.429^2 + 29.051^2} \cdot \Omega = 104.417 \cdot \text{V}$