

ECE 2210 / 00 Lecture 8 Notes Basic AC

A. Stolp
1/27/03,
9/9/20


AC stands for **A**lternating **C**urrent as opposed to DC, **D**irect **C**urrent. AC refers to voltages and currents that change with time, usually the voltage is + sometimes and - at other times. This results in currents with go one direction when the voltage is + and the reverse direction when the voltage is -.

AC is important for two reasons.
Power is created and distributed as AC. Signals are AC.

AC Power

Power is generated by rotating magnetic fields.
This naturally produces sinusoidal AC waveforms.

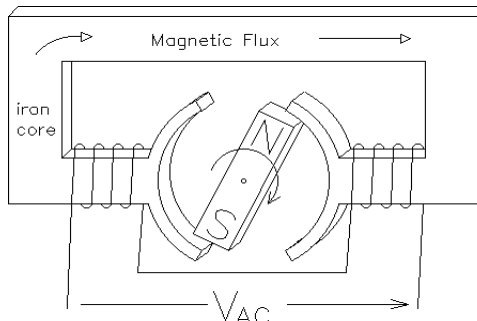
It is easier to make AC motors than DC motors.



AC Power allows use of transformers to reduce line losses

Transformers work with AC, but not DC. Transformers can be used to raise or lower AC voltages (with an opposite change of current). This can be very useful in power distribution systems. Power is voltage times current. You can distribute the same amount of power with high voltage and low current as you can with low voltage and high current. However, the lower the current, the lower the I^2R losses in the wires (all real wires have some resistance). So you'd like to distribute power at the highest possible voltage. Transformers allow you to do this with AC, but won't work with DC.


primary secondary

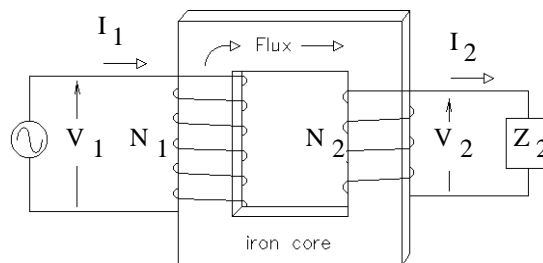


Ideal: power in = power out

$$\text{Ideal transformation of voltage and current: } \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$


Example:

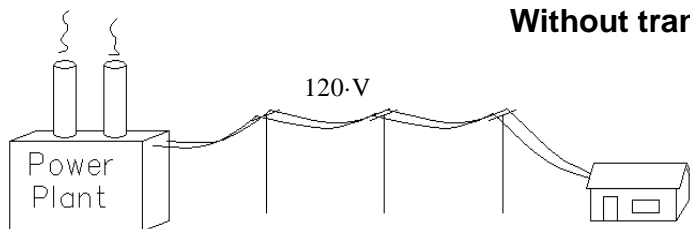


Without transformers

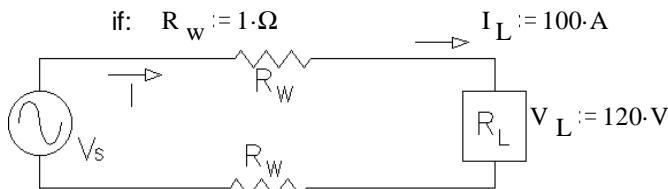

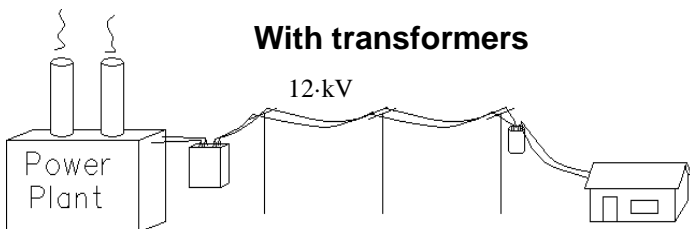Wire loss: $P_W = I_L^2 \cdot 2 \cdot R_W = 20 \cdot \text{kW}$



With transformers

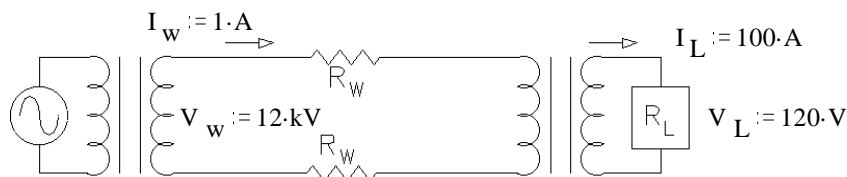

Wire loss: $P_W = I_w^2 \cdot 2 \cdot R_W = 2 \cdot \text{W}$

In this example, the power lost in the transmission lines is only 1/10,000th what it is without transformers.

That's why they raise the voltage in transmission lines to the point where they crackle and buzz. That crackle is the sound of the losses into the surrounding air and can become significant if the voltage is too high.

Signals

A time-varying voltage or current that carries information. If it varies in time, then it has an AC component.



|
Audio, video, position, temperature, digital data, etc...

In some unpredictable fashion

DC is not a signal, Neither is a pure sine wave. If you can predict it, what information can it provide?

Neither DC nor pure sine wave have any "bandwidth". In fact, no periodic waveform is a signal & no periodic waveform has bandwidth. You need bandwidth to transmit information.

Signal sources

- | | |
|-------------------------------------------------|-------------|
| Microphone | Audio |
| Camera | Video |
| Thermistor or other thermal sensor | Temperature |
| Potentiometer | Position |
| LVDT (Linear Variable Differential Transformer) | Position |
| Light sensor | |
| Computer switch | |
| etc... | |

A transducer is a device which transforms one form of energy to another. Some sensors are transducers, many are not

Most often a signal comes from some other system.

Periodic waveforms: Waveshape repeats


T = Period = repeat time

$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi \cdot f$$

A = amplitude

DC = average

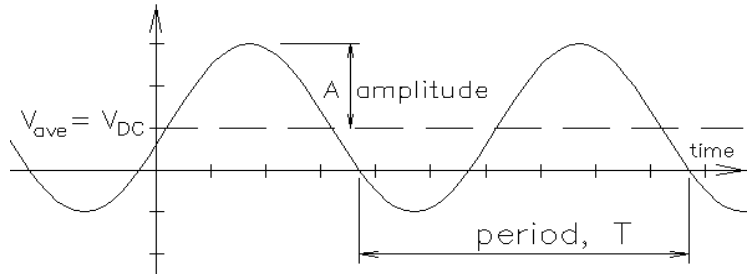


Sinusoidal AC

$$y(t) = A \cdot \cos(\omega \cdot t + \phi)$$







$$\text{voltage: } v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega \cdot t + \phi)$$
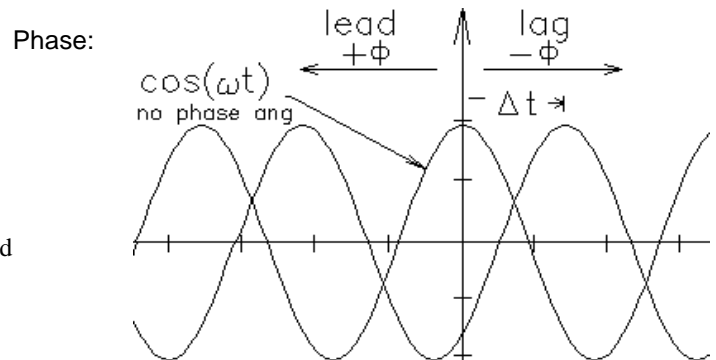
$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360\text{-deg} \quad \text{or:} \quad \phi = -\frac{\Delta t}{T} \cdot 2\pi\text{-rad}$$



Other common periodic waveforms

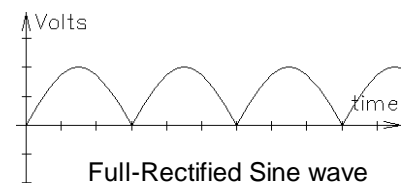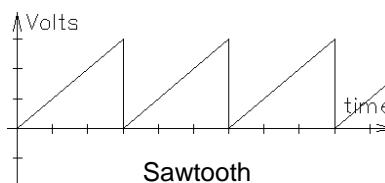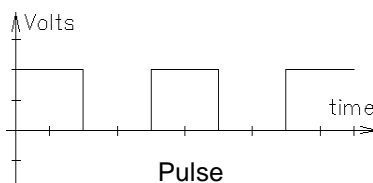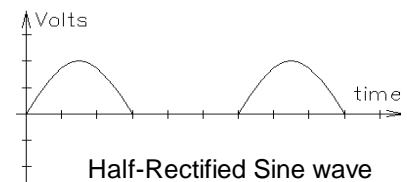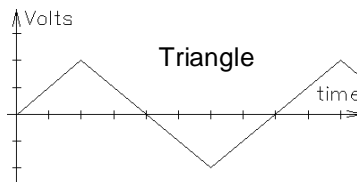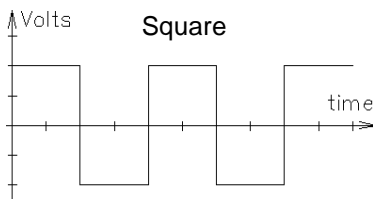


All but the square and triangle waves have a DC component as well as AC.

ECE 2210 / 00 Capacitor Lecture Notes

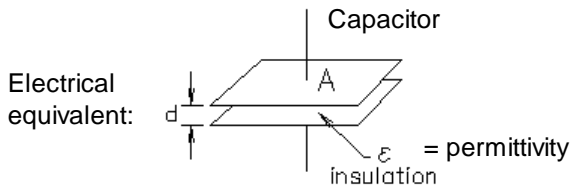A. Stolp
2/17/03
rev 9/16/09
12/15 & 9/19

Now that we have voltages and currents which can be functions of time, it's time to introduce the capacitor and the inductor.



Electrical equivalent:

$$C = \epsilon \cdot \frac{A}{d} = \frac{Q}{V} = \frac{dq}{dv}$$


Units: farad = $\frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}}$

$\mu\text{F} = 1 \cdot 10^{-6} \cdot \text{farad}$

$\text{pF} = 1 \cdot 10^{-12} \cdot \text{farad}$

For drawings of capacitors and info about tolerances, see Ch.3 of textbook.

Fluid Model:

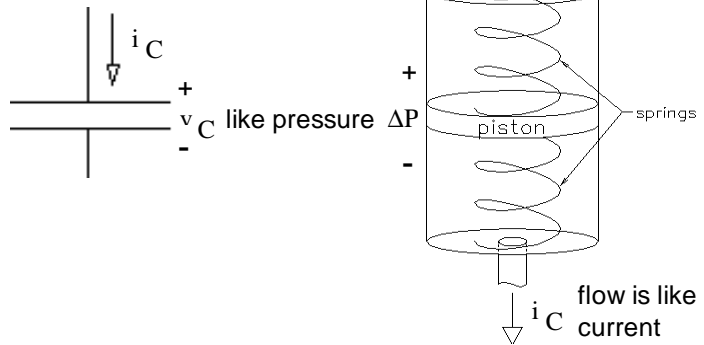

Basic equations you should know:

$$C = \frac{Q}{V}$$

$$i_C = C \cdot \frac{d}{dt} v_C$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt$$

/ initial voltage


Or...
$$v_C = \frac{1}{C} \int_0^t i_C dt + v_C(0)$$

Or...
$$\Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$$


Energy stored in electric field: $W_C = \frac{1}{2} \cdot C \cdot V_C^2$

Capacitor voltage **cannot** change instantaneously

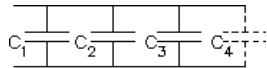parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$



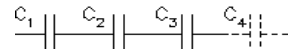series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Capacitors are the only "backwards" components.


Sinusoids

$$i_C(t) = I_p \cdot \cos(\omega \cdot t)$$

$$v_C(t) = \frac{1}{C} \int i_C dt = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \sin(\omega \cdot t) = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \cos(\omega \cdot t - 90\text{-deg})$$

indefinite integral $\underbrace{\quad}_{V_p}$ $\underbrace{\quad}_{V_p}$

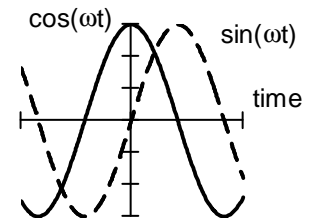Voltage "lags" current, makes sense, current has to flow in first to charge capacitor.




Steady-state or Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} v_C = 0 \quad i_C = C \cdot \frac{d}{dt} v_C = 0$$

no current means it looks like an open

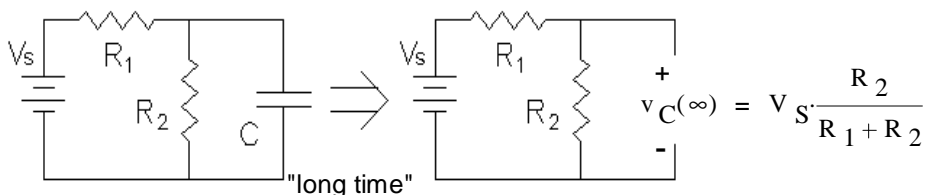


Example

The voltage across a $0.5 \mu\text{F}$ capacitor is shown below. Make an accurate drawing of the capacitor current. Label the y-axis of your graph (I've already done the time-axis).

The accuracy of your plot at 0, 2, 6, and 8 ms is important, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

$C := 0.5 \mu\text{F}$

The curve is 2nd order

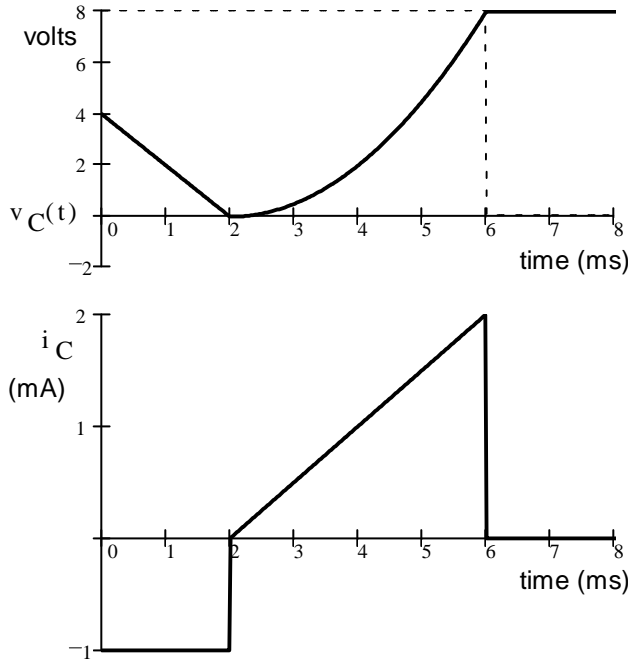

1 - 2ms: $i_C = C \cdot \frac{\Delta V}{\Delta t} = 0.5 \mu\text{F} \cdot \frac{-4 \cdot \text{V}}{2 \cdot \text{ms}} = -1 \cdot \text{mA}$

2ms - 6ms: Initial slope is zero and the final slope is positive, so the current must be a triangle that starts at zero and ends at some height.

$$\Delta v_C(t) = \frac{1}{C} \int_0^t i_C(t) dt$$


$$8 \cdot \text{V} = \frac{1}{C} \cdot \left(\frac{4 \cdot \text{ms} \cdot \text{height}}{2} \right)$$

$$\text{height} = 8 \cdot \text{V} \cdot \frac{C \cdot 2}{4 \cdot \text{ms}} = 2 \cdot \text{mA}$$

6ms - 8ms: Slope is zero, so the current must be zero.

ECE 2210 / 00 Inductor Lecture Notes

Fluid Model:

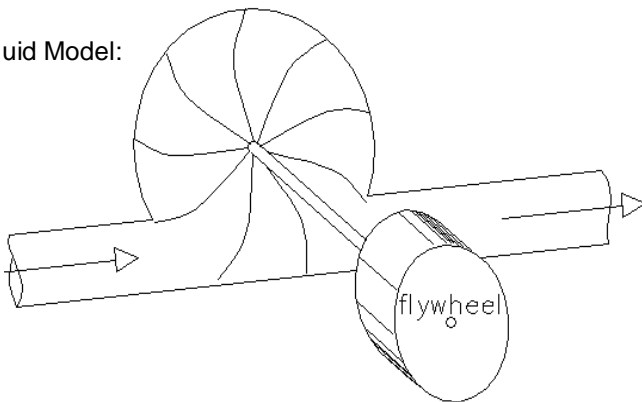

Basic equations you should know:

$$v_L = L \frac{d}{dt} i_L$$

Energy stored in electric field: $W_L = \frac{1}{2} \cdot L \cdot I_L^2$


Inductor current **cannot** change instantaneously

Units: henry = $\frac{\text{volt} \cdot \text{sec}}{\text{amp}}$

mH = $10^{-3} \cdot \text{H}$

$\mu\text{H} = 10^{-6} \cdot \text{H}$

Electrical equivalent:

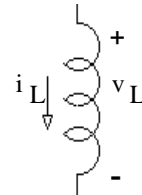

$$L = \mu_0 \cdot N^2 \cdot K$$

μ is the permeability of the inductor core

K is a constant which depends on the inductor geometry


N is the number of turns of wire

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L dt$$


Or... $i_L = \frac{1}{L} \int_0^t v_L dt + i_L(0)$ / initial current

Or... $\Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p3
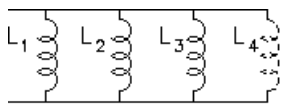
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$$

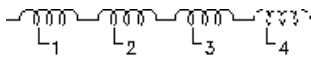
series: $L_{eq} = L_1 + L_2 + L_3 + \dots$




parallel:

Sinusoids $i_L(t) = I_p \cdot \cos(\omega \cdot t)$

$$v_L(t) = L \frac{d}{dt} i_L = L \cdot \omega \cdot (-I_p \cdot \sin(\omega \cdot t)) = L \cdot \omega \cdot I_p \cdot \cos(\omega \cdot t + 90\text{-deg})$$


$\underbrace{\quad}_{V_p}$

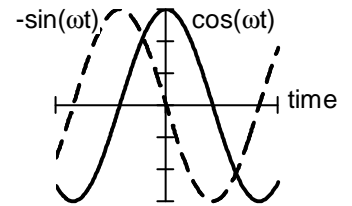Voltage "leads" current, makes sense, voltage has to present to make current change, so voltage comes first.




Resonance

Series resonance

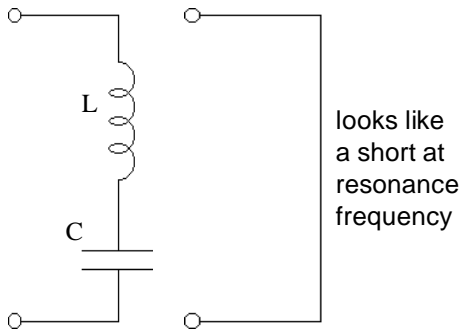

Parallel resonance

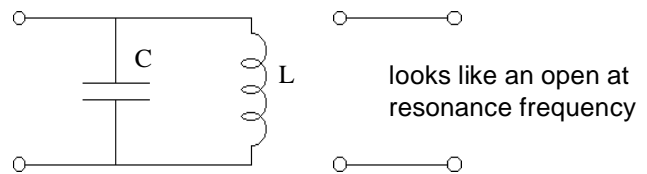

The resonance frequency is calculated the same way for either case:


$$\omega_o = \frac{1}{\sqrt{L \cdot C}} \left(\frac{\text{rad}}{\text{sec}} \right) \quad \text{OR..} \quad \omega_o = \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \text{If you have multiple capacitors or inductors which can be combined.} \quad f_o = \frac{\omega_o}{2 \cdot \pi} \text{ (Hz)}$$

Steady-state of Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} i_L = 0 \quad v_L = L \frac{d}{dt} i_L = 0$$


no voltage means it looks like a short

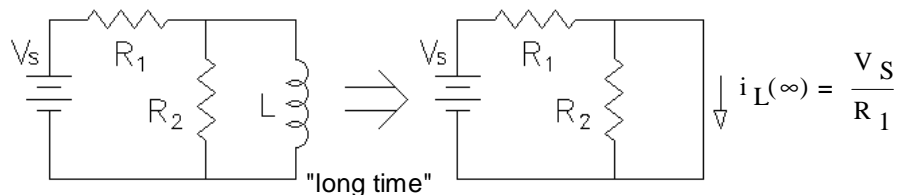

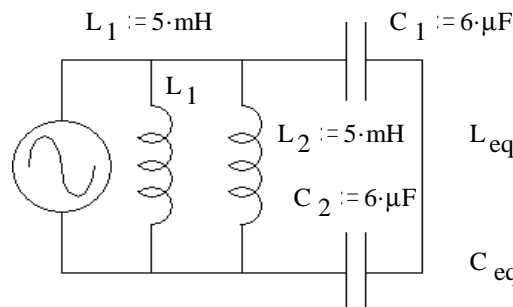Examples

Ex 1

Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



$$L_{eq} := \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \quad L_{eq} = 2.5 \cdot \text{mH}$$

$$C_{eq} := \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad C_{eq} = 3 \cdot \mu\text{F}$$


$$\omega_o := \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \omega_o = 11547 \cdot \frac{\text{rad}}{\text{sec}} \quad f_o = \frac{\omega_o}{2 \cdot \pi} = 1838 \cdot \text{Hz}$$

Ex 2

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4

The current through a 0.3mH inductor is shown below. Make an accurate drawing of the inductor voltage. Make reasonable assumptions where necessary. Label your graph.

$L := 0.3 \cdot \text{mH}$

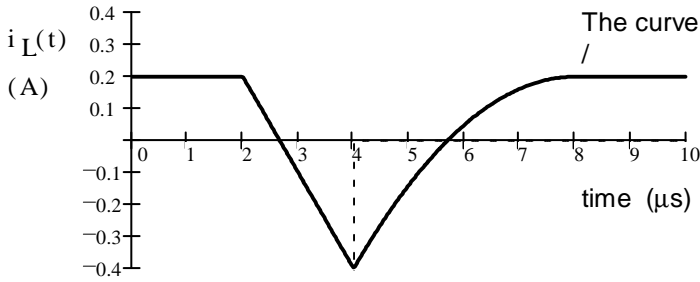


The curve is 2nd order and ends at 8μs

0 - 2μs: No change in current, so: $v_L = 0$

$$2\mu\text{s} - 4\mu\text{s}: v_L = L \cdot \frac{\Delta I}{\Delta t} = 0.3 \cdot \text{mH} \cdot \frac{-0.6 \cdot \text{A}}{2 \cdot \mu\text{s}} = -90 \cdot \text{V}$$

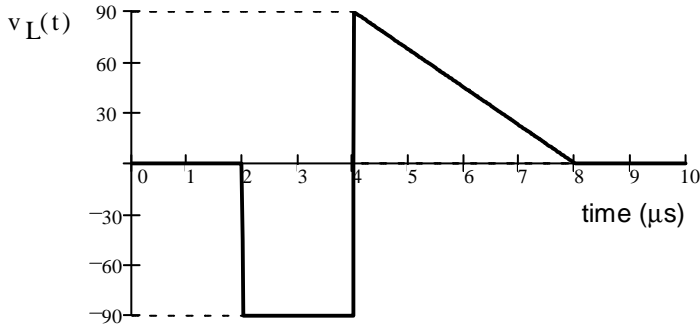4μs - 8μs: Initial slope is positive and the final slope is zero, so the voltage must be a triangle that starts at some height and ends at zero.



$$\Delta i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt$$

$$0.6 \cdot \text{A} = \frac{1}{0.3 \cdot \text{mH}} \left(\frac{4 \cdot \mu\text{s} \cdot \text{height}}{2} \right)$$

$$\text{height} = 0.6 \cdot \text{A} \cdot \frac{0.3 \cdot \text{mH} \cdot 2}{4 \cdot \mu\text{s}} = 90 \cdot \text{V}$$

8μs - 10μs: No change in current, so: $v_L = 0$


Ex 3 Given a voltage, find the current, $L := 4 \cdot \text{mH}$

$$\Delta i_L(t) = \frac{1}{L} \int_{1 \cdot \mu\text{s}}^{2 \cdot \mu\text{s}} 20 \cdot \text{V} dt = 5 \cdot \text{mA}$$


$$\frac{1}{L} \int_{4 \cdot \mu\text{s}}^{8 \cdot \mu\text{s}} -10 \cdot \text{V} dt + 5 \cdot \text{mA} = -5 \cdot \text{mA}$$

$$\frac{1}{L} \int_{8 \cdot \mu\text{s}}^{10 \cdot \mu\text{s}} V(t) dt + -5 \cdot \text{mA}$$

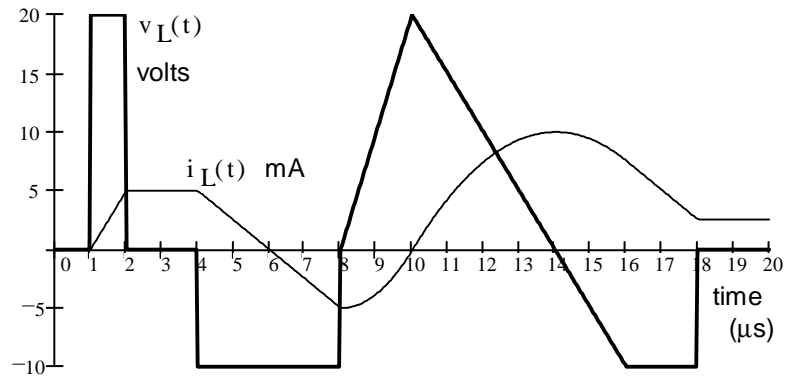
$$= \frac{1}{L} \cdot \frac{20 \cdot \text{V} \cdot 2 \cdot \mu\text{s}}{2} - 5 \cdot \text{mA} = 0 \cdot \text{mA} \quad \text{etc...}$$



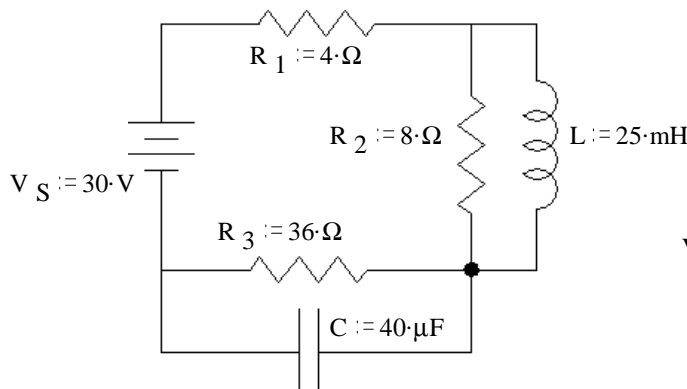Ex 4 The following circuit has been connected as shown for a long time. Find the energy stored in the capacitor and the inductor.



Redraw:

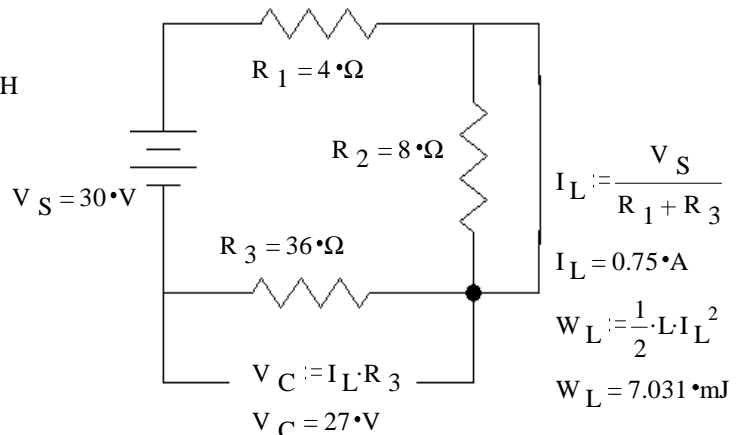

$$I_L := \frac{V_S}{R_1 + R_3}$$

$$I_L = 0.75 \cdot \text{A}$$

$$W_L := \frac{1}{2} \cdot L \cdot I_L^2$$

$$W_L = 7.031 \cdot \text{mJ}$$

$$V_C := I_L \cdot R_3$$

$$V_C = 27 \cdot \text{V}$$

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4

$$W_C := \frac{1}{2} \cdot C \cdot V_C^2$$

$$W_C = 14.58 \cdot \text{mJ}$$

Capacitor, Inductor Notes

ECE 2210 / 00


A.Stolp
2/27/00,
9/13/05

Capacitors


$$C = \frac{Q}{V} \quad \text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}} \quad v_C = \frac{1}{C} \int_{-\infty}^t i_C dt + v_C(0) \quad \text{initial voltage} \quad i_C = C \frac{d}{dt} v_C$$

Energy stored in electric field: $W_C = \frac{1}{2} \cdot C \cdot V_C^2$ Capacitor voltage **cannot** change instantaneously

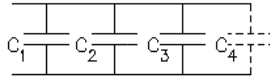parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$



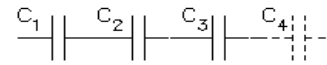series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Steady-state sinusoids:


Impedance: $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$ Current leads voltage by 90 deg

Inductors


$$\text{henry} = \frac{\text{volt}\cdot\text{sec}}{\text{amp}} \quad i_L = \frac{1}{L} \int_{-\infty}^t v_L dt + i_L(0) \quad \text{initial current} \quad v_L = L \frac{d}{dt} i_L$$

Energy stored in magnetic field: $W_L = \frac{1}{2} \cdot L \cdot I_L^2$ Inductor current **cannot** change instantaneously

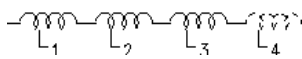series: $L_{eq} = L_1 + L_2 + L_3 + \dots$



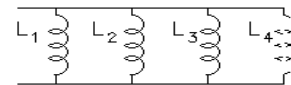parallel: $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$



Steady-state sinusoids:

Impedance: $Z_L = j \cdot \omega \cdot L$ Current lags voltage by 90 deg

RC and RL first-order transient circuits

For all first order transients: $v_X(t) = v_X(\infty) + (v_X(0) - v_X(\infty)) \cdot e^{-\frac{t}{\tau}}$ $i_X(t) = i_X(\infty) + (i_X(0) - i_X(\infty)) \cdot e^{-\frac{t}{\tau}}$




Find initial Conditions (v_C and/or i_L)

Find conditions just before time $t = 0$, $v_C(0^-)$ and $i_L(0^-)$. These will be the same just after time $t = 0$, $v_C(0^+)$ and $i_L(0^+)$ and will be your initial conditions. (If initial conditions are zero: Capacitors are shorts, Inductors are opens.) Use normal circuit analysis to find your desired variable: $v_X(0)$ or $i_X(0)$




Find final conditions ("steady-state" or "forced" solution)

Inductors are shorts Capacitors are opens Solve by DC analysis $v_X(\infty)$ or $i_X(\infty)$

RC Time constant $= \tau = RC$

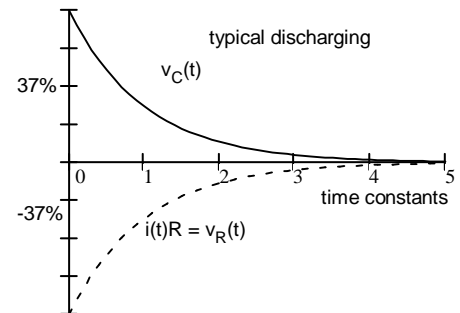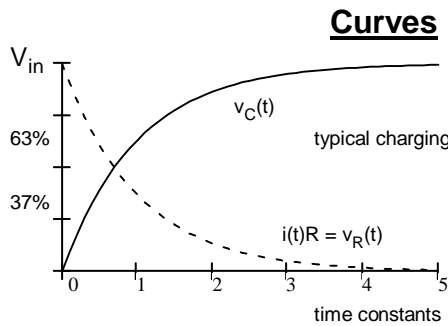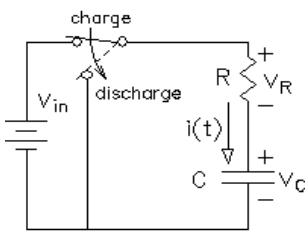

RL Time constant $= \tau = \frac{L}{R}$

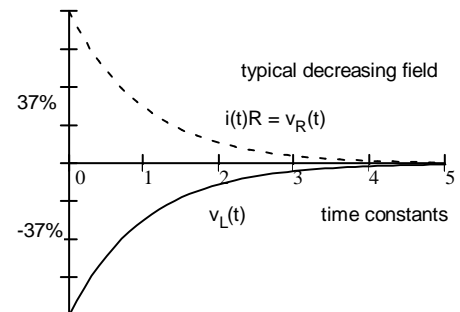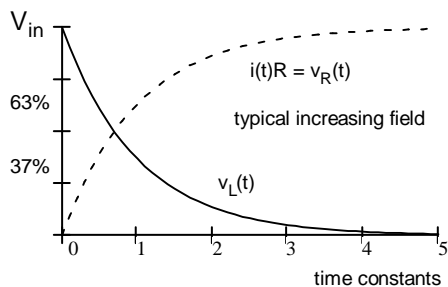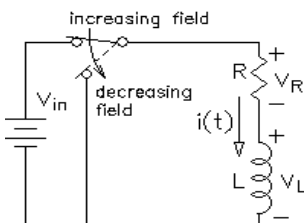




ECE 2210 / 00 homework # 7

Due: Tue, 2/16/21




a

Answer the following problems on your own paper.

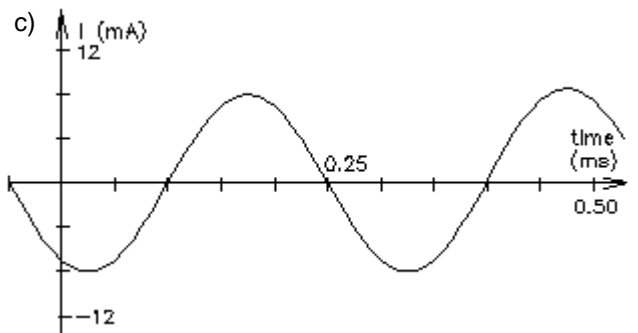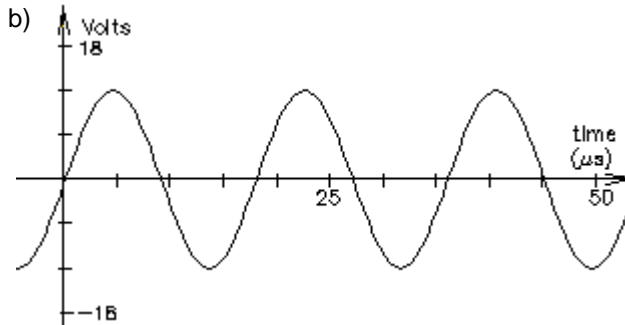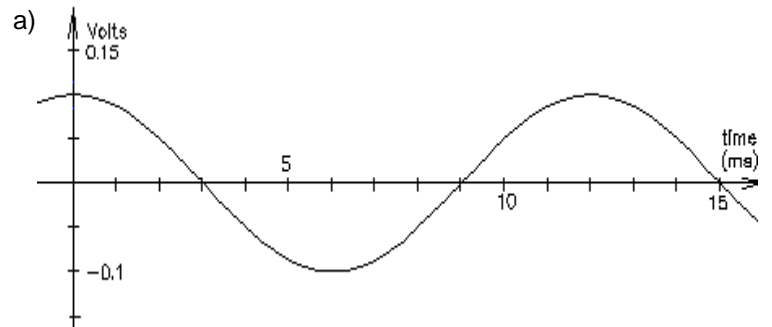- For each of the following sinusoidal waves, find:
 - peak-to-peak voltage or current, V_{pp} or I_{pp}
 - amplitude, A , V_p , or I_p
 - period, T
 - frequency f in cycles/sec or Hz
 - an expression for $v(t)$ or $i(t)$ in terms of $A\cos(\omega t + \phi)$
 the frequency ω is in radians/sec
 the phase angle ϕ is in rad/sec or degrees



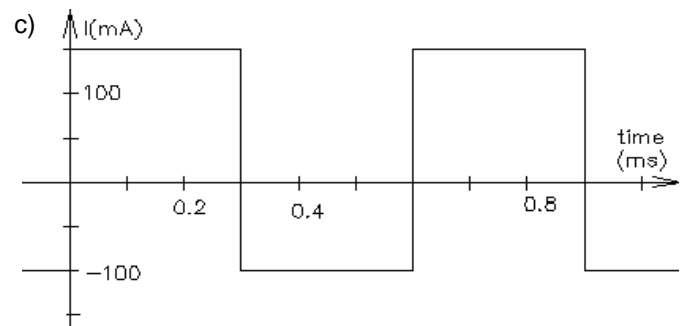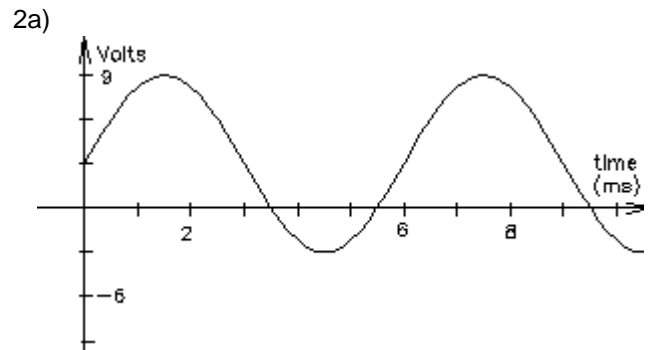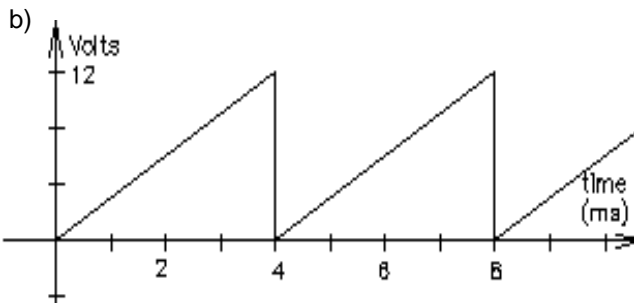- For each of the following waveforms, find:
 - Peak-to-peak voltage or current, V_{pp} or I_{pp}
 - Average, (V_{DC} , I_{DC} , V_{ave} , or I_{ave})
 - Period, T
 - Frequency f in cycles/sec or Hz



- For problem 2a above, write a full expression for $v(t)$ in terms of $v(t) = A\cos(\omega t + \phi) + V_{DC}$




Answers

- 0.2-V 0.1-V 12-ms 83.3-Hz $0.1 \cdot V \cdot \cos(523.6 \cdot t)$
 - 24-V 12-V 0.018-ms 55.6-kHz
 $v(t) := 12 \cdot V \cdot \cos(349100 \cdot t - 90 \cdot \text{deg})$
 - 16-mA 8-mA 0.3-ms 3333-Hz
 $8 \cdot \text{mA} \cdot \cos(20940 \cdot t + 150 \cdot \text{deg})$




- 12-V 3-V 6-ms 167-Hz
 - 12-V 6-V 4-ms 250-Hz
 - 250-mA 25-mA 0.6-ms 1.667-kHz

- $v(t) := 6 \cdot V \cdot \cos(1047 \cdot t - 90 \cdot \text{deg}) + 3 \cdot V$

1) Find C_{eq} in each case

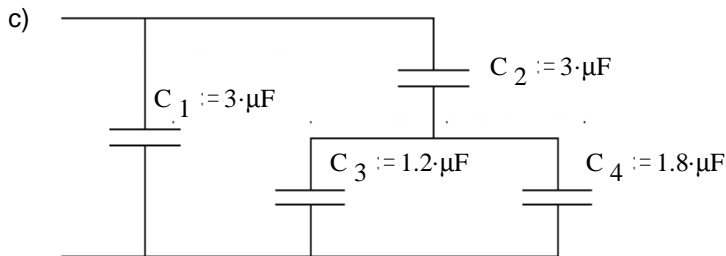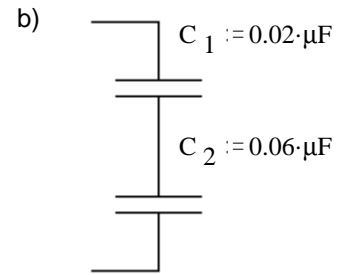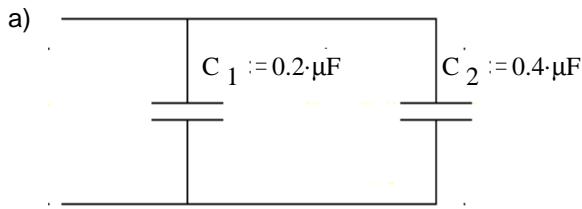

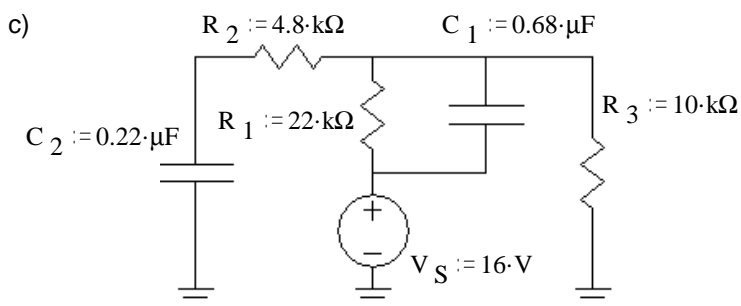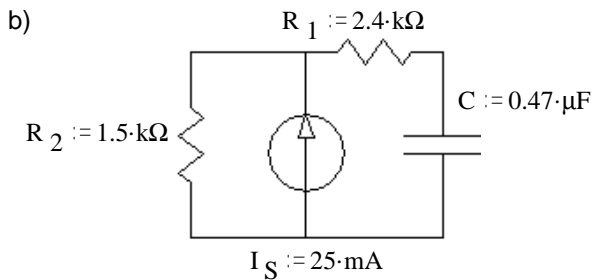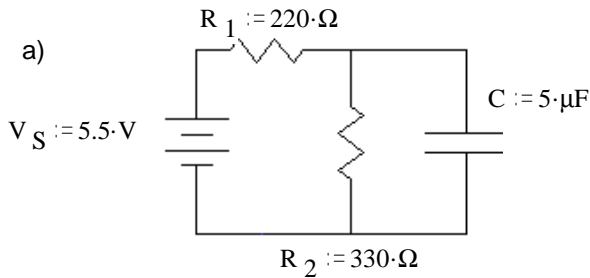
2. Each of the following circuits have been connected as shown for a long time. Find the voltage across each capacitor and the energy stored in each.




ECE 2210 / 00 homework # 8

Name: _____ You may want to hand in this page with answers to problems 3 & 4.

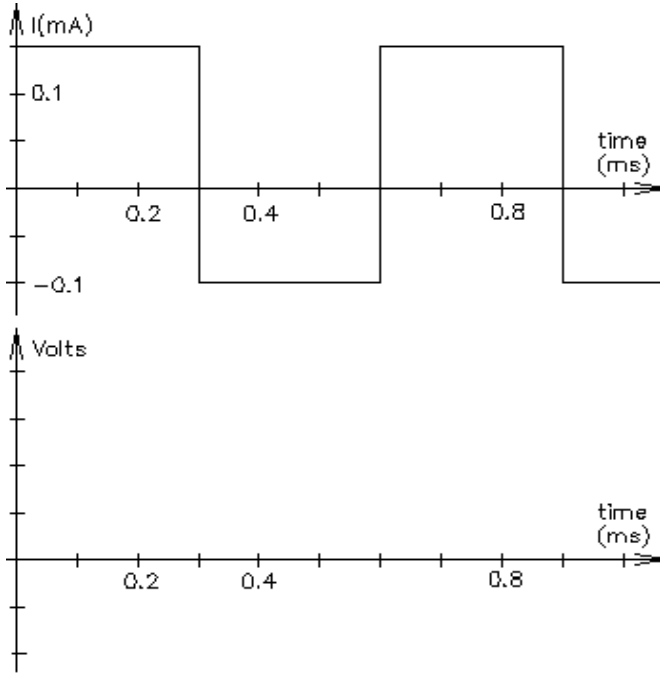3. The current waveform shown below flows through a $0.025 \mu\text{F}$ capacitor. Make an accurate drawing of the voltage across it. Label your graph. Assume the initial voltage across the capacitor is 0 V .



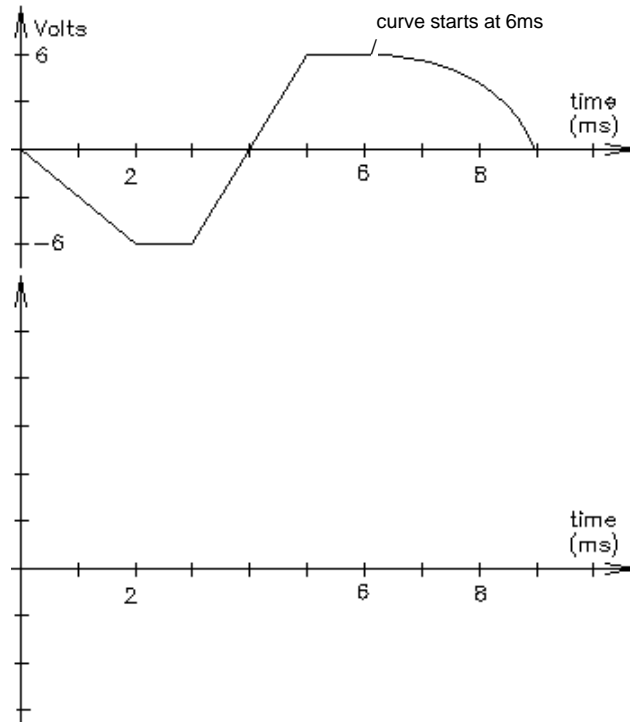
4. The voltage across a $2 \mu\text{F}$ capacitor is shown below. Make an accurate drawing of the capacitor current. Label your graph.



5. The voltage across a $0.68 \mu\text{F}$ capacitor is $v_c = 6 \cdot V \cdot \cos\left(200 \cdot t + \frac{\pi}{2}\right)$ find i_c .

6. The current through a $0.0047 \mu\text{F}$ capacitor is $i_c = 18 \cdot \mu\text{A} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_c .

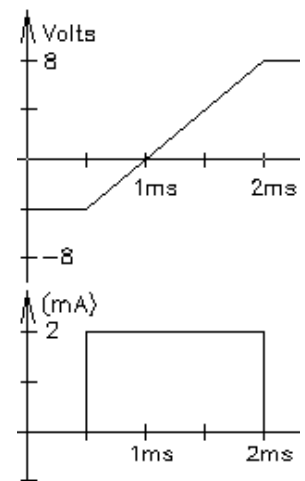7. A capacitor voltage and current are shown at right. What value is the capacitor?



Answers

1. a) $0.6 \mu\text{F}$ b) $0.015 \mu\text{F}$ c) $4.5 \mu\text{F}$
 2. a) 3.3 V 0.027 mJ b) 37.5 V 0.33 mJ c) 11 V 0.0411 mJ 5 V $2.75 \mu\text{J}$
 3. 1.8 V 0.6 V 2.4 V 4. -6 mA 12 mA ramp to -8 mA
 5. $i_c = 0.816 \text{ mA} \cdot \cos(200 \cdot t + \pi)$ 6. $v_c = 6.1 \text{ V} \cdot \cos\left(628 \cdot t - \frac{3 \cdot \pi}{4}\right)$ 7. $0.25 \mu\text{F}$



Name: _____

ECE 2210 / 00 hw # 9



Due: Tue, 2/23/21

You will need another paper for your calculations, but you may want to hand this sheet in with your drawings.



1. Find L_{eq} in each case

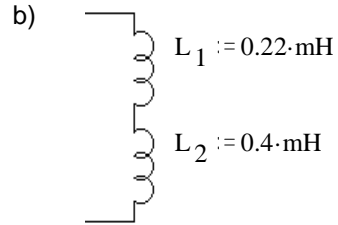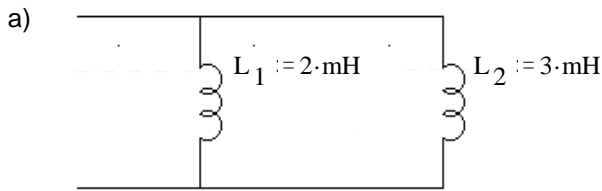

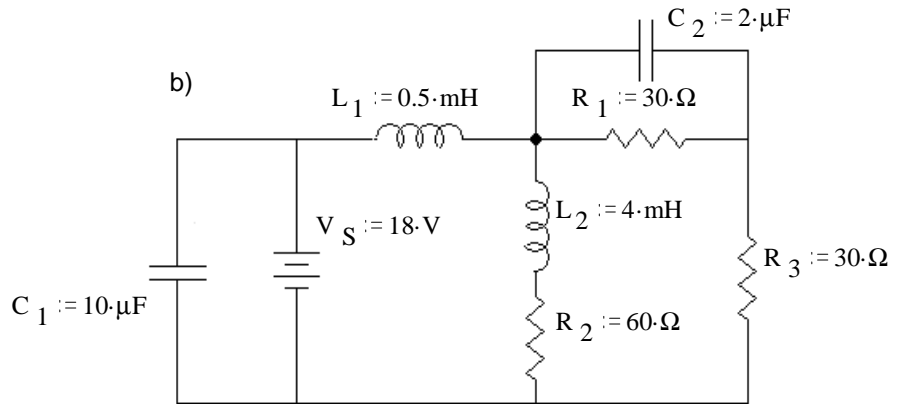
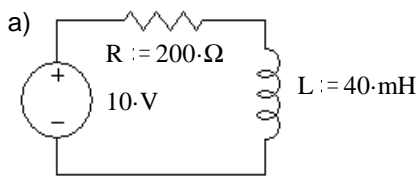
2. Find the stored energy in each capacitor and/or inductor under steady-state conditions. Note: Treat caps as opens and inductors as shorts to find DC voltages and currents.



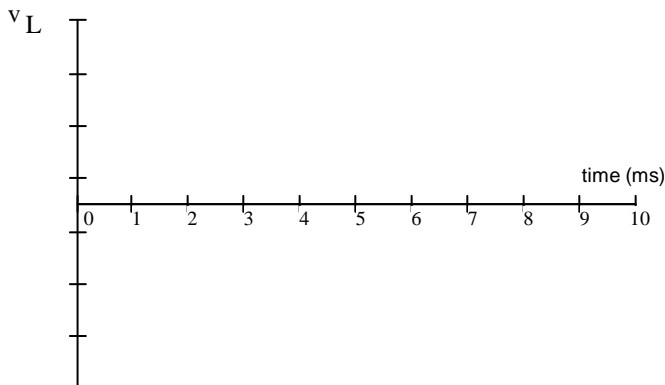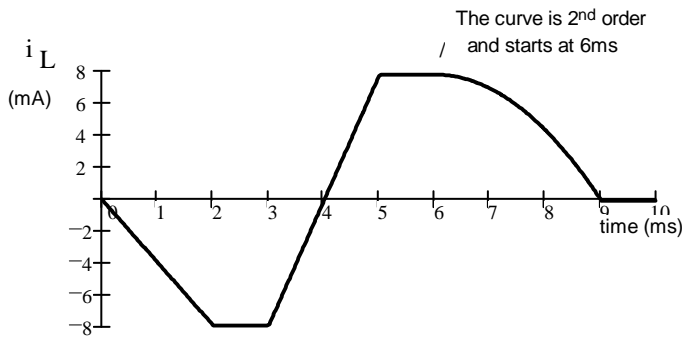3. The current waveform shown below flows through a 2 mH inductor. Make an accurate drawing of the voltage across it. Label your graph.



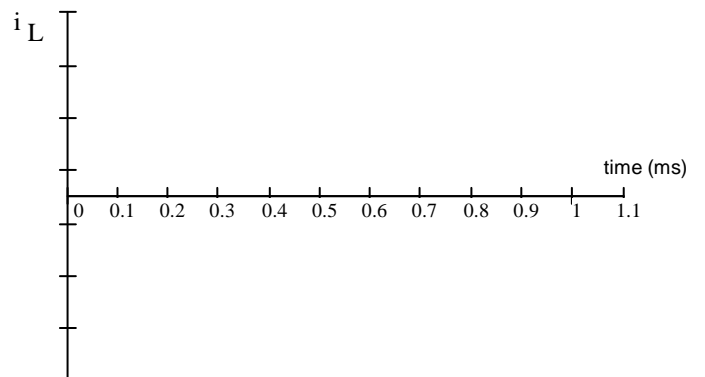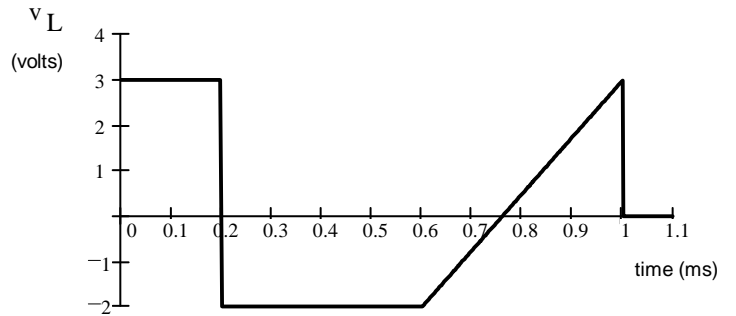4. The voltage across a 0.5 mH inductor is shown below. Make an accurate drawing of the inductor current. Assume the initial current is 0 mA.



ECE 2210 / 00 homework # 9


5. The voltage across a 1.2 mH inductor is $v_L = 4 \cdot \text{mV} \cdot \cos(300 \cdot t)$ find i_L .

6. The current through a 0.08 mH inductor is $i_L = 20 \cdot \text{mA} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_L .


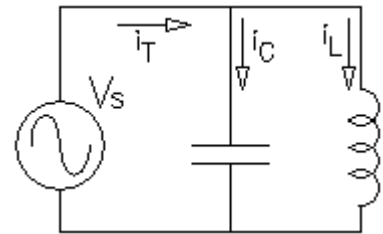
7. Refer to the circuit shown. Assume that V_s is a sinusoidal input voltage whose frequency can be adjusted. At some frequency of V_s this circuit can resonate. At that frequency $i_C(t) = -i_L(t)$. ($i_C(t)$ is 180 degrees out-of-phase with $i_L(t)$).

Show that resonance occurs at this frequency:

$$\omega_o = \frac{1}{\sqrt{L \cdot C}}, \quad f_o = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$



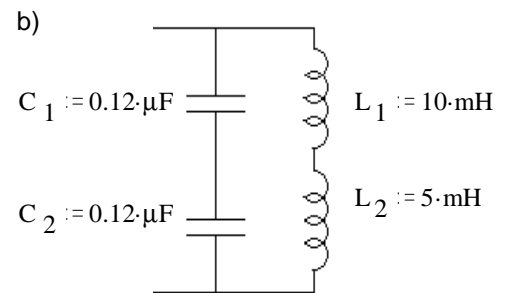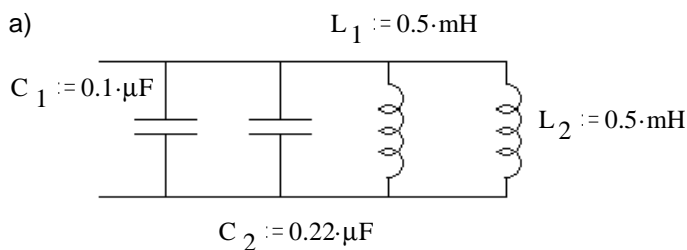8. Find the resonant frequency, f_o in each case.



Answers

1. 1.2·mH 0.62·mH 2. a) 0.05·mJ b) 1.62·mJ 0.081·mJ 0.09·mJ 0.18·mJ

3. Straight lines between the following points: (0ms,-8mV), (2ms,-8mV), (2ms,0mV), (3ms,0mV), (3ms,16mV), (5ms,16mV), (5ms,0mV), (6ms,0mV), (9ms,-10.67mV), (9ms,0mV), (10ms,0mV)

4. Straight lines between the following points: (0ms,0A), (0.2ms,1.2A), (0.6ms,-0.4A), curves until it's flat at (0.76ms, -0.72A), continues to curve up to (1ms, 0A), (1.1ms,0A)

5. $i_L = 11.1 \cdot \text{mA} \cdot \cos(300 \cdot t - 90 \cdot \text{deg})$ 6. $v_L = 1 \cdot \text{mV} \cdot \cos\left(628 \cdot t + \frac{1}{4} \cdot \pi\right)$

7. Assume a sinusoidal voltage, find i_C and i_L by integration and differentiation, and show that they are equal and opposite at the resonant frequency.

8. a) 17.79·kHz b) 5305·Hz