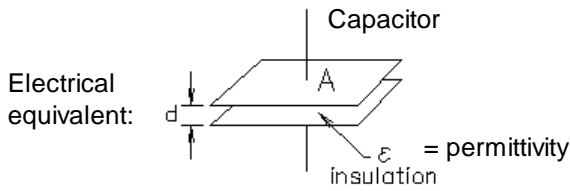


ECE 2210 / 00 Capacitor Lecture Notes

A. Stolp
2/17/03
rev 9/16/09
12/15 & 9/19

Now that we have voltages and currents which can be functions of time, it's time to introduce the capacitor and the inductor.



Electrical equivalent:

$$C = \epsilon \cdot \frac{A}{d} = \frac{Q}{V} = \frac{dq}{dv}$$


Units: farad = $\frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}}$

$\mu\text{F} = 1 \cdot 10^{-6} \cdot \text{farad}$

$\text{pF} = 1 \cdot 10^{-12} \cdot \text{farad}$

For drawings of capacitors and info about tolerances, see Ch.3 of textbook.

Fluid Model:

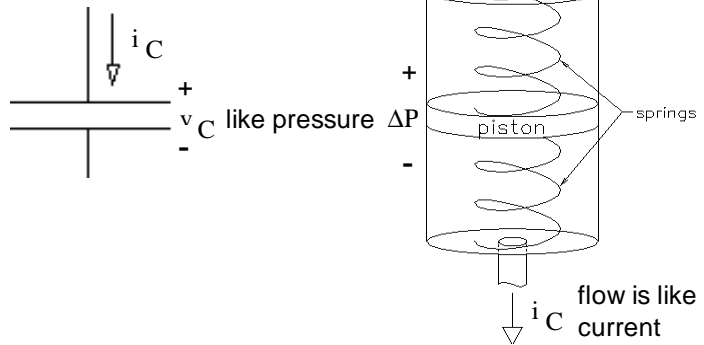

Basic equations you should know:

$$C = \frac{Q}{V}$$

$$i_C = C \cdot \frac{d}{dt} v_C$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt$$

/ initial voltage


Or...
$$v_C = \frac{1}{C} \int_0^t i_C dt + v_C(0)$$

Or...
$$\Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$$


Energy stored in electric field: $W_C = \frac{1}{2} \cdot C \cdot V_C^2$

Capacitor voltage **cannot** change instantaneously

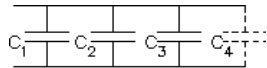parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$



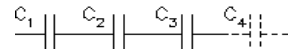series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Capacitors are the only "backwards" components.


Sinusoids

$$i_C(t) = I_p \cdot \cos(\omega \cdot t)$$

$$v_C(t) = \frac{1}{C} \int i_C dt = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \sin(\omega \cdot t) = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \cos(\omega \cdot t - 90\text{-deg})$$

indefinite integral $\underbrace{\quad}_{V_p}$ $\underbrace{\quad}_{V_p}$

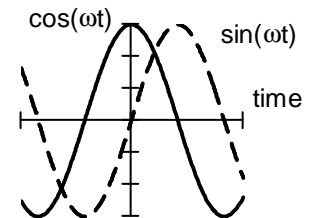Voltage "lags" current, makes sense, current has to flow in first to charge capacitor.




Steady-state or Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} v_C = 0 \quad i_C = C \cdot \frac{d}{dt} v_C = 0$$

no current means it looks like an open

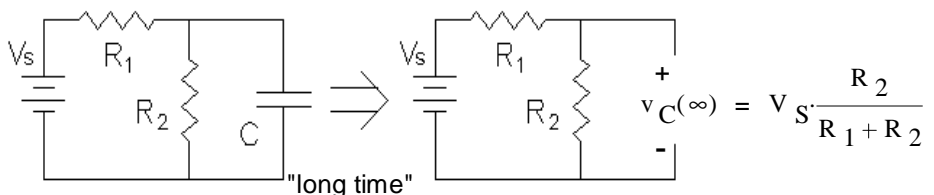


Example

The voltage across a $0.5 \mu\text{F}$ capacitor is shown below. Make an accurate drawing of the capacitor current. Label the y-axis of your graph (I've already done the time-axis).

The accuracy of your plot at 0, 2, 6, and 8 ms is important, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

$C := 0.5 \mu\text{F}$

The curve is 2nd order

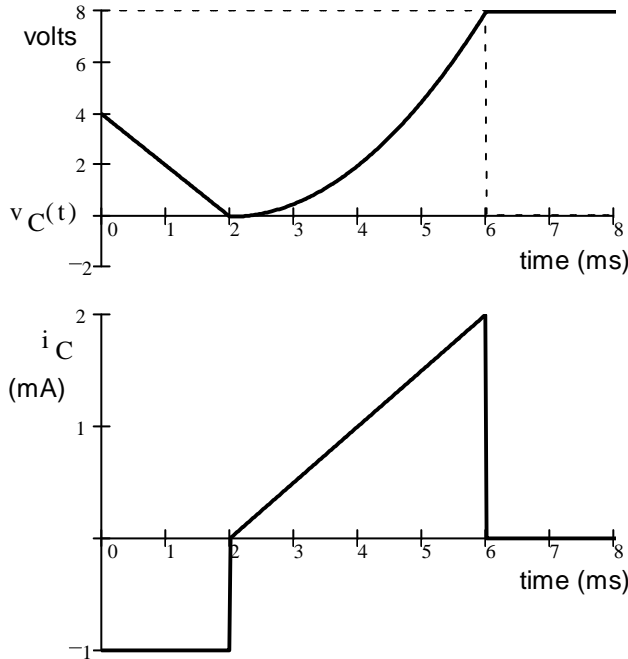

1 - 2ms: $i_C = C \cdot \frac{\Delta V}{\Delta t} = 0.5 \mu\text{F} \cdot \frac{-4 \cdot \text{V}}{2 \cdot \text{ms}} = -1 \text{ mA}$

2ms - 6ms: Initial slope is zero and the final slope is positive, so the current must be a triangle that starts at zero and ends at some height.

$$\Delta v_C(t) = \frac{1}{C} \int_0^t i_C(t) dt$$


$$8 \cdot \text{V} = \frac{1}{C} \cdot \left(\frac{4 \cdot \text{ms} \cdot \text{height}}{2} \right)$$

$$\text{height} = 8 \cdot \text{V} \cdot \frac{C \cdot 2}{4 \cdot \text{ms}} = 2 \cdot \text{mA}$$

6ms - 8ms: Slope is zero, so the current must be zero.

ECE 2210 / 00 Inductor Lecture Notes

Fluid Model:

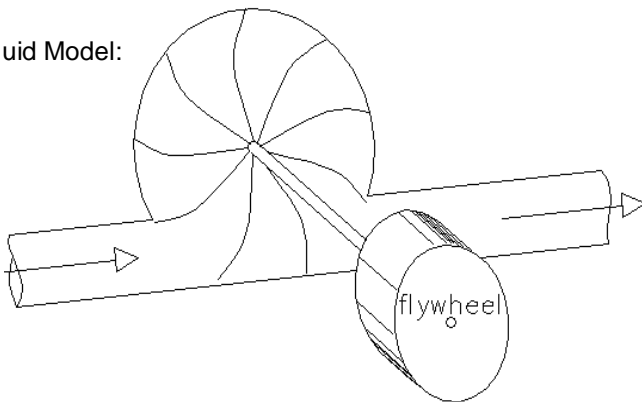

Basic equations you should know:

$$v_L = L \frac{d}{dt} i_L$$

Energy stored in electric field: $W_L = \frac{1}{2} \cdot L \cdot I_L^2$


Inductor current **cannot** change instantaneously

Units: henry = $\frac{\text{volt} \cdot \text{sec}}{\text{amp}}$

mH = $10^{-3} \cdot \text{H}$

$\mu\text{H} = 10^{-6} \cdot \text{H}$

Electrical equivalent:

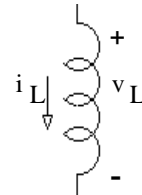

$$L = \mu_0 \cdot N^2 \cdot K$$

μ is the permeability of the inductor core

K is a constant which depends on the inductor geometry


N is the number of turns of wire

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L dt$$


Or... $i_L = \frac{1}{L} \int_0^t v_L dt + i_L(0)$ / initial current

Or... $\Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p3
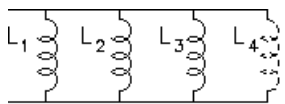
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$$

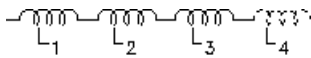
series: $L_{eq} = L_1 + L_2 + L_3 + \dots$




parallel:

Sinusoids $i_L(t) = I_p \cdot \cos(\omega \cdot t)$

$$v_L(t) = L \frac{d}{dt} i_L = L \cdot \omega \cdot (-I_p \cdot \sin(\omega \cdot t)) = L \cdot \omega \cdot I_p \cdot \cos(\omega \cdot t + 90\text{-deg})$$


$\underbrace{\quad}_{V_p}$

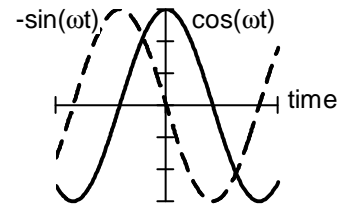Voltage "leads" current, makes sense, voltage has to present to make current change, so voltage comes first.




Resonance

Series resonance

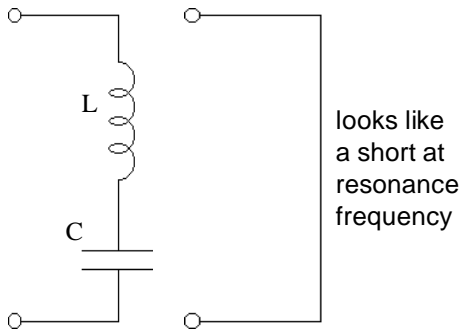

Parallel resonance

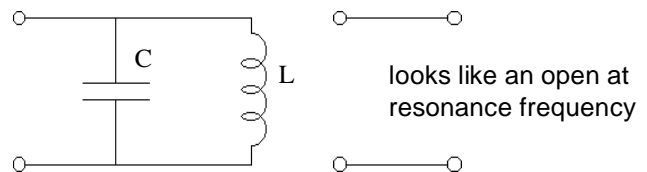

The resonance frequency is calculated the same way for either case:


$$\omega_o = \frac{1}{\sqrt{L \cdot C}} \left(\frac{\text{rad}}{\text{sec}} \right) \quad \text{OR..} \quad \omega_o = \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \text{If you have multiple capacitors or inductors which can be combined.} \quad f_o = \frac{\omega_o}{2 \cdot \pi} \text{ (Hz)}$$

Steady-state of Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} i_L = 0 \quad v_L = L \frac{d}{dt} i_L = 0$$


no voltage means it looks like a short

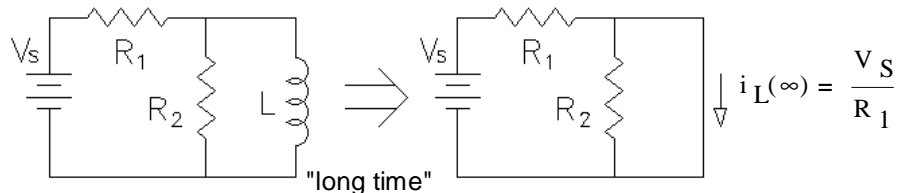

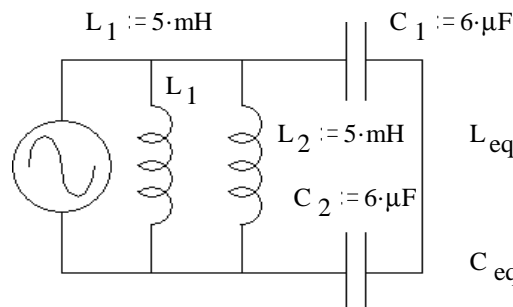Examples

Ex 1

Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



$$L_{eq} := \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \quad L_{eq} = 2.5 \cdot \text{mH}$$

$$C_{eq} := \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad C_{eq} = 3 \cdot \mu\text{F}$$


$$\omega_o := \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \omega_o = 11547 \cdot \frac{\text{rad}}{\text{sec}} \quad f_o = \frac{\omega_o}{2 \cdot \pi} = 1838 \cdot \text{Hz}$$

Ex 2

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4

The current through a 0.3mH inductor is shown below. Make an accurate drawing of the inductor voltage. Make reasonable assumptions where necessary. Label your graph.

$L := 0.3 \cdot \text{mH}$

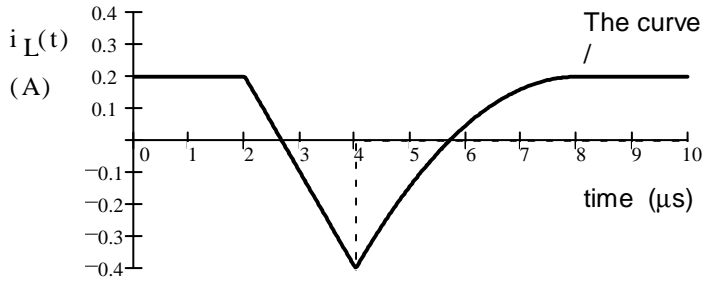


The curve is 2nd order and ends at 8μs

0 - 2μs: No change in current, so: $v_L = 0$

$$2\mu\text{s} - 4\mu\text{s}: v_L = L \cdot \frac{\Delta I}{\Delta t} = 0.3 \cdot \text{mH} \cdot \frac{-0.6 \cdot \text{A}}{2 \cdot \mu\text{s}} = -90 \cdot \text{V}$$

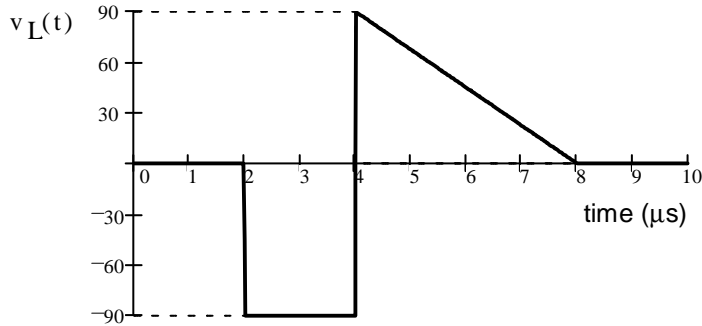4μs - 8μs: Initial slope is positive and the final slope is zero, so the voltage must be a triangle that starts at some height and ends at zero.



$$\Delta i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt$$

$$0.6 \cdot \text{A} = \frac{1}{0.3 \cdot \text{mH}} \left(\frac{4 \cdot \mu\text{s} \cdot \text{height}}{2} \right)$$

$$\text{height} = 0.6 \cdot \text{A} \cdot \frac{0.3 \cdot \text{mH} \cdot 2}{4 \cdot \mu\text{s}} = 90 \cdot \text{V}$$

8μs - 10μs: No change in current, so: $v_L = 0$


Ex 3 Given a voltage, find the current, $L := 4 \cdot \text{mH}$

$$\Delta i_L(t) = \frac{1}{L} \int_{1 \cdot \mu\text{s}}^{2 \cdot \mu\text{s}} 20 \cdot \text{V} dt = 5 \cdot \text{mA}$$


$$\frac{1}{L} \int_{4 \cdot \mu\text{s}}^{8 \cdot \mu\text{s}} -10 \cdot \text{V} dt + 5 \cdot \text{mA} = -5 \cdot \text{mA}$$

$$\frac{1}{L} \int_{8 \cdot \mu\text{s}}^{10 \cdot \mu\text{s}} V(t) dt + -5 \cdot \text{mA}$$

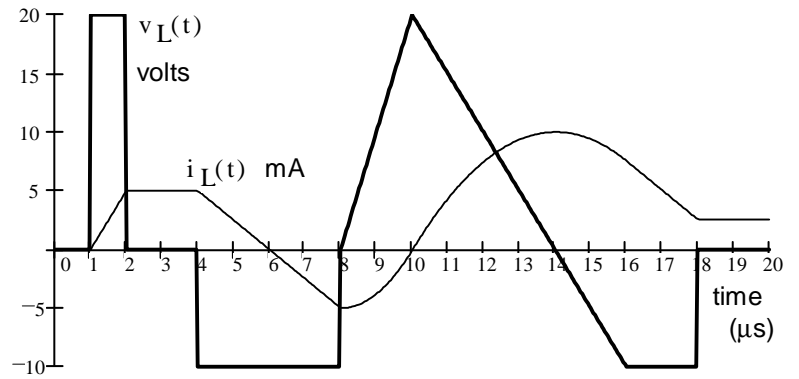
$$= \frac{1}{L} \cdot \frac{20 \cdot \text{V} \cdot 2 \cdot \mu\text{s}}{2} - 5 \cdot \text{mA} = 0 \cdot \text{mA} \quad \text{etc...}$$



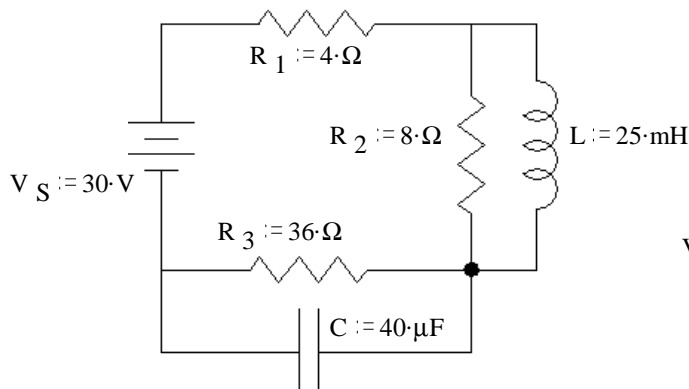Ex 4 The following circuit has been connected as shown for a long time. Find the energy stored in the capacitor and the inductor.



Redraw:

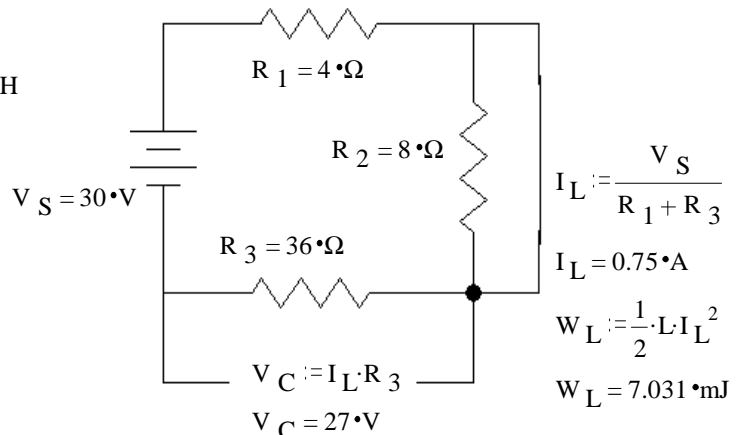

$$I_L := \frac{V_S}{R_1 + R_3}$$

$$I_L = 0.75 \cdot \text{A}$$

$$W_L := \frac{1}{2} \cdot L \cdot I_L^2$$

$$W_L = 7.031 \cdot \text{mJ}$$

$$V_C := I_L \cdot R_3$$

$$V_C = 27 \cdot \text{V}$$

ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4

$$W_C := \frac{1}{2} \cdot C \cdot V_C^2$$

$$W_C = 14.58 \cdot \text{mJ}$$

Capacitor, Inductor Notes

ECE 2210 / 00


A.Stolp
2/27/00,
9/13/05

Capacitors


$$C = \frac{Q}{V} \quad \text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}} \quad v_C = \frac{1}{C} \int_{-\infty}^t i_C dt + v_C(0) \quad \text{initial voltage} \quad i_C = C \frac{d}{dt} v_C$$

Energy stored in electric field: $W_C = \frac{1}{2} \cdot C \cdot V_C^2$ Capacitor voltage **cannot** change instantaneously

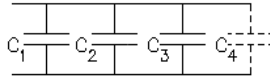parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$



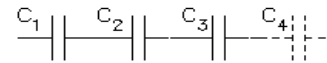series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Steady-state sinusoids:


Impedance: $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$ Current leads voltage by 90 deg

Inductors


$$\text{henry} = \frac{\text{volt}\cdot\text{sec}}{\text{amp}} \quad i_L = \frac{1}{L} \int_{-\infty}^t v_L dt + i_L(0) \quad \text{initial current} \quad v_L = L \frac{d}{dt} i_L$$

Energy stored in magnetic field: $W_L = \frac{1}{2} \cdot L \cdot I_L^2$ Inductor current **cannot** change instantaneously

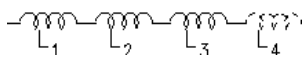series: $L_{eq} = L_1 + L_2 + L_3 + \dots$



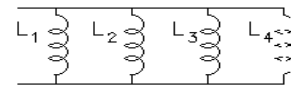parallel: $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$



Steady-state sinusoids:

Impedance: $Z_L = j \cdot \omega \cdot L$ Current lags voltage by 90 deg

RC and RL first-order transient circuits

For all first order transients: $v_X(t) = v_X(\infty) + (v_X(0) - v_X(\infty)) \cdot e^{-\frac{t}{\tau}}$ $i_X(t) = i_X(\infty) + (i_X(0) - i_X(\infty)) \cdot e^{-\frac{t}{\tau}}$




Find initial Conditions (v_C and/or i_L)

Find conditions just before time $t = 0$, $v_C(0^-)$ and $i_L(0^-)$. These will be the same just after time $t = 0$, $v_C(0^+)$ and $i_L(0^+)$ and will be your initial conditions. (If initial conditions are zero: Capacitors are shorts, Inductors are opens.)
Use normal circuit analysis to find your desired variable: $v_X(0)$ or $i_X(0)$




Find final conditions ("steady-state" or "forced" solution)

Inductors are shorts Capacitors are opens Solve by DC analysis $v_X(\infty)$ or $i_X(\infty)$




RC Time constant $= \tau = RC$

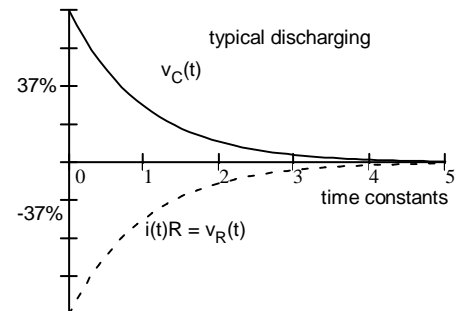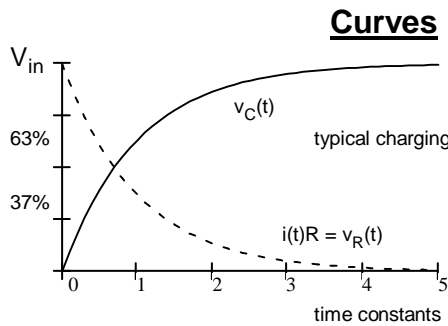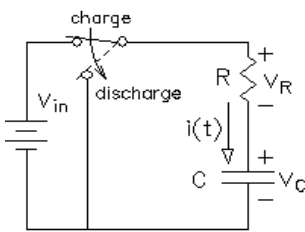




RL Time constant $= \tau = \frac{L}{R}$

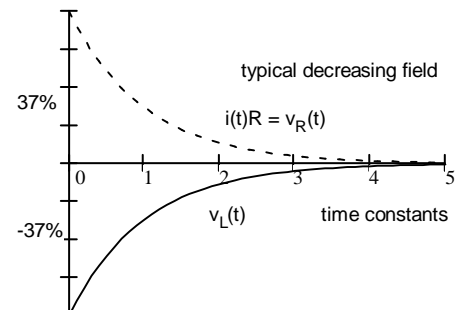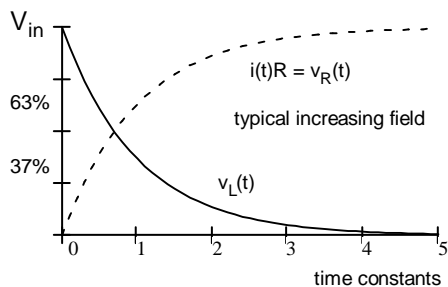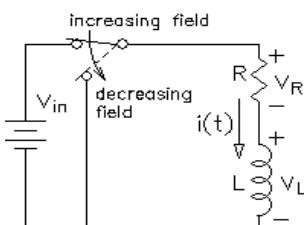

1) Find C_{eq} in each case

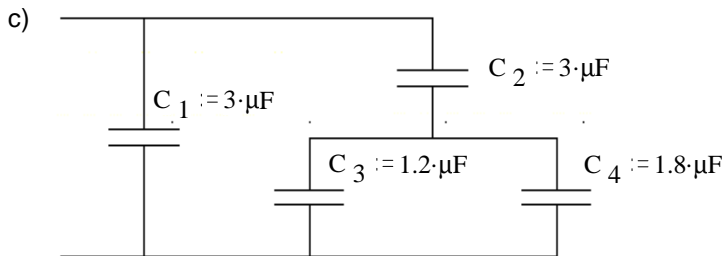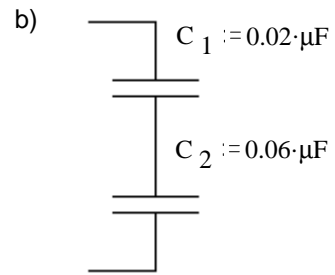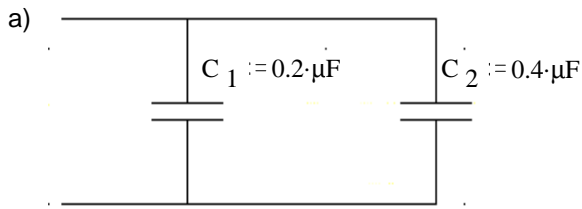

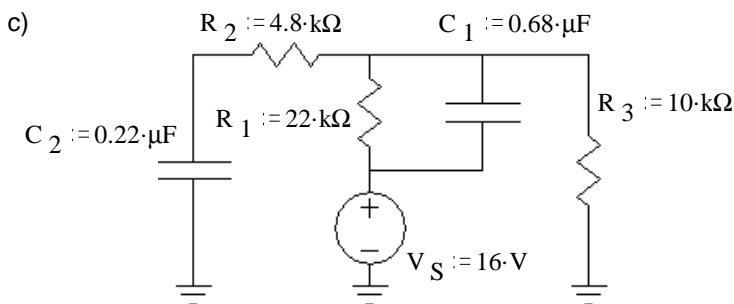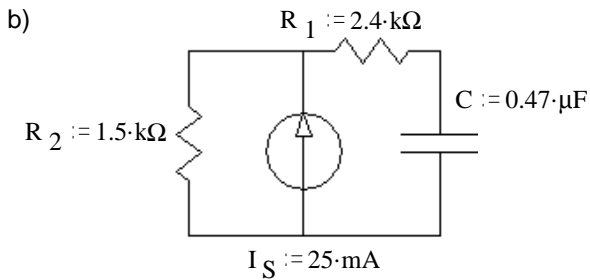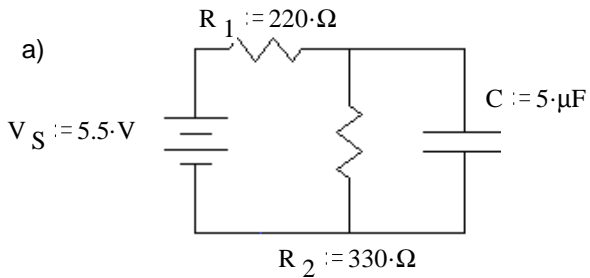
2. Each of the following circuits have been connected as shown for a long time. Find the voltage across each capacitor and the energy stored in each.




ECE 2210 / 00 homework # 8

Name: _____ You may want to hand in this page with answers to problems 3 & 4.

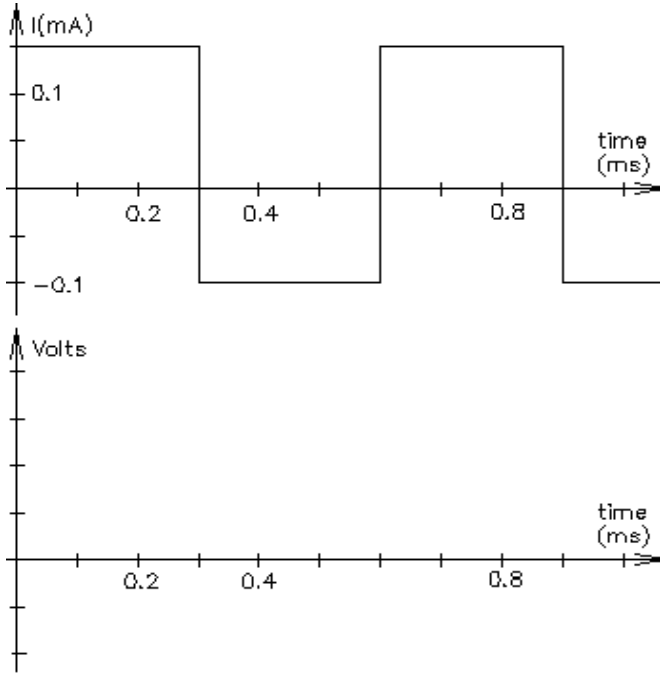3. The current waveform shown below flows through a $0.025 \mu\text{F}$ capacitor. Make an accurate drawing of the voltage across it. Label your graph. Assume the initial voltage across the capacitor is 0 V .



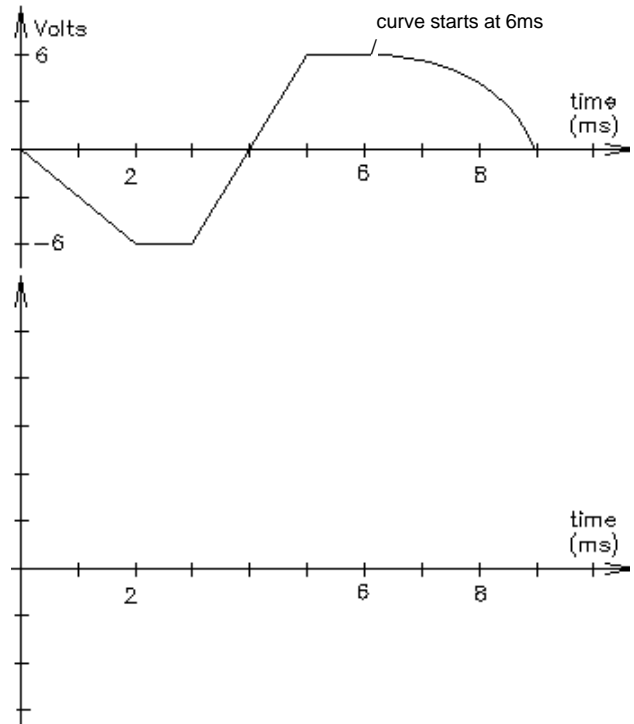
4. The voltage across a $2 \mu\text{F}$ capacitor is shown below. Make an accurate drawing of the capacitor current. Label your graph.



5. The voltage across a $0.68 \mu\text{F}$ capacitor is $v_c = 6 \cdot V \cdot \cos\left(200 \cdot t + \frac{\pi}{2}\right)$ find i_c .

6. The current through a $0.0047 \mu\text{F}$ capacitor is $i_c = 18 \cdot \mu\text{A} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_c .

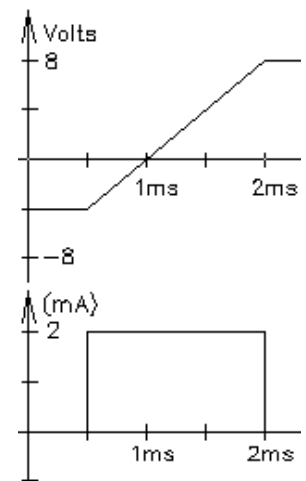7. A capacitor voltage and current are shown at right. What value is the capacitor?



Answers

1. a) $0.6 \mu\text{F}$ b) $0.015 \mu\text{F}$ c) $4.5 \mu\text{F}$
 2. a) 3.3 V 0.027 mJ b) 37.5 V 0.33 mJ c) 11 V 0.0411 mJ 5 V $2.75 \mu\text{J}$
 3. 1.8 V 0.6 V 2.4 V 4. -6 mA 12 mA ramp to -8 mA
 5. $i_c = 0.816 \text{ mA} \cdot \cos(200 \cdot t + \pi)$ 6. $v_c = 6.1 \cdot \text{V} \cdot \cos\left(628 \cdot t - \frac{3 \cdot \pi}{4}\right)$ 7. $0.25 \mu\text{F}$



Name: _____

ECE 2210 / 00 hw # 9



Due: Fri , 10/1/21

You will need another paper for your calculations, but you may want to hand this sheet in with your drawings.



1. Find L_{eq} in each case

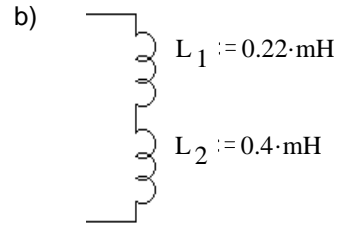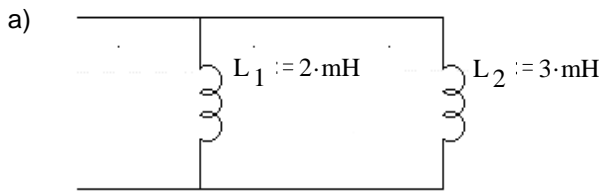

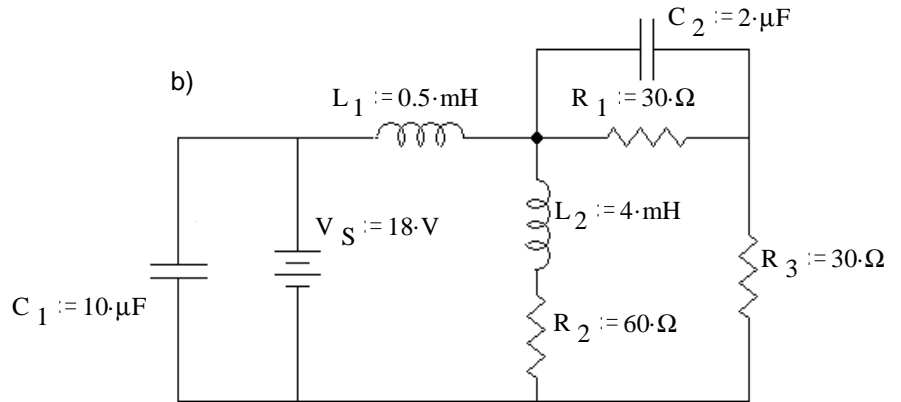
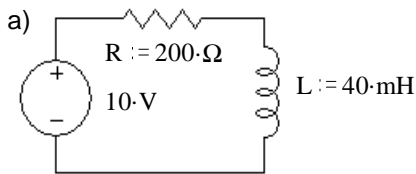
2. Find the stored energy in each capacitor and/or inductor under steady-state conditions. Note: Treat caps as opens and inductors as shorts to find DC voltages and currents.



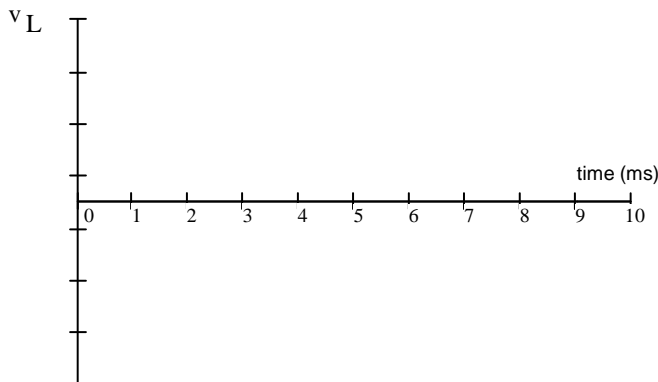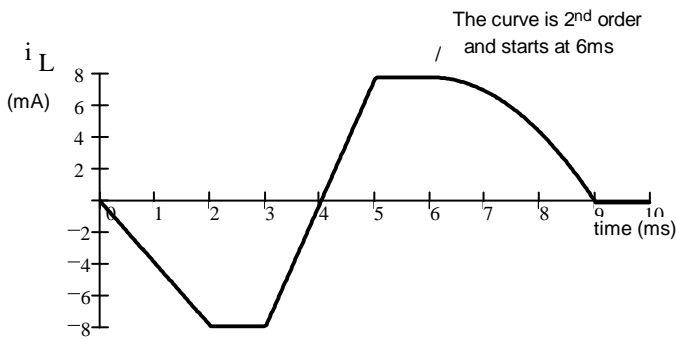3. The current waveform shown below flows through a 2 mH inductor. Make an accurate drawing of the voltage across it. Label your graph.



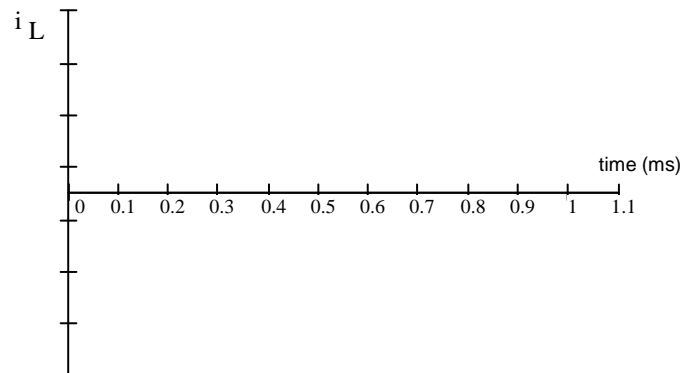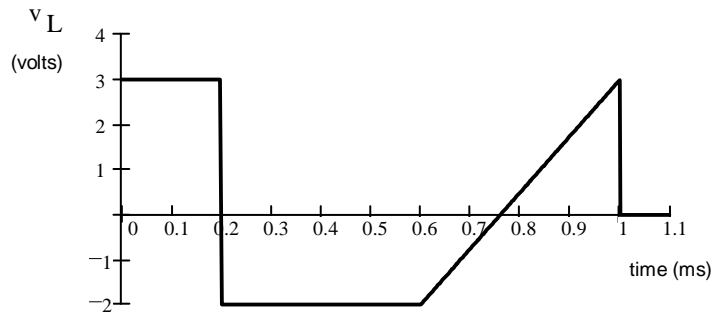4. The voltage across a 0.5 mH inductor is shown below. Make an accurate drawing of the inductor current. Label your graph. Assume the initial current is 0 mA.



ECE 2210 / 00 homework # 9


5. The voltage across a 1.2 mH inductor is $v_L = 4 \cdot \text{mV} \cdot \cos(300 \cdot t)$ find i_L .

6. The current through a 0.08 mH inductor is $i_L = 20 \cdot \text{mA} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_L .


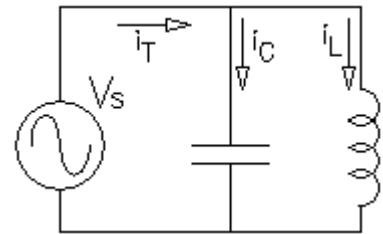
7. Refer to the circuit shown. Assume that V_s is a sinusoidal input voltage whose frequency can be adjusted. At some frequency of V_s this circuit can resonate. At that frequency $i_C(t) = -i_L(t)$. ($i_C(t)$ is 180 degrees out-of-phase with $i_L(t)$).

Show that resonance occurs at this frequency:

$$\omega_o = \frac{1}{\sqrt{L \cdot C}}, \quad f_o = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$



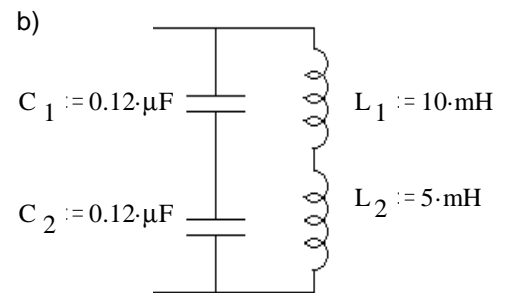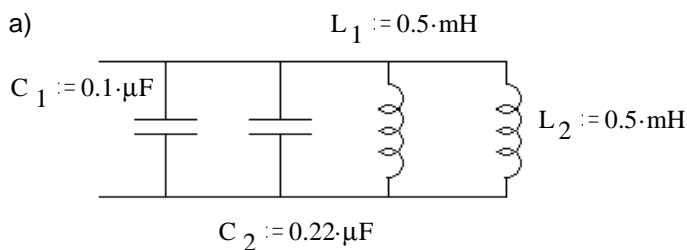8. Find the resonant frequency, f_o in each case.



Answers

1. 1.2·mH 0.62·mH 2. a) 0.05·mJ b) 1.62·mJ 0.081·mJ 0.09·mJ 0.18·mJ

3. Straight lines between the following points: (0ms,-8mV), (2ms,-8mV), (2ms,0mV), (3ms,0mV), (3ms,16mV), (5ms,16mV), (5ms,0mV), (6ms,0mV), (9ms,-10.67mV), (9ms,0mV), (10ms,0mV)

4. Straight lines between the following points: (0ms,0A), (0.2ms,1.2A), (0.6ms,-0.4A), curves until it's flat at (0.76ms, -0.72A), continues to curve up to (1ms, 0A), (1.1ms,0A)

5. $i_L = 11.1 \cdot \text{mA} \cdot \cos(300 \cdot t - 90\text{-deg})$ 6. $v_L = 1 \cdot \text{mV} \cdot \cos\left(628 \cdot t + \frac{1}{4} \cdot \pi\right)$

7. Assume a sinusoidal voltage, find i_C and i_L by integration and differentiation, and show that they are equal and opposite at the resonant frequency.

8. a) 17.79·kHz b) 5305·Hz