

Complex Numbers

ECE 2210 / 00

A.Stolp
10/18/00
1/12/06

$$j = \sqrt{-1} \quad \text{the imaginary number}$$

Rectangular Form $\mathbf{A} = a + b \cdot j$

$$\operatorname{Re}(\mathbf{A}) = a \quad \operatorname{Im}(\mathbf{A}) = b$$

Polar Form $\mathbf{A} = A \cdot e^{j \cdot \theta}$

$$\operatorname{Re}(\mathbf{A}) = A \cdot \cos(\theta) \quad \operatorname{Im}(\mathbf{A}) = A \cdot \sin(\theta)$$

Conversions $A = |\mathbf{A}| = \sqrt{a^2 + b^2}$

$$\theta = \arg(\mathbf{A}) = \operatorname{atan}\left(\frac{b}{a}\right)$$

$$a = A \cdot \cos(\theta) \quad b = A \cdot \sin(\theta)$$

$$\mathbf{A} = A \cdot e^{j \cdot \theta} = A \cdot \cos(\theta) + A \cdot \sin(\theta) \cdot j$$

$$\mathbf{A} = a + b \cdot j = \left(\sqrt{a^2 + b^2}\right) \cdot e^{j \cdot \operatorname{atan}\left(\frac{b}{a}\right)}$$

Special Cases $j := \sqrt{-1} = e^{j \cdot 90\text{-deg}}$ $\frac{1}{j} = -j = e^{-j \cdot 90\text{-deg}}$ $e^{j \cdot 0\text{-deg}} = 1$ $e^{-j \cdot 180\text{-deg}} = e^{-j \cdot 180\text{-deg}} = -1$
 $j \cdot e^{j \cdot \theta} = e^{j \cdot (\theta + 90\text{-deg})}$

Define a 2nd number: rect: $\mathbf{D} = c + d \cdot j$ polar: $\mathbf{D} = D \cdot e^{j \cdot \phi}$

Equality $\mathbf{A} = \mathbf{D}$ if and only if $a = c$ and $b = d$ OR $A = D$ and $\theta = \phi$

Addition and Subtraction $\mathbf{A} + \mathbf{D} = (a + b \cdot j) + (c + d \cdot j) = (a + c) + (b + d) \cdot j$

$$\mathbf{A} - \mathbf{D} = (a + b \cdot j) - (c + d \cdot j) = (a - c) + (b - d) \cdot j$$

Convert polars to rectangular form first

Multiplication and Division $\mathbf{A} \cdot \mathbf{D} = (a + b \cdot j) \cdot (c + d \cdot j) = (a \cdot c - b \cdot d) + (b \cdot c + a \cdot d) \cdot j$

$$\text{Rectangular: } \frac{\mathbf{A}}{\mathbf{D}} = \frac{a + b \cdot j}{c + d \cdot j} = \frac{a + b \cdot j \cdot c - d \cdot j}{c + d \cdot j \cdot c - d \cdot j} = \frac{a \cdot c + b \cdot d}{c^2 + d^2} + \frac{b \cdot c - a \cdot d}{c^2 + d^2} \cdot j$$

$$\text{Polar: } \mathbf{A} \cdot \mathbf{D} = A \cdot e^{j \cdot \theta} \cdot D \cdot e^{j \cdot \phi} = A \cdot D \cdot e^{j \cdot (\theta + \phi)}$$

$$\frac{\mathbf{A}}{\mathbf{D}} = \frac{A \cdot e^{j \cdot \theta}}{D \cdot e^{j \cdot \phi}} = \frac{A}{D} \cdot e^{j \cdot (\theta - \phi)}$$

Powers $\mathbf{A}^n = A^n \cdot e^{j \cdot n \cdot \theta} = A^n \cdot \cos(n \cdot \theta) + A^n \cdot \sin(n \cdot \theta) \cdot j$ Convert rectangulairs first, usually

Conjugates

complex number

$$\mathbf{A} = a + b \cdot j$$

$$\mathbf{A} = A \cdot e^{j \cdot \theta}$$

$$\mathbf{F} = \frac{3 + 5 \cdot j}{(2 - 6 \cdot j) \cdot e^{-j \cdot 40\text{-deg}}}$$

Conjugate

$$\overline{\mathbf{A}} = a - b \cdot j$$

$$\overline{\overline{\mathbf{A}}} = \mathbf{A}$$

$$\overline{\mathbf{A}} = A \cdot e^{-j \cdot \theta}$$

$$\overline{\mathbf{F}} = \frac{3 - 5 \cdot j}{(2 + 6 \cdot j) \cdot e^{-j \cdot 40\text{-deg}}}$$

Euler's equation

$$e^{j \cdot \alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$$

$$\text{OR: } \cos(\alpha) = \frac{e^{j \cdot \alpha} + e^{-j \cdot \alpha}}{2}$$

$$\sin(\alpha) = \frac{e^{j \cdot \alpha} - e^{-j \cdot \alpha}}{2 \cdot j}$$

$$e^{j \cdot (\omega \cdot t + \theta)} = \cos(\omega \cdot t + \theta) + j \cdot \sin(\omega \cdot t + \theta)$$

$$\operatorname{Re}[e^{j \cdot (\omega \cdot t + \theta)}] = \cos(\omega \cdot t + \theta)$$



If we freeze this at time $t=0$, then we can represent $\cos(\omega \cdot t + \theta)$ by $e^{j \cdot \theta}$

Calculus


Remember, when we write $e^{j \cdot \theta}$, we really mean $e^{j \cdot (\omega \cdot t + \theta)}$

$$\frac{d}{dt} \mathbf{A} = \frac{d}{dt} (A \cdot e^{j \cdot \theta}) = j \cdot \omega \cdot A \cdot e^{j \cdot \theta} = \omega \cdot A \cdot e^{j \cdot (\theta + 90\text{-deg})}$$
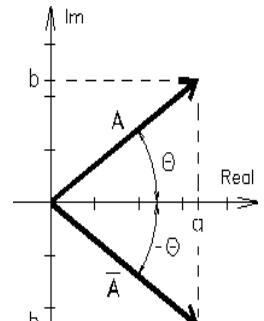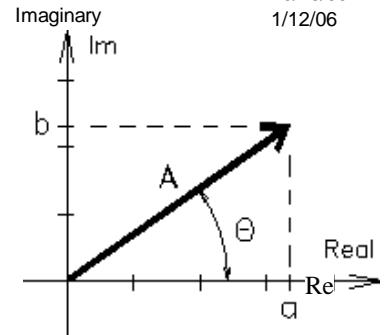
$$\int \mathbf{A} dt = \int A \cdot e^{j \cdot \theta} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j \cdot \theta} = \frac{1}{\omega} \cdot A \cdot e^{j \cdot (\theta - 90\text{-deg})}$$



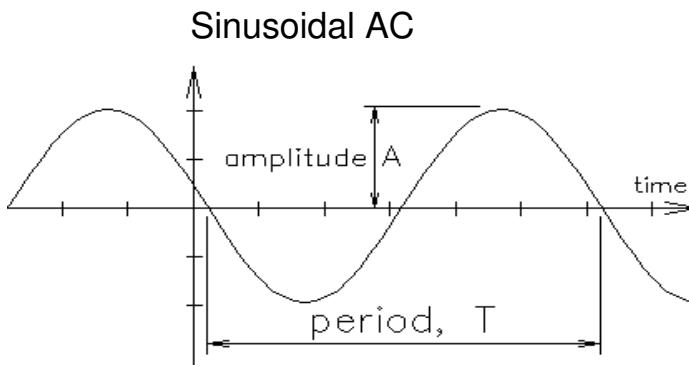Phasor analysis with impedances, For steady-state sinusoidal response ONLY



T = Period = repeat time

$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$


$$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi f$$

A = amplitude

$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360\text{-deg}$$

$$\text{or: } \phi = -\frac{\Delta t}{T} \cdot 2\pi \text{ rad}$$
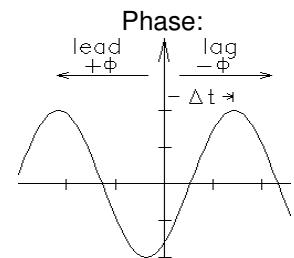
$$y(t) = A \cdot \cos(\omega \cdot t + \theta)$$



Phasor analysis

The math is all based on the Euler's equation

Euler's equation

$$e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$$

OR:


$$\cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$$

$$\sin(\theta) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$$

$$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j \cdot \sin(\omega t + \theta)$$

$$\text{Re}[e^{j(\omega t + \theta)}] = \cos(\omega t + \theta)$$

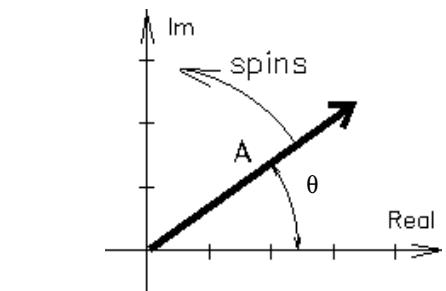If we freeze this at time $t=0$, then we can represent $\cos(\omega t + \theta)$ by $e^{j\theta}$



That's the phasor

Phasor

$$\text{voltage: } v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$$

$$V(\omega) = V_p \cdot e^{j\phi}$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega \cdot t + \phi)$$

$$I(\omega) = I_p \cdot e^{j\phi}$$

Phasors are used for adding and subtracting sinusoidal waveforms.

Ex1. Add the sinusoidal voltages $v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30\text{-deg})$

$$\text{and } v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15\text{-deg})$$

using phasor notation, draw a phasor diagram of the three phasors, then convert back to time domain form.

$$v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30\text{-deg})$$

$$V_1(\omega) = 4.5V \angle -30^\circ \quad \text{or: } V_1(\omega) = 4.5 \cdot V \cdot e^{-j30\text{deg}}$$

and

$$v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15\text{-deg})$$



$$V_2(\omega) = 3.2V \angle 15^\circ \quad \text{or: } V_2(\omega) = 3.2 \cdot V \cdot e^{j15\text{deg}}$$

I'm going to drop the (ω) notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain..

$$V_1 = 4.5V \angle -30^\circ \quad \text{or: } V_1 := 4.5 \cdot V \cdot e^{-j30\text{deg}}$$

$$V_2 = 3.2V \angle 15^\circ \quad \text{or: } V_2 := 3.2 \cdot V \cdot e^{j15\text{deg}}$$

Phasors are drawn on a complex plane.

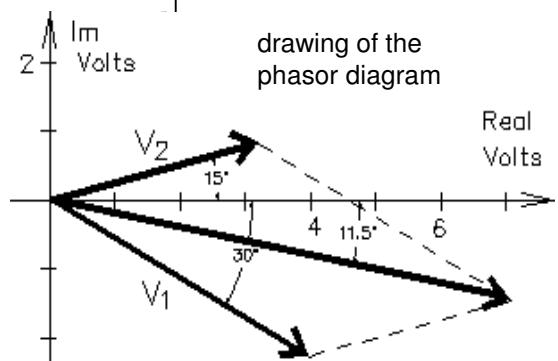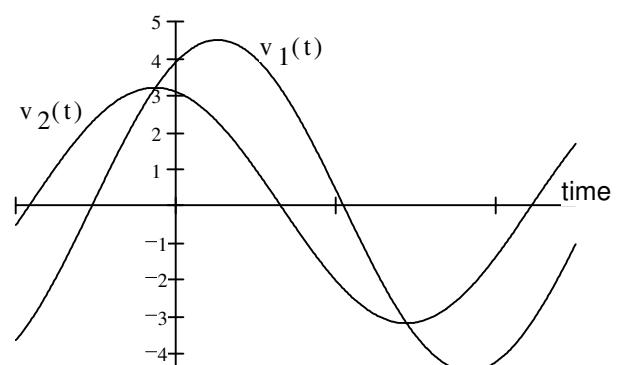

ECE 2210 / 00 Intro to Phasors p2

Add like vectors, first change to the rectangular form

$$\mathbf{V}_1 = 4.5 \text{ V} \angle -30^\circ \quad 4.5 \cdot \text{V} \cdot \cos(-30^\circ) = 3.897 \text{ V}$$

$$4.5 \cdot \text{V} \cdot \sin(-30^\circ) = -2.25 \text{ V}$$

$$\mathbf{V}_1 = 3.897 - 2.25j \text{ V} \quad \} \text{ add}$$

$$\mathbf{V}_2 = 3.2 \text{ V} \angle 15^\circ \quad 3.2 \cdot \text{V} \cdot \cos(15^\circ) = 3.091 \text{ V}$$

$$3.2 \cdot \text{V} \cdot \sin(15^\circ) = 0.828 \text{ V}$$

$$\mathbf{V}_2 = 3.091 + 0.828j \text{ V} \quad /$$

Add real parts:

$$3.897 + 3.091 = 6.988$$

$$\mathbf{V}_3 := \mathbf{V}_1 + \mathbf{V}_2$$

Add imaginary parts:

$$-2.25 + 0.828 = -1.422$$

$$\mathbf{V}_3 = 6.988 - 1.422j \text{ V} \quad \text{sum}$$

Change \mathbf{V}_3 back to polar coordinates:

$$\sqrt{6.988^2 + 1.422^2} = 7.131$$

$$\text{atan}\left(\frac{-1.422}{6.988}\right) = -11.502^\circ$$

OR, in Mathcad notation (you'll see these in future solutions):

$$|\mathbf{V}_3| = 7.131 \text{ V}$$

$$\arg(\mathbf{V}_3) = -11.5^\circ$$

Change \mathbf{V}_3 back to the time domain:

$$v_3(t) = v_1(t) + v_2(t) = 7.13 \cdot \cos(\omega t - 11.5^\circ) \text{ V}$$

Ex 2. Two sinusoidal voltages: $v_1(t) = 5 \cdot \text{V} \cdot \cos(\omega t + 36.87^\circ)$ and $v_2(t) = 3.162 \cdot \text{V} \cdot \cos(\omega t - 18.44^\circ)$

a) using phasor notation, find $v_3 = v_1 - v_2$

$$\mathbf{V}_1 := 5 \cdot \text{V} \cdot e^{j(36.87^\circ)}$$

$$5 \cdot \text{V} \cdot \cos(36.87^\circ) = 4 \text{ V}$$

$$5 \cdot \text{V} \cdot \sin(36.87^\circ) = 3 \text{ V}$$

$$\mathbf{V}_1 = 4 + 3j \text{ V}$$

$$\mathbf{V}_2 := 3.162 \cdot \text{V} \cdot e^{j(-18.44^\circ)}$$

$$3.162 \cdot \text{V} \cdot \cos(-18.44^\circ) = 3 \text{ V}$$

$$3.162 \cdot \text{V} \cdot \sin(-18.44^\circ) = -1 \text{ V}$$

$$\mathbf{V}_2 = 3 - j \text{ V}$$

$$\text{Subtract real parts: } 4 \cdot \text{V} - 3 \cdot \text{V} = 1 \text{ V}$$

$$\text{Subtract imaginary parts: } 3 \cdot \text{V} - (-1 \cdot \text{V}) = 4 \text{ V}$$

$$\mathbf{V}_3 := \mathbf{V}_1 - \mathbf{V}_2 \quad \mathbf{V}_3 = 1 + 4j \text{ V}$$

$$\text{Magnitude: } \sqrt{(1 \cdot \text{V})^2 + (4 \cdot \text{V})^2} = 4.123 \text{ V}$$


OR:

$$|\mathbf{V}_3| = 4.123 \text{ V}$$

$$\text{Angle: } \text{atan}\left(\frac{4 \cdot \text{V}}{1 \cdot \text{V}}\right) = 75.96^\circ$$

$$\arg(\mathbf{V}_3) = 75.96^\circ$$
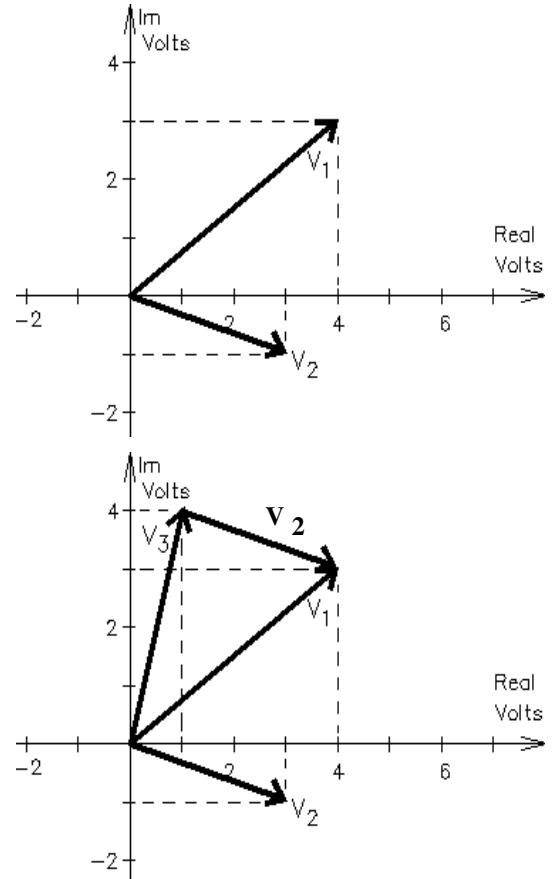
$$\text{So: } v_3(t) = v_1(t) - v_2(t) = 4.123 \cdot \text{V} \cdot \cos(\omega t + 75.96^\circ) \text{ V}$$



What about Capacitors and Inductors?

Capacitors and Inductors in AC circuits cause 90° phase shifts between voltages and currents because they integrate and differentiate. But... integration and differentiation is a piece-of-cake in phasors.

ECE 2210 / 00 Intro to Phasors p2

ECE 2210 / 00 Intro to Phasors p3

Calculus


$$\frac{d}{dt} \left[A \cdot e^{j(\omega t + \theta)} \right] = j \cdot \omega \cdot A \cdot e^{j(\omega t + \theta)} = \omega \cdot A \cdot e^{j(\omega t + \theta + 90^\circ)} = \omega \cdot A \cdot e^{j(\theta + 90^\circ)}$$

$$\int A \cdot e^{j(\omega t + \theta)} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j(\omega t + \theta)} = \frac{1}{\omega} \cdot A \cdot e^{j(\omega t + \theta - 90^\circ)} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90^\circ)}$$

Drop the ωt ($t=0$) to get:

Impedance (like resistance)

Inductor

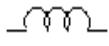

$$v_L = L \frac{d}{dt} i_L = L \frac{d}{dt} I_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot L \left[I_p \cdot e^{j(\omega t + \theta)} \right]$$

in phasor notation ----> $V_L(\omega) = j \cdot \omega \cdot L \cdot I(\omega)$

AC impedance

$$Z_L = j \cdot \omega \cdot L$$

Capacitor



$$i_C = C \frac{d}{dt} v_C = C \frac{d}{dt} V_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot C \left[V_p \cdot e^{j(\omega t + \theta)} \right]$$

in phasor notation ----> $I_C(\omega) = j \cdot \omega \cdot C \cdot V(\omega)$

$$V_C(\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot I(\omega)$$

$$Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

Resistor




$$v_R = i_R \cdot R$$

$$V_R(\omega) = R \cdot I(\omega)$$

$$Z_R = R$$

You can use impedances just like resistances as long as you deal with the complex arithmetic.
ALL the DC circuit analysis techniques will work with AC.

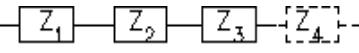series: 

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots$$

Example:

$f := 500 \cdot Hz$

$$\omega := 2 \cdot \pi \cdot f = \omega = 3141.6 \cdot \frac{rad}{sec}$$

$R := 200 \cdot \Omega$

$C := 0.6 \cdot \mu F$

$L := 80 \cdot mH$

$j \cdot \omega \cdot L = 251.327j \cdot \Omega$

$$\frac{1}{j \cdot \omega \cdot C} = -530.516j \cdot \Omega$$

$$Z_{eq} := R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 200 \cdot \Omega - 530.5 \cdot j \cdot \Omega + 251.3 \cdot j \cdot \Omega = 200 - 279.2j \cdot \Omega \quad \text{rectangular form}$$

$$\sqrt{(200 \cdot \Omega)^2 + (279.2 \cdot \Omega)^2} = 343.4 \cdot \Omega$$

$$\text{atan} \left(\frac{-279.2 \cdot \Omega}{200 \cdot \Omega} \right) = -54.38 \cdot deg$$

$$Z_{eq} = 343.4 \Omega / -54.4^\circ \quad \text{polar form}$$

If: $V := 12 \cdot V \cdot e^{j0^\circ}$

$$I := \frac{V}{Z_{eq}} = \frac{12 \cdot V}{343.4 \cdot \Omega} = 34.945 \cdot mA \quad \angle 0 - - 54.4 = 54.4 \quad deg$$

$$I = 34.95mA / 54.4^\circ = I = 20.348 + 28.405j \cdot mA$$

Voltage divider:


$$V_{Zn} = V_{total} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$

Note: $\frac{1}{j} = -j = 1 / -90^\circ$

Eg: $V_C := V \cdot \frac{j \cdot \omega \cdot C}{Z_{eq}} = 12 \cdot V \cdot e^{j0^\circ} \cdot \frac{530.516 \cdot e^{-j90^\circ} \cdot \Omega}{343.4 \cdot e^{-j54.38^\circ} \cdot \Omega}$

$$12 \cdot V \cdot \frac{530.516 \cdot \Omega}{343.4 \cdot \Omega} = 18.539 \cdot V \quad \angle 0 + - 90 - - 54.4 = -35.6 \quad deg$$


parallel:

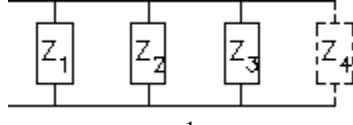

$$Z_{\text{eq}} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

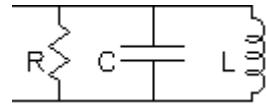Example:

$$f := 500 \cdot \text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 3141.6 \frac{\text{rad}}{\text{sec}}$$



$$L := 80 \cdot \text{mH}$$

$$R := 200 \cdot \Omega \quad C := 0.6 \cdot \mu\text{F} \quad j \cdot \omega \cdot L = 251.327j \cdot \Omega$$

$$\frac{1}{\omega \cdot L} = 3.979 \cdot 10^{-3} \frac{1}{\Omega}$$

$$\frac{1}{j \cdot \omega \cdot C} = -530.516j \cdot \Omega$$

$$\omega \cdot C = 1.885 \cdot 10^{-3} \frac{1}{\Omega}$$

$$\begin{aligned} Z_{\text{eq}} &:= \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C - \frac{j}{\omega \cdot L}} = \frac{1}{\frac{1}{200 \cdot \Omega} + 1.885 \cdot 10^{-3} \cdot j \cdot \frac{1}{\Omega} - 3.979 \cdot 10^{-3} \cdot j \cdot \frac{1}{\Omega}} \\ &= \frac{1}{\left(5 \cdot 10^{-3} - 2.094 \cdot 10^{-3} \cdot j\right) \cdot \frac{1}{\Omega} \cdot \left(5 \cdot 10^{-3} + 2.094 \cdot 10^{-3} \cdot j\right)} = 170.156 + 71.261j \cdot \Omega \\ &\quad 2.93848 \cdot 10^{-5} \end{aligned}$$

If you want the answer in polar form, it's easier to convert the denominator first.

$$\sqrt{\left(5 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2 + \left(2.094 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2} = 5.4 \cdot 10^{-3} \frac{1}{\Omega} \quad \text{atan}\left(\frac{-2.094 \cdot 10^{-3} \cdot \Omega}{5 \cdot 10^{-3} \cdot \Omega}\right) = -22.72^\circ$$

$$\frac{1}{5.4 \cdot 10^{-3} \cdot \frac{1}{\Omega}} = 185.185 \cdot \Omega$$

$$Z_{\text{eq}} = 185.2 \angle -22.7^\circ$$

$$\text{If: } V := 12 \cdot \text{V} \cdot e^{j \cdot 0^\circ} \quad I := \frac{V}{Z_{\text{eq}}} = \frac{12 \cdot \text{V}}{185.2 \cdot \Omega} = 64.795 \cdot \text{mA} \quad \angle 0 - 22.7 = -22.7^\circ$$

$$I = 60 - 25.127j \cdot \text{mA}$$

Current divider:

$$I_{Zn} = I_{\text{total}} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$


$$\text{Eg: } I_L := I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\frac{1}{R} + j \cdot \omega \cdot C + \frac{1}{j \cdot \omega \cdot L}} = I \cdot \frac{Z_{\text{eq}}}{j \cdot \omega \cdot L}$$

$$= 64.795 \cdot \text{mA} \cdot e^{j \cdot 22.7^\circ} \cdot \frac{185.2 \cdot e^{-j \cdot 22.7^\circ} \cdot \Omega}{251.327 \cdot e^{j \cdot 90^\circ} \cdot \Omega}$$

$$= 64.795 \cdot \text{mA} \cdot \frac{185.2 \cdot \Omega}{251.327 \cdot \Omega} = 47.747 \cdot \text{mA} \quad \angle 22.7 + -22.7 - 90 = -90^\circ \quad I_L = -47.746j \cdot \text{mA}$$

ECE 2210 / 00 Phasor Examples

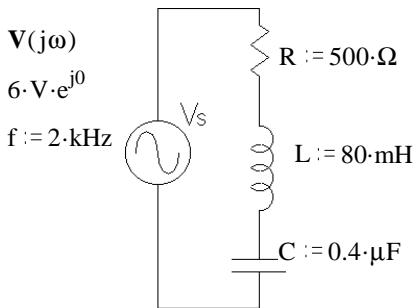Ex. 1 Find \mathbf{V}_R , \mathbf{V}_L , and \mathbf{V}_C in polar phasor form. $f := 2\text{-kHz}$



$$\omega := 2 \cdot \pi \cdot f \quad \omega = 12566.371 \frac{\text{rad}}{\text{sec}}$$

$$L := 80 \cdot \text{mH}$$

$$Z_L := j \cdot \omega \cdot L$$

$$Z_L = 1005.31i \cdot \Omega$$

$$C := 0.4 \cdot \mu\text{F}$$

$$Z_C := \frac{1}{j \cdot \omega \cdot C}$$

$$Z_C = -198.944j \cdot \Omega$$

$$Z_{\text{eq}} := R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}$$

$$Z_{\text{eq}} = 500 + 806.366j \cdot \Omega$$

find the current: (The hard way)

$$\begin{aligned} I := \frac{6 \cdot V \cdot e^{j0}}{Z_{\text{eq}}} &= \frac{6 \cdot V}{500 + 806.37j} \cdot \left(\frac{500 - 806.37j}{500 - 806.37j} \right) = \frac{6 \cdot V}{(500 + 806.37j) \cdot \Omega} \cdot \left(\frac{500 - 806.37j}{500 - 806.37j} \right) \\ &= \frac{6 \cdot V \cdot (500 - 806.37j)}{(500^2 + 806.37^2) \cdot \Omega} = \frac{3000 - 4838.2j}{900232.6} \cdot A = \left(\frac{3000}{900232.6} - \frac{4838.2j}{900232.6} \right) \cdot A = 3.332 - 5.374j \cdot \text{mA} \end{aligned}$$

It's much easier to convert the impedance to polar form first $\sqrt{500^2 + 806.37^2} = 948.806 \quad \text{atan}\left(\frac{806.37}{500}\right) = 58.198 \cdot \text{deg}$

$$\text{find the current: } I := \frac{6 \cdot V \cdot e^{j0}}{Z_{\text{eq}}} \quad \text{magnitude: } \frac{6 \cdot V}{948.8 \cdot \Omega} = 6.324 \cdot \text{mA}$$

$$\text{angle: } 0 \cdot \text{deg} - 58.2 \cdot \text{deg} = -58.2 \cdot \text{deg} \quad I = 6.324 \text{mA} / -58.2^\circ$$

find the magnitude

$$\mathbf{V}_R := I \cdot R \quad 6.324 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.162 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 0 \cdot \text{deg} = -58.2 \cdot \text{deg}$$

$$\mathbf{V}_R = 3.162 \text{V} / -58.2^\circ$$

$$\mathbf{V}_L := I \cdot Z_L \quad 6.324 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.356 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 90 \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$\mathbf{V}_L = 6.356 \text{V} / 31.8^\circ$$

$$\mathbf{V}_C := I \cdot Z_C \quad 6.324 \cdot \text{mA} \cdot (-199) \cdot \Omega = -1.258 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + (90) \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$\mathbf{V}_C = -1.258 \text{V} / 31.8^\circ$$

$$\text{OR: } 6.324 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.258 \cdot \text{V} \quad -58.2 \cdot \text{deg} + (-90) \cdot \text{deg} = -148.2 \cdot \text{deg} \quad \mathbf{V}_C = 1.258 \text{V} / -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find \mathbf{V}_C directly:

$$\begin{aligned} \mathbf{V}_C &:= \frac{\frac{1}{j \cdot \omega \cdot C}}{R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega \cdot C) + j \cdot \omega \cdot L \cdot (j \cdot \omega \cdot C) + 1} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega \cdot C) - \omega^2 \cdot L \cdot C + 1} \cdot 6 \cdot V \\ &= \frac{1}{(1 - \omega^2 \cdot L \cdot C) + j \cdot \omega \cdot R \cdot C} \cdot 6 \cdot V \quad (1 - \omega^2 \cdot L \cdot C) = -4.053 \\ &\quad j \cdot \omega \cdot R \cdot C = 2.513j \end{aligned}$$



$$= \frac{6 \cdot V}{-4.053 + 2.513j} \quad \text{Let's convert denominator to polar first}$$

$$\sqrt{(-4.053)^2 + 2.513^2} = 4.769 \quad \text{atan}\left(\frac{2.513}{-4.053}\right) = -31.8 \cdot \text{deg} \quad \text{NO!!}$$

$$\text{add } 180^\circ \\ 148.2 \cdot \text{deg}$$

but this is actually in the third quadrant,
so modify your calculator's results:

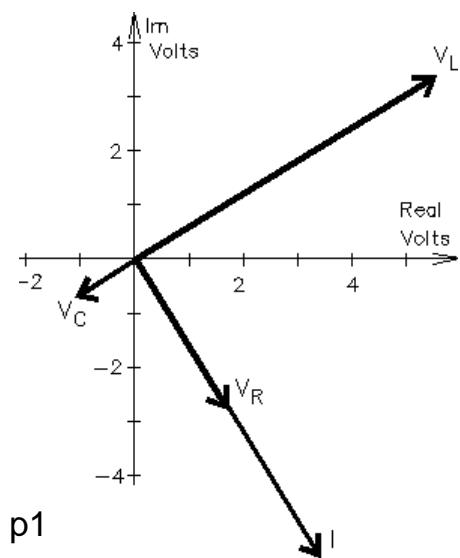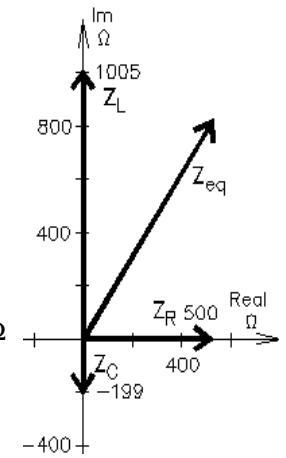
$$\begin{aligned} \text{magnitude: } \frac{6 \cdot V}{4.769} &= 1.258 \cdot \text{V} \quad \text{angle: } 0 \cdot \text{deg} - 148.2 \cdot \text{deg} = -148.2 \cdot \text{deg} \\ &= 1.258 \text{V} / -148.2^\circ \end{aligned}$$



ECE 2210 / 00 Phasor Examples p2

Ex. 2 a) Find Z_{eq} . $f := 2.5 \cdot \text{kHz}$ $\omega := 2 \cdot \pi \cdot f$ $\omega = 15708 \frac{\text{rad}}{\text{sec}}$
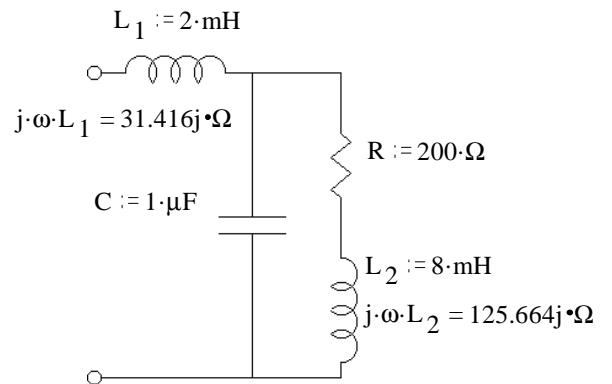
$$Z_{eq} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{j \cdot \omega \cdot C} + \frac{1}{R + j \cdot \omega \cdot L_2}}$$



But it's easier to split the problem up

Left branch

$$Z_L := \frac{1}{j \cdot \omega \cdot C} \quad Z_L = -63.662j \cdot \Omega$$

$$\frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} = j \cdot \omega \cdot C = 0.01571i \cdot \frac{1}{\Omega}$$

Right branch

$$Z_R := j \cdot \omega \cdot L_2 + R \quad Z_R = 200 + 125.664j \cdot \Omega$$

$$\frac{1}{200 + 125.664 \cdot j} = 3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3}j$$

$$\text{denominator: } j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2} = 0.01571 \cdot j + (3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3} \cdot j) = 3.585 \cdot 10^{-3} + 1.346 \cdot 10^{-2}i \quad \frac{1}{\Omega}$$

rectangular division:

$$\frac{1}{(3.585 \cdot 10^{-3} + 1.346 \cdot 10^{-2} \cdot j)} \cdot \frac{(3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2} \cdot j)}{(3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2} \cdot j)} = \frac{3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2} \cdot j}{1.94 \cdot 10^{-4}} = 18.479 - 69.381j \quad \Omega$$

$$(3.585 \cdot 10^{-3})^2 + (1.346 \cdot 10^{-2})^2 = 1.94 \cdot 10^{-4}$$

$$\text{add: } j \cdot \omega \cdot L_1 = 31.416j \cdot \Omega \quad 31.416 \cdot j + (18.479 - 69.381 \cdot j) = 18.479 - 37.965j \quad \Omega$$

$$\text{convert to polar (if needed): } \sqrt{18.48^2 + 37.97^2} = 42.228 \quad \text{atan}\left(\frac{-37.97}{18.48}\right) = -64.048 \cdot \text{deg} \quad Z_{eq} = 42.23 \Omega \angle -64.05^\circ$$

Another Way

Sometimes you might simplify a little before putting in numbers.

$$Z_{eq} := j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{j \cdot \omega \cdot C}} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C} = j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 + j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2)}$$

$$= j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$$

$$Z_{eq} = 31.416 \cdot j \cdot \Omega + \frac{(200 + 125.664 \cdot j) \cdot \Omega}{-0.974 + 3.142 \cdot j} \cdot \frac{(-0.974 - 3.142 \cdot j)}{(-0.974 - 3.142 \cdot j)} = 31.416 \cdot j \cdot \Omega + \frac{(200 + 125.664 \cdot j) \cdot (-0.974 - 3.142 \cdot j)}{0.974^2 + 3.142^2}$$

$$= 31.416 \cdot j \cdot \Omega + \frac{((200 \cdot -0.974) - 125.664 \cdot (-3.142)) + (125.664 \cdot -0.974) - 200 \cdot 3.142 \cdot j) \cdot \Omega}{0.974^2 + 3.142^2}$$

$$= 31.416 \cdot j \cdot \Omega + \frac{(200.036288 - 750.796736 \cdot j) \cdot \Omega}{10.82084} = 31.416 \cdot j \cdot \Omega + 18.486 \cdot \Omega - 69.384 \cdot j \cdot \Omega = 18.486 - 37.968j \cdot \Omega$$

$$\sqrt{18.49^2 + 37.97^2} = 42.233 \quad \text{atan}\left(\frac{-37.97}{18.49}\right) = -64.036 \cdot \text{deg} \quad Z_{eq} = 42.23 \Omega \angle -64.04^\circ$$

b) $V_{in} := 12 \cdot V \cdot e^{j \cdot 20^\circ \text{deg}}$ Find I_{L1} , V_C $I_{L1} := \frac{V_{in}}{Z_{eq}} = \frac{12 \cdot V}{42.23 \cdot \Omega} = 284.16 \cdot \text{mA}$ $20^\circ \text{deg} - (-64.04^\circ \text{deg}) = 84.04^\circ \text{deg}$

$$I_{L1} = 284 \text{mA} / 84.04^\circ$$

$$V_C := I_{L1} \cdot (18.479 - 69.381 \cdot j) \cdot \Omega = 284 \cdot \text{mA} \cdot \sqrt{18.479^2 + 69.381^2} \cdot \Omega = 20.391 \cdot V$$

$$84.04^\circ \text{deg} + \text{atan}\left(\frac{-69.381}{18.479}\right) = 8.954^\circ \text{deg}$$

$$V_C = 20.4V / 8.95^\circ$$

You could then use another voltage divider to find V_R or V_{L2} .

convert to rectangular (if needed): $20.391 \cdot V \cdot \cos(8.954^\circ \text{deg}) = 20.143 \cdot V$
 $20.391 \cdot V \cdot \sin(8.954^\circ \text{deg}) = 3.174 \cdot V$

$$V_C = 20.14 + 3.174 \cdot j \text{ V}$$

Another Way

To find V_C directly:

$$V_C := \frac{\frac{1}{R + j \cdot \omega \cdot L_2}}{\frac{1}{j \cdot \omega \cdot L_1} + \frac{1}{R + j \cdot \omega \cdot C}} \cdot V_{in}$$

--> math --> $V_C = 20.153 + 3.178j \text{ V}$ Same but for a little roundoff difference

c) Let's find I_{L2} . $Z_r = 200 + 125.664j \cdot \Omega = \sqrt{200^2 + 125.664^2} = 236.202$ $\text{atan}\left(\frac{125.664}{200}\right) = 32.142^\circ \text{deg}$

$$I_{L2} := \frac{V_C}{Z_r} = \frac{20.4 \cdot V \cdot e^{j \cdot 8.95^\circ \text{deg}}}{236.202 \cdot \Omega \cdot e^{j \cdot 32.142^\circ \text{deg}}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} / 8.95 - 32.142^\circ = 86.4 \text{mA} / -23.19$$

Another Way

Directly by Current divider: $I_{L2} := \frac{\frac{1}{R + j \cdot \omega \cdot L_2}}{\frac{1}{j \cdot \omega \cdot C} + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = \frac{1}{j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2) + 1} \cdot I_{L1} = \frac{I_{L1}}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$

real part is negative

denominator: $\sqrt{(1 - \omega^2 \cdot C \cdot L_2)^2 + (\omega \cdot C \cdot R)^2} = 3.289$ $\text{atan}\left(\frac{\omega \cdot C \cdot R}{1 - \omega^2 \cdot C \cdot L_2}\right) + 180^\circ \text{deg} = 107.224^\circ \text{deg}$

$$I_{L2} = \frac{284 \cdot \text{mA} \cdot e^{j \cdot 84.04^\circ \text{deg}}}{3.289 \cdot e^{j \cdot 107.224^\circ \text{deg}}} = \frac{284 \cdot \text{mA}}{3.289} / 84.04 - 107.224^\circ = 86.4 \text{mA} / -23.18^\circ$$

d) How about I_C ? $I_C := \frac{V_C}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} = V_C \cdot j \cdot \omega \cdot C = 20.4V / 8.95^\circ \cdot 0.015708 / 90^\circ \cdot \frac{1}{\Omega} = 320 \text{mA} / 98.95^\circ$

Another Way Could also be found directly by current divider: $I_C := \frac{j \cdot \omega \cdot C}{j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = 320 \text{mA} / 98.95^\circ$

Something Weird

I_C is greater than the input current (I_{L1}). What's going on?

The angle between I_C & I_{L2} is big enough that they somewhat cancel each other out (partially resonate).

Check Kirchoff's Current Law: $I_C + I_{L2} = 29.485 + 282.569j \cdot \text{mA}$ $= I_{L1} = 29.485 + 282.569j \cdot \text{mA}$
 yes

ECE 2210 / 00 Phasor Examples p4

Ex. 3 a) Find Z_2 .


$$I := 25 \cdot \text{mA} \cdot e^{j \cdot 10^\circ}$$

$$V_{\text{in}} := 10 \cdot \text{V} \cdot e^{-j \cdot 20^\circ}$$

$$Z_T := \frac{V_{\text{in}}}{I} = \frac{10 \cdot \text{V}}{25 \cdot \text{mA}} \cdot \underline{-20^\circ - 10^\circ} = 400 \Omega \cdot \underline{-30^\circ}$$

$$Z_T = 346.41 - 200j \cdot \Omega$$
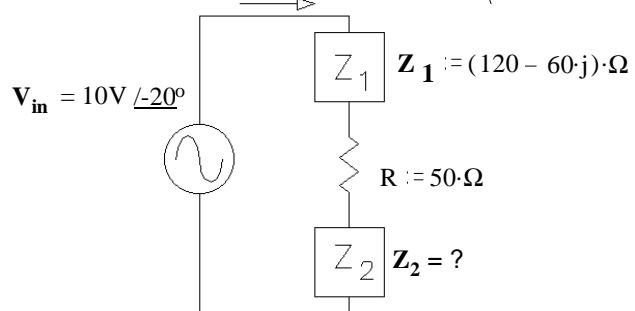
$$i(t) = 25 \cdot \text{mA} \cdot \cos \left(377 \cdot \frac{\text{rad}}{\text{sec}} \cdot t + 10^\circ \right)$$



$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j) \cdot \Omega - 50 \cdot \Omega - (120 - 60j) \cdot \Omega = 176.41 - 140j \cdot \Omega$$

- b) Circle 1: i) The source current leads the source voltage
ii) The source voltage leads the source current
- answer, because $10^\circ > -20^\circ$.

Ex 4. a) Find V_{in} in polar form.

$$I_Z := 100 \cdot \text{mA}$$

$$Z := (80 - 60j) \cdot \Omega$$


$$\omega := 1000 \cdot \frac{\text{rad}}{\text{sec}}$$

$$V_{\text{in}} := I_Z \cdot Z$$

$$V_{\text{in}} = 8 - 6j \cdot \text{V}$$

$$\sqrt{8^2 + 6^2} = 10 \quad \text{atan}\left(\frac{-6}{8}\right) = -36.87^\circ$$
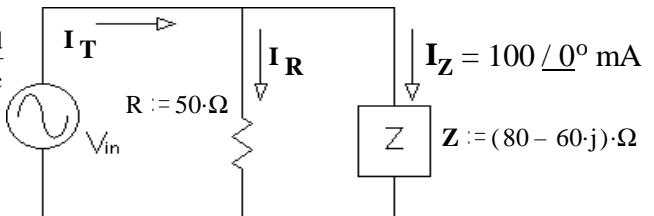
$$V_{\text{in}} = 10 \text{V} \cdot \underline{-36.9^\circ}$$



$$\text{b) Find } I_T \text{ in polar form.} \quad I_R := \frac{V_{\text{in}}}{R} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \underline{-36.9^\circ} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \cos(-36.9^\circ) + j \cdot \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \sin(-36.9^\circ) = 160 - 120j \cdot \text{mA}$$

$$I_T := I_R + I_Z = (160 - 120j) \cdot \text{mA} + 100 \cdot \text{mA} = 260 - 120j \cdot \text{mA}$$

$$\sqrt{260^2 + 120^2} = 286.356 \quad \text{atan}\left(\frac{-120}{260}\right) = -24.78^\circ \quad I_T = 286 \text{mA} \cdot \underline{-24.8^\circ}$$

- c) Circle 1: i) The source current leads the source voltage
ii) The source voltage leads the source current
- answer i), $-24.8^\circ > -36.9^\circ$


d) The impedance Z (above) is made of two components in series. What are they and what are their values?

$$Z = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.

$$R := \text{Re}(Z)$$

$$R = 80 \cdot \Omega$$

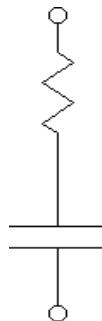

Must have a capacitor because the imaginary part is negative.

$$\text{Im}(Z) = -60 \cdot \Omega \quad = \frac{-1}{\omega \cdot C} \quad C := \frac{-1}{\omega \cdot \text{Im}(Z)}$$

$$C = 16.667 \cdot \mu\text{F}$$

ECE 2210 / 00 Phasor Examples p5

Ex. 5 The impedance $Z = 80 - 60j \Omega$ is made of two components in parallel. What are they and what are their values?

Must have a resistor because there is a real part.

Must have an capacitor because the imaginary part is negative.

$$Z = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C} \quad \frac{1}{Z} = \frac{1}{(80 - 60j) \cdot \Omega} \cdot \left(\frac{80 + 60j}{80 + 60j} \right) = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \cdot \frac{1}{\Omega}$$

$$\frac{1}{Z} = 0.008 + 0.006i \cdot \Omega^{-1} = \frac{1}{R} + j \cdot \omega \cdot C$$

$$\frac{1}{R} = .008 \cdot \frac{1}{\Omega}$$


$$R := \frac{1}{.008 \cdot \Omega^{-1}}$$

$$R = 125 \Omega$$

$$\omega \cdot C = .006 \cdot \frac{1}{\Omega}$$

$$C := \frac{.006 \cdot \Omega^{-1}}{\omega}$$

$$C = 6 \mu F$$

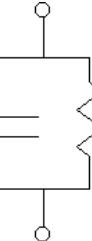

$$R = 125 \Omega$$

Positive imaginary parts would require inductors


Ex. 6 a) Find I_1

$$\omega := 20000 \frac{\text{rad}}{\text{sec}}$$

$$V_{in} := 20 \cdot V \cdot e^{j \cdot 30 \cdot \text{deg}}$$

$$I_1 := \frac{V_{in}}{R} = \frac{20 \cdot V}{250 \cdot \Omega} \cdot e^{j \cdot 30 \cdot \text{deg}} = 80 \cdot \text{mA} \cdot e^{j \cdot 30 \cdot \text{deg}}$$

polar division

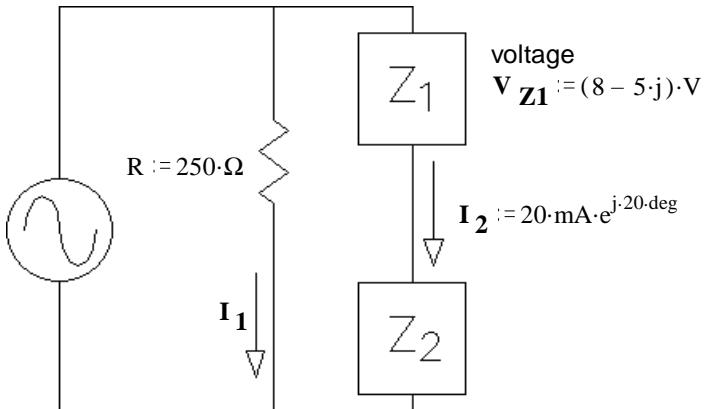

b) Circle 1:

i) V_{in} leads I_2

ii) V_{in} lags I_2

Why? Show numbers:

$$30 > 20$$

$$_____ < _____$$

c) Find Z_2 in polar form

Convert V_{in} to rectangular coordinates

$$20 \cdot V \cdot \cos(30 \cdot \text{deg}) = 17.321 \cdot V$$

$$20 \cdot V \cdot \sin(30 \cdot \text{deg}) = 10 \cdot V$$

pol to rect

$$V_{in} = 17.321 + 10j \cdot V$$

$$V_{Z2} := V_{in} - V_{Z1}$$

$$V_{Z2} = 9.321 + 15j \cdot V$$

subtract

$$\text{rect to pol} \quad \sqrt{9.321^2 + 15^2} = |V_{Z2}| = 17.66 \cdot V$$

$$\text{atan}\left(\frac{15}{9.321}\right) = \arg(V_{Z2}) = 58.145 \cdot \text{deg}$$

$$\text{div } Z_2 := \frac{V_{Z2}}{I_2} \quad \frac{17.66 \cdot V}{20 \cdot \text{mA}} = 883 \cdot \Omega \quad / \quad 58.145 \cdot \text{deg} - 20 \cdot \text{deg} = 38.145 \cdot \text{deg} \quad Z_2 = 883 \underline{/ 38.145^\circ} \Omega$$

$$Z_2 = 694.436 + 545.379j \cdot \Omega$$


Ex. 7 You need to design a circuit in which the "output" voltage leads the input voltage ($v_S(t)$) by 40° of phase.

a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } 40^\circ.$$

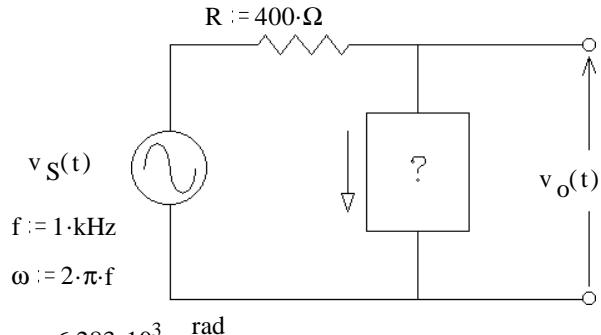This can only happen if the angle of Z_{box} is positive,
so Z_{box} is a inductor



b) Find its value. $V_o = \frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L} \cdot V_S$ angle $\frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L}$ is $90 - \text{atan}\left(\frac{\omega \cdot L}{R}\right) = 40^\circ$.

$$\text{So: } \text{atan}\left(\frac{\omega \cdot L}{R}\right) = 50^\circ \quad \frac{\omega \cdot L}{R} = \tan(50 \cdot \text{deg}) = 1.192 \quad L = \frac{R \cdot 1.192}{\omega} = 75.9 \cdot \mu\text{H}$$

c) Repeat if the "output" voltage should lag the input voltage ($v_S(t)$) by 20° of phase.

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } -20^\circ.$$


This can only happen if the angle of Z_{box} is negative,
so Z_{box} is a capacitor

$$V_o = \frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}} \cdot V_S \quad \text{angle } \frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}} \text{ is } -90 - \text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -90 - \text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right)$$

$$\text{atan}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -70^\circ. \quad -\frac{1}{\omega \cdot C \cdot R} = \tan(-70 \cdot \text{deg}) = -2.747 \quad C = \frac{1}{\omega \cdot R \cdot 2.747} = 0.145 \cdot \mu\text{F}$$

Ex. 8 Find V_o in the circuit shown. Express it as a magnitude and phase angle (polar).
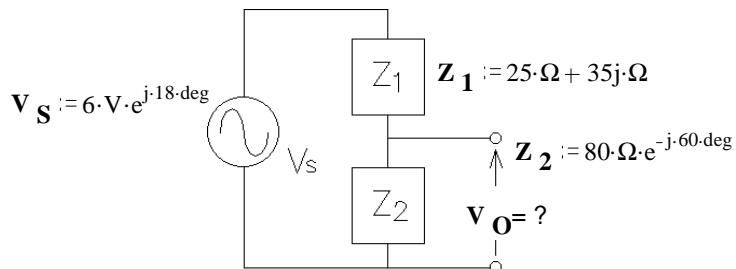
$$V_o := \frac{Z_2}{Z_1 + Z_2} \cdot V_S \quad \text{Simple voltage divider}$$



$$|Z_2| \cdot \cos(-60 \cdot \text{deg}) = 40 \cdot \Omega$$

$$|Z_2| \cdot \sin(-60 \cdot \text{deg}) = -69.282 \cdot \Omega$$

$$Z_2 = 40 - 69.282j \cdot \Omega$$

$$Z_1 + Z_2 = 25 \cdot \Omega + 35j \cdot \Omega + 40 \cdot \Omega - 69.282 \cdot j \cdot \Omega = 65 - 34.282j \cdot \Omega = 73.486 \cdot \Omega \cdot e^{-j27.81 \cdot \text{deg}}$$

$$V_o := \frac{Z_2}{Z_1 + Z_2} \cdot V_S = \frac{80 \cdot \Omega \cdot e^{-j60 \cdot \text{deg}}}{73.486 \cdot \Omega \cdot e^{-j27.81 \cdot \text{deg}}} \cdot (6 \cdot \text{V} \cdot e^{j18 \cdot \text{deg}}) = \frac{80 \cdot \Omega}{73.486 \cdot \Omega} \cdot 6 \cdot \text{V} \cdot e^{j(-60 - (-27.81) + 18) \cdot \text{deg}} = 6.53 \cdot \text{V} \cdot e^{-j14.2 \cdot \text{deg}}$$