

# ECE 2210/00 Exam 1 given: Fall 09


(The space between problems has been removed.)

1. (23 pts) Find the values below.  
Show your work

Note: feel free to show answers & work right on the schematic

- a)  $R_1 = ?$
- b)  $R_3 = ?$
- c)  $P_S = ?$

$R_2 := 150\cdot\Omega$

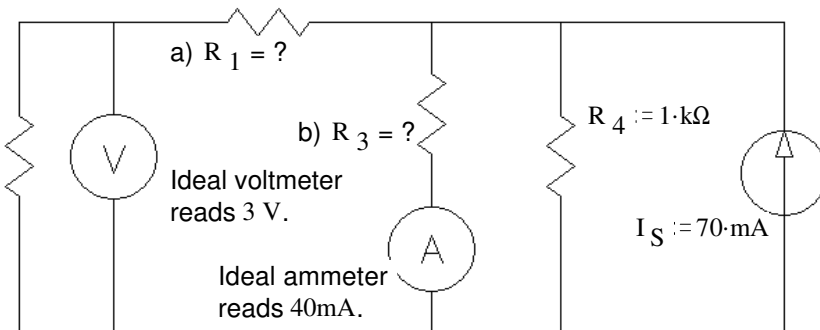


c)  $P_S = ?$

Remember, You were asked for 3 things,  $R_1$ ,  $R_3$ , &  $P_S$ . Circle your answers!

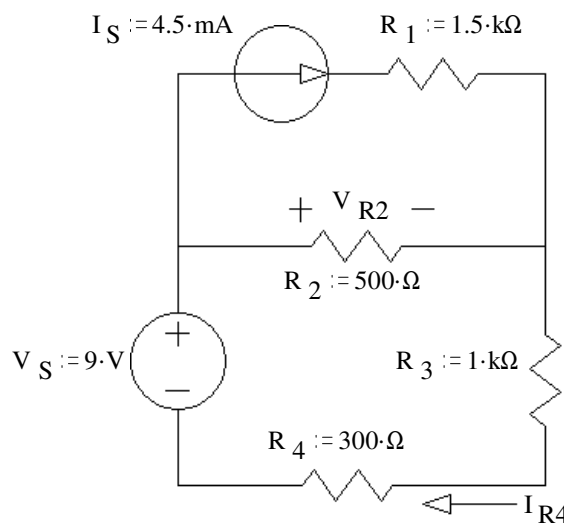2. (20 pts) Use the method of superposition to find the voltage across  $R_2$  ( $V_{R2}$ ) and the current through  $R_4$  ( $I_{R4}$ ).

Be sure to redraw the circuit as needed and to clearly show and **circle** your intermediate results.




Remember, You were asked for 2 things,  $V_{R2}$  and  $I_{R4}$ .

3. (18 pts) A rechargeable battery is shorted with an ideal ammeter. The ammeter reads 1.5 A. The ammeter is replaced with an ideal voltmeter. The voltmeter reads 12 V.

- a) Draw a simple, reasonable model of the battery pack using ideal parts. Find the value of each part.
- b) The battery is hooked to a load resistor and the terminal voltage drops to 10 V. Find the value of the load resistor.
- c) What voltage would be required to charge this battery at 200 mA?
- d) What is the maximum power this battery can supply to a load resistor ( $R_L$ )? You may use whatever  $R_L$  you want.

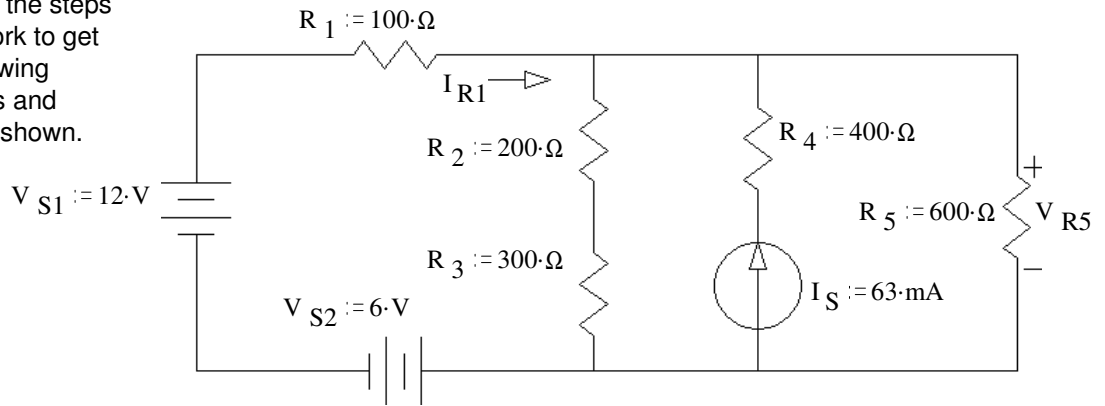4. (23 pts) Use nodal analysis to find the voltage across  $R_5$  ( $V_{R5}$ ) and the current through  $R_1$  ( $I_{R1}$ ).


You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



Remember, You were asked for 2 things,  $V_{R5}$  and  $I_{R1}$ .


5. (16 pts) For the waveform shown, find:

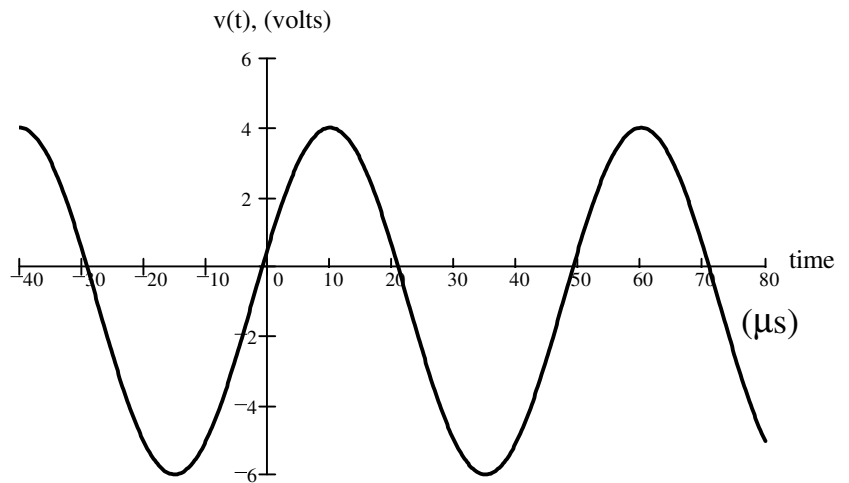- a) peak-to-peak voltage,  $V_{pp}$
- b) amplitude, A
- c) period, T
- d) frequency  $f$  in cycles/sec or Hz
- e) frequency  $\omega$  in radians/sec
- f) the phase angle in degrees
- g) a complete expression for  $v(t)$ , include numbers and units



**Answers**

1. a)  $350\cdot\Omega$     b)  $250\cdot\Omega$     c)  $700\cdot\text{mW}$                       2.  $2.5\cdot\text{V} - 1.625\cdot\text{V} = 0.875\cdot\text{V}$        $5\cdot\text{mA} + 1.25\cdot\text{mA} = 6.25\cdot\text{mA}$

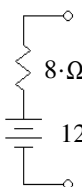3. a)     b)  $40\cdot\Omega$     4.  $9\cdot\text{V}$      $-30\cdot\text{mA}$   
 c)  $13.6\cdot\text{V}$     5. a)  $10\cdot\text{V}$     b)  $5\cdot\text{V}$     c)  $50\cdot\mu\text{s}$   
 d)  $4.5\cdot\text{W}$     d)  $20\cdot\text{kHz}$     e)  $1.26\cdot 10^5 \cdot \frac{\text{rad}}{\text{sec}}$     f)  $-72^\circ$   
 g)  $5\cdot\text{V}\cdot\cos\left(1.26\cdot 10^5 \cdot \frac{\text{rad}}{\text{sec}}\cdot t - 72\cdot\text{deg}\right) - 1\cdot\text{V}$

ECE 2210 / 00 Midterm #1 Arn Stolp

Name \_\_\_\_\_

Scores: \_\_\_\_\_

Pages 1&2 \_\_\_\_\_ of a possible 43 pts

Pages 3&4 \_\_\_\_\_ of a possible 41 pts

Page 5 \_\_\_\_\_ of a possible 16 pts

Total \_\_\_\_\_ of a possible 100 pts