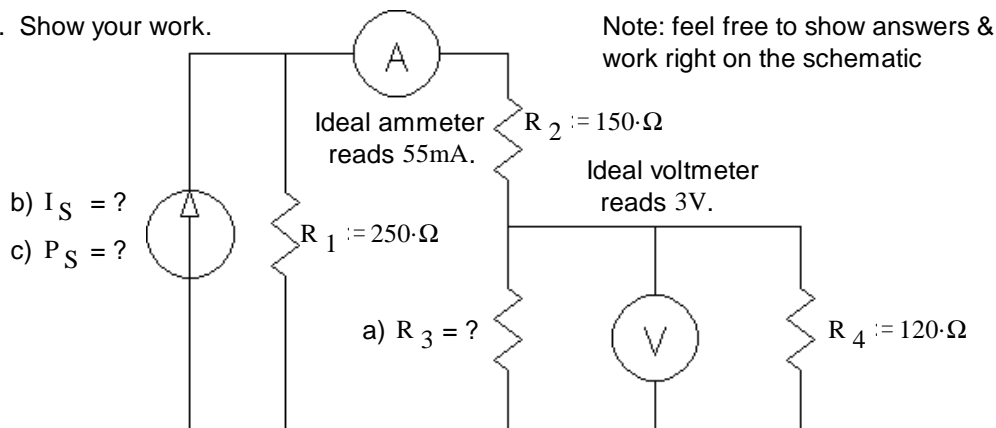


ECE 2210/00 Exam 1 given: Fall 13

(The space between problems has been removed.)


1. (23 pts) Find the values below. Show your work.

- a) $R_3 = ?$
- b) $I_S = ?$
- c) $P_S = ?$



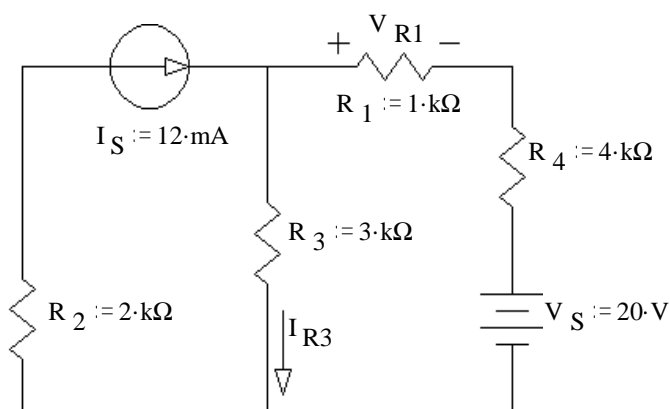
2. (23 pts) Use the method of superposition to find I_{R3} and V_{R1} .

Be sure to redraw the circuit as needed and to clearly show and **circle** your intermediate results.



3. (23 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is R_L .

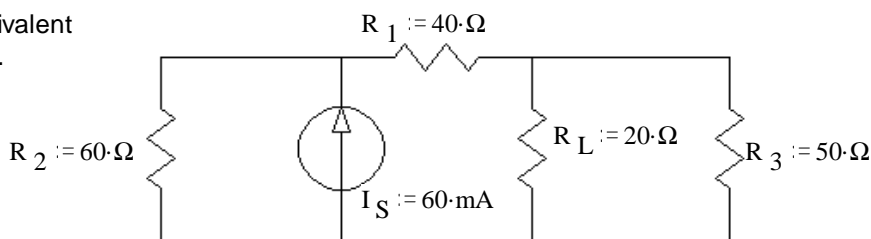
- b) Find and draw the Norton equivalent of the same circuit.
- c) Find the load current using your Thévenin equivalent circuit.




ECE 2210/00 Exam 1 Fall 13 p2

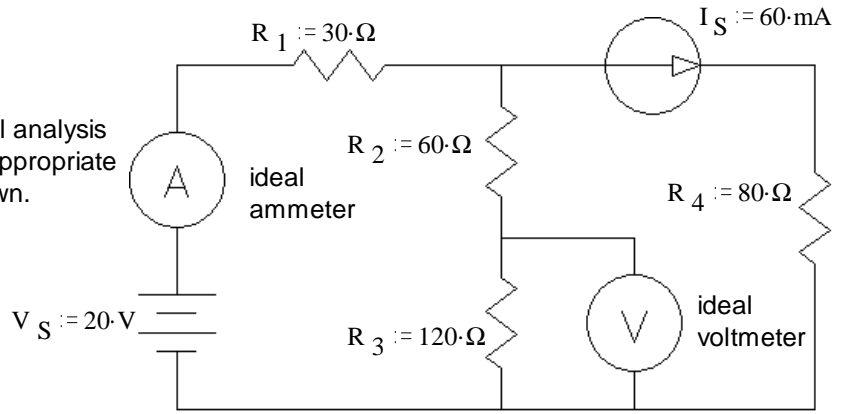4. (23 pts) Use nodal analysis to find the readings of the two ideal meters.



You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



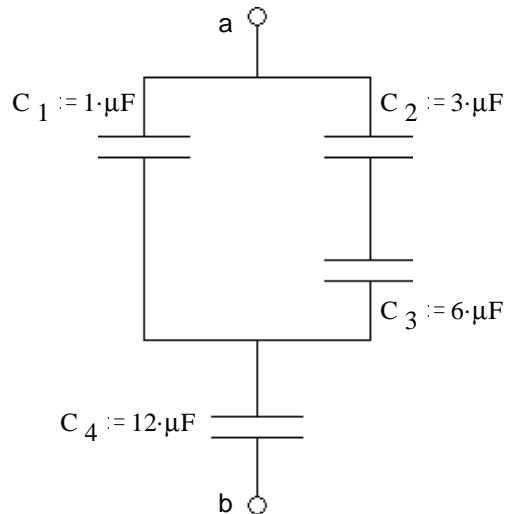5. (8 pts) Find C_{eq} between terminals a and b.



Answers

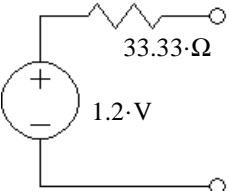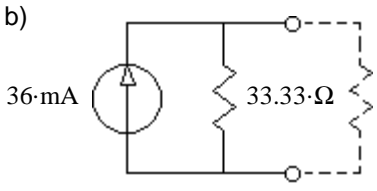1. a) $100\cdot\Omega$ b) $100\cdot\text{mA}$ c) $1125\cdot\text{mW}$ 2. $7.5\cdot\text{mA} + 2.5\cdot\text{mA} = 10\cdot\text{mA}$ $4.5\cdot\text{V} - 2.5\cdot\text{V} = 2\cdot\text{V}$
3. a)  b)  c) $22.5\cdot\text{mA}$ 4. $10.4\cdot\text{V}$ $146.7\cdot\text{mA}$
5. $2.4\cdot\mu\text{F}$