

ECE 2210/00 Exam 1 given: Fall 15


(The space between problems has been removed.)

Closed Book, Closed notes, Calculators OK, Show all work to receive credit


Circle answers, show units, and round off reasonably

1. (20 pts) Find the values below. Show your work, which may appear right on the schematic.

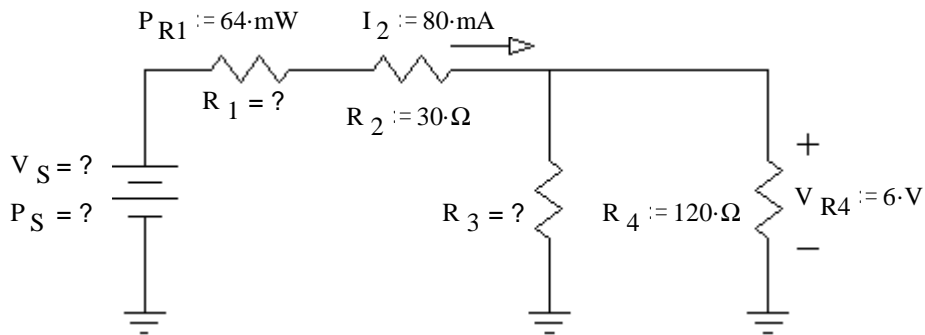
- a) $R_1 = ?$
- b) $R_3 = ?$
- c) $V_S = ?$
- d) $P_S = ?$



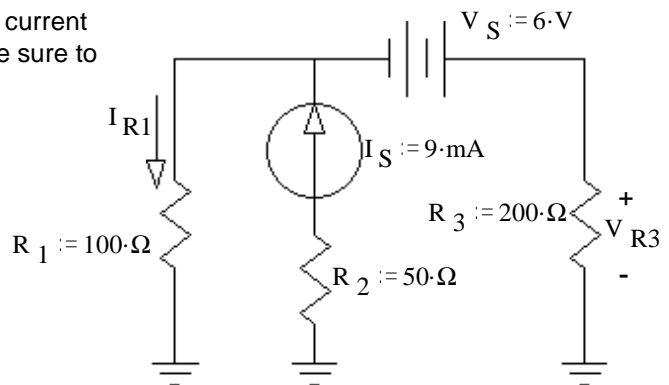2. (23 pts) Use the method of superposition to find the current through R_1 (I_{R1}) and the voltage across R_3 (V_{R3}). Be sure to clearly show and **circle** your intermediate results.



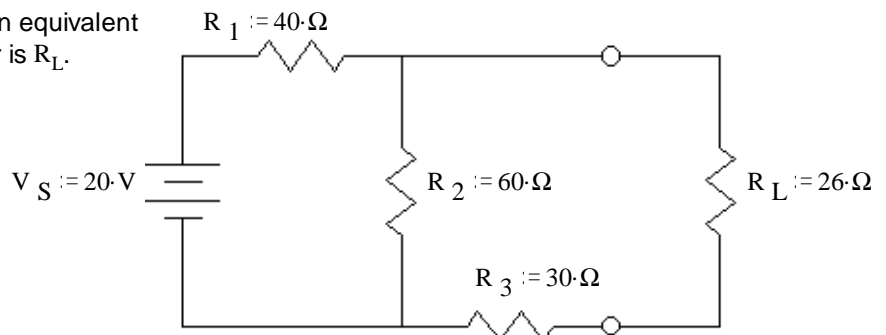
3. (24 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is R_L .



- b) Find and draw the Norton equivalent of the same circuit.
- c) Find the load current using your Thévenin equivalent circuit.
- d) Choose a different value of R_L so as to maximize the power dissipated in R_L . Find that maximum power, P_L .

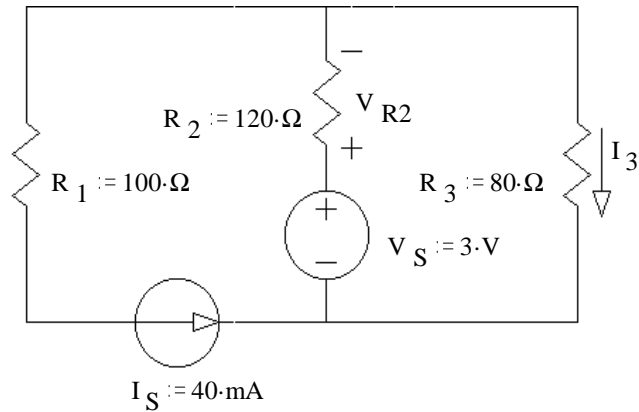
4. (23 pts) Use nodal analysis to find the voltage across R_2 (V_{R2}).

You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



b) Find the current through R_3 (I_3).

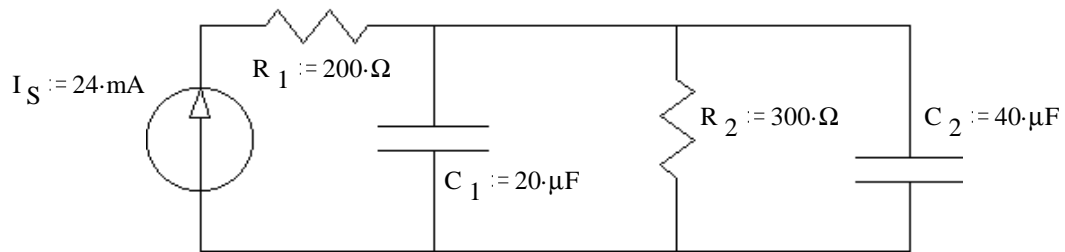5. (10 pts) The circuit below has been connected as shown for a long time



a) Find the voltage across each capacitor. $V_{C1} = ?$ $V_{C2} = ?$



b) How much energy is stored in capacitor C_2 .

Answers

1. a) $10 \cdot \Omega$ b) $200 \cdot \Omega$ c) $9.2 \cdot V$ $736 \cdot mW$

2. $-14 \cdot mA$ $4.6 \cdot V$

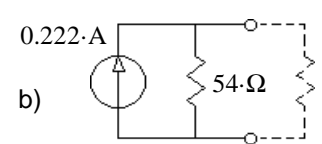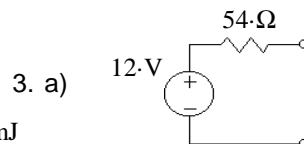4. $3.72 \cdot V$ $-9 \cdot mA$ 5. a) $7.2 \cdot V$ $7.2 \cdot V$ b) $1.04 \cdot mJ$



c) $150 \cdot mA$ d) $54 \cdot \Omega$ $667 \cdot mW$