

# ECE 2210/00 Exam 1 given: Fall 18


(The space between problems has been removed.)

Closed Book, Closed notes, Calculators OK, Show all work to receive credit


Circle answers, show units, and round off reasonably

1. (24 pts) Find the values below. Show your work. Feel free to show answers & work right on the schematic.

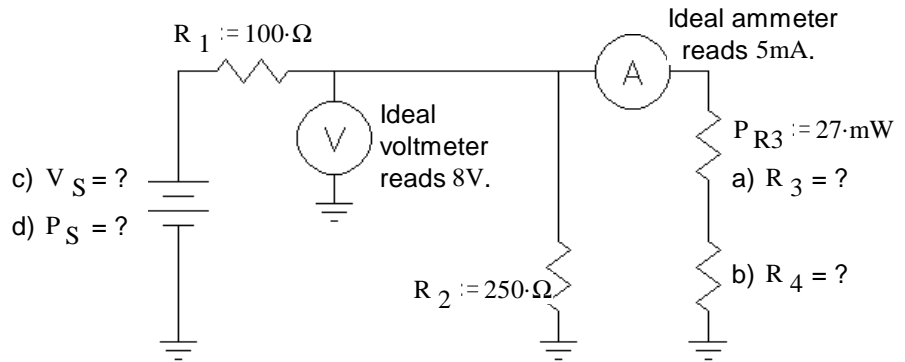
- a)  $R_3 = ?$
- b)  $R_4 = ?$
- c)  $V_S = ?$
- d)  $P_S = ?$



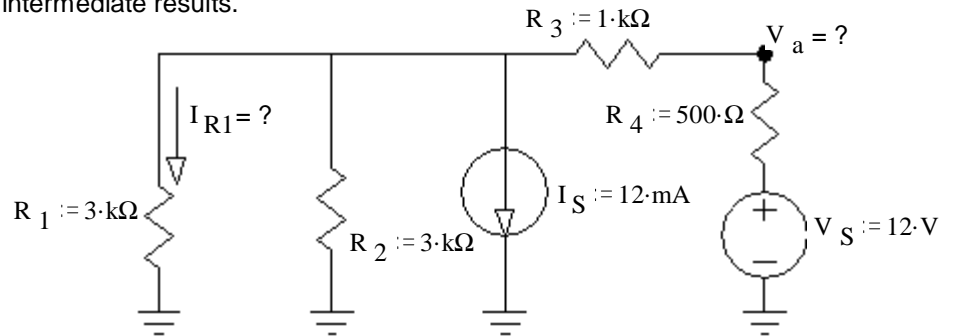2. (27 pts) Use the method of superposition to find the nodal voltage,  $V_a$  and the current through  $R_1$  ( $I_{R1}$ ). Be sure to clearly show and **circle** your intermediate results.




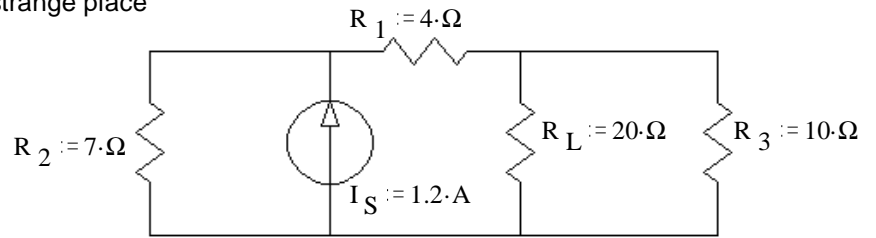3. (23 pts) a) Find and draw the Thévenin equivalent of the circuit shown.  
The load resistor is  $R_L$ . Be careful, it is in a strange place




- b) Find the load current using your Thévenin equivalent circuit.  
c) Select a load resistor to maximize the power delivered to the load and find that maximum power.  $P_{R_{Lmax}} = ?$

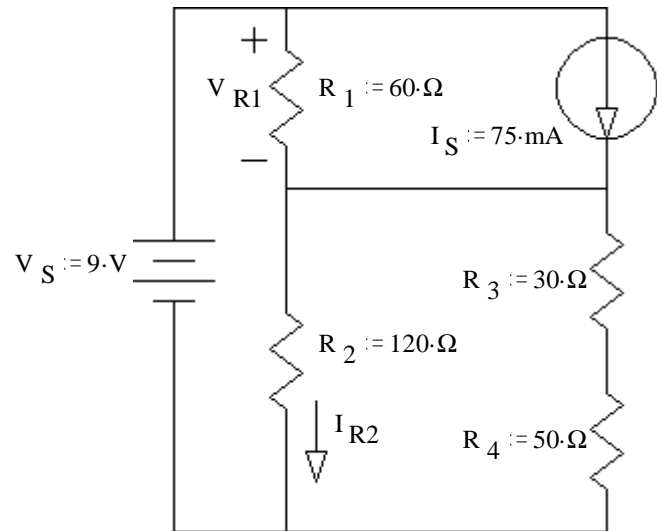4. (26 pts) Use nodal analysis to find  $V_{R1}$  and  $I_{R2}$ .  
You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



**Answers**

1. a)  $1080 \cdot \Omega$     b)  $520 \cdot \Omega$     c)  $11.7 \cdot V$     d)  $433 \cdot mW$

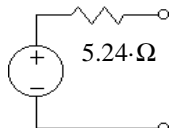3. a)     b)  $158.5 \cdot mA$   
c)  $5.24 \cdot \Omega$      $764 \cdot mW$

Folder Number \_\_\_\_\_

2.  $7 \cdot V$      $-1 \cdot mA$   
4. a)  $3.8 \cdot V$     b)  $43.33 \cdot mA$