


ECE 2210 / 00

Exam 1 Information

Useful Information


KCL, Kirchhoff's Current Law

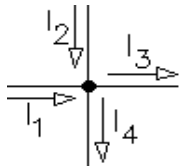$I_{in} = I_{out}$ of any point, part, or section




KVL, Kirchhoff's Voltage Law

$V_{gains} = V_{drops}$ around any loop

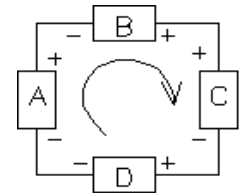


Node = all points connected by wire, all at same voltage (potential)

Ohm's law (resistors)

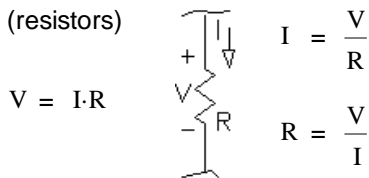

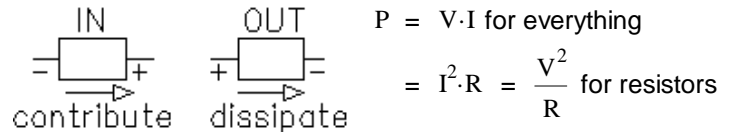
Power $P_{IN} = P_{OUT}$ for resistor circuits



Maximum power transfer: $R_L = R_{Th}$

Load = Thevenin's

Resistors

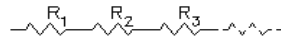


series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

Voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

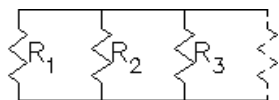parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$



Exactly the **same voltage** across each resistor


current divider:

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

Superposition and Thevenin

To zero out a source: Voltage source \Rightarrow short Current source \Rightarrow open

Basic AC

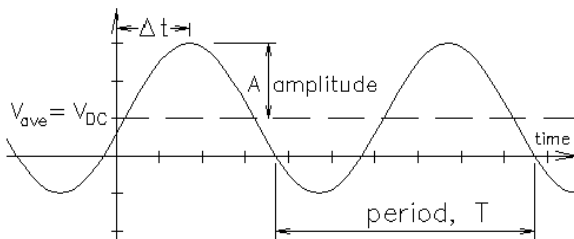

$$f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$\omega = 2\pi \cdot f \quad \phi = -\frac{\Delta t}{T} \cdot 360 \cdot \text{deg}$$

$$v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$$

current is similar

Capacitors

parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$

series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$

$$W_C = \frac{1}{2} \cdot C \cdot V_C^2$$