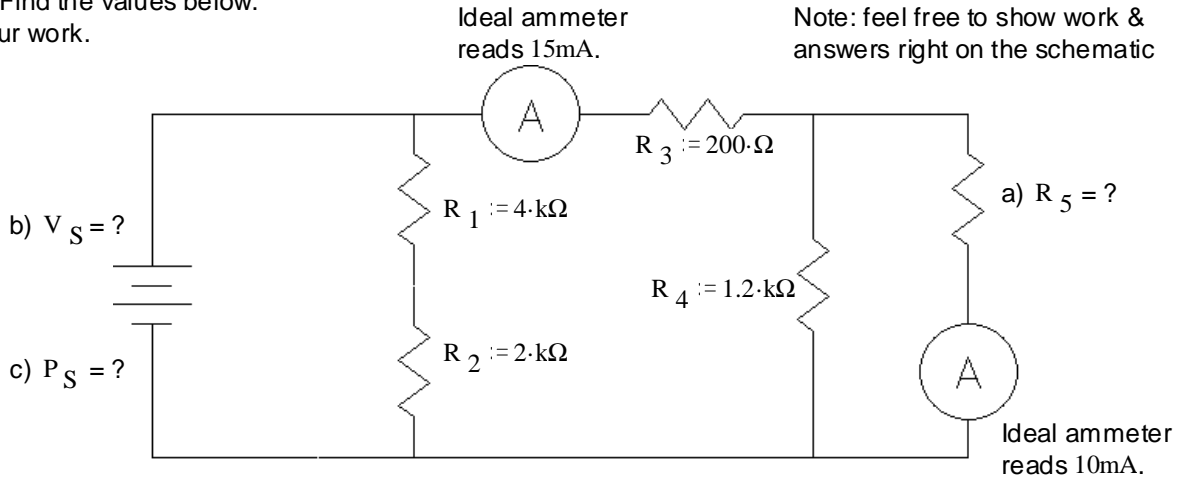


ECE 2210/00 Exam 1 given: Spring 10 (The space between problems has been removed.)


1. (21 pts) Find the values below.
Show your work.

- a) $R_5 = ?$
- b) $V_S = ?$
- c) $P_S = ?$




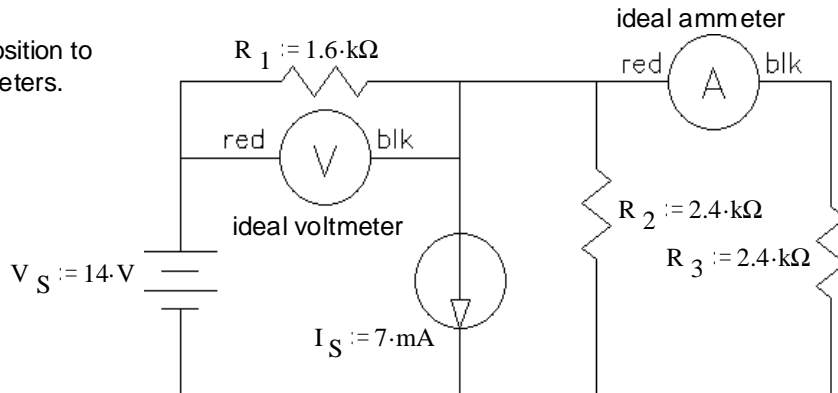2. (22 pts) Use the method of superposition to find the readings of the two ideal meters.

Be sure to redraw the circuit as needed and to clearly show and **circle** your intermediate results.



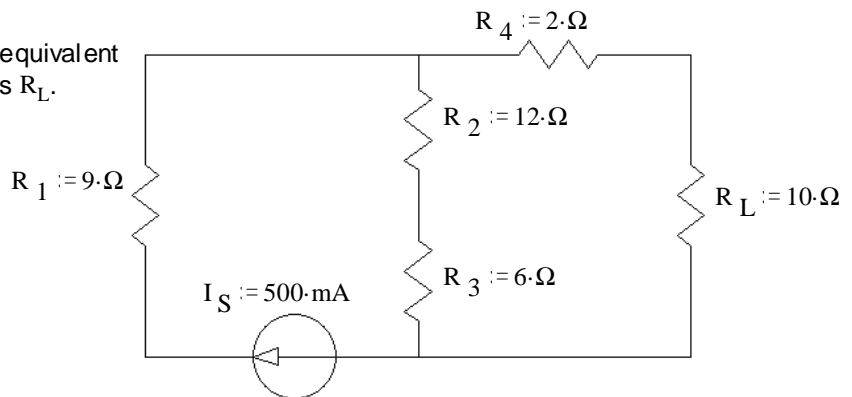3. (22 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is R_L .




- b) Find the load current using your Thévenin equivalent circuit.
- c) Find and draw the Norton equivalent of the same circuit.
- d) Find the load voltage using your Norton equivalent circuit.

ECE 2210/00 Exam 1 Spring 10 p2

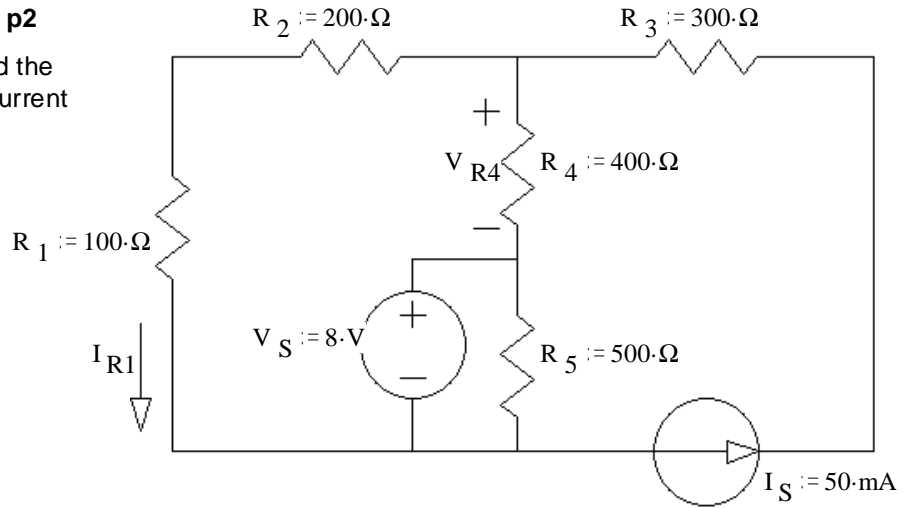
4. (19 pts) Use nodal analysis to find the voltage across R_4 (V_{R4}) and the current through R_1 (I_{R1}).

You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



5. (16 pts) For the waveform shown, find:
INCLUDE UNITS IN YOUR ANSWERS

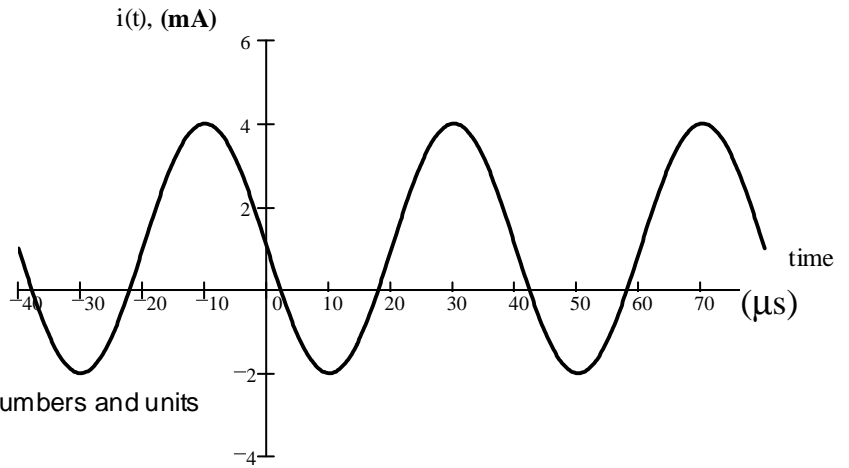- a) peak-to-peak current, I_{pp}
- b) amplitude, A
- c) period, T
- d) frequency f in cycles/sec or Hz
- e) frequency ω in radians/sec
- f) the phase angle in degrees
- g) a complete expression for $i(t)$, include numbers and units



Answers

1. a) $600\cdot\Omega$ b) $9\cdot V$ c) $149\cdot mW$ 2. $0.5\cdot mA$ $12.8\cdot V$

3. a) b) $300\cdot mA$ c) d) $3\cdot V$

4. a) $4\cdot V$
b) $40\cdot mA$

5 a) $6\cdot mA$ b) $3\cdot mA$ c) $40\cdot \mu s$ d) $25\cdot kHz$ e) $1.57\cdot 10^5 \cdot \frac{rad}{sec}$
f) 90° g) $3\cdot mA \cdot \cos\left(1.57\cdot 10^5 \cdot \frac{rad}{sec} \cdot t + 90\cdot deg\right) + 1\cdot mA$

ECE 2210 / 00 Midterm #1 Arn Stolp

Name _____

Scores:

Pages 1&2 _____ of a possible 43 pts

Pages 3&4 _____ of a possible 41 pts

Page 5 _____ of a possible 16 pts

Total _____ of a possible 100 pts