

# ECE 2210/00 Exam 1 given: Spring 20


(The space between problems has been removed.)

Closed Book, Closed notes, Calculators OK, Show all work to receive credit

Circle answers, show units, and round off reasonably


1. (26 pts) Find the values below.  
Show your work, which may appear right on the schematic.

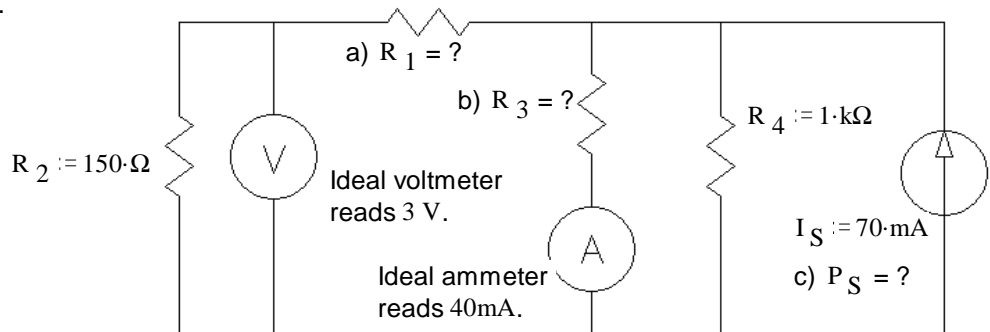- a)  $R_1 = ?$
- b)  $R_3 = ?$
- c)  $P_S = ?$



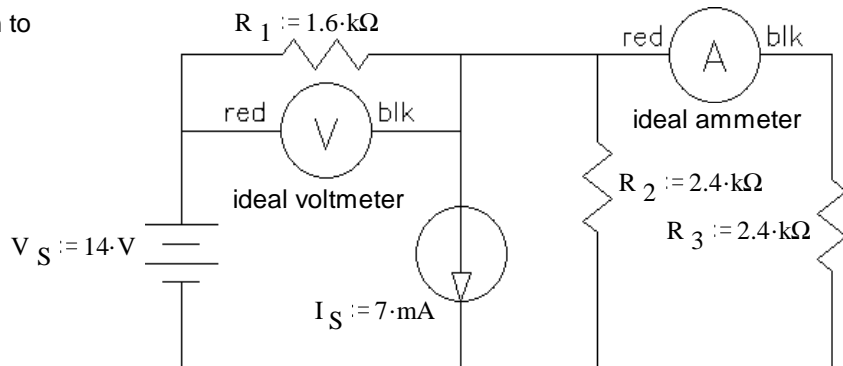
2. (24 pts) Use the method of superposition to find the readings of the two ideal meters.

Be sure to redraw the circuit as needed and to clearly show and **circle** your intermediate results.



ECE 2210/00 Exam 1 Spring 20 p2

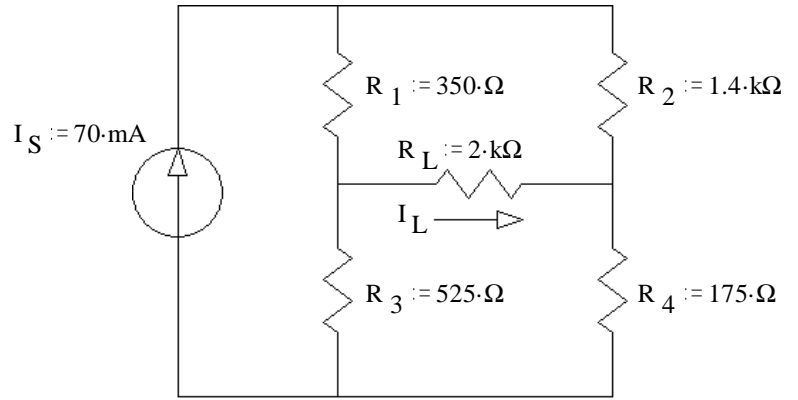3. (26 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is  $R_L$ .




b) Find the load current using your Thévenin equivalent circuit.

c) Choose a different value of  $R_L$  so as to maximize the power dissipated in  $R_L$ . Find that maximum power  $P_{RLmax} = ?$

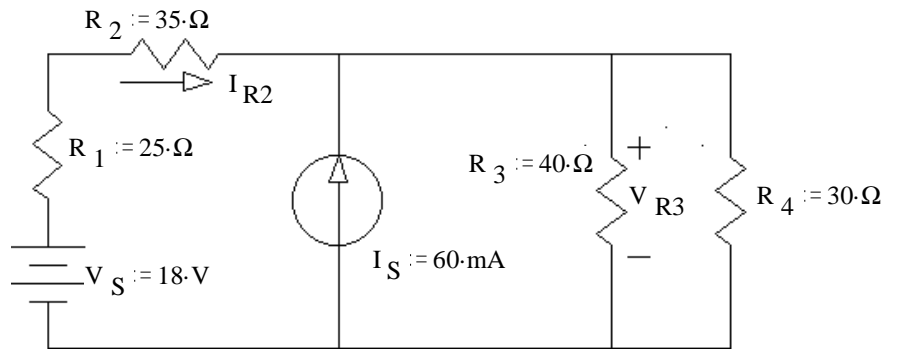4. (24 pts) Use nodal analysis to find the voltage  $V_{R3}$  and the current  $I_{R2}$ .

You **MUST** show all the steps of nodal analysis work to get credit, including drawing appropriate symbols and labels on the circuit shown.



**Answers**

1. a)  $350 \cdot \Omega$     b)  $250 \cdot \Omega$     c)  $0.7 \cdot W$

2.  $0.5 \cdot mA$      $12.8 \cdot V$

3. a)  $19.25 \cdot V$     b)  $7.7 \cdot mA$     c)  $500 \cdot \Omega$      $185 \cdot mW$

4. a)  $4.8 \cdot V$     b)  $220 \cdot mA$

**Folder Number** \_\_\_\_\_

