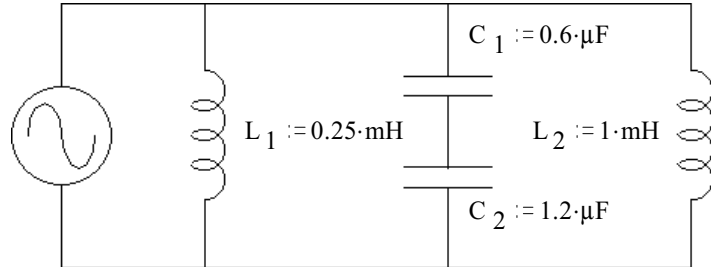


ECE1050/60 Exam 2 given: Fall 03

(The space between problems has been removed.)

1. (9 pts) The voltage across a 0.8 mH inductor is $v_L(t) = 0.6 \cdot V \cdot \cos(20000 \cdot t + 30 \cdot \text{deg})$
 find $i_L(t)$, express it as a cosine wave with the correct phase angle.



2. (10 pts) Find the resonant frequency (or frequencies) of the circuit (in cycles/sec or Hz).



3. (19 pts) The voltage across a 0.03 μF capacitor is shown below. Make an accurate drawing of the capacitor current. Label the y-axis of your graph (I've already done the x-axis).

Note: You will be graded on the accuracy of your plot at 0, 2, 2, and 8 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

$C := 0.03 \cdot \mu\text{F}$

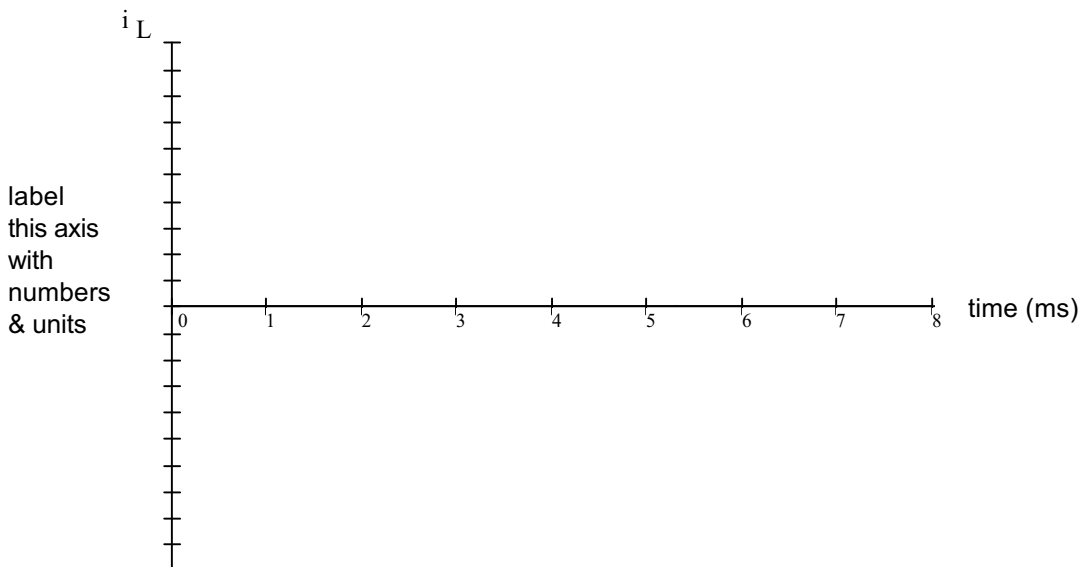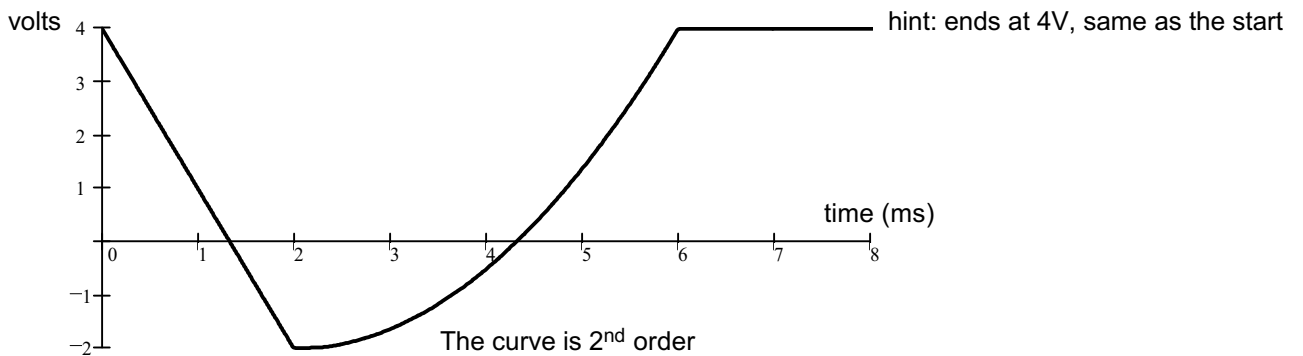


ECE1050/60 Exam 2 Fall 03 p2

4. (23 pts) a) The switch has been in the open position for a long time and is closed (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $i_L(t)$, including all the constants that you find.


b) What is i_L at 0.25ms?

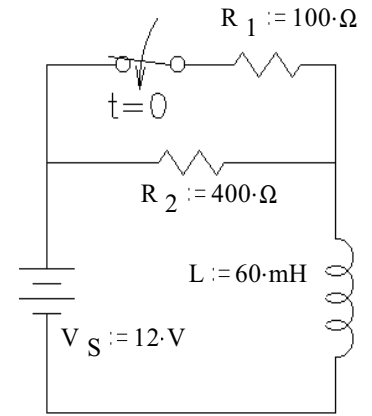c) At time $t = 0.25\text{ms}$ the switch is opened again. Find the complete expression for $i_L(t')$, where t' starts at $t = 0.25\text{ms}$. Be sure to clearly show the time constant.



5. (21 pts)

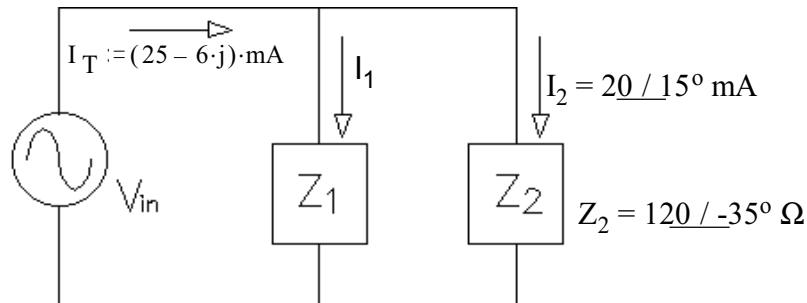a) Find Z_1 . For partial credit, you must show work and/or intermediate results.



b) To make Z_1 in the simplest way, what part(s) would you need? Just circle the needed part(s), don't find the values.

- | | | | | |
|-------------------|-------------------|-----------|--------------|----------------|
| resistor | capacitor | inductor | power supply | current source |
| Thevenin resistor | Ideal transformer | voltmeter | ammeter | scope |

c) Circle 1: i) I_2 leads the source voltage (V_{in})

ii) I_2 lags the source voltage (V_{in})


2. (18 pts) Z_{eq} is the total impedance between the two terminals.

Find Z_{eq} in simple polar or rectangular form (give me numbers).

For partial credit, you must show work and/or intermediate results.

Hint: First find an expression for Z_{eq} without any numbers, just in terms of j , ω , L , C , & the R 's and simplified that (get j 's out of denominators).

$f := 10 \cdot \text{kHz}$

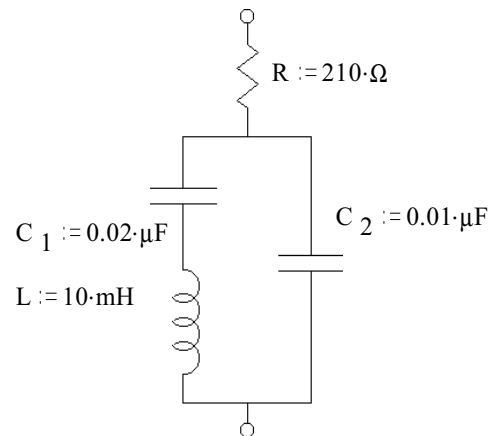

Answers

1. $i_L(t) = 37.5 \cdot \text{mA} \cdot \cos(20000 \cdot t - 60 \cdot \text{deg})$

2. 17.8-kHz

3. (0ms, -0.09mA), (2ms, -0.09mA), (2ms, 0mA), (6ms, 0.09mA), (6ms, 0mA), (8ms, 0mA)

4.a) $150 \cdot \text{mA} - 120 \cdot \text{mA} \cdot e^{-\frac{t}{0.75 \cdot \text{ms}}}$

b) 64-mA

c) $30 \cdot \text{mA} + 34 \cdot \text{mA} \cdot e^{-\frac{t}{150 \cdot \mu\text{s}}}$

5.a) $Z_1 = 191 \Omega / 43.1^\circ$

b) resistor & inductor

c) i)

6. $Z_{eq} = 259 \Omega / -35.8^\circ$

ECE 1050/60 Exam 2

Name _____

Scores:

Page 1&2 _____ of a possible 39 pts

Page 3&4 _____ of a possible 43 pts

Page 5 _____ of a possible 18 pts

Total _____ of a possible 100 pts