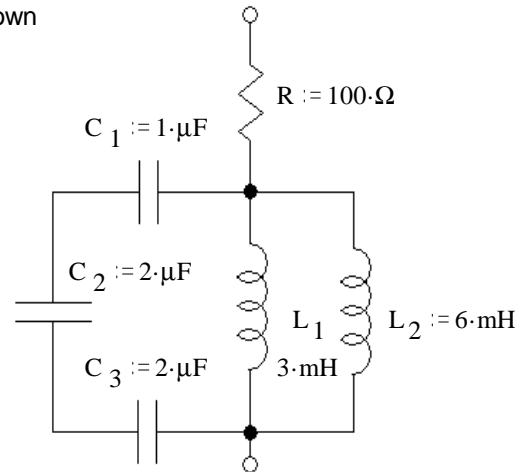



ECE 2210/00 Exam 2 given: Fall 10

(The space between problems has been removed.)

1. (11 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



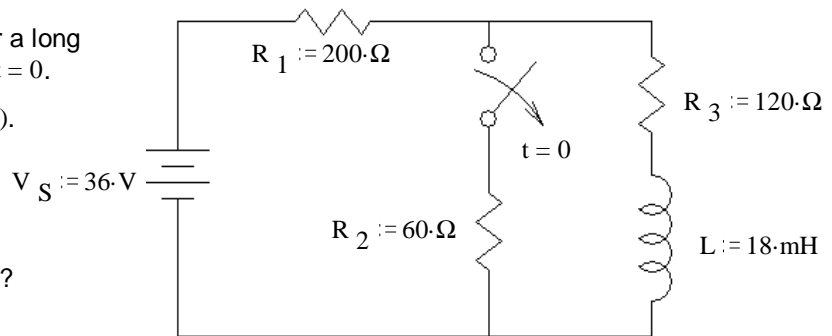
2. (26 pts) The switch has been closed for a long time and is opened (as shown) at time $t = 0$.



- a) Find the complete expression for $i_L(t)$.
- b) Find i_L at time $t = 1.5\tau$. $i_L(1.5\tau) = ?$
- c) At time $t = 1.5\tau$ the switch is closed again. Will the time constant be different now? If yes, find the new time constant.

3. (25 pts) For partial credit, you must show work and/or intermediate results.

- a) Find I_2

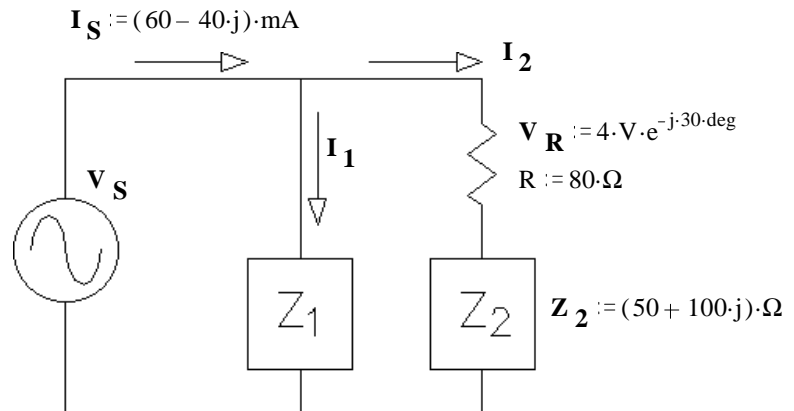


- b) Find V_S

- c) Find I_1 in polar form.

4. (20 pts) Find Z_{eq} in simple polar form (give me numbers & units).

$f := 220 \text{ Hz}$

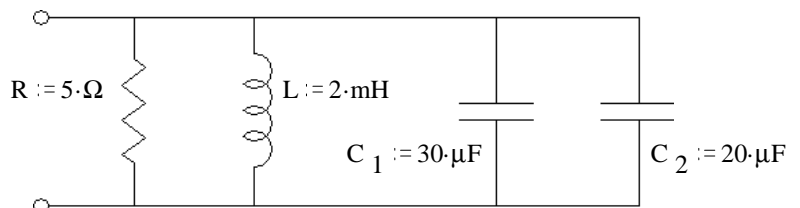

ECE 2210/00 Exam 2 Fall 10 p2


5. 18 pts) The voltage across a capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 4, 9 and 10 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.


You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

That is: **Start with the interger and/or differential equations for the capacitor!**

$$C := 3 \cdot \mu\text{F}$$

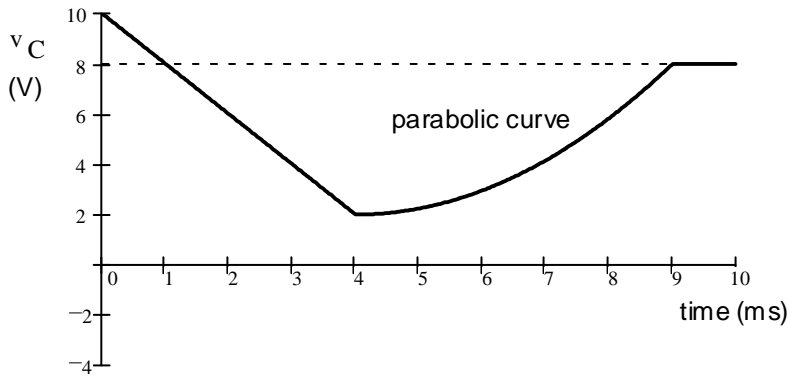

label
this axis
with
numbers
& units

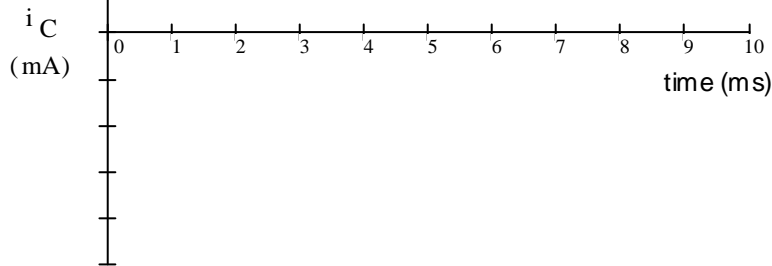

Answers

1. 5033-Hz 2. a) $112.5 \cdot \text{mA} - 62.5 \cdot \text{mA} \cdot e^{\frac{-t}{56.25 \cdot \mu\text{s}}}$ b) 98.6-mA c) $108.3 \cdot \mu\text{s}$

3. a) 50mA $\angle -30^\circ$ b) $(8.13 + 1.08 \cdot j) \cdot \text{V}$ c) 22.4mA $\angle -41.9^\circ$

4. $2.82 \Omega \angle 55.6^\circ$

5. 0 - 4ms: flat at -6mA

4ms - 9ms: ramps up from 0 to 7.2mA

Beyond 9ms: flat at 0A

