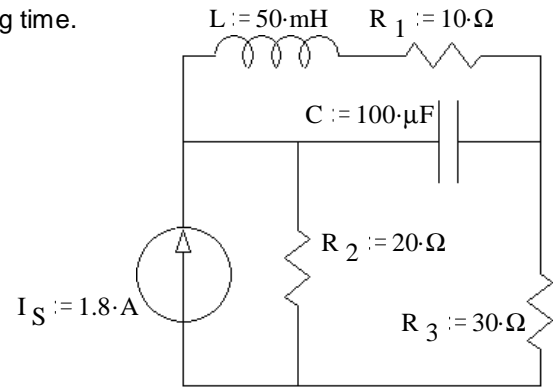


ECE 2210/00 Exam 2 given: Fall 19

(The space between problems has been removed.)


1. (13 pts) The following circuit has been connected as shown for a long time.

Find the energy stored in the capacitor and in the inductor.
Also show the values of the voltage(s) and current(s) necessary to answer this question.



2. (30 pts) The switch has been closed for a long time and is opened (as shown) at time $t = 0$.

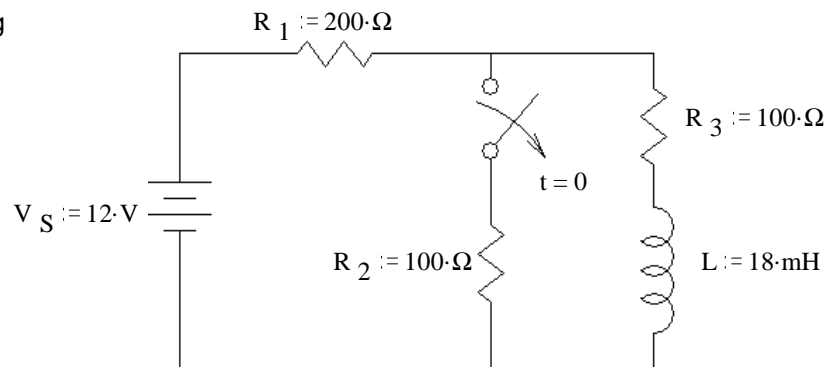
a) Find the complete expression for $i_L(t)$.



b) What is i_L when $t = 1.2\tau$? $i_L(1.2\tau) = ?$


c) At time $t = 1.2\tau$ the switch is closed again. Find the complete expression for $i_L(t')$, where t' starts at $t = 1.2\tau$.
Be sure to clearly show the time constant.

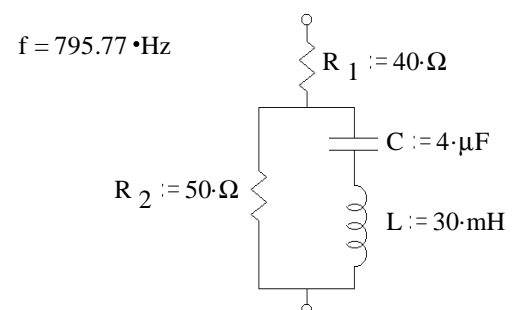3. (17 pts) Find Z_{in} in simple polar form (give me numbers).
For partial credit, you must show work and/or intermediate results.



ECE 2210/00 Exam 2 Fall 19 p2

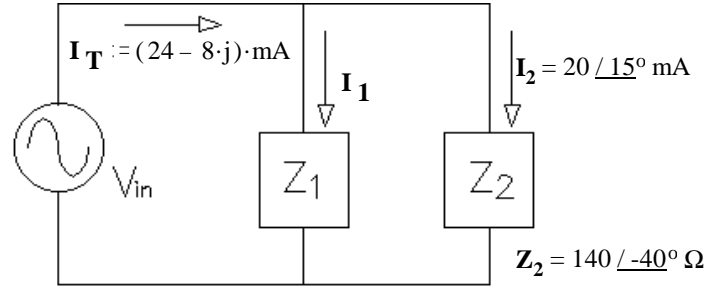4. (22 pts) a) Find V_{in} . For partial credit, you must show work and/or intermediate results.



b) Find Z_1 in polar form.

c) To make Z_1 in the simplest way, what part(s) would you need? Just circle the needed part(s), don't find the values.


resistor	capacitor	inductor	power supply	current source
Thevenin resistor		Ideal transformer	voltmeter	ammeter
				scope

d) i) I_2 leads the source voltage (V_{in})
 Circle 1: ii) I_2 lags the source voltage (V_{in}) by _____ degrees give number

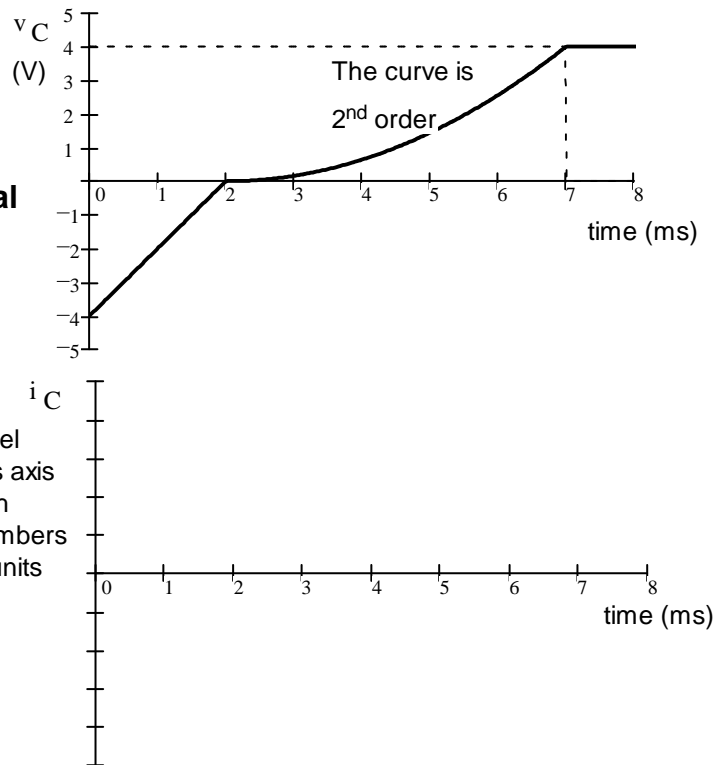5. (18 pts) The voltage across a $5 \mu F$ capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph. $C := 5 \cdot \mu F$

Note: You will be graded on the accuracy of your plot at 0, 2, 7 and 8 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.
 You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

That is: **Start with the interger and/or differential equations for the capacitor!**



Answers

1. $0.6 \cdot A$ $9 \cdot mJ$, $6 \cdot V$ $1.8 \cdot mJ$ 2. a) $40 \cdot mA - 16 \cdot mA \cdot e^{\frac{-t}{60 \cdot \mu s}}$ b) $35.2 \cdot mA$ c) $24 \cdot mA + 11.2 \cdot mA \cdot e^{\frac{-t'}{108 \cdot \mu s}}$

3. $82.5 \Omega / 14^\circ$ 4. a) $2.8 / -25^\circ V$ b) $200 / 45.4^\circ \Omega$ c) resistor inductor d) i) 40° **ECE Exam 2 Fall 19 p2**

5. Flat at 10mA to 2ms. Instantly down to 0mA. Ramp from 0 at 2ms to 8mA at 7ms. Instantly down to 0mA. Remains at 0mA