

ECE1050/60 Exam 2 given: Spring 03


(The space between problems has been removed.)

1. (16 pts)

a) Find Z_2 . For partial credit, you must show work and/or intermediate results.

b) Circle 1:

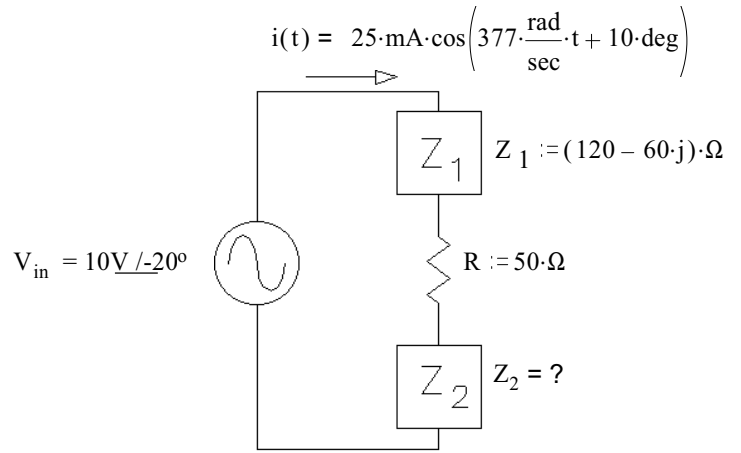- i) The source current leads the source voltage
- ii) The source voltage leads the source current




2. (16 pts) Z_{eq} is the total impedance between the two terminals


a) Find an expression for Z_{eq} without any numbers, just in terms of j , ω , L , C , & the R s.

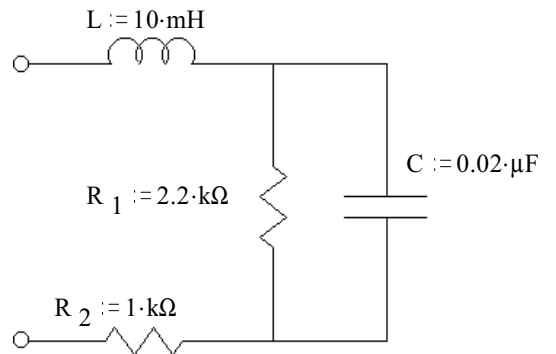b) Find Z_{eq} in polar numeric form. For partial credit, you must show work and/or intermediate results.

$Z_{\text{eq}} = \frac{\text{---}}{\text{---}} \angle \text{---}^\circ$
 Find numbers in polar form
 $f := 5 \cdot \text{kHz}$




3. (10 pts)

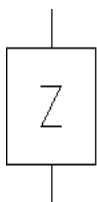

$Z := (120 - j \cdot 40) \cdot \Omega$
 $\omega := 1000 \cdot \frac{\text{rad}}{\text{sec}}$


Assume Z is two components in series. Draw the inside of Z and find the value of each component.

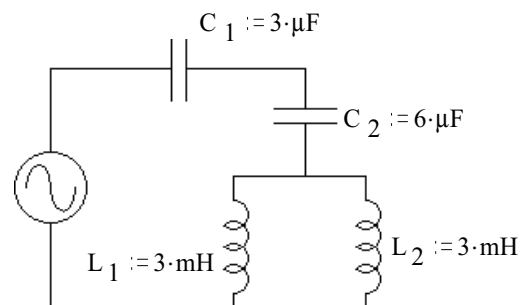4. (9 pts) Find the resonant frequency (or frequencies) of the circuit (in cycles/sec or Hz).



ECE1050/60 Exam 2 Spring 03 p2

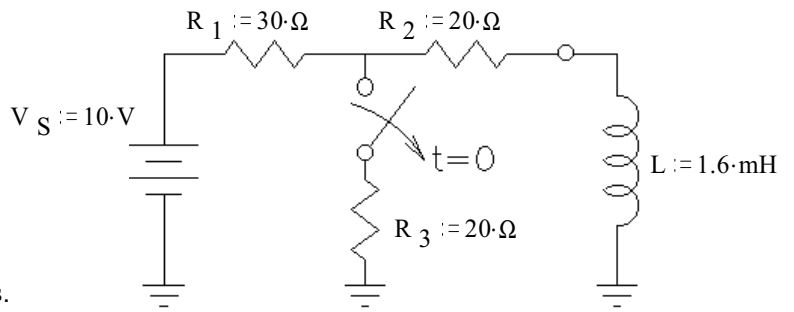5. (31 pts) a) The switch has been in the closed position for a long time and is opened (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $i_L(t)$, including all the constants that you find.





b) What is i_L at $40\mu s$?

c) At time $t = 40\mu s$ the switch is closed again. Find the complete expression for $i_L(t')$, where t' starts at $t = 40\mu s$. Be sure to clearly show the time constant.

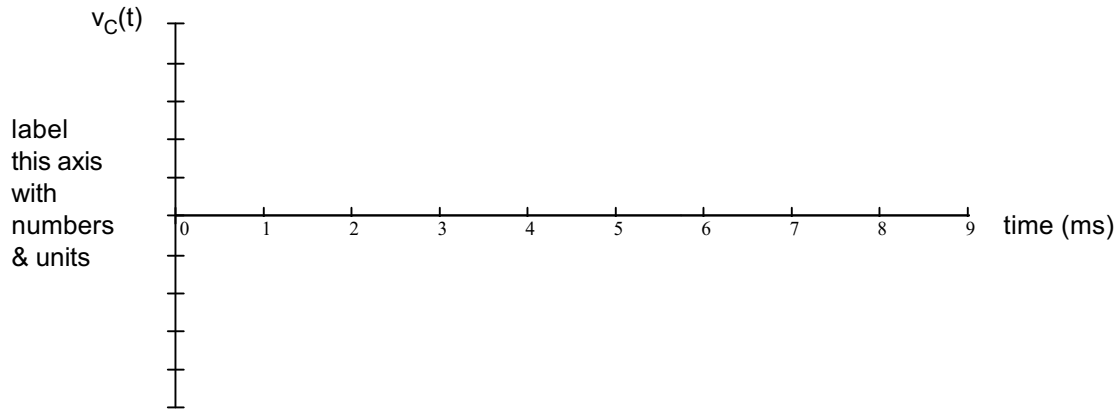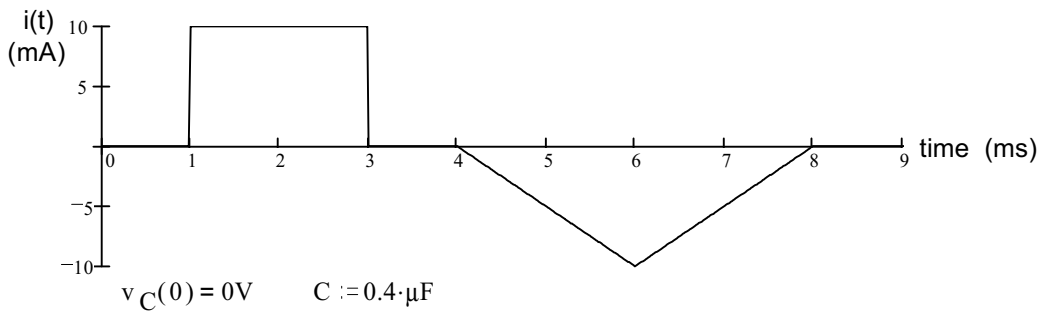
6. (18 pts) The current through a $0.4\mu F$ capacitor is shown below. Make an accurate drawing of the capacitor voltage. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy (volt level) of your plot at 0, 1, 3, 4, 6, 8, and 9 ms, so calculate those values and plot them carefully or label them. Between those points your plot must simply be the correct shape. The initial voltage across the capacitor is 0V.



Answers

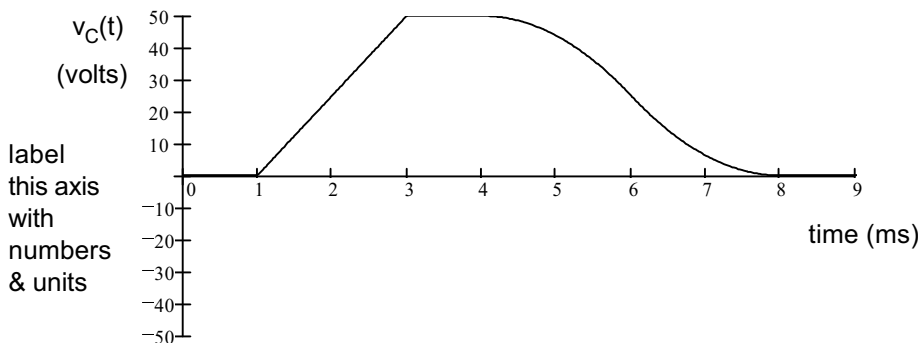- 1.a) $(176.41 - 140j) \cdot \Omega$ b) i 2.a) $j \cdot \omega \cdot L + \frac{1}{\frac{1}{R_1} + j \cdot \omega \cdot C} + R_2$ b) $Z_{eq} = 1902\Omega / -22.6^\circ$ 3. $120 \cdot \Omega$ and $25 \cdot \mu F$
4. 2.9-kHz 5.a) $200 \cdot mA - 75 \cdot mA \cdot e^{-\frac{t}{32\mu s}}$ b) 178.5-mA c) $125 \cdot mA + 53.5 \cdot mA \cdot e^{-\frac{t}{50\mu s}}$



ECE 1050/60 Exam 2

Name _____

Scores:

Page 1&2 _____ of a possible 32 pts

Page 3&4 _____ of a possible 50 pts

Page 5 _____ of a possible 18 pts

Total _____ of a possible 100 pts