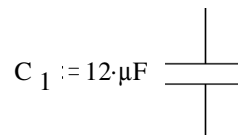


# ECE1050/60 Exam 2 given: Spring 05


(The space between problems has been removed.)

1. (6 pts) Add another capacitor to the one at left to make an equivalent capacitance of  $4\mu\text{F}$ . You may add it in series or in parallel, but make sure that it is clear to me what your connection is.

$$C_{eq} := 4\cdot\mu\text{F}$$



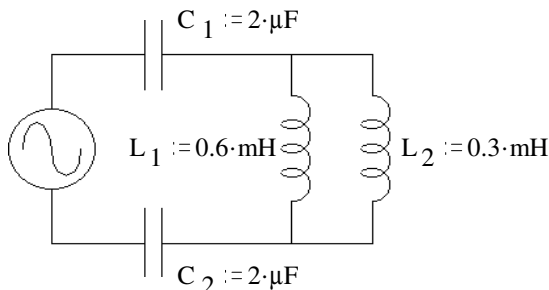2. (10 pts) Find the resonant frequency (or frequencies) of the circuit (in cycles/sec or Hz).




3. (19 pts) The current through a  $0.3\mu\text{F}$  capacitor is shown below. Make an accurate drawing of the capacitor voltage. Label the y-axis of your graph (I've already done the x-axis). The initial voltage is  $1\text{V}$ .

Note: You will be graded on the accuracy of your plot at  $0, 2, 6,$  and  $8\text{ms}$ , so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.


$$C := 0.3\cdot\mu\text{F}$$

$$v(0) = 1\cdot\text{V}$$

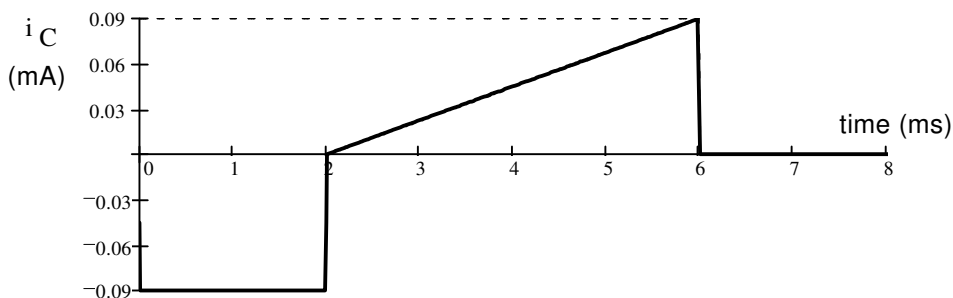

$$v(0) = 1\cdot\text{V}$$


label this axis with numbers & units

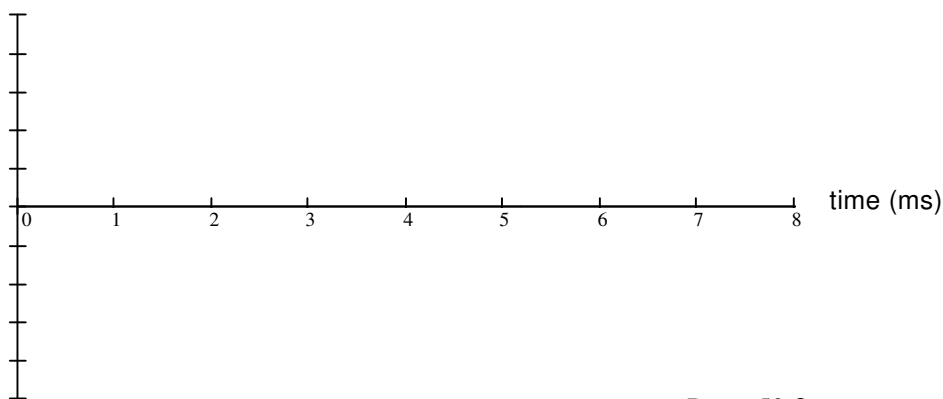

4. (24 pts) The switch has been closed (making contact) for a long time and is switched open (as shown) at time  $t = 0$ .

a) Find the complete expression for  $i_L(t)$ .

b) What is  $i_L(0.5\text{ms}) = ?$

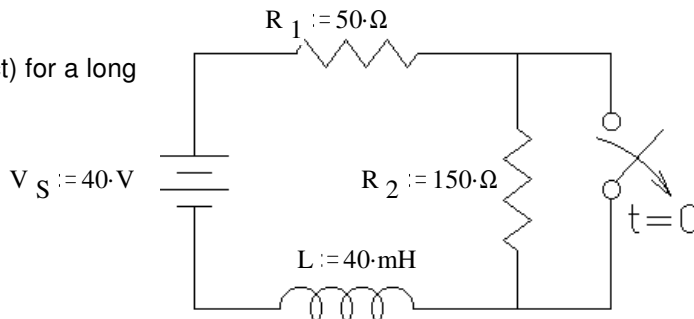

c) At time  $t = 0.5\text{ms}$  the switch is closed again. Find the complete expression for  $i_L(t')$ , where  $t'$  starts at  $t = 0.5\text{ms}$ . Be sure to clearly show the time constant.

**ECE1050/60 Exam 2 Spring 05 p2**

5. (9 pts) **Subtract** the sinusoidal voltages.

$$v_1(t) = 12 \cdot V \cdot \cos(377 \cdot t + 30)$$

$$v_2(t) = 8 \cdot V \cdot \cos(377 \cdot t - 45)$$

$$v_1(t) - v_2(t) = ? \quad \text{Give your answer in time domain form.}$$

6. (20 pts) Note: each part of this problem can be worked out separately.


a) Find  $Z_1$ . For partial credit, you must show work and/or intermediate results.

b) Find the voltage across  $R_1$ ,  $V_{R1}$ .

c)  $Z_2 = 120 \angle -30^\circ \Omega$ , To make  $Z_2$  in the simplest way, what part(s) would you need? Just circle the needed part(s), don't find the values.

- resistor                      capacitor                      inductor                      power supply                      current source  
 Thevenin resistor                      Ideal transformer                      voltmeter                      ammeter                      scope

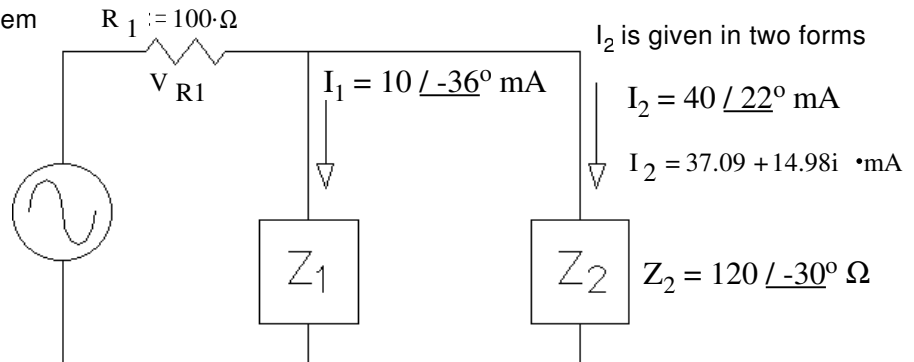d) Circle 1:    i)  $I_1$  leads  $I_2$                       ii)  $I_1$  lags  $I_2$




7. (12 pts)  $Z_{eq}$  is the total impedance between the two terminals.

Find  $Z_{eq}$  in simple polar form (give me numbers).

For partial credit, you must show work and/or intermediate results.

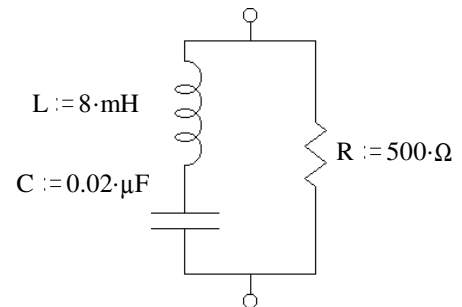
$f := 8000 \cdot \text{Hz}$                        $Z_{eq} = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ$   
**Polar Form**



**Answers**

1.  $C_2 = 6 \cdot \mu\text{F}$  in series

2.  $f_o = 11.3 \cdot \text{kHz}$

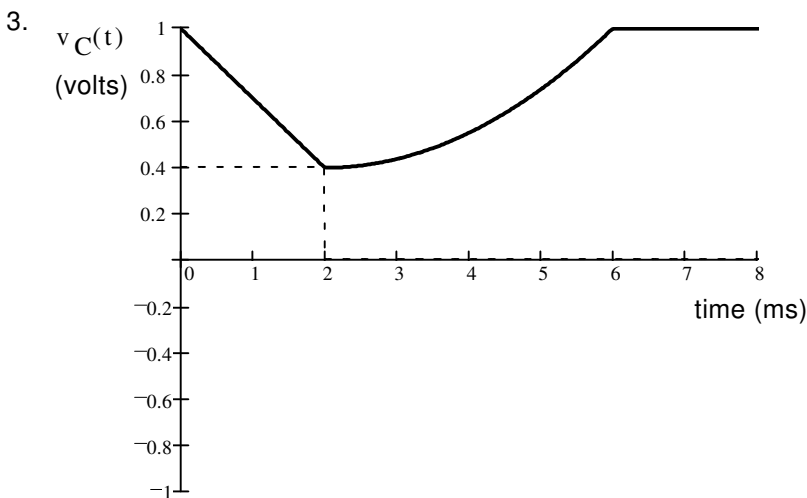

4. a)  $i_L(t) = 200 \cdot \text{mA} + 600 \cdot \text{mA} \cdot e^{-\frac{t}{0.2 \cdot \text{ms}}}$

b)  $i_L(0.5 \cdot \text{ms}) = 250 \cdot \text{mA}$

c)  $i_L(t') = 800 \cdot \text{mA} - 550 \cdot \text{mA} \cdot e^{-\frac{t'}{0.8 \cdot \text{ms}}}$

5.  $v_1(t) - v_2(t) = 12.6 \cdot \cos(377 \cdot t + 67.9 \cdot \text{deg}) \cdot V$

ECE 1050/60 Exam 2

Name \_\_\_\_\_

Scores:

Page 1&2 \_\_\_\_\_ of a possible 35 pts

Page 3&4 \_\_\_\_\_ of a possible 33 pts

Page 5&6 \_\_\_\_\_ of a possible 32 pts

Total \_\_\_\_\_ of a possible 100 pts

6. a)  $Z_1 = 480 \angle 28^\circ \Omega$

b)  $V_{R1} := 4.52 \cdot V + 0.911 \cdot j \cdot V$

c) resistor & capacitor

$= 4.61 \angle 11.4^\circ V$

d) ii,  $-36^\circ < 22^\circ$

7.  $Z_{eq} = 382.1 \Omega \angle -40.2^\circ$