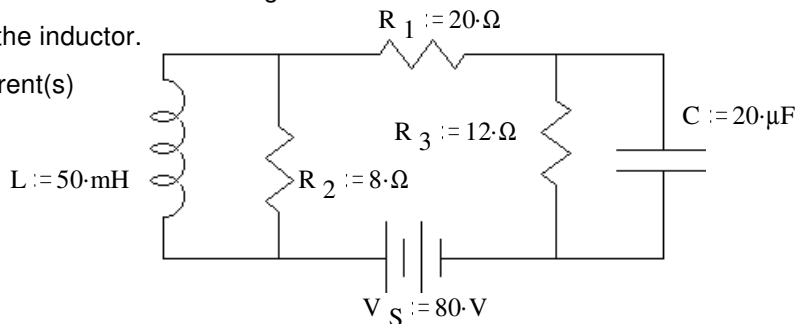


ECE2210/00 Exam 2 given: Spring 07 (The space between problems has been removed.)


1. (13 pts) The following circuit has been connected as shown for a long time.

Find the energy stored in the capacitor and in the inductor.

Also show the values of the voltage(s) and current(s) necessary to answer this question.




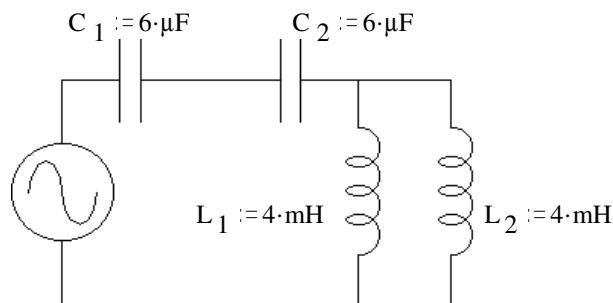
2. (10 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).




3. (13 pts) The voltage across a 0.2 H inductor is shown below. Make an accurate drawing of the inductor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 2, 4, and 6 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

$L := 0.2 \cdot H$

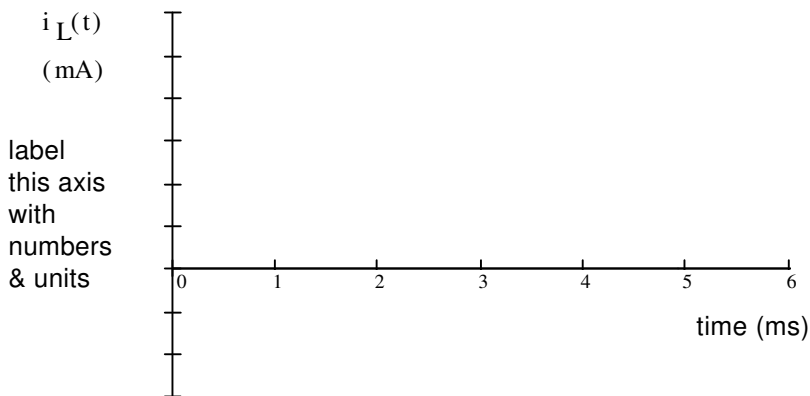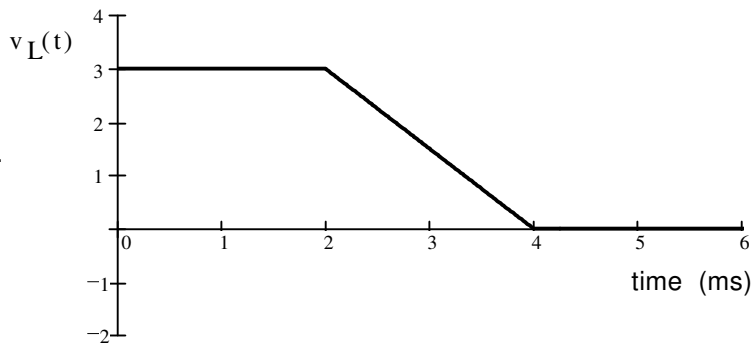

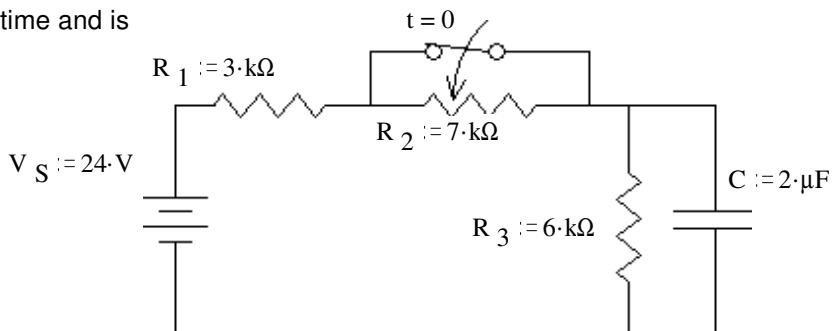4. (21 pts) The switch has been open for a long time and is closed (as shown) at time $t = 0$. Find the complete expression for $v_C(t)$.




b) What is v_C when $t = 2\tau$? $v_C(2\tau) = ?$

ECE2210/00 Exam 2 Spring 07 p1

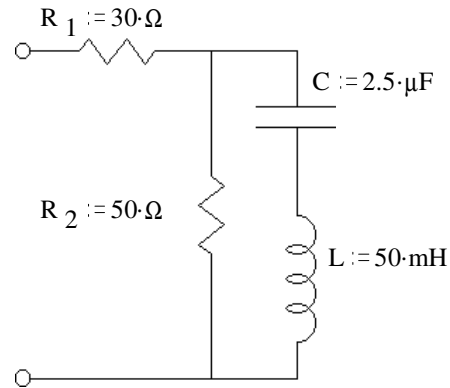5. (16 pts) Find Z_{eq} in simple polar form (give me numbers).

For partial credit, you must show work and/or intermediate results.

$$\omega := 2000 \frac{\text{rad}}{\text{s}}$$




$$Z_{eq} = \frac{\quad}{\quad} \angle \frac{\quad}{\quad}^\circ$$

Polar Form

6. (19 pts)

a) Find V_{in} in polar form.

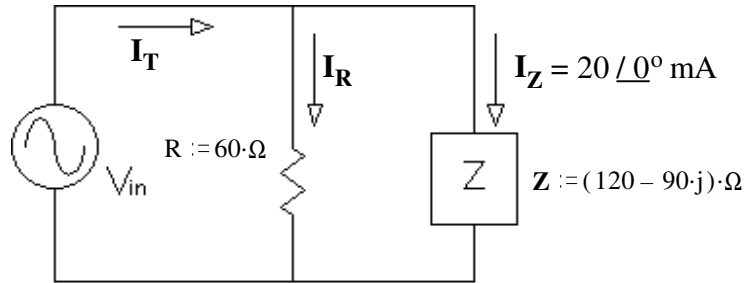

b) Circle 1:

i) V_{in} leads I_Z

ii) V_{in} lags I_Z

Why? Show numbers: _____ > _____

_____ < _____

Or explain by other means:

c) Find I_T in any form.


7. (8 pts) $Z := 400 \cdot \Omega \cdot e^{-j60 \text{ deg}}$
 $f := 500 \text{ Hz}$

To make Z in the simplest way, what part(s) would you need?
 Draw the parts and find the values.

Answers

1. $W_L := 156 \text{ mJ}$ $W_C := 9 \text{ mJ}$

2. $f_o = 2055 \text{ Hz}$

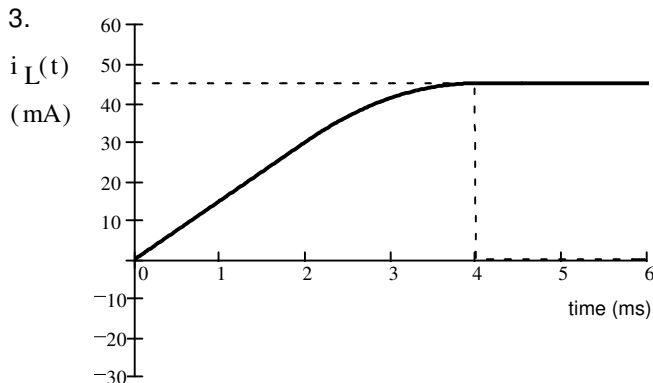

4. a) $v_C(t) = 16 \cdot V - 7 \cdot V \cdot e^{-\frac{t}{4 \text{ ms}}}$

b) $15.05 \cdot V$

5. $Z_{eq} = 72.8 \Omega \angle -15.95^\circ$

ECE 2210/00 Exam 2

Name _____

Scores:

Page 1&2 _____ of a possible 36 pts

Page 3&4 _____ of a possible 37 pts

Page 5&6 _____ of a possible 27 pts

Total _____ of a possible 100 pts

6 a) $V_{in} = 3V \angle -36.9^\circ$

b) ii) $-37 < 0$

V_{in} has negative imaginary part,
 I_Z has no phase angle

OR

c) $I_T = 60 - 30j \text{ mA} = 67.1 \text{ mA} \angle -26.6^\circ$

